 


## Introduction

I started studying digital electronics in the first months of year 1989; at that time I wanted to build digitally controlled volume and tuning for an AM RADIO. I was a 100% analog engineer and digital electronic concepts were new to me. It is an entirely different story so I failed miserably the first, second, third, ..... (n+1)th time to design a working model of the above. When I started, I was fascinated by the binary system and by the way microprocessors work. It took me nearly one year to fully understand the concepts of digital. Digital means anything which has to do with digits, but in today's world digital means CMOS, TTL gates, flip-flops, processors, computers. In the next few pages I will be sharing my knowledge, experience and also some tidbits from my friends and from the net. You are always welcome to suggest and help me make this page really useful for the whole digital world.

## Diagram of analog voltage vs time




## Digital Representation

Systems which process discrete values are called digital systems. In digital representation the quantities are represented not by proportional quantities but by symbols called digits. As an example, consider the digital watch, which provides the time of the day in the form of decimal digits representing hours and minutes (and sometimes seconds). As we know, time of day changes continuously, but the digital watch reading does not change continuously; rather, it changes in steps of one per minute (or per second). In other words, time of day digital representation changes in discrete steps, as compared to the representation of time provided by an analog watch, where the dial reading changes continuously.

Below is a diagram of digital voltage vs time: here input voltage changes from +4 Volts to -4 Volts; it can be converted to digital form by Analog to Digital converters (ADC). An ADC converts continuous signals into samples per second. Well, this is an entirely different theory.

## Diagram of Digital voltage vs time

 

The major difference between analog and digital quantities, then, can be stated simply as follows:

- Analog = continuous
- Digital = discrete (step by step)

### Advantages of Digital Techniques

- Easier to design. Exact values of voltage or current are not important, only the range (HIGH or LOW) in which they fall.
- Information storage is easy.
- Accuracy and precision are greater.
- Operations can be programmed. Analog systems can also be programmed, but the available operations variety and complexity is severely limited.
- Digital circuits are less affected by noise, as long as the noise is not large enough to prevent us from distinguishing HIGH from LOW (we discuss this in detail in an advanced digital tutorial section).
- More digital circuitry can be fabricated on IC chips.


### Limitations of Digital Techniques

Most physical quantities in real world are analog in nature, and these quantities are often the inputs and outputs that are being monitored, operated on, and controlled by a system. Thus conversion to digital format and re-conversion to analog format is needed.






.

 

.

 

.

## Numbering System

Many number systems are in use in digital technology. The most common are the decimal, binary, octal, and hexadecimal systems. The decimal system is clearly the most familiar to us because it is a tool that we use every day. Examining some of its characteristics will help us to better understand the other systems. In the next few pages we shall introduce four numerical representation systems that are used in the digital system. There are other systems, which we will look at briefly.

- Decimal
- Binary
- Octal
- Hexadecimal

### Decimal System

The decimal system is composed of 10 numerals or symbols. These 10 symbols are 0, 1, 2, 3, 4, 5, 6, 7, 8, 9. Using these symbols as digits of a number, we can express any quantity. The decimal system is also called the base-10 system because it has 10 digits.

$10^3$	$10^2$	$10^1$	$10^0$	.	$10^{-1}$	$10^{-2}$	$10^{-3}$
=1000	=100	=10	=1	.	=0.1	=0.01	=0.001
Most Significant Digit				Decimal point			Least Significant Digit

Even though the decimal system has only 10 symbols,

any number of any magnitude can be expressed by using our system of positional weighting.

### ◆ Decimal Examples

- $3.14_{10}$
- $52_{10}$
- $1024_{10}$
- $64000_{10}$

### ◆ Binary System

In the binary system, there are only two symbols or possible digit values, 0 and 1. This base-2 system can be used to represent any quantity that can be represented in decimal or other base system.

$2^3$	$2^2$	$2^1$	$2^0$		$2^{-1}$	$2^{-2}$	$2^{-3}$
=8	=4	=2	=1	.	=0.5	=0.25	=0.125
Most Significant Digit				Binary point			Least Significant Digit

### ◆ Binary Counting

The Binary counting sequence is shown in the table:

$2^3$	$2^2$	$2^1$	$2^0$	Decimal
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

## Representing Binary Quantities


In digital systems the information that is being processed is usually presented in binary form. Binary quantities can be represented by any device that has only two operating states or possible conditions. E.g., a switch is only open or closed. We arbitrarily (as we define them) let an open switch represent binary 0 and a closed switch represent binary 1. Thus we can represent any binary number by using series of switches.

### ◆ Typical Voltage Assignment

**Binary 1:** Any voltage between 2V to 5V

**Binary 0:** Any voltage between 0V to 0.8V

 **Not used:** Voltage between 0.8V to 2V in 5 Volt CMOS and TTL Logic, this may cause error in a digital circuit. Today's digital circuits work at 1.8 volts, so this statement may not hold true for all logic circuits.



We can see another significant difference between digital and analog systems. In digital systems, the exact voltage value is not important; eg, a voltage of 3.6V means the same as a voltage of 4.3V. In analog systems, the exact voltage value is important.

The binary number system is the most important one in digital systems, but several others are also important. The decimal system is important because it is universally used to represent quantities outside a digital system. This means that there will be situations where decimal values have to be converted to binary values before they are entered into the digital system.

In addition to binary and decimal, two other number systems find wide-spread applications in digital systems. The octal (base-8) and hexadecimal (base-16) number systems are both used for the same purpose- to provide an efficient means for

representing large binary system.

### ❖ Octal System

The octal number system has a base of eight, meaning that it has eight possible digits: 0,1,2,3,4,5,6,7.

$8^3$	$8^2$	$8^1$	$8^0$	.	$8^{-1}$	$8^{-2}$	$8^{-3}$
=512	=64	=8	=1	.	=1/8	=1/64	=1/512
Most Significant Digit				Octal point			Least Significant Digit

### ❖ Octal to Decimal Conversion

- $237_8 = 2 \times (8^2) + 3 \times (8^1) + 7 \times (8^0) = 159_{10}$
- $24.6_8 = 2 \times (8^1) + 4 \times (8^0) + 6 \times (8^{-1}) = 20.75_{10}$
- $11.1_8 = 1 \times (8^1) + 1 \times (8^0) + 1 \times (8^{-1}) = 9.125_{10}$
- $12.3_8 = 1 \times (8^1) + 2 \times (8^0) + 3 \times (8^{-1}) = 10.375_{10}$

### ❖ Hexadecimal System

The hexadecimal system uses base 16. Thus, it has 16 possible digit symbols. It uses the digits 0 through 9 plus the letters A, B, C, D, E, and F as the 16 digit symbols.

$16^3$	$16^2$	$16^1$	$16^0$	.	$16^{-1}$	$16^{-2}$	$16^{-3}$
=4096	=256	=16	=1	.	=1/16	=1/256	=1/4096
Most Significant Digit				Hexa Decimal point			Least Significant Digit

### ❖ Hexadecimal to Decimal Conversion

- $24.6_{16} = 2 \times (16^1) + 4 \times (16^0) + 6 \times (16^{-1}) = 36.375_{10}$
- $11.1_{16} = 1 \times (16^1) + 1 \times (16^0) + 1 \times (16^{-1}) = 17.0625_{10}$
- $12.3_{16} = 1 \times (16^1) + 2 \times (16^0) + 3 \times (16^{-1}) = 18.1875_{10}$

## Code Conversion

Converting from one code form to another code form is called code conversion, like converting from binary to decimal or converting from hexadecimal to decimal.

### ❖ Binary-To-Decimal Conversion

Any binary number can be converted to its decimal equivalent simply by summing together the weights

of the various positions in the binary number which contain a 1.

Binary	Decimal
11011 <sub>2</sub>	
$2^4+2^3+0^1+2^1+2^0$	=16+8+0+2+1
Result	27 <sub>10</sub>

and

Binary	Decimal
10110101 <sub>2</sub>	
$2^7+0^6+2^5+2^4+0^3+2^2+0^1+2^0$	=128+0+32+16+0+4+0+1
Result	181 <sub>10</sub>

You should have noticed that the method is to find the weights (i.e., powers of 2) for each bit position that contains a 1, and then to add them up.

### ❖ Decimal-To-Binary Conversion

There are 2 methods:

- Reverse of Binary-To-Decimal Method
- Repeat Division

### ✦ Reverse of Binary-To-Decimal Method

Decimal	Binary
45 <sub>10</sub>	=32 + 0 + 8 + 4 + 0 + 1
	= $2^5+0+2^3+2^2+0+2^0$
Result	=101101 <sub>2</sub>

### ✦ Repeat Division-Convert decimal to binary


This method uses repeated division by 2.

Convert 25<sub>10</sub> to binary

Division	Remainder	Binary
25/2	= 12+ remainder of 1	1 (Least Significant Bit)
12/2	= 6 + remainder of 0	0
6/2	= 3 + remainder of 0	0

	0	
3/2	= 1 + remainder of 1	1
1/2	= 0 + remainder of 1	1 (Most Significant Bit)
Result	25 <sub>10</sub>	= 11001 <sub>2</sub>

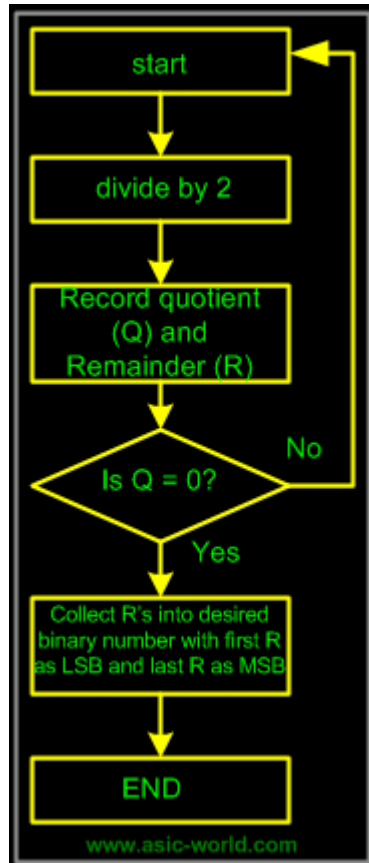The Flow chart for repeated-division method is as follows:



### Binary-To-Octal / Octal-To-Binary Conversion

Octal Digit	0	1	2	3	4	5	6	7
Binary Equivalent	000	001	010	011	100	101	110	111

Each Octal digit is represented by three binary digits.

**Example:**



$$100\ 111\ 010_2 = (100)\ (111)\ (010)_2 = 4\ 7\ 2_8$$

### Repeat Division-Convert decimal to octal

This method uses repeated division by 8.

**Example:** Convert  $177_{10}$  to octal and binary

Division	Result	Binary
177/8	= 22+ remainder of 1	1 (Least Significant Bit)
22/ 8	= 2 + remainder of 6	6
2 / 8	= 0 + remainder of 2	2 (Most Significant Bit)
Result	$177_{10}$	= $261_8$
Binary		= $010110001_2$

### Hexadecimal to Decimal/Decimal to Hexadecimal Conversion

**Example:**

$$2AF_{16} = 2 \times (16^2) + 10 \times (16^1) + 15 \times (16^0) = 687_{10}$$

### Repeat Division- Convert decimal to hexadecimal

This method uses repeated division by 16.

**Example:** convert  $378_{10}$  to hexadecimal and binary:

Division	Result	Hexadecimal
378/16	= 23+ remainder of 10	A (Least Significant Bit)23
23/16	= 1 + remainder of 7	7
1/16	= 0 + remainder of 1	1 (Most Significant Bit)
Result	$378_{10}$	= $17A_{16}$
Binary		= $0001\ 0111\ 1010_2$

### Binary-To-Hexadecimal /Hexadecimal-To-Binary Conversion

Hexadecimal Digit	0	1	2	3	4	5	6	7
Binary Equivalent	0000	0001	0010	0011	0100	0101	0110	0111

Hexadecimal	8	9	A	B	C	D	E	F
-------------	---	---	---	---	---	---	---	---

Digit								
Binary Equivalent	1000	1001	1010	1011	1100	1101	1110	1111

Each Hexadecimal digit is represented by **four** bits of binary digit.

**Example:**

$$1011\ 0010\ 1111_2 = (1011)\ (0010)\ (1111)_2 = B\ 2\ F_{16}$$

### Octal-To-Hexadecimal Hexadecimal-To-Octal Conversion

- Convert Octal (Hexadecimal) to Binary first.
- Regroup the binary number by three bits per group **starting from LSB** if Octal is required.
- Regroup the binary number by four bits per group starting from LSB if Hexadecimal is required.

Example:

Convert  $5A8_{16}$  to Octal.

Hexadecimal	Binary/Octal
5A816	= <b>0101 1010 1000</b> (Binary)
	= <b>010 110 101 000</b> (Binary)
Result	= 2 6 5 0 (Octal)

## Binary Codes

Binary codes are codes which are represented in binary system with modification from the original ones. Below we will be seeing the following:

- Weighted Binary Systems
- Non Weighted Codes

### Weighted Binary Systems

Weighted binary codes are those which obey the positional weighting principles, each position of the number represents a specific weight. The binary counting

sequence is an example.

Decimal	8421	2421	5211	Excess-3
0	0000	0000	0000	0011
1	0001	0001	0001	0100
2	0010	0010	0011	0101
3	0011	0011	0101	0110
4	0100	0100	0111	0111
5	0101	1011	1000	1000
6	0110	1100	1010	1001
7	0111	1101	1100	1010
8	1000	1110	1110	1011
9	1001	1111	1111	1100

#### ✦ 8421 Code/BCD Code

The BCD (Binary Coded Decimal) is a straight assignment of the binary equivalent. It is possible to assign weights to the binary bits according to their positions. The weights in the BCD code are 8,4,2,1.

**Example:** The bit assignment 1001, can be seen by its weights to represent the decimal 9 because:

$$1 \times 8 + 0 \times 4 + 0 \times 2 + 1 \times 1 = 9$$

#### ✦ 2421 Code

This is a weighted code, its weights are 2, 4, 2 and 1. A decimal number is represented in 4-bit form and the total four bits weight is  $2 + 4 + 2 + 1 = 9$ . Hence the 2421 code represents the decimal numbers from 0 to 9.

#### ✦ 5211 Code

This is a weighted code, its weights are 5, 2, 1 and 1. A decimal number is represented in 4-bit form and the total four bits weight is  $5 + 2 + 1 + 1 = 9$ . Hence the 5211 code represents the decimal numbers from 0 to 9.

## Reflective Code

A code is said to be reflective when code for 9 is complement for the code for 0, and so is for 8 and 1 codes, 7 and 2, 6 and 3, 5 and 4. Codes 2421, 5211, and excess-3 are reflective, whereas the 8421 code is not.

## ◆ Sequential Codes

A code is said to be sequential when two subsequent codes, seen as numbers in binary representation, differ by one. This greatly aids mathematical manipulation of data. The 8421 and Excess-3 codes are sequential, whereas the 2421 and 5211 codes are not.

## ◆ Non Weighted Codes

Non weighted codes are codes that are not positionally weighted. That is, each position within the binary number is not assigned a fixed value.

## ◆ Excess-3 Code

Excess-3 is a non weighted code used to express decimal numbers. The code derives its name from the fact that each binary code is the corresponding 8421 code plus 0011(3).

**Example:** 1000 of 8421 = 1011 in Excess-3

## ◆ Gray Code

The gray code belongs to a class of codes called minimum change codes, in which only one bit in the code changes when moving from

one code to the next. The Gray code is non-weighted code, as the position of bit does not contain any weight. The gray code is a reflective digital code which has the special property that any two subsequent numbers codes differ by only one bit. This is also called a unit-distance code. In digital Gray code has got a special place.

Decimal Number	Binary Code	Gray Code
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

#### ❖ Binary to Gray Conversion

- Gray Code MSB is binary code MSB.
- Gray Code MSB-1 is the XOR of binary code MSB and MSB-1.
- MSB-2 bit of gray code is XOR of MSB-1 and MSB-2 bit of binary code.
- MSB-N bit of gray code is XOR of MSB-

N-1 and MSB-N bit of binary code.

## Floating Point Numbers

A real number or floating point number is a number which has both an integer and a fractional part. Examples for real decimal numbers are 123.45, 0.1234, -0.12345, etc. Examples for real binary numbers are 1100.1100, 0.1001, -1.001, etc. In general, floating point numbers are expressed in exponential notation.

For example the decimal number

- 30000.0 can be written as  $3 \times 10^4$ .
- 312.45 can be written as  $3.1245 \times 10^2$ .

Similarly, the binary number 1010.001 can be written as  $1.010001 \times 10^3$ .

The general form of a number N can be expressed as


$$N = \pm m \times b^{\pm e}$$

Where m is mantissa, b is the base of number system and e is the exponent. A floating point number is represented by two parts. The number first part, called mantissa, is a signed fixed point number and the second part, called exponent, specifies the decimal or binary position.
 
## Representation of Floating Point Numbers

A floating point binary number is also represented as in the case of decimal numbers. It means that mantissa and exponent are expressed using signed magnitude notation in which one bit is reserved for sign bit.

Consider a 16-bit word used to store the floating point numbers; assume that 9 bits are reserved for mantissa and 7 bits for exponent and also assume that the mantissa part is represented in fraction system. This implies the assumed binary point is at the mantissa sign bit immediate right.



### ◆ Example


A binary number 1101.01 is represented as  
 Mantissa = 110101 =  $(1101.01)_2 = 0.110101 \times 2^4$

Exponent =  $(4)_{10}$

Expanding mantissa to 8 bits we get 11010100

Binary representation of exponent  $(4)_{10} = 000100$

The required representation is

 

## Symbolic Logic

Boolean algebra derives its name from the mathematician George

Boole. Symbolic Logic uses values, variables and operations :

- **True** is represented by the value **1**.
- **False** is represented by the value **0**.

Variables are represented by letters and can have one of two values, either 0 or 1. Operations are functions of one or more variables.

- **AND** is represented by  $X.Y$
- **OR** is represented by  $X + Y$
- **NOT** is represented by  $X'$  . Throughout this tutorial the  $X'$  form will be used and sometime  $!X$  will be used.

These basic operations can be combined to give expressions.

**Example :**

- $X$
- $X.Y$
- $W.X.Y + Z$

### **Precedence**

As with any other branch of mathematics, these operators have an order of precedence. NOT operations have the highest precedence, followed by AND operations, followed by OR operations. Brackets can be used as with other forms of algebra. e.g.

$X.Y + Z$  and  $X.(Y + Z)$  are not the same function.



## ❖ Function Definitions

The logic operations given previously are defined as follows :

Define  $f(X,Y)$  to be some function of the variables  $X$  and  $Y$ .

$$f(X,Y) = X.Y$$

- 1 if  $X = 1$  and  $Y = 1$
- 0 Otherwise

$$f(X,Y) = X + Y$$

- 1 if  $X = 1$  or  $Y = 1$
- 0 Otherwise

$$f(X) = X'$$

- 1 if  $X = 0$
- 0 Otherwise

## ❖ Truth Tables

Truth tables are a means of representing the results of a logic function using a table. They are constructed by defining all possible combinations of the inputs to a function, and then calculating the output for each combination in turn. For the three functions we have just defined, the truth tables are as follows.

### AND

X	Y	F(X,Y)
0	0	0
0	1	0
1	0	0
1	1	1

### OR

X	Y	F(X,Y)
0	0	0

0	1	1
1	0	1
1	1	1

### NOT

X	F(X)
0	1
1	0

## Symbolic Logic

Boolean algebra derives its name from the mathematician George Boole. Symbolic Logic uses values, variables and operations :

- **True** is represented by the value **1**.
- **False** is represented by the value **0**.

Variables are represented by letters and can have one of two values, either 0 or 1. Operations are functions of one or more variables.

- **AND** is represented by  $X.Y$
- **OR** is represented by  $X + Y$
- **NOT** is represented by  $X'$ . Throughout this tutorial the  $X'$  form will be used and sometime  $!X$  will be used.

These basic operations can be combined to give expressions.

### Example :

- $X$
- $X.Y$
- $W.X.Y + Z$

### ❖ Precedence

As with any other branch of mathematics, these operators have an order of precedence. NOT operations have the highest precedence, followed by AND operations, followed by OR operations. Brackets can be used as with other forms of algebra. e.g.

$X.Y + Z$  and  $X.(Y + Z)$  are not the same function.

### ❖ Function Definitions

The logic operations given previously are defined as follows :

Define  $f(X,Y)$  to be some function of the variables  $X$  and  $Y$ .

$$f(X,Y) = X.Y$$

- 1 if  $X = 1$  and  $Y = 1$
- 0 Otherwise

$$f(X,Y) = X + Y$$

- 1 if  $X = 1$  or  $Y = 1$
- 0 Otherwise

$$f(X) = X'$$

- 1 if  $X = 0$
- 0 Otherwise

### ❖ Truth Tables

Truth tables are a means of representing the results of a logic function using a table. They are constructed by defining all possible combinations of the inputs to a function, and then calculating the output for each combination in turn. For

the three functions we have just defined, the truth tables are as follows.

### AND

X	Y	F(X,Y)
0	0	0
0	1	0
1	0	0
1	1	1

### OR

X	Y	F(X,Y)
0	0	0
0	1	1
1	0	1
1	1	1

### NOT

X	F(X)
0	1
1	0

Truth tables may contain as many input variables as desired

$$F(X,Y,Z) = X.Y + Z$$

X	Y	Z	F(X,Y,Z)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

## Boolean Switching Algebras

A Boolean Switching Algebra is one which deals only with two-valued variables. Boole's general theory covers algebras which deal with

variables which can hold n values.

### ◆ Axioms

Consider a set  $S = \{0, 1\}$   
Consider two binary operations, + and . , and one unary operation, -- , that act on these elements.  $[S, ., +, --, 0, 1]$  is called a switching algebra that satisfies the following axioms S

### ◆ Closure

If  $X \in S$  and  $Y \in S$  then  $X.Y \in S$   
If  $X \in S$  and  $Y \in S$  then  $X+Y \in S$

### ◆ Identity

$\exists$ an identity 0 for + such that  $X + 0 = X$   
 $\exists$ an identity 1 for . such that  $X . 1 = X$

### ◆ Commutative Laws

$X + Y = Y + X$   
 $X . Y = Y . X$

### ◆ Distributive Laws

$X.(Y + Z) = X.Y + X.Z$   
 $X + Y.Z = (X + Y) . (X + Z)$

### ◆ Complement

$\forall X \in S \exists$ a complement  $X'$  such that  
 $X + X' = 1$   
 $X . X' = 0$   
The complement  $X'$  is unique.

Truth tables may contain as many input variables as desired

$$F(X,Y,Z) = X.Y + Z$$

X	Y	Z	F(X,Y,Z)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

### Boolean Switching Algebras

A Boolean Switching Algebra is one which deals only with two-valued variables. Boole's general theory covers algebras which deal with variables which can hold  $n$  values.

### Axioms

Consider a set  $S = \{0, 1\}$   
 Consider two binary operations,  $+$  and  $\cdot$ , and one unary operation,  $--$ , that act on these elements.  $[S, \cdot, +, --, 0, 1]$  is called a switching algebra that satisfies the following axioms  $S$

#### ◆ Closure

If  $X \in S$  and  $Y \in S$  then  $X \cdot Y \in S$   
 If  $X \in S$  and  $Y \in S$  then  $X + Y \in S$

#### ◆ Identity

$\exists$  an identity 0 for  $+$  such that  $X + 0 = X$   
 $\exists$  an identity 1 for  $\cdot$  such that  $X \cdot 1 = X$

#### ◆ Commutative Laws

$X + Y = Y + X$   
 $X \cdot Y = Y \cdot X$

◆ **Distributive Laws**

$$X.(Y + Z) = X.Y + X.Z$$

$$X + Y.Z = (X + Y) . (X + Z)$$

◆ **Complement**

$\forall X \in S \exists a$  complement  $X'$  such that  
 $X + X' = 1$   
 $X . X' = 0$   
 The complement  $X'$  is unique.

**Theorems**

A number of theorems may be proved for switching algebras

◆ **Idempotent Law**

$$X + X = X$$

$$X . X = X$$

◆ **DeMorgan's Law**

$(X + Y)' = X' . Y'$ , These can be proved by the use of truth tables.

Proof of  $(X + Y)' = X' . Y'$

X	Y	X+Y	(X+Y)'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

X	Y	X'	Y'	X'.Y'
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

The two truth tables are identical, and so the two expressions are identical.

$(X.Y) = X' + Y'$ , These can be proved by the use of truth tables.

Proof of  $(X.Y) = X' + Y'$

X	Y	X.Y	(X.Y)'
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

X	Y	X'	Y'	X'+Y'
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

**Note** : DeMorgans Laws are applicable for any number of variables.

#### ◆ Boundedness Law

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

#### ◆ Absorption Law

$$X + (X \cdot Y) = X$$

$$X \cdot (X + Y) = X$$

#### ◆ Elimination Law

$$X + (X' \cdot Y) = X + Y$$

$$X \cdot (X' + Y) = X \cdot Y$$

#### ◆ Unique Complement theorem

If  $X + Y = 1$  and  $X \cdot Y = 0$  then  $X = Y'$

#### ◆ Involution theorem

$$X'' = X$$

$$0' = 1$$

#### ◆ Associative Properties



$$X + (Y + Z) = (X + Y) + Z$$

$$X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

### ◆ Duality Principle

In Boolean algebras the duality Principle can be obtained by interchanging AND and OR operators and replacing 0's by 1's and 1's by 0's. Compare the identities on the left side with the identities on the right.

### Example

$$X \cdot Y + Z' = (X' + Y') \cdot Z$$

### ◆ Consensus theorem

$$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$$

or dual form as below

$$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$$

Proof of  $X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$ :

$X \cdot Y + X' \cdot Z + Y \cdot Z$	$= X \cdot Y + X' \cdot Z$
$X \cdot Y + X' \cdot Z + (X + X') \cdot Y \cdot Z$	$= X \cdot Y + X' \cdot Z$
$X \cdot Y \cdot (1 + Z) + X' \cdot Z \cdot (1 + Y)$	$= X \cdot Y + X' \cdot Z$
$X \cdot Y + X' \cdot Z$	$= X \cdot Y + X' \cdot Z$

$$(X \cdot Y' + Z) \cdot (X + Y) \cdot Z = X \cdot Z + Y \cdot Z$$

instead of  $X \cdot Z + Y' \cdot Z$

$$X \cdot Y' Z + X \cdot Z + Y \cdot Z$$

$$(X \cdot Y' + X + Y) \cdot Z$$

$$(X + Y) \cdot Z$$

$$X \cdot Z + Y \cdot Z$$

The term which is left out is called the consensus term.

Given a pair of terms for which a variable appears in one term, and its complement in the other, then the consensus term is

formed by ANDing the original terms together, leaving out the selected variable and its complement.

Example :

The consensus of  $X.Y$  and  $X'.Z$  is  $Y.Z$

The consensus of  $X.Y.Z$  and  $Y'.Z'.W'$  is  $(X.Z).(Z.W')$

### ✦ Shannon Expansion Theorem

The Shannon Expansion Theorem is used to expand a Boolean logic function ( $F$ ) in terms of (or with respect to) a Boolean variable ( $X$ ), as in the following forms.

$$F = X \cdot F(X = 1) + X' \cdot F(X = 0)$$

where  $F(X = 1)$  represents the function  $F$  evaluated with  $X$  set equal to 1;  $F(X = 0)$  represents the function  $F$  evaluated with  $X$  set equal to 0.

Also the following function  $F$  can be expanded with respect to  $X$ ,

$$\begin{aligned} F &= X' \cdot Y + X \cdot Y \cdot Z' + X' \cdot Y' \cdot Z \\ &= X \cdot (Y \cdot Z') + X' \cdot (Y + Y' \cdot Z) \end{aligned}$$

Thus, the function  $F$  can be split into two smaller functions.

$$F(X = '1') = Y \cdot Z'$$

This is known as the cofactor of  $F$  with respect to  $X$  in the previous logic equation. The cofactor of  $F$  with respect to  $X$  may also be represented as  $F_X$  (the cofactor of  $F$  with respect to  $X'$  is  $F_{X'}$ ). Using the Shannon Expansion Theorem, a Boolean function may be expanded with respect to any of its variables.

For example, if we expand F with respect to Y instead of X,

$$F = X' \cdot Y + X \cdot Y \cdot Z' + X' \cdot Y' \cdot Z$$

$$= Y \cdot (X' + X \cdot Z') + Y' \cdot (X' \cdot Z)$$

A function may be expanded as many times as the number of variables it contains until the canonical form is reached. The canonical form is a unique representation for any Boolean function that uses only minterms. A minterm is a product term that contains all the variables of F, such as  $X \cdot Y' \cdot Z$ .

Any Boolean function can be implemented using multiplexer blocks by representing it as a series of terms derived using the Shannon Expansion Theorem.

### Summary of Laws And Theorems

Identity	Dual
<b>Operations with 0 and 1</b>	
$X + 0 = X$ (identity)	$X \cdot 1 = X$
$X + 1 = 1$ (null element)	$X \cdot 0 = 0$
<b>Idempotency theorem</b>	
$X + X = X$	$X \cdot X = X$
<b>Complementarity</b>	
$X + X' = 1$	$X \cdot X' = 0$
<b>Involution theorem</b>	
$(X')' = X$	
<b>Cummutative law</b>	
$X + Y = Y + X$	$X \cdot Y = Y \cdot X$
<b>Associative law</b>	
$(X + Y) + Z = X + (Y + Z) = X + Y + Z$	$(XY)Z = X(YZ) = XYZ$
<b>Distributive law</b>	
$X(Y + Z) = XY + XZ$	$X \cdot Y + X \cdot Z = X(Y + Z)$

	$(YZ) = (X + Y)(X + Z)$
<b>DeMorgan's theorem</b>	
$(X + Y + Z + \dots)' = X'Y'Z'\dots$ or $\{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)\}' = \{f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)\}$	$(XYZ\dots)' = X' + Y' + Z' + \dots$
<b>Simplification theorems</b>	
$XY + XY' = X$ (uniting)	$(X + Y)(X + Y') = X$
$X + XY = X$ (absorption)	$X(X + Y) = X$
$(X + Y')Y = XY$ (adsorption)	$XY' + Y = X + Y$
<b>Consensus theorem</b>	
$XY + X'Z + YZ = XY + X'Z$	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$
<b>Duality</b>	
$(X + Y + Z + \dots)^D = XYZ\dots$ or $\{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)\}^D = f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$	$(XYZ\dots)^D = X + Y + Z + \dots$
<b>Shannon Expansion Theorem</b>	
$f(X_1, \dots, X_k, \dots, X_n)$	$X_k + f(X_1, \dots, 1, \dots, X_n) + X_k' + f(X_1, \dots, 0, \dots, X_n)$
$f(X_1, \dots, X_k, \dots, X_n)$	$[X_k + f(X_1, \dots, 0, \dots, X_n)] + [X_k' + f(X_1, \dots, 1, \dots, X_n)]$

## Algebraic Manipulation

## Minterms and Maxterms

Any boolean expression may be expressed in terms of either minterms or maxterms. To do this we must first define the concept of a literal. A literal is a single variable within a term which may or may not be complemented. For an expression with N variables, minterms and maxterms are defined as follows :

- A minterm is the product of N distinct literals where each literal occurs exactly once.
- A maxterm is the sum of N distinct literals where each literal occurs exactly once.

For a two-variable expression, the minterms and maxterms are as follows

X	Y	Minterm	Maxterm
0	0	$X'.Y'$	$X+Y$
0	1	$X'.Y$	$X+Y'$
1	0	$X.Y'$	$X'+Y$
1	1	$X.Y$	$X'+Y'$

For a three-variable expression, the minterms and maxterms are as follows

X	Y	Z	Minterm	Maxterm
0	0	0	$X'.Y'.Z'$	$X+Y+Z$
0	0	1	$X'.Y'.Z$	$X+Y+Z'$
0	1	0	$X'.Y.Z'$	$X+Y'+Z$
0	1	1	$X'.Y.Z$	$X+Y'+Z'$
1	0	0	$X.Y'.Z'$	$X'+Y+Z$
1	0	1	$X.Y'.Z$	$X'+Y+Z'$

1	1	0	X.Y.Z'	X'+Y'+Z
1	1	1	X.Y.Z	X'+Y'+Z'

This allows us to represent expressions in either Sum of Products or Product of Sums forms

### ✦ Sum Of Products (SOP)

The Sum of Products form represents an expression as a sum of minterms.

$$F(X, Y, \dots) = \text{Sum } (a_k \cdot m_k)$$

where  $a_k$  is 0 or 1 and  $m_k$  is a minterm.

To derive the Sum of Products form from a truth table, OR together all of the minterms which give a value of 1.

### ✦ Example - SOP

Consider the truth table

X	Y	F	Minterm
0	0	0	X'.Y'
0	1	0	X'Y
1	0	1	X.Y'
1	1	1	X.Y

Here SOP is  $f(X,Y) = X.Y' + X.Y$

### ✦ Product Of Sum (POS)

The Product of Sums form represents an expression as a product of maxterms.

$$F(X, Y, \dots) = \text{Product } (b_k + M_k), \text{ where } b_k \text{ is 0 or 1 and } M_k \text{ is a maxterm.}$$

To derive the Product of

Sums form from a truth table, AND together all of the maxterms which give a value of 0.

**Example - POS**

Consider the truth table from the previous example.

X	Y	F	Maxterm
0	0	1	X+Y
0	1	0	X+Y'
1	0	1	X'+Y
1	1	1	X'+Y'

Here POS is  $F(X,Y) = (X+Y')$

**✦ Exercise**

Give the expression represented by the following truth table in both Sum of Products and Product of Sums forms.

X	Y	Z	F(X,Y,Z)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

**🔲 Conversion between POS and SOP**

Conversion between the two forms is done by application of DeMorgans Laws.

**✦ Simplification**

As with any other form of algebra you have encountered, simplification of expressions can be

performed with Boolean algebra.

#### ❖ Example

Show that  $X.Y.Z' + X'.Y.Z' + Y.Z = Y$

$$X.Y.Z' + X'.Y.Z' + Y.Z = Y.Z' + Y.Z = Y$$

#### ❖ Example

Show that  $(X.Y' + Z).(X + Y).Z = X.Z + Y.Z$

$$\begin{aligned} &(X.Y' + Z).(X + Y).Z \\ &= (X.Y' + Z.X + Y'.Z).Z \\ &= X.Y'Z + Z.X + Y'.Z \\ &= Z.(X.Y' + X + Y') \\ &= Z.(X+Y') \end{aligned}$$

## Logic Circuits

Boolean algebra is ideal for expressing the behavior of logic circuits.

A circuit can be expressed as a logic design and implemented as a collection of individual connected logic gates.

### ❖ Fixed Logic Systems

A fixed logic system has two possible choices for representing true and false.

#### ✦ Positive Logic

In a positive logic system, a high voltage is used to represent logical true (1), and a low voltage for a logical false (0).

#### ✦ Negative Logic

In a negative logic system, a low voltage is used to




represent logical true (1), and a high voltage for a logical false (0).

In positive logic circuits it is normal to use +5V for true and 0V for false.


## Switching Circuits

The abstract logic described previously can be implemented as an actual circuit. Switches are left open for logic 0 and closed for logic 1.


### Two variable AND circuit X.Y

 

### Two variable OR circuit X + Y

 

### Four variable circuit U.V.(X + Y)

 


### Truth Table

A truth table is a means for describing how a logic circuit's

output depends on the logic levels present at the circuit's inputs.

 In the following twos-inputs logic circuit, the table lists all possible combinations of logic levels present at inputs X and Y along with the corresponding output level F.



X	Y	F = X*Y
0	0	0
0	1	0
1	0	0
1	1	1

When either input X AND Y is 1, the output F is 1. Therefore the "?" in the box is an AND gate.

## Logic Gates

A logic gate is an electronic circuit/device which makes the logical decisions. To arrive at this decisions, the most common logic gates used are OR, AND, NOT, NAND, and NOR gates. The NAND and NOR gates are called universal gates. The exclusive-OR gate is another logic gate which can be constructed using AND, OR and NOT gate.


Logic gates have one or more inputs and only one output. The output is active only for certain input combinations. Logic gates are the building blocks of any digital circuit. Logic gates are also called switches. With the advent of integrated circuits, switches have been replaced by TTL (Transistor Transistor Logic) circuits and CMOS circuits. Here I give example circuits on how to construct simples gates.

Symbolic Logic

Boolean algebra derives its name from the mathematician George Boole. Symbolic Logic uses values, variables and operations.
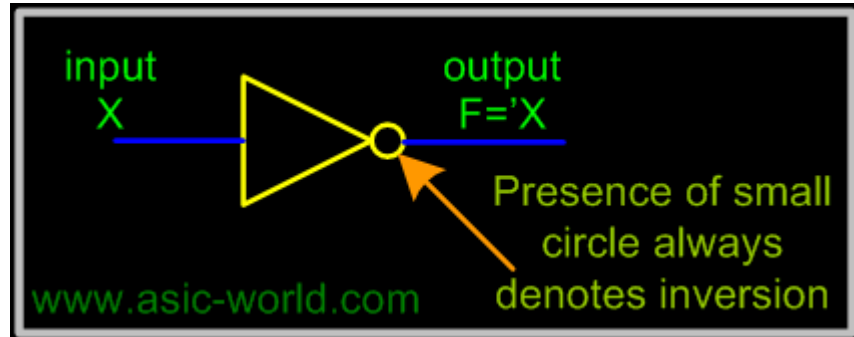
## ❖ Inversion

A small circle on an input or an output indicates inversion. See the NOT, NAND and NOR gates given below for examples.



## ❖ Multiple Input Gates

Given commutative and associative laws, many logic gates can be implemented with more than two inputs, and for reasons of space in circuits, usually multiple input, complex gates are made. You will encounter such gates in real world (maybe you could analyze an ASIC lib to find this).

## ❖ Gates Types


- AND
- OR
- NOT
- BUF
- NAND
- NOR
- XOR
- XNOR

## Universal Gates


Universal gates are the ones which can be used for implementing any gate like AND, OR and NOT, or any combination of these basic gates; NAND and NOR gates are universal gates. But there are some rules that need to be followed when implementing NAND or NOR based gates.

To facilitate the conversion to NAND and NOR logic, we have two new graphic symbols for these gates.

### NAND Gate

 

### NOR Gate

 


### Realization of logic function using NAND gates

Any logic function can be implemented using NAND gates. To achieve this, first the logic function has to be written in Sum of Product (SOP) form. Once logic function is converted to SOP, then it is very easy to implement using NAND gates. In other words any logic circuit with AND gates in first level and OR gates in second level can be converted into a NAND-NAND gate circuit.

Consider the following SOP expression


$$F = W.X.Y + X.Y.Z + Y.Z.W$$

 The above expression can be implemented with three AND gates in first stage and one OR gate in second stage as shown in figure.




If bubbles are introduced at AND gates output and OR gates inputs (the same for

 NOR gates), the above circuit becomes as shown in figure.



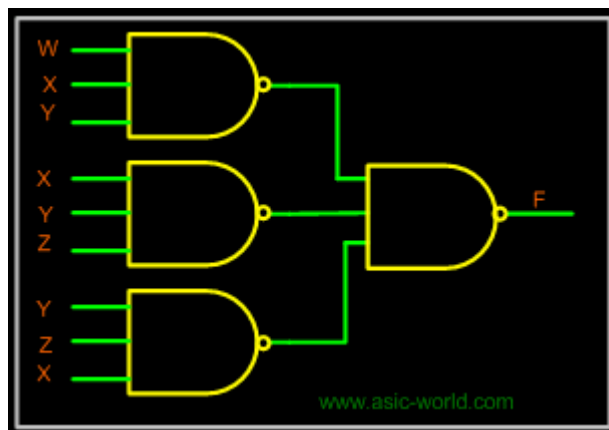Now replace OR gate with input bubble with the NAND gate. Now we have circuit which is fully implemented with just NAND gates.



❖ Realization of logic gates using NAND gates


❖ Implementing an inverter using NAND gate

Input	Output	Rule
$(X.X)'$	$= X'$	Idempotent




❖ Implementing AND using NAND gates

Input	Output	Rule
$((XY)'(XY))'$	$= ((XY))'$	Idempotent
	$= (XY)$	Involution

 


✦ Implementing OR using NAND gates

Input	Output	Rule
$((XX)'(YY))'$	$= (X'Y)'$	Idempotent
	$= X''+Y''$	DeMorgan
	$= X+Y$	Involution

 

Implementing NOR using NAND gates

Input	Output	Rule
$((XX)'(YY))'$	$= (X'Y)'$	Idempotent
	$= X''+Y''$	DeMorgan
	$= X+Y$	Involution
	$= (X+Y)'$	Idempotent

 

✦ Realization of logic function using NOR gates


Any logic function can be implemented using NOR gates. To

achieve this, first the logic function has to be written in Product of Sum (POS) form. Once it is converted to POS, then it's very easy to implement using NOR gate. In other words any logic circuit with OR gates in first level and AND gates in second level can be converted into a NOR-NOR gate circuit.


Consider the following POS expression

$$F = (X+Y) \cdot (Y+Z)$$

 
The above expression can be implemented with three OR gates in first stage and one AND gate in second stage as shown in figure.



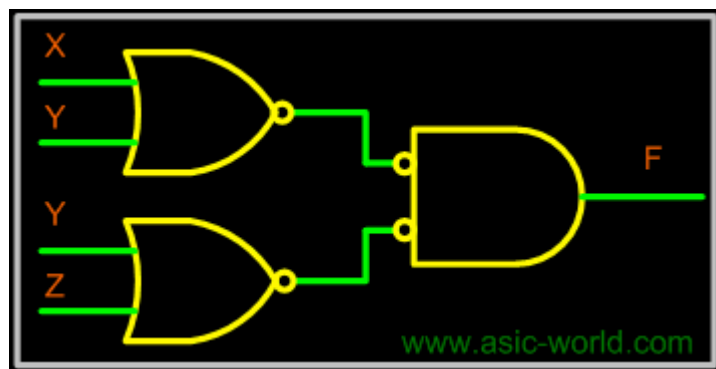If bubble are introduced at the output of the OR gates and the inputs of AND gate, the above circuit becomes as shown in figure.



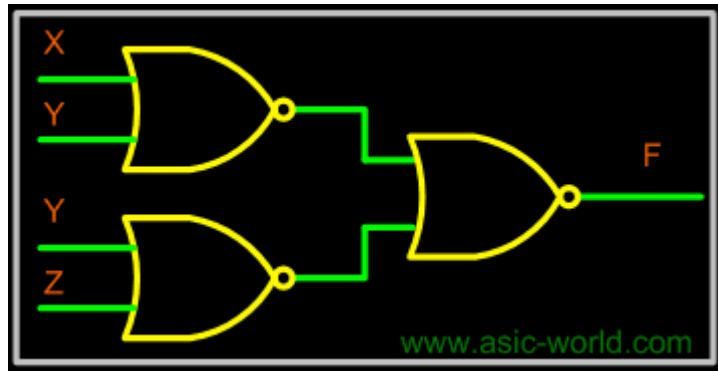
Now replace AND gate with input bubble with the NOR gate. Now we have circuit which is fully implemented with just NOR gates.



◆ Realization of logic gates using NOR gates


◆ Implementing an inverter using NOR gate

Input	Output	Rule
$(X+X)'$	$= X'$	Idempotent

 

◆ Implementing AND using NOR gates

Input	Output	Rule
$((X+X)'+(Y+Y))'$	$= (X'+Y)'$	Idempotent
	$= X'' \cdot Y''$	DeMorgan
	$= (X \cdot Y)$	Involution

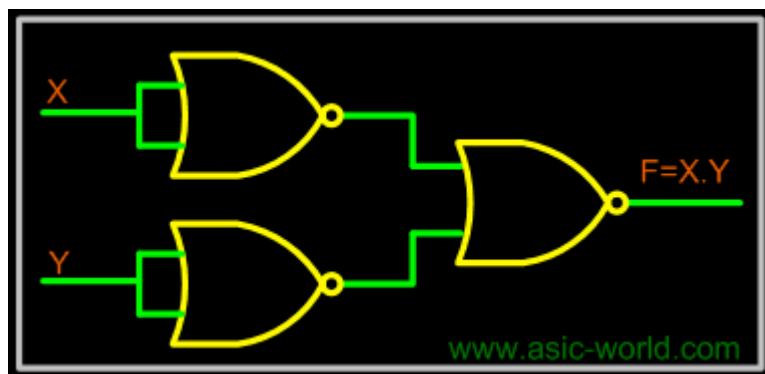


◆ Implementing OR using NOR gates

Input	Output	Rule
$((X+Y)'+(X+Y))'$	$= ((X+Y))'$	Idempotent




$= X+Y$       Involution

 

◆ Implementing NAND using NOR gates

Input	Output	Rule
$((X+Y)' + (X+Y)')$	$((X+Y)')$	Idempotent
	$= X+Y$	Involution
	$= (X+Y)'$	Idempotent

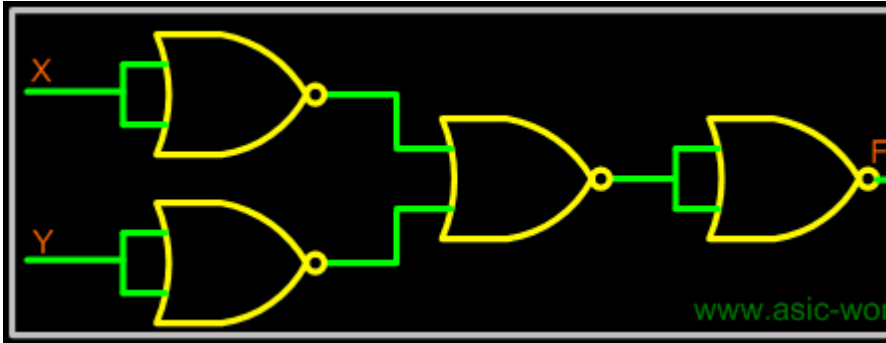

Introduction

Simplification of Boolean functions is mainly used to reduce the gate count of a design. Less number of gates means less power consumption, sometimes the circuit works faster and also when number of gates is reduced, cost also comes down.

There are many ways to simplify a logic design, some of them are given below. We will be looking at each of these in detail in the next few pages.

- Algebraic Simplification.
- ->Simplify symbolically using theorems/postulates.
- ->Requires good skills

- Karnaugh Maps.
- ->Diagrammatic technique using 'Venn-like diagram'.
- ->Limited to no more than 6 variables.

We have already seen how Algebraic Simplification works, so lets concentrate on Karnaugh Maps or simply k-maps.

## Karnaugh Maps

Karnaugh maps provide a systematic method to obtain simplified sum-of-products (SOPs) Boolean expressions. This is a compact way of representing a truth table and is a technique that is used to simplify logic expressions. It is ideally suited for four or less variables, becoming cumbersome for five or more variables. Each square represents either a minterm or maxterm. A K-map of  $n$  variables will have  $2^n$  squares. For a Boolean expression, product terms are denoted by 1's, while sum terms are denoted by 0's - but 0's are often left blank.

A K-map consists of a grid of squares, each square representing one canonical minterm combination of the variables or their inverse. The map is arranged so that squares representing minterms which differ by only one variable are adjacent both vertically and horizontally. Therefore  $XY'Z'$  would be adjacent to  $X'Y'Z'$  and would also be adjacent to  $XY'Z$  and  $XYZ'$ .

## ❖ Minimization Technique


- Based on the Unifying Theorem:  $X + X' = 1$
- The expression to be minimized should generally be in sum-of-product form (If necessary, the conversion process is applied to create the sum-of-product form).
- The function is mapped onto the K-map by marking a 1 in those squares corresponding to the terms in the expression to be simplified (The other squares may be filled with 0's).
- Pairs of 1's on the map which are adjacent are combined using the theorem  $Y(X+X') = Y$  where Y is any Boolean expression (If two pairs are also adjacent, then these can also be combined using the same theorem).
- The minimization procedure consists of recognizing those pairs and multiple pairs.
- ->These are circled indicating reduced terms.
  - Groups which can be circled are those which have two ( $2^1$ ) 1's, four ( $2^2$ ) 1's, eight ( $2^3$ ) 1's, and so on.
- ->Note that because squares on one edge of the map are considered adjacent to those on the opposite edge, group

can be formed with these squares.

- ->Groups are allowed to overlap.
- The objective is to cover all the 1's on the map in the fewest number of groups and to create the largest groups to do this.
- Once all possible groups have been formed, the corresponding terms are identified.
- ->A group of two 1's eliminates one variable from the original minterm.
- ->A group of four 1's eliminates two variables from the original minterm.
- ->A group of eight 1's eliminates three variables from the original minterm, and so on.
- ->The variables eliminated are those which are different in the original minterms of the group.
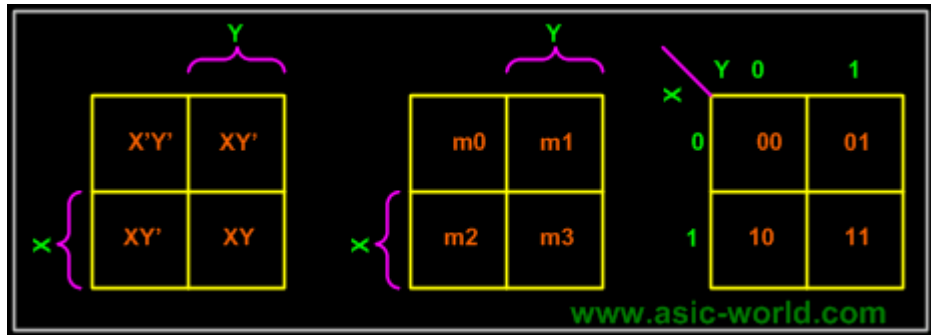
## 2- Variable K-Map


In any K-Map, each square represents a minterm. Adjacent squares always differ by just one literal (So that the unifying theorem may apply:  $X + X' = 1$ ). For the 2-variable case (e.g.: variables X, Y), the map can be drawn as below. Two variable map is the one which has got only two variables as input.



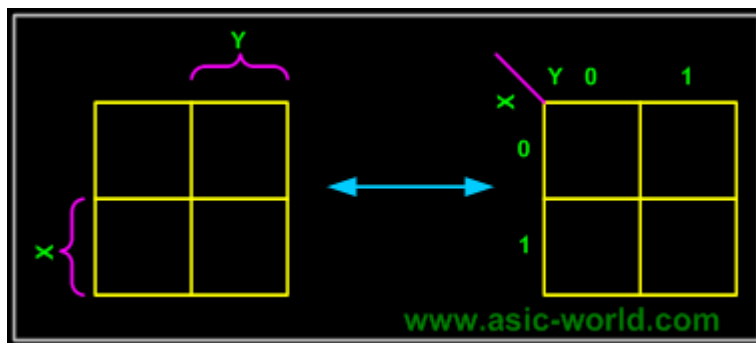
### ◆ Equivalent labeling

K-map needs not follow the ordering as shown in the figure above. What this means is that we can change the position of  $m_0$ ,  $m_1$ ,  $m_2$ ,  $m_3$  of the above figure as shown in the two figures below.

Position assignment is the same as the default k-maps positions. This is the one which we will be using throughout this tutorial.



 This figure is with changed position of  $m_0$ ,  $m_1$ ,  $m_2$ ,  $m_3$ .




The K-map for a function is specified by putting a '1' in the square corresponding to a minterm, a '0' otherwise.

### ◆ Example- Carry and Sum of a half adder

In this example we have the truth table as input, and we have two output functions. Generally we may have  $n$  output functions for  $m$  input variables. Since we have two output functions, we need to draw two k-maps (i.e. one for each function). Truth table of 1 bit adder is shown below. Draw the k-map for Carry and Sum as

shown below.


X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

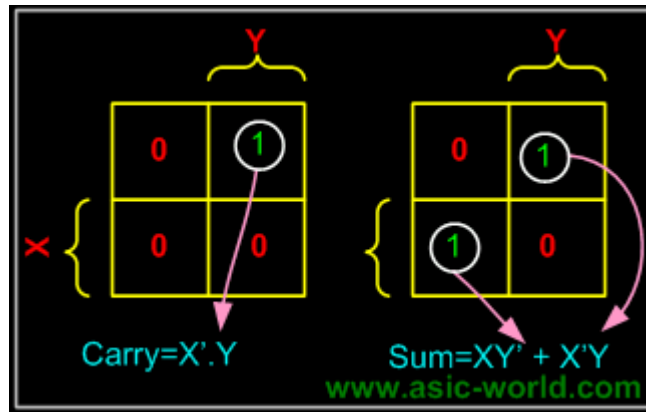
 
#### ❖ Grouping/Circling K-maps



The power of K-maps is in minimizing the terms, K-maps can be minimized with the help of grouping the terms to form single terms. When forming groups of squares, observe/consider the following:

- Every square containing 1 must be considered at least once.
- A square containing 1 can be included in as many groups as desired.
- A group must be as large as possible.




- If a square containing 1 cannot be placed in a group, then leave it out to include in final expression.
- The number of squares in a group must be equal to 2
- , i.e. 2,4,8,.

  - The map is considered to be folded or spherical, therefore squares at the end of a row or column are treated as adjacent squares.
- The simplified logic expression obtained from a K-map is not always unique. Groupings can be made in different ways.
- Before drawing a K-map the logic expression must be in canonical form.



In the next few pages we will see some examples on grouping.


### Example of invalid groups

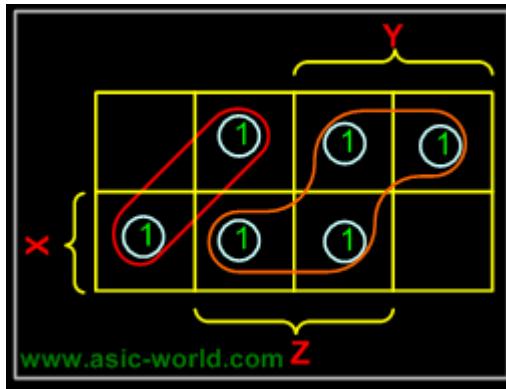

◆ **Example -  $X'Y + XY$**

In this example we have the equation as input, and we have one output function. Draw the k-map for function F with marking 1 for  $X'Y$  and  $XY$  position. Now combine two 1's as shown in figure to form the single term. As you can see X and X' get canceled and only Y remains.


$$F = Y$$

 

◆ **Example -  $X'Y + XY + XY'$**

In this example we have the equation as input, and we have one output function. Draw the k-map for function F with marking 1 for  $X'Y$ ,  $XY$  and  $XY'$  position. Now combine two 1's as shown in figure to form the two single terms.


$$F = X + Y$$

 



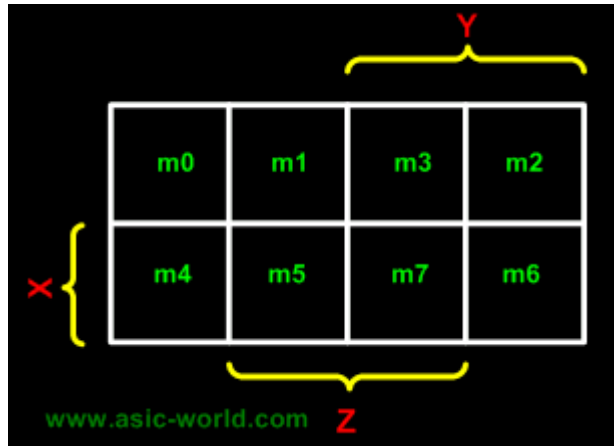
### 3-Variable K-Map

There are 8 minterms for 3 variables (X, Y, Z). Therefore, there are 8 cells in a 3-variable K-map. One important thing to note is that K-maps follow the gray code sequence, not the binary one.




Using gray code arrangement ensures that minterms of adjacent cells differ by only ONE literal. (Other arrangements which satisfy this criterion may also be used.)

 Each cell in a 3-variable K-map has 3 adjacent neighbours. In general, each cell in an n-variable K-map has n adjacent neighbours.




There is wrap-around in the K-map

 - $X'Y'Z'$  (m0) is adjacent to  $X'YZ'$  (m2)
- $XY'Z'$  (m4) is adjacent to  $XYZ'$  (m6)



◆ Example


$$F = XYZ' + XYZ + X'YZ$$

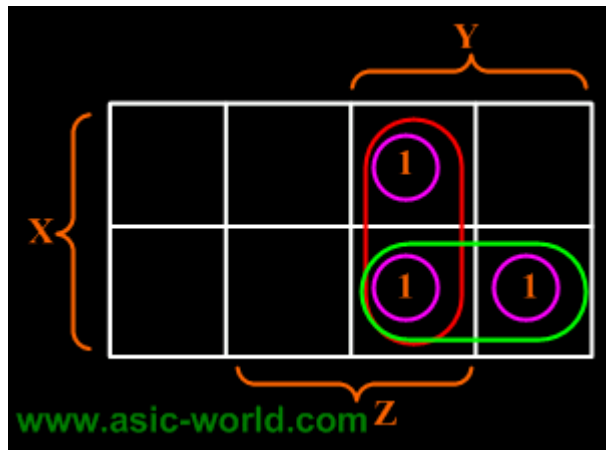

$$F = XY + YZ$$

◆ Example

$$F(X,Y,Z) = \Sigma(1,3,4,5,6,7)$$

 

$$F = X + Z$$

QUINE-McCLUSKEY MINIMIZATION

Quine-McCluskey minimization

method  
uses the  
same  
theorem to  
produce the  
solution as  
the K-map  
method,  
namely  
 $X(Y+Y')=X$

## Minimization Technique

- The expression is represented in the canonical SOP form if not already in that form.
- The function is converted into numeric notation.
- The numbers are converted into binary form.
- The minterms are arranged in a column divided into groups.
- Begin with the minimization procedure.
- -> Each minterm of one group is compared with each minterm in the group immediately below.
- -> Each time a number is found in one group which is the same as a number in the group below except for one digit, the numbers pair is ticked and a new composite is created.
- -> This composite number has the same number of digits as the numbers in the pair except the digit different which is replaced by an "x".
- The above procedure is repeated on the second column to generate a third column.
- The next step is to identify the essential prime implicants, which can be done using a prime implicant chart.

- -> Where a prime implicant covers a minterm, the intersection of the corresponding row and column is marked with a cross.
- -> Those columns with only one cross identify the essential prime implicants. -> These prime implicants must be in the final answer.
- -> The single crosses on a column are circled and all the crosses on the same row are also circled, indicating that these crosses are covered by the prime implicants selected.
- -> Once one cross on a column is circled, all the crosses on that column can be circled since the minterm is now covered.
- -> If any non-essential prime implicant has all its crosses circled, the prime implicant is redundant and need not be considered further.
- Next, a selection must be made from the remaining nonessential prime implicants, by considering how the non-circled crosses can be covered best.
- -> One generally would take those prime implicants which cover the greatest number of crosses on their row.
- -> If all the crosses in one row also occur on another row which includes further crosses, then the latter is said to dominate the former and can be selected.
- -> The dominated prime implicant can then be deleted.

#### ◆ Example

Find the minimal sum of products for the Boolean expression,  $f = \sum$

(1,2,3,7,8,9,10,11,14,15), using Quine-McCluskey method.

Firstly these minterms are represented in the binary form as shown in the table below. The above binary representations are grouped into a number of sections in terms of the number of 1's as shown in the table below.

Binary representation of minterms

Minterms	U	V	W	X
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
14	1	1	1	0
15	1	1	1	1

Group of minterms for different number of 1's

No of 1's	Minterms	U	V	W	X
1	1	0	0	0	1
1	2	0	0	1	0
1	8	1	0	0	0
2	3	0	0	1	1
2	9	1	0	0	1
2	10	1	0	1	0
3	7	0	1	1	1
3	11	1	0	1	1
3	14	1	1	1	0
4	15	1	1	1	1

Any two numbers in these groups which differ from each other by only one variable can be chosen and

combined, to get 2-cell combination, as shown in the table below.

### 2-Cell combinations

Combinations	U	V	W	X
(1,3)	0	0	-	1
(1,9)	-	0	0	1
(2,3)	0	0	1	-
(2,10)	-	0	1	0
(8,9)	1	0	0	-
(8,10)	1	0	-	0
(3,7)	0	-	1	1
(3,11)	-	0	1	1
(9,11)	1	0	-	1
(10,11)	1	0	1	-
(10,14)	1	-	1	0
(7,15)	-	1	1	1
(11,15)	1	-	1	1
(14,15)	1	1	1	-

From the 2-cell combinations, one variable and dash in the same position can be combined to form 4-cell combinations as shown in the figure below.

### 4-Cell combinations

Combinations	U	V	W	X
(1,3,9,11)	-	0	-	1
(2,3,10,11)	-	0	1	-
(8,9,10,11)	1	0	-	-
(3,7,11,15)	-	-	1	1
(10,11,14,15)	1	-	1	-

The cells (1,3) and (9,11) form the same 4-cell combination as the cells (1,9) and (3,11). The order in which the cells are placed in a combination does not have any effect. Thus the (1,3,9,11) combination could be written as (1,9,3,11).

From above 4-cell combination

table, the prime implicants table can be plotted as shown in table below.

### Prime Implicants Table

Prime Implicants	1	2	3	7	8	9	10	11	14	15
(1,3,9,11)	X	-	X	-	-	X	-	X	-	-
(2,3,10,11)	-	X	X	-	-	-	X	X	-	-
(8,9,10,11)	-	-	-	-	X	X	X	X	-	-
(3,7,11,15)	-	-	-	-	-	-	X	X	X	X
-	X	X	-	X	X	-	-	-	X	-

The columns having only one cross mark correspond to essential prime implicants. A yellow cross is used against every essential prime implicant. The prime implicants sum gives the function in its minimal SOP form.


$$Y = V'X + V'W + UV' + WX + UW$$

## Decoders

A decoder is a multiple-input, multiple-output logic circuit that converts coded inputs into coded outputs, where the input and output codes are different; e.g. n-to-2n, BCD decoders.


Enable inputs must be on for the decoder to function, otherwise its outputs assume a single "disabled" output code word.

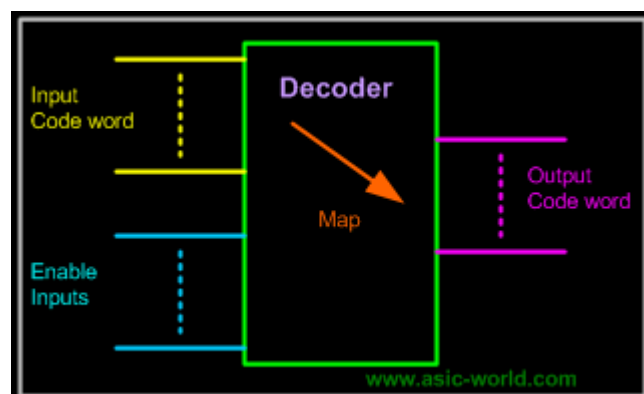Decoding is necessary in applications such as data multiplexing, 7 segment display and memory address decoding. Figure below shows the pseudo block of a decoder.


 
### ❖ Basic Binary Decoder

An AND gate can be used as the basic decoding element, because its output is HIGH only when all its inputs are HIGH. For example, if the input binary number is 0110, then, to make all the inputs to the AND gate HIGH, the two outer bits must be inverted using two inverters as shown in figure below.



### ❖ Binary n-to-2<sup>n</sup> Decoders

A binary decoder has  $n$  inputs and  $2^n$  outputs. Only one output is active at any one time, corresponding to the input value. Figure below shows a representation of Binary n-to- $2^n$  decoder



### Example - 2-to-4 Binary Decoder

A 2 to 4 decoder consists of two inputs and four outputs, truth table and symbols of which is shown below.

**Truth Table**

X	Y	F0	F1	F2	F3
0	0	1	0	0	0
0	1	0	1	0	0



1	0	0	0	1	0
1	1	0	0	0	1


### Symbol



To minimize the above truth table we may use kmap, but doing that you will realize that it is a waste of time. One can directly write down the function for each of the outputs. Thus we can draw the circuit as shown in figure below.

**Note:** Each output is a 2-variable minterm ( $X'Y'$ ,  $X'Y$ ,  $XY'$ ,  $XY$ )

### Circuit

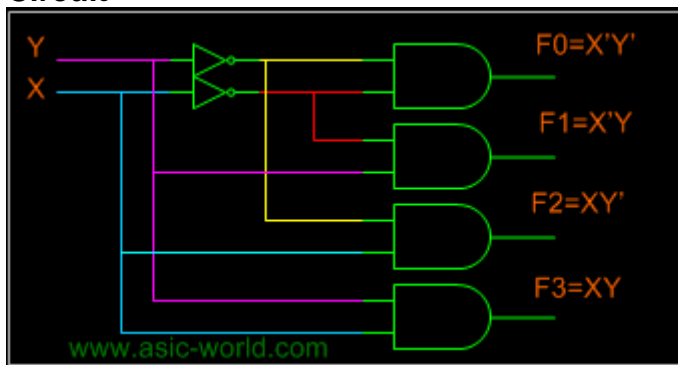

### ◆ Example - 3-to-8 Binary Decoder


A 3 to 8 decoder consists of three inputs and eight outputs, truth table and symbols of which is shown below.

### Truth Table

X	Y	Z	F0	F1	F2	F3	F4	F5	F6	F7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0


1 1 1 0 0 0 0 0 0 0 1

### Symbol

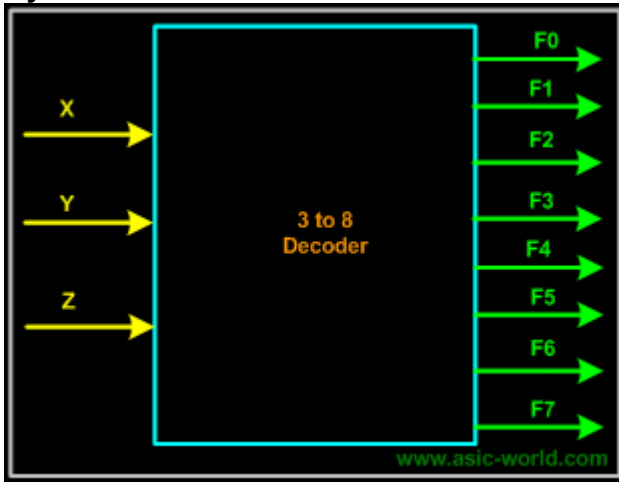

From the truth table we can draw the circuit diagram as shown in figure below.

### Circuit

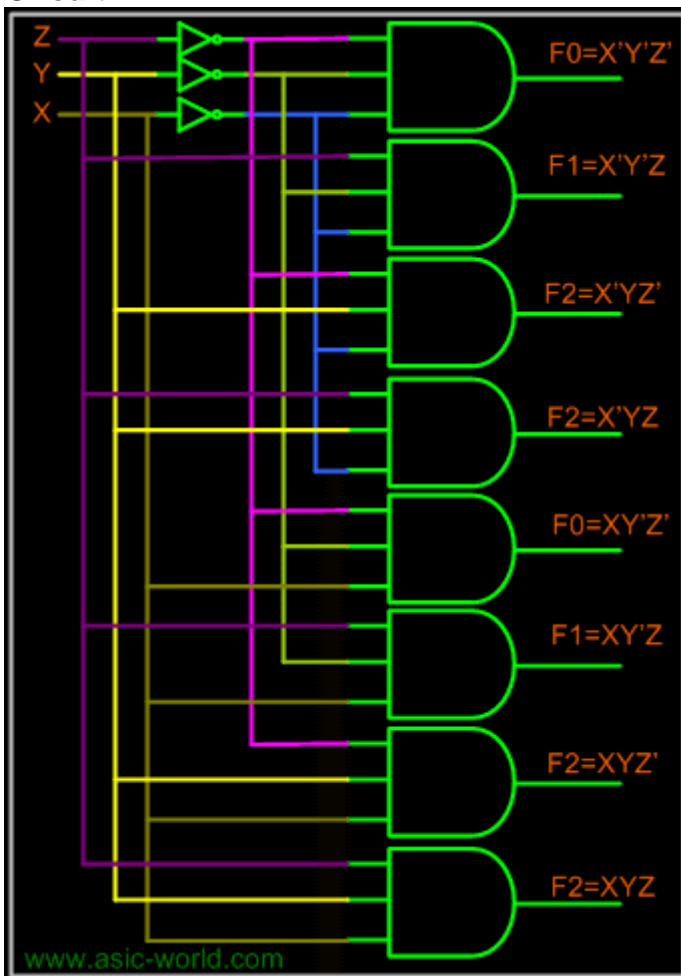

## ❖ Implementing Functions Using Decoders

- Any n-variable logic function, in canonical sum-of-minterms form can be implemented using a single n-to- $2^n$  decoder to generate the minterms, and an OR gate to form the sum.
- ->The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.
- Any combinational circuit with n inputs and m outputs can be implemented with an n-to- $2^n$  decoder with m OR gates.
- Suitable when a circuit has many outputs, and each output function is expressed with few minterms.

## Introduction

Arithmetic circuits are the ones which perform arithmetic operations like addition, subtraction, multiplication, division, parity calculation. Most of the time, designing these circuits is the same as designing muxers, encoders and decoders.

In the next few pages we will see few of these circuits in detail.

## Adders

Adders are the basic building blocks of all arithmetic circuits; adders add two binary numbers and give out sum and carry as output. Basically we have two types of adders.

- Half Adder.
- Full Adder.


## Half Adder

Adding two single-bit binary values X, Y produces a sum S bit and a carry out C-out bit. This operation is called half addition and the circuit to realize it is called a half adder.

### Truth Table

X	Y	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### Symbol

 

$$S(X,Y) = \Sigma(1,2)$$


$$S = X'Y + XY'$$

$$S = X \oplus Y$$

$$CARRY(X,Y) = \Sigma(3)$$

$$CARRY = XY$$

### Circuit

 

### Full Adder

Full adder takes a three-bit input. Adding two single-bit binary values X, Y with a carry input bit C-in produces a sum bit S and a carry out C-out bit.

### Truth Table


X	Y	Z	SUM	CARRY
0	0	0	0	0

0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM } (X,Y,Z) = \Sigma(1,2,4,7)$$

$$\text{CARRY } (X,Y,Z) = \Sigma(3,5,6,7)$$


### Kmap-SUM

 

$$\text{SUM} = X'Y'Z + XY'Z' + X'YZ'$$

$$\text{SUM} = X \oplus Y \oplus Z$$

### Kmap-CARRY

 


$$\text{CARRY} = XY + XZ + YZ$$


### ✦ Full Adder using AND-OR

The below implementation shows implementing the full adder with AND-OR gates, instead of using XOR gates. The basis of the circuit below is from the above Kmap.

### Circuit-SUM

 


Circuit-CARRY

 


◆ Full Adder using AND-OR

Circuit-SUM

 

Circuit-CARRY

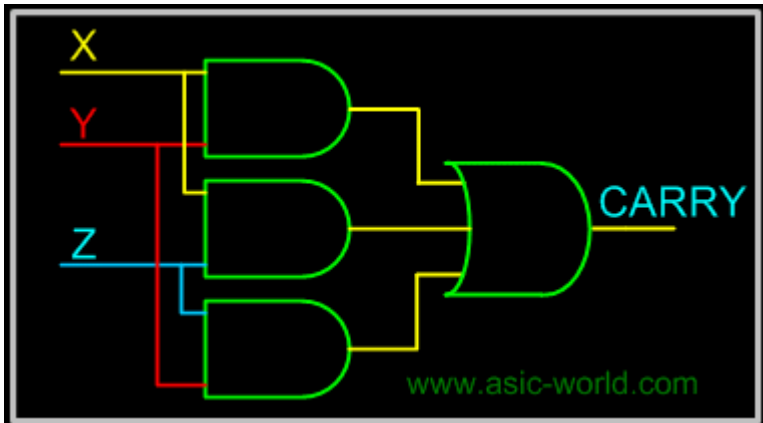

## ◆ Example - Full adder

### Equation

$$S(x, y, z) = \Sigma(1,2,4,7)$$


$$C(x, y, z) = \Sigma(3,5,6,7)$$

### Truth Table

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

From the truth table we know the values for which the sum (s) is active and also the carry (c) is active. Thus we have the equation as shown above and a circuit can be drawn as shown below from the equation derived.

### Circuit

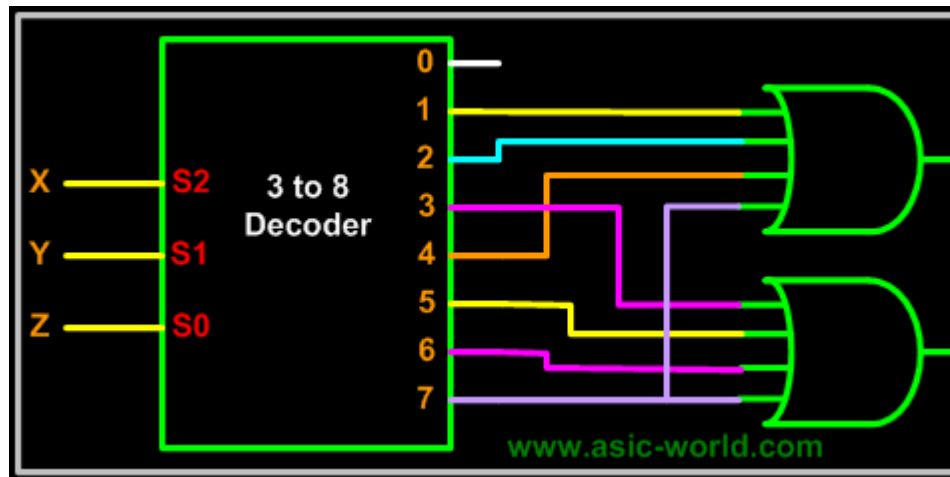

## Encoders

An encoder is a combinational circuit that performs the inverse operation of a decoder. If a device output code has fewer bits than the input code has, the device is usually called an encoder. e.g.  $2^n$ -to-n, priority encoders.

The simplest encoder is a  $2^n$ -to-n binary encoder, where it has only one of  $2^n$  inputs = 1 and the output is the n-bit binary number corresponding to the active input.



### Example - Octal-to-Binary Encoder

Octal-to-Binary take 8 inputs and provides 3 outputs, thus doing the opposite of what the 3-to-8 decoder does. At any one time, only one input line has a value of 1. The figure below shows the truth table of an Octal-to-binary encoder.

#### Truth Table

I0	I1	I2	I3	I4	I5	I6	I7	Y2	Y1	Y0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

For an 8-to-3 binary encoder with inputs I0-I7 the logic expressions of the outputs Y0-Y2 are:

$$Y0 = I1 + I3 + I5 + I7$$


$$Y1 = I2 + I3 + I6 + I7$$

$$Y2 = I4 + I5 + I6 + I7$$

Based on the above equations, we can draw the circuit as shown below

#### Circuit



 

**Example -  
Decimal-to-Binary  
Encoder**

Decimal-to-Binary take 10 inputs and provides 4 outputs, thus doing the opposite of what the 4-to-10 decoder does. At any one time, only one input line has a value of 1. The figure below shows the truth table of a Decimal-to-binary encoder.

**Truth Table**

I0	I1	I2	I3	I4	I5	I6	I7	I8	I9	Y3	Y2	Y1	Y0
1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1

From the above truth table , we can derive the functions Y3, Y2, Y1 and Y0 as given below.

$$Y3 = I8 + I9$$

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_0 = I_1 + I_3 + I_5 + I_7 + I_9$$

### Priority Encoder

If we look carefully at the Encoder circuits that we got, we see the following limitations. If more than two inputs are active simultaneously, the output is unpredictable or rather it is not what we expect it to be.

This ambiguity is resolved if priority is established so that only one input is encoded, no matter how many inputs are active at a given point of time.

The priority encoder includes a priority function. The operation of the priority encoder is such that if two or more inputs are active at the same time, the input having the highest priority will take precedence.

### Example - 4to3 Priority Encoder

The truth table of a 4-input priority encoder is as shown below. The input D3 has the highest priority, D2 has next highest priority, D0 has the lowest priority. This means output Y2 and Y1 are 0 only when none of the inputs D1, D2, D3 are high and only D0 is high.


A 4 to 3 encoder consists of four inputs and three outputs, truth table and symbols of which is shown below.

#### Truth Table


D3	D2	D1	D0	Y2	Y1	Y0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	x	0	1	0
0	1	x	x	0	1	1
1	x	x	x	1	0	0

Now that we have the truth table, we can draw the Kmaps as shown below.

#### Kmaps

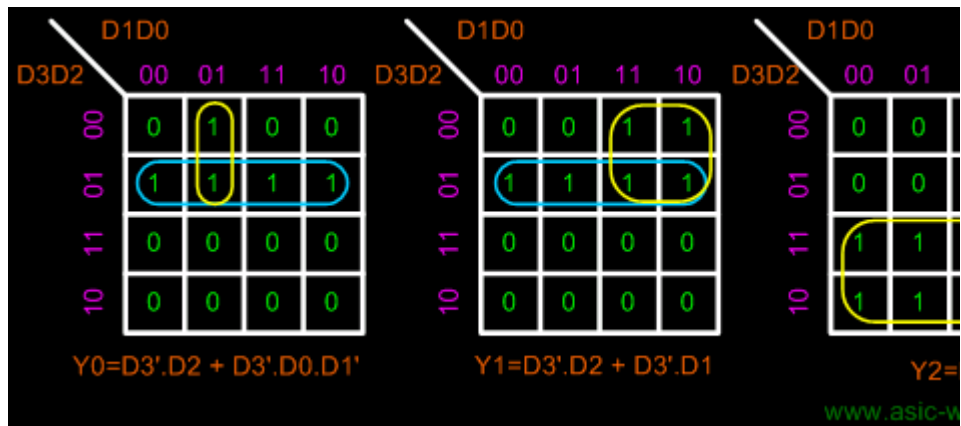

 
From the Kmap we can draw the circuit as shown below. For Y2, we connect directly to D3.



We can apply the same logic to get higher order priority encoders.
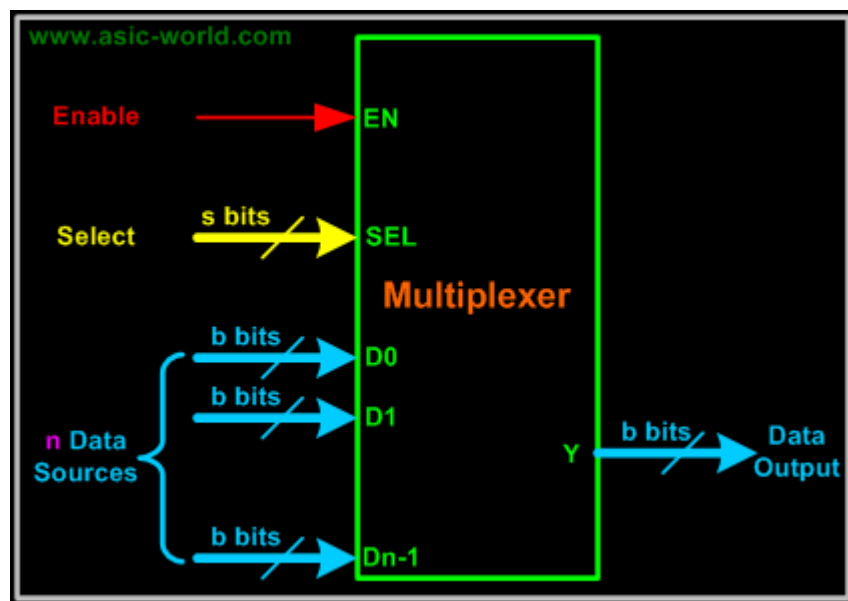
### Multiplexer

A multiplexer (MUX) is a digital switch which connects data from one of  $n$  sources to the output. A number of select inputs determine which data source is connected to the output. The block diagram of MUX with  $n$  data sources of  $b$  bits wide and  $s$  bits wide select line is shown in below figure.



MUX acts like a digitally controlled multi-position switch where the binary code applied to the select inputs controls the input source that will be switched on to the output as shown in the figure below. At any given point of time only one input gets selected and is connected to output, based on the select input signal.

**❖ Mechanical Equivalent of a Multiplexer**


The operation of a multiplexer can be better explained using a mechanical switch as shown in the figure below. This rotary switch can touch any of the inputs, which is connected to the output. As you can see at any given point of time only one input gets transferred to output.



**❖ Example - 2x1 MUX**

A 2 to 1 line multiplexer is shown in figure below, each 2 input lines A to B is applied to one input of an AND gate. Selection lines S are decoded to select a particular AND gate. The truth table for the 2:1 mux is given in the table below.

**Symbol**

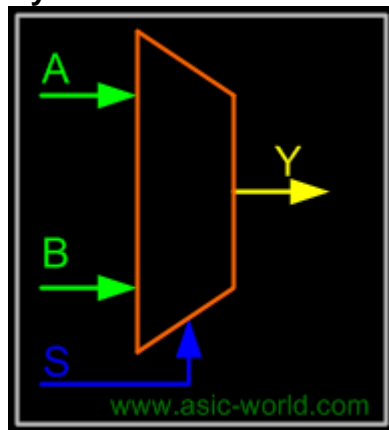

**Truth Table**

S	Y
0	A
1	B

**Design of a**

## 2:1 Mux

To derive the gate level implementation of 2:1 mux we need to have truth table as shown in figure. And once we have the truth table, we can draw the K-map as shown in figure for all the cases when Y is equal to '1'.


Combining the two 1' as shown in figure, we can derive the output y as shown below

$$Y = A.S' + B.S$$


### Truth Table

B	A	S	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

### Kmap

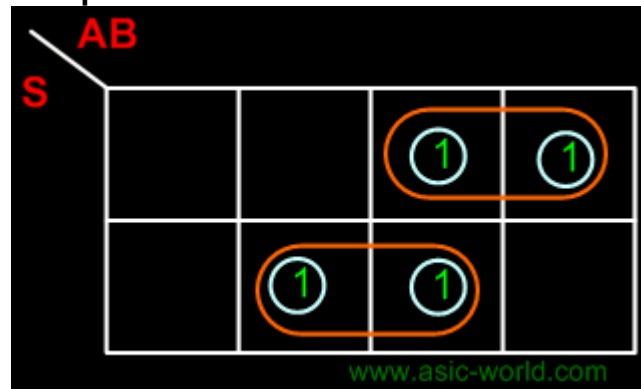


### Circuit

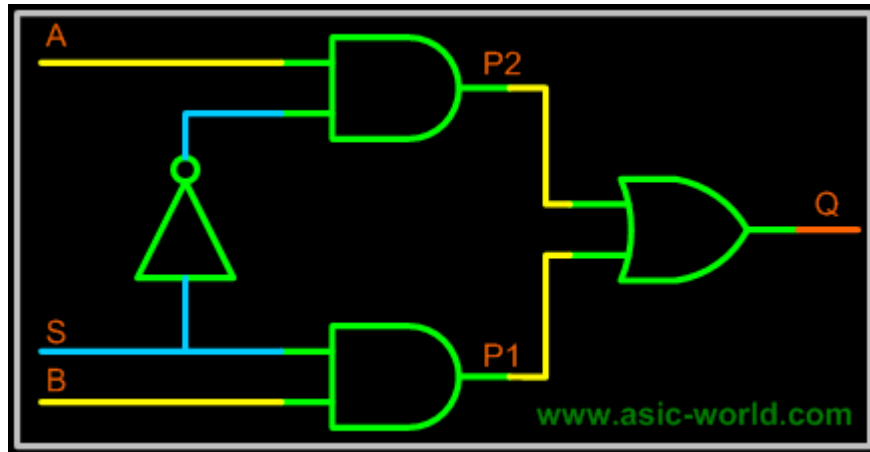

**Example : 4:1 MUX**

A 4 to 1 line multiplexer is shown in figure below, each of 4 input lines I<sub>0</sub> to I<sub>3</sub> is applied to one input of an AND gate. Selection lines S<sub>0</sub> and S<sub>1</sub> are decoded to select a particular AND gate. The truth table for the 4:1 mux is given in the table below.


**Symbol**

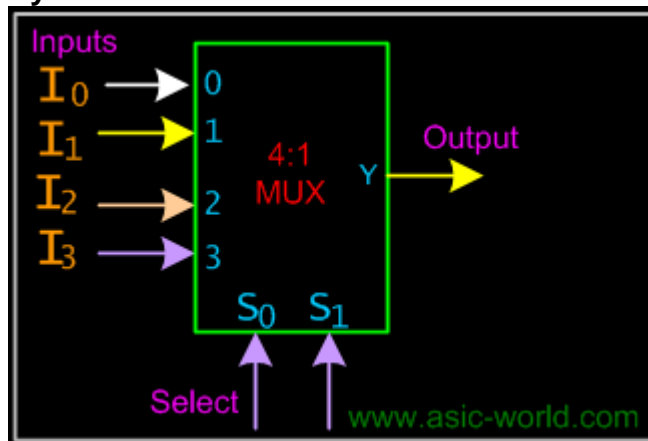

**Truth Table**

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>

**Circuit**

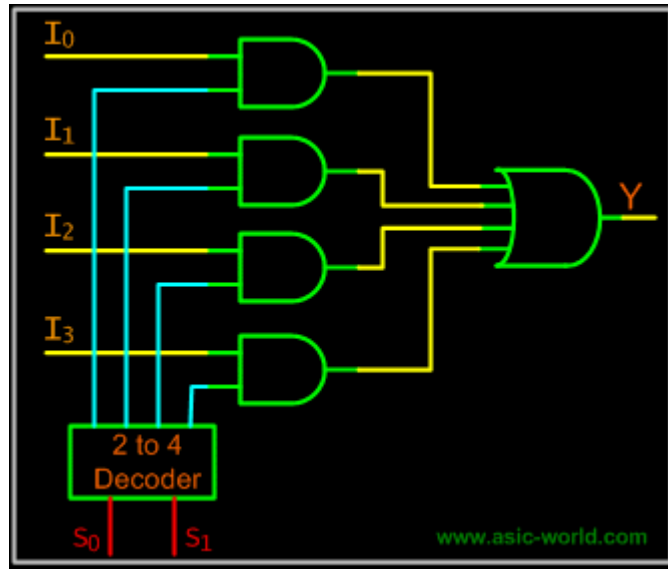

### ❖ Larger Multiplexers


Larger multiplexers can be constructed from smaller ones. An 8-to-1 multiplexer can be constructed from smaller multiplexers as shown below.

### ❖ Example - 8-to-1 multiplexer from Smaller MUX


Truth Table

S2	S1	S0	F
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

Circuit

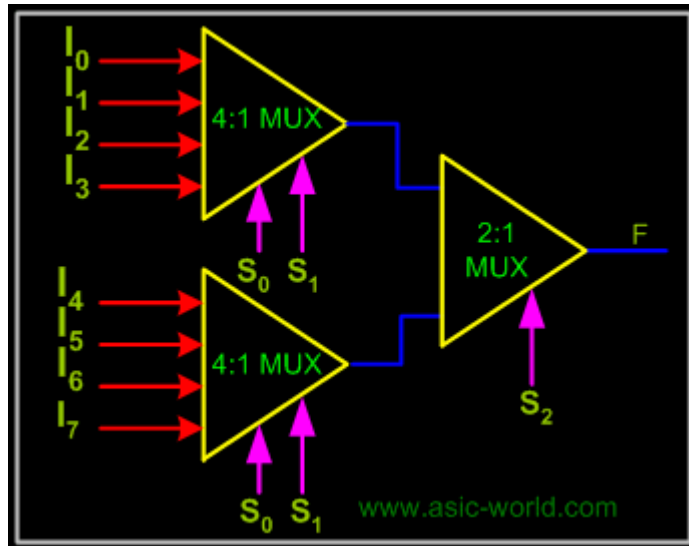

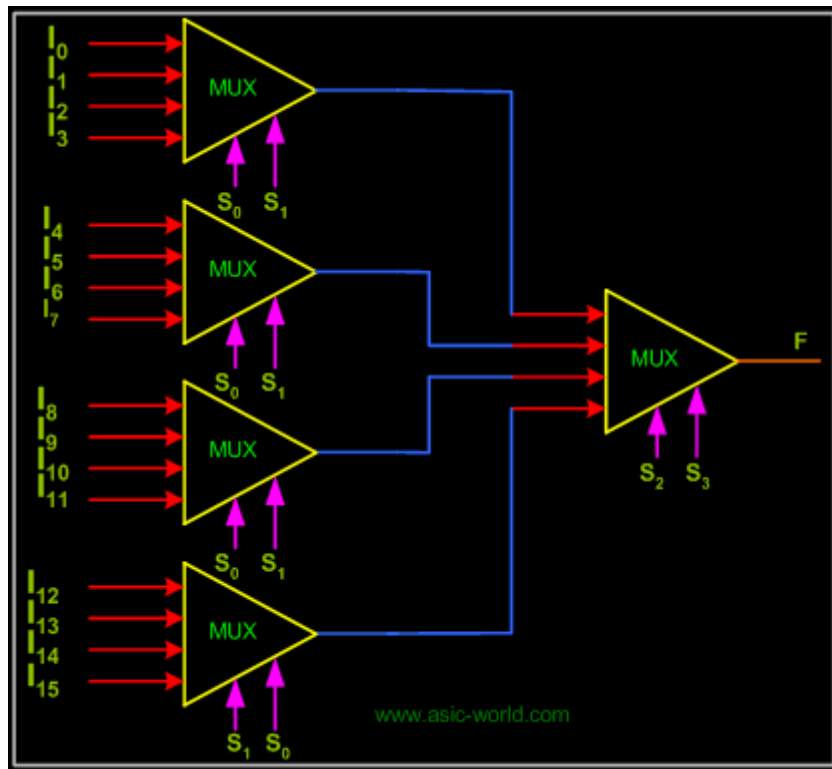◆ Example - 16-to-1 multiplexer from 4:1 mux



**De-multiplexers**

They are digital switches which connect data from one input source to one of n outputs.


Usually implemented by using n-to-2<sup>n</sup> binary decoders where the decoder enable line is used for data input of the de-multiplexer.




The figure below shows a de-multiplexer block diagram which has got s-bits-wide select input, one b-bits-wide data input and n b-bits-wide outputs.

 **Mechanical Equivalent of a De-Multiplexer**

The operation of a de-multiplexer can be better explained using a mechanical switch as shown in the figure below. This rotary switch can touch any of the outputs, which is connected to the input. As you can see at any given point of time only one output gets connected to input.




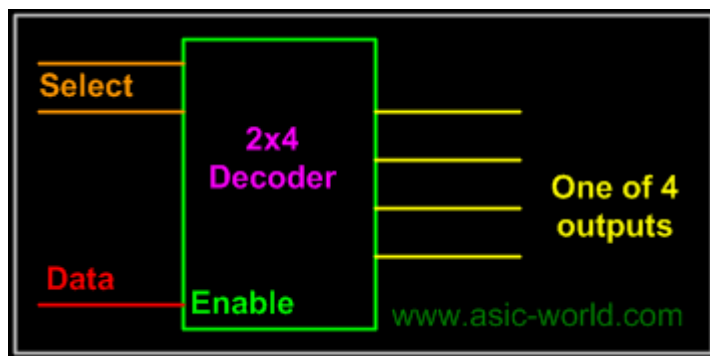1-bit 4-output de-multiplexer using a 2x4 binary decoder.



**Example: 1-to-4 De-multiplexer**

Symbol

 

Truth Table

S1	S0	F0	F1	F2	F3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

## Boolean Function Implementation

Earlier we had seen that it is possible to implement Boolean functions using decoders. In the same way it is also possible to implement Boolean functions using muxers and de-muxers.

### Implementing Functions Multiplexers

Any n-variable logic function can be implemented using a smaller  $2^{n-1}$ -to-1 multiplexer and a single inverter (e.g 4-to-1 mux to implement 3 variable functions) as follows.

Express function in canonical sum-of-minterms form. Choose n-1 variables as inputs to mux select lines. Construct the truth table for the function, but grouping inputs by selection line values (i.e select lines as most significant inputs).

Determine multiplexer input


line  $i$  values by comparing the remaining input variable and the function  $F$  for the corresponding selection lines value  $i$ .

We have four possible mux input line  $i$  values:

- Connect to 0 if the function is 0 for both values of remaining variable.
- Connect to 1 if the function is 1 for both values of remaining variable.
- Connect to remaining variable if function is equal to the remaining variable.
- Connect to the inverted remaining variable if the function is equal to the remaining variable inverted.

 **Example: 3-variable Function Using 8-to-1 mux**

Implement the function  $F(X,Y,Z) = \Sigma(1,3,5,6)$  using an 8-to-1 mux. Connect the input variables  $X, Y, Z$  to mux select lines. Mux data input lines 1, 3, 5, 6 that correspond to the function minterms are connected to 1. The remaining mux data input lines 0, 2, 4, 7 are connected to 0.



◆ **Example: 3-variable Function Using 4-to-1 mux**


Implement the function  $F(X,Y,Z) = S(0,1,3,6)$  using a single 4-to-1 mux and an inverter. We choose the two most significant inputs X, Y as mux select lines.

Construct truth table.

**Truth Table**

Select i	X	Y	Z	F	Mux Input i
0	0	0	0	1	1
0	0	0	1	1	1
1	0	1	0	0	Z
1	0	1	1	1	Z
2	1	0	0	0	0
2	1	0	1	0	0
3	1	1	0	1	Z'
3	1	1	1	0	Z'


**Circuit**

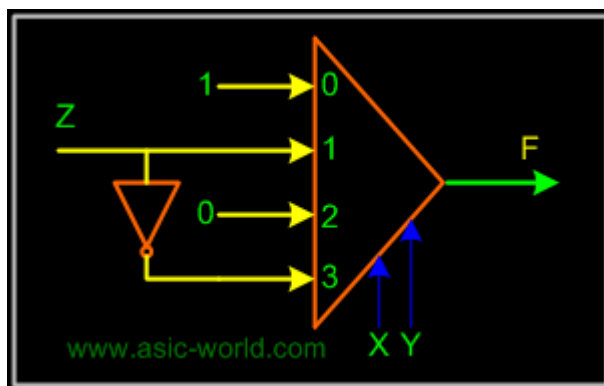

We determine multiplexer input line i values by comparing the remaining input variable Z and the function F for the corresponding selection lines value i


- when  $XY=00$  the function  $F$  is 1 (for both  $Z=0, Z=1$ ) thus mux input0 = 1
- when  $XY=01$  the function  $F$  is  $Z$  thus mux input1 =  $Z$
- when  $XY=10$  the function  $F$  is 0 (for both  $Z=0, Z=1$ ) thus mux input2 = 0
- when  $XY=11$  the function  $F$  is  $Z'$  thus mux input3 =  $Z'$

**Example: 2 to 4 Decoder using Demux**

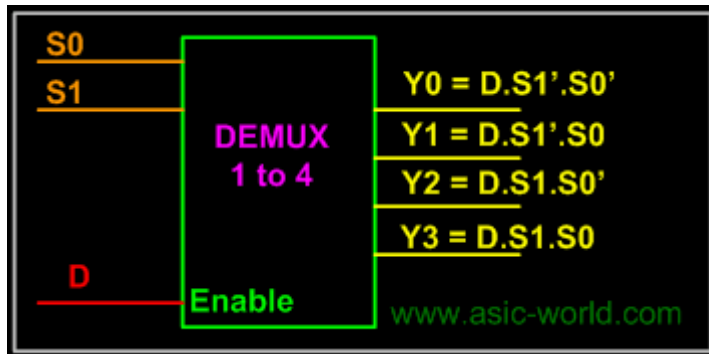

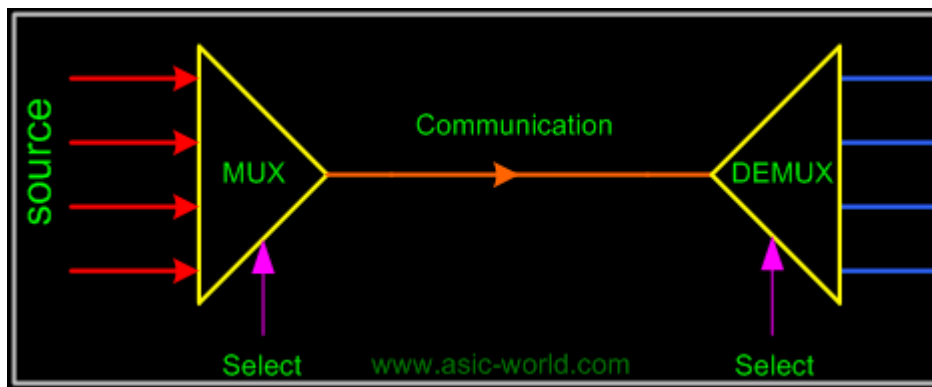**Mux-Demux Application Example**

This enables sharing a single communication line among a number of devices. At any time, only one source and one destination can use the communication line.



**Introduction**

Arithmetic circuits are the ones which perform arithmetic operations like addition, subtraction, multiplication, division, parity calculation. Most of the time, designing these circuits is the same as designing muxers, encoders and decoders.

In the next few pages we will see few of these circuits in detail.

## ● Adders

Adders are the basic building blocks of all arithmetic circuits; adders add two binary numbers and give out sum and carry as output. Basically we have two types of adders.

- Half Adder.
- Full Adder.


## Half Adder

Adding two single-bit binary values X, Y produces a sum S bit and a carry out C-out bit. This operation is called half addition and the circuit to realize it is called a half adder.

### Truth Table

X	Y	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### Symbol

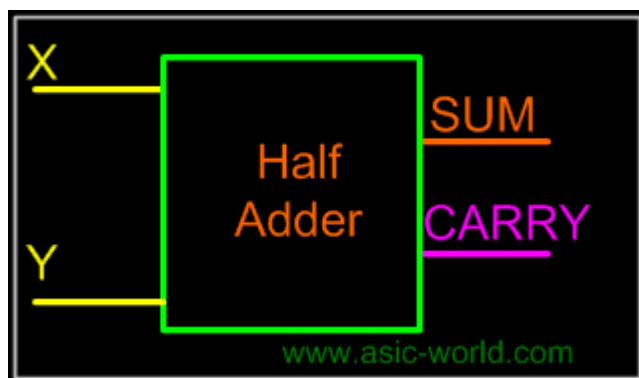

$$S(X,Y) = \Sigma(1,2)$$


$$S = X'Y + XY'$$

$$S = X \oplus Y$$

$$CARRY(X,Y) = \Sigma(3)$$

$$CARRY = XY$$

## Circuit

 

## Full Adder

Full adder takes a three-bit input. Adding two single-bit binary values  $X$ ,  $Y$  with a carry input bit  $C$ -in produces a sum bit  $S$  and a carry out  $C$ -out bit.


### Truth Table

X	Y	Z	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM}(X,Y,Z) = \Sigma(1,2,4,7)$$

$$\text{CARRY}(X,Y,Z) = \Sigma(3,5,6,7)$$


### Kmap-SUM

 

$$\text{SUM} = X'Y'Z + XY'Z' + X'YZ'$$

$$\text{SUM} = X \oplus Y \oplus Z$$

### Kmap-CARRY

 


$$\text{CARRY} = XY + XZ + YZ$$


### Full Adder using AND-OR

The below implementation shows implementing the full adder with AND-OR gates, instead of using XOR gates. The basis of the circuit below is from the above Kmap.

#### Circuit-SUM

 


#### Circuit-CARRY

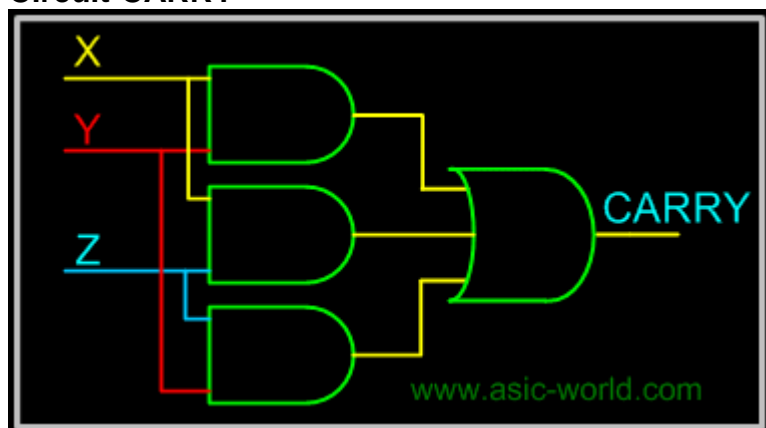


### Full Adder using AND-OR

#### Circuit-SUM



 

**Circuit-CARRY**

 

## Subtractor


Subtractor circuits take two binary numbers as input and subtract one binary number input from the other binary number input. Similar to adders, it gives out two outputs, difference and borrow (carry-in the case of Adder). There are two types of subtractors.

- Half Subtractor.
- Full Subtractor.

### ❖ Half Subtractor

The half-subtractor is a combinational circuit which is used to perform subtraction of two bits. It has two inputs, X (minuend) and Y (subtrahend) and two outputs D (difference) and B (borrow). The logic symbol and truth table are shown below.


#### Symbol

 


**Truth Table**

X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

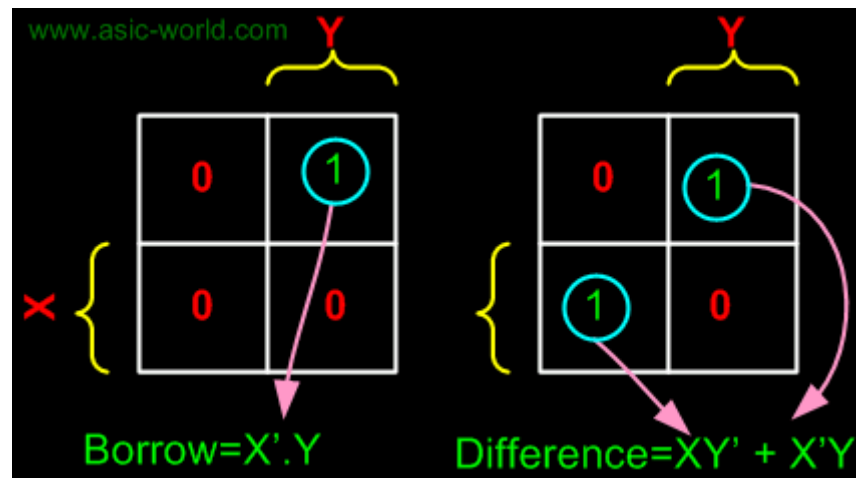From the above table we can draw the Kmap as shown below for "difference" and "borrow". The boolean expression for the difference and Borrow can be written.



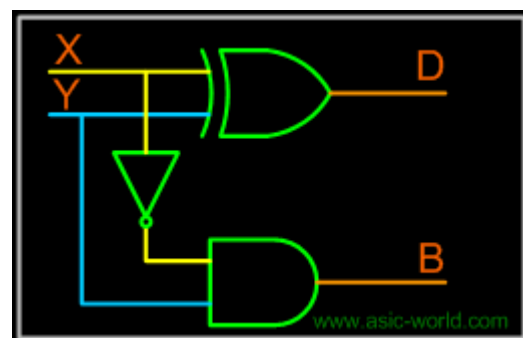
From the equation we can draw the half-subtractor as shown in the figure below.



## Full Subtractor


A full subtractor is a combinational circuit that performs subtraction involving three bits, namely minuend, subtrahend, and borrow-in. The logic symbol and truth table are shown below.

### Symbol

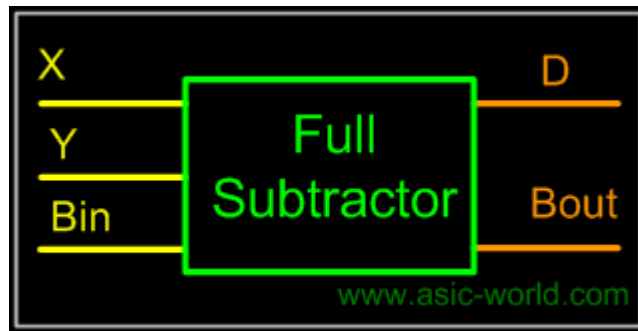

### Truth Table

X	Y	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

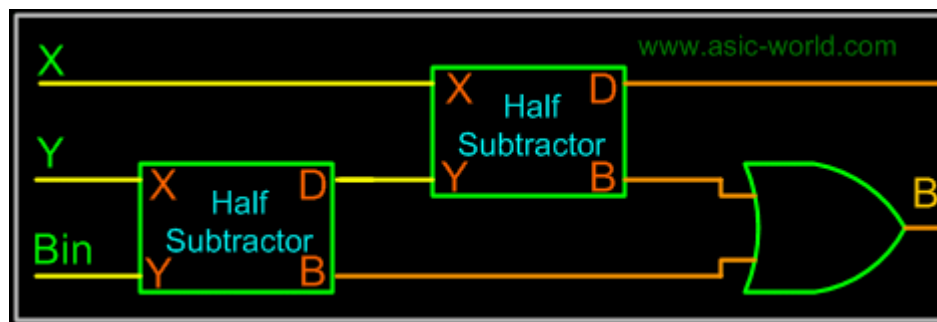


From above table we can draw the Kmap as shown below for "difference" and "borrow". The boolean expression for difference and borrow can be written.


$$\begin{aligned}
 D &= X'Y'Bin + X'YBin' + XY'Bin' + XYBin \\
 &= (X'Y' + XY)Bin + (X'Y + XY')Bin'
 \end{aligned}$$

$$\begin{aligned}
 &= (X \oplus Y)' \text{Bin} + (X \oplus Y) \text{Bin}' \\
 &= X \oplus Y \oplus \text{Bin} \\
 \text{Bout} &= X' \cdot Y + X' \cdot \text{Bin} + Y \cdot \text{Bin}
 \end{aligned}$$

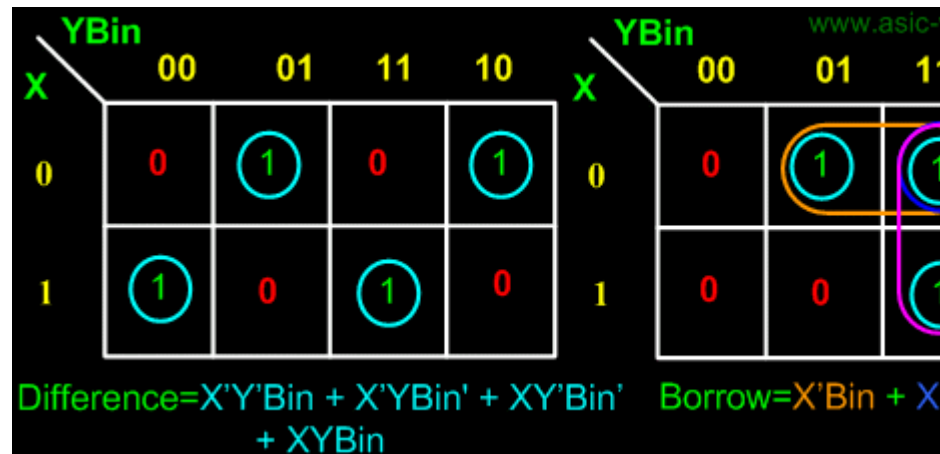From the equation we can draw the half-subtractor as shown in figure below.



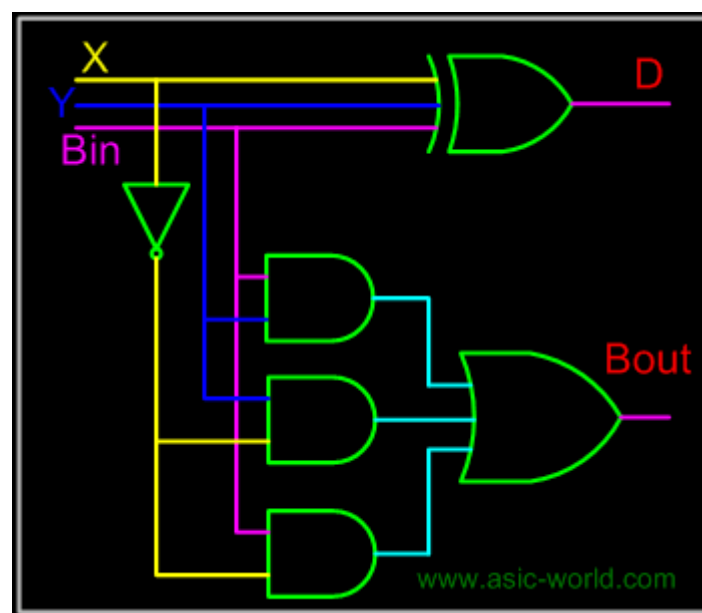From the above expression, we can draw the circuit below. If you look carefully, you will see that a full-subtractor circuit is more or less same as a full-adder with slight modification.




### ❖ Parallel Binary Subtractor

Parallel binary subtractor can be implemented by cascading several full-subtractors. Implementation and associated problems are those of a parallel binary adder, seen before in parallel binary adder section.

Below is the block level representation of a 4-bit parallel binary subtractor, which subtracts 4-bit  $Y_3Y_2Y_1Y_0$  from 4-bit

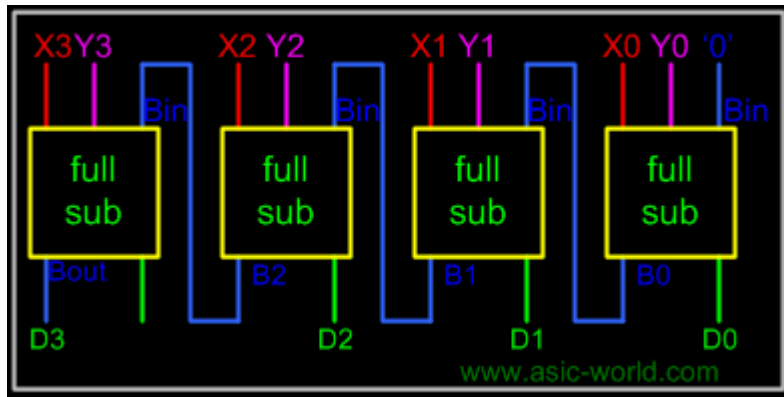
$X_3X_2X_1X_0$ . It has 4-bit difference output  $D_3D_2D_1D_0$  with borrow output  $B_{out}$ .


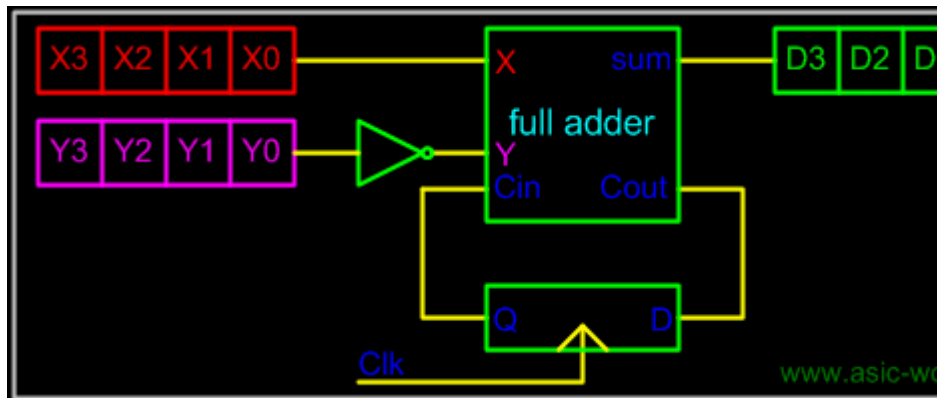
### Serial Binary Subtractor

A serial subtractor can be obtained by converting the serial adder using the 2's complement system. The subtrahend is stored in the Y register and must be 2's complemented before it is added to the minuend stored in the X register.

The circuit for a 4-bit serial subtractor using full-adder is shown in the figure below.



### Comparators

Comparators can compare either a variable number  $X$  ( $x_n x_{n-1} \dots x_3 x_2 x_1$ ) with a predefined constant  $C$  ( $c_n c_{n-1} \dots c_3 c_2 c_1$ ) or two variable numbers  $X$  and  $Y$ . In the first case the implementation reduces to a series of cascaded AND and OR logic gates. If the comparator answers the question ' $X > C$ ?' then its hardware implementation is designed according to the following rules:

- The number  $X$  has two types of binary figures: bits corresponding to '1' in the predefined constant and bits corresponding to '0' in the predefined constant.
- The bits of the number  $X$  corresponding to '1' are supplied to AND gates

- The bits corresponding to '0' are supplied to OR logic gates
- If the least significant bits of the predefined constant are '10' then bit X0 is supplied to the same AND gate as bit X1.

If the least significant bits of the constant are all '1' then the corresponding bits of the number X are not included in the hardware implementation. All other relations between X and C can be transformed in equivalent ones that use the operator '>' and the NOT logic operator as shown in the table below.

Initial relationship to be tested	Equivalent relationship to be implemented
$X < C$	$\text{NOT}(X > C - 1)$
$X \leq C$	$\text{NOT}(X > C)$
$X \geq C$	$X > C - 1$

The comparison process of two positive numbers X and Y is performed in a bit-by-bit manner starting with the most significant bit:


- If the most significant bits are  $X_n = '1'$  and  $Y_n = '0'$  then number X is larger than Y.
- If  $X_n = '0'$  and  $Y_n = '1'$  then number X is smaller than Y.
- If  $X_n = Y_n$  then no decision can be taken about X and Y based only on these two bits.

If the most significant bits are equal then the result of the comparison is determined by the less significant bits  $X_{n-1}$  and  $Y_{n-1}$ . If these bits are equal as well, the process continues with the next pair of bits. If all bits are equal then the two numbers are equal.
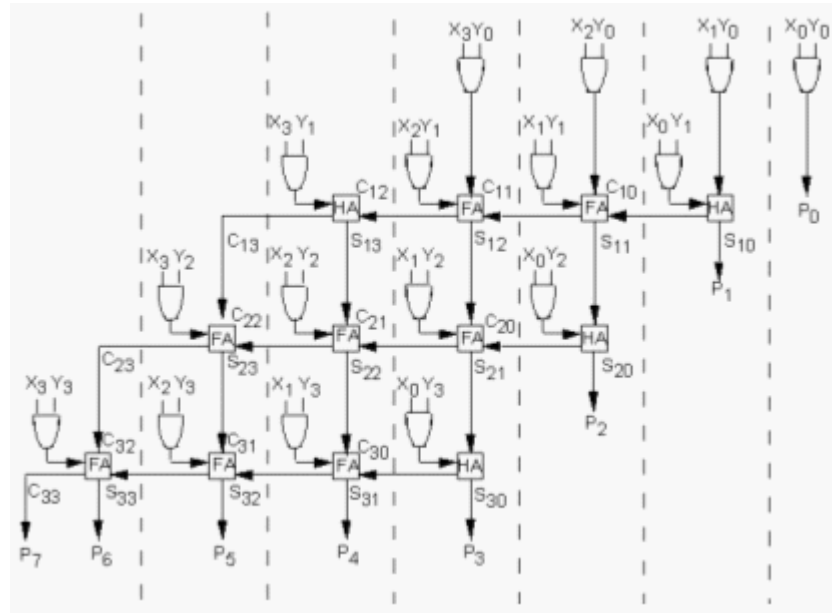
## Multipliers

Multiplication is achieved by adding a list of shifted multiplicands according to the digits of the multiplier. An n-bit X n-bit multiplier can be realized in combinational circuitry by using an array of n-1 n-bit adders where each adder is shifted by one position. For each adder one input is the shifted multiplicand multiplied by 0 or 1 (using AND gates) depending on the multiplier bit, the other input is n partial product bits.

$$\begin{array}{r}
 10011 \times 1001 \\
 \hline
 10011 \\
 00000 \\
 00000 \\
 10011 \\
 \hline
 10101011
 \end{array}$$




## Dividers

The binary divisions are performed in a very similar manner to the decimal divisions, as shown in the below figure examples. Thus, the second number is repeatedly subtracted from the figures of the first number after being multiplied either with '1' or with '0'. The multiplication bit ('1' or '0') is selected for each subtraction step in such a manner that the subtraction result is not negative. The division result is composed from all the successive multiplication bits while the remainder is the result of the last subtraction step.


$$\begin{array}{r}
 1101011 : 101 = 10101 \\
 \underline{101} \times 1 \\
 11 - \\
 \underline{101} \times 0 \\
 110 - \\
 \underline{101} \times 1 \\
 11 - \\
 \underline{101} \times 0 \\
 111 - \\
 \underline{101} \times 1 \\
 10
 \end{array}$$

This algorithm can be implemented by a series of subtractors composed of modified elementary cells. Each subtractor calculates the difference between two input numbers, but if the

result is negative the operation is canceled and replaced with a subtraction by zero. Thus, each divider cell has the normal inputs of a subtracter unit as in the figure below but a supplementary input ('div\_bit') is also present. This input is connected to the b\_req\_out signal generated by the most significant cell of the subtracter. If this signal is '1', the initial subtraction result is negative and it has to be replaced with a subtraction by zero. Inside each divider cell the div\_bit signal controls an equivalent 2:1 multiplexer that selects between bit 'x' and the bit included in the subtraction result X-Y. The complete division can therefore be implemented by a matrix of divider cells connected on rows and columns as shown in figure below. Each row performs one multiplication-and-subtraction cycle where the multiplication bit is supplied by the NOT logic gate at the end of each row. Therefore the NOT logic gates generate the bits of the division result.

 

### ● Parity Circuit

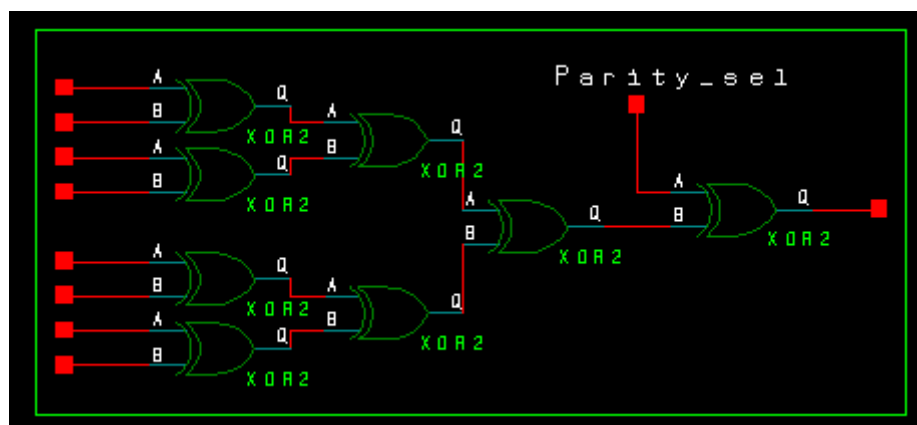

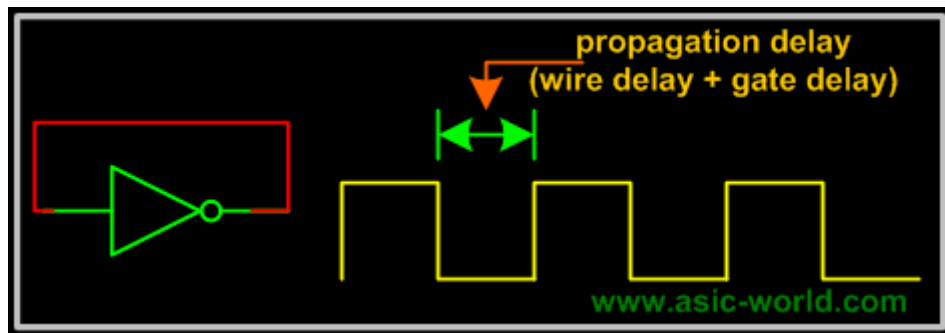
### Concept of Sequential Logic


A sequential circuit as seen in the last page, is combinational logic



with some feedback to maintain its current value, like a memory cell. To understand the basics let's consider the basic feedback logic circuit below, which is a simple NOT gate whose output is connected to its input. The effect is that output oscillates between HIGH and LOW (i.e. 1 and 0). Oscillation frequency depends on gate delay and wire delay. Assuming a wire delay of 0 and a gate delay of 10ns, then oscillation frequency would be (on time + off time = 20ns) 50Mhz.




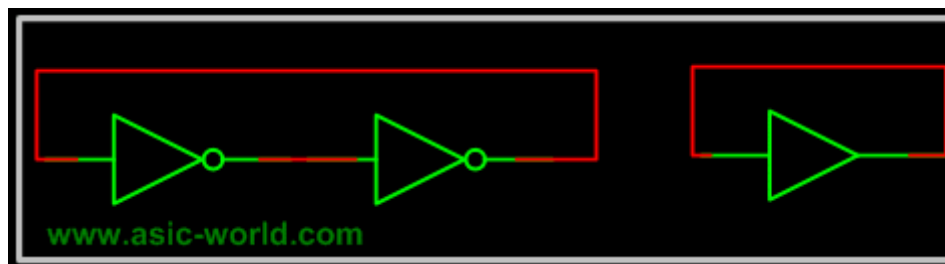The basic idea of having the feedback is to store the value or hold the value, but in the above circuit, output keeps toggling. We can overcome this problem with the circuit below, which is basically cascading two inverters, so that the feedback is in-phase, thus avoids toggling. The equivalent circuit is the same as having a buffer with its output connected to its input.



But there is a problem here too: each gate output value is stable, but what will it be? Or in other words buffer output can not be known. There is no way to tell. If we could know or set the value we would have a simple 1-bit storage/memory element.

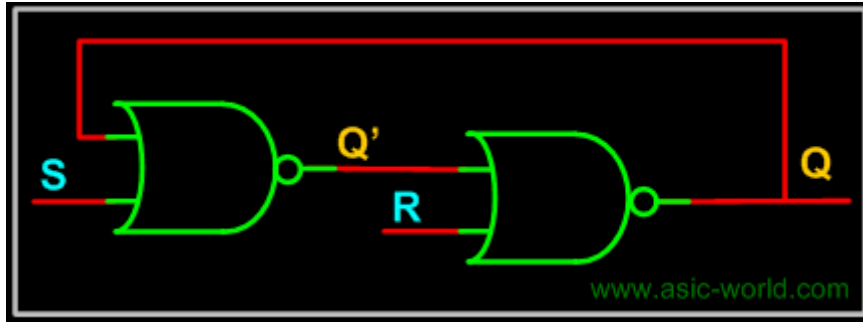The circuit below is the same as the inverters connected back to back with provision to set the state of each gate (NOR gate with both inputs shorted is like a inverter). I am not going to explain the operation, as it is clear from the truth table. **S** is called **set** and **R** is called **Reset**.




S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	X	0
1	0	X	1
1	1	X	0

There still seems to be some problem with the above configuration, we can not control when the input should be sampled, in other words there is no enable signal to control when the input is sampled. Normally input enable signals can be of two types.


- Level Sensitive or ( LATCH)
- Edge Sensitive or (Flip-Flop)

**Level Sensitive:** The circuit below is a modification of the above one to have level sensitive enable input. Enable, when LOW, masks the input S and R. When HIGH, presents S and R to the sequential logic input (the above circuit two NOR Gates). Thus Enable, when HIGH, transfers input S and R to the sequential cell transparently, so this kind of sequential circuits are called **transparent Latch**. The memory element we get is an RS Latch with active high Enable.

 

**Edge Sensitive:** The circuit below is a cascade of two level sensitive memory elements, with a phase shift in the enable input between first memory element and second memory element. The first RS latch (i.e. the first memory element) will be enabled when

 CLK input is HIGH and the second RS latch will be enabled when CLK is LOW. The net effect is input RS is moved to Q and Q' when CLK changes state from HIGH to LOW, this HIGH to LOW transition is called falling edge. So the Edge Sensitive element we get is called negative edge RS flip-flop.



Now that we know the sequential circuits basics, let's look at each of them in detail in accordance to what is taught in colleges. You are always welcome to suggest if this can be written better in any way.

## Latches and Flip-Flops

There are two types types of sequential circuits.


- Asynchronous Circuits.
- Synchronous Circuits.

As seen in last section, Latches and Flip-flops are one and the same with a slight variation: Latches have level sensitive control signal input and Flip-flops have edge sensitive control signal input. Flip-flops and latches which use this control signals are called synchronous circuits. So if they don't use clock inputs, then they are called asynchronous circuits.
 
### RS Latch

RS latch have two inputs, S and R. S is called set and R is called reset. The S input is used to produce HIGH on Q ( i.e. store binary 1 in flip-flop). The R input is used to produce LOW on Q (i.e. store binary 0 in flip-flop). Q' is Q complementary output, so it always holds the opposite value of Q. The output of the S-R latch depends on current as well as previous inputs or state, and its state (value stored) can change as soon as its inputs change. The circuit and the truth table of RS latch is shown

below. (This circuit is as we saw in the last page, but arranged to look beautiful :-).



S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	X	0
1	0	X	1
1	1	X	0


The operation has to be analyzed with the 4 inputs combinations together with the 2 possible previous states.

- **When S = 0 and R = 0:** If we assume Q = 1 and Q' = 0 as initial condition, then output Q after input is applied would be  $Q = (R + Q')' = 1$  and  $Q' = (S + Q)' = 0$ . Assuming Q = 0 and Q' = 1 as initial condition, then output Q after the input applied would be  $Q = (R + Q')' = 0$  and  $Q' = (S + Q)' = 1$ . So it is clear that when both S and R inputs are LOW, the output is retained as before the application of inputs. (i.e. there is no state change).
- **When S = 1 and R = 0:** If we assume Q = 1 and Q' = 0 as initial condition, then output Q after input is applied would be  $Q = (R + Q')' = 1$  and  $Q' = (S + Q)' = 0$ . Assuming Q = 0 and Q' = 1 as initial condition, then output Q after the input applied would be  $Q = (R + Q')' = 1$  and  $Q' = (S + Q)' = 0$ . So in simple words when S is HIGH and R is LOW, output Q is HIGH.
- **When S = 0 and R = 1:** If we assume Q = 1 and Q' = 0 as initial condition, then output Q after input is applied would be  $Q = (R + Q')' = 0$  and  $Q' = (S + Q)' = 1$ . Assuming Q = 0 and


$Q' = 1$  as initial condition, then output  $Q$  after the input applied would be  $Q = (R + Q)' = 0$  and  $Q' = (S + Q)' = 1$ . So in simple words when  $S$  is LOW and  $R$  is HIGH, output  $Q$  is LOW.

- **When  $S = 1$  and  $R = 1$**  : No matter what state  $Q$  and  $Q'$  are in, application of 1 at input of NOR gate always results in 0 at output of NOR gate, which results in both  $Q$  and  $Q'$  set to LOW (i.e.  $Q = Q'$ ). LOW in both the outputs basically is wrong, so this case is invalid.

 The waveform below shows the operation of NOR gates based RS Latch.



 It is possible to construct the RS latch using NAND gates (of course as seen in Logic gates section). The only difference is that NAND is NOR gate dual form (Did I say that in Logic gates section?). So in this case the  $R = 0$  and  $S = 0$  case becomes the invalid case. The circuit and Truth table of RS latch using NAND is shown below.




S	R	Q	Q+
1	1	0	0
1	1	1	1
0	1	X	0
1	0	X	1
0	0	X	1

If you look closely, there is no control signal (i.e. no clock and no enable), so this kind of latches or flip-flops are called asynchronous logic elements. Since all the sequential circuits are built around the RS latch, we will concentrate on synchronous circuits and not on asynchronous circuits.


**JK  
Master  
Slave  
Flip-  
Flop**

All sequential circuits that we have seen in the last few pages have a problem (All level sensitive sequential circuits have this problem). Before the enable input changes state from HIGH to LOW (assuming HIGH is ON and LOW is OFF state), if inputs changes, then another state transition occurs for the same enable pulse. This sort of multiple transition problem is called racing.

 If we make the sequential element sensitive to edges, instead of levels, we can overcome this problem, as input is evaluated only during enable/clock edges.



 In the figure above there are two latches, the first latch on the left is called master latch and the one on the right is called slave latch. Master latch is positively clocked and slave latch is negatively clocked.



### Sequential Circuits Design

We saw in the combinational circuits section how to design a combinational circuit from the given problem. We convert the problem into a truth table, then draw K-map for the truth table, and then finally draw the gate level circuit for the problem. Similarly we have a flow for the sequential circuit design. The steps are given below.

- Draw state diagram.
- Draw the state table (excitation table) for each output.
- Draw the K-map for each output.
- Draw the circuit.

Looks like sequential circuit design flow is very much the same as for combinational circuit.

### Digital Logic Families

Logic families can be classified broadly according to the technologies they are built with. In earlier days we had vast number of these technologies, as you can see in the list below.

- DL : Diode Logic.
- RTL : Resistor Transistor Logic.
- DTL : Diode Transistor Logic.
- HTL : High threshold Logic.
- TTL : Transistor Transistor Logic.
- I<sup>2</sup>L : Integrated Injection Logic.
- ECL : Emitter coupled logic.
- MOS : Metal Oxide Semiconductor Logic (PMOS and NMOS).
- CMOS : Complementary Metal Oxide Semiconductor

Logic.

Among these, only CMOS is most widely used by the ASIC (Chip) designers; we will still try to understand a few of the extinct / less used technologies. More in-depth explanation of CMOS will be covered in the VLSI section.


## Basic Concepts

Before we start looking at the how gates are built using various technologies, we need to understand a few basic concepts. These concepts will go long way i.e. if you become a ASIC designer or Board designer, you may need to know these concepts very well.

- Fan-in.
- Fan-out.
- Noise Margin.
- Power Dissipation.
- Gate Delay.
- Wire Delay.
- Skew.
- Voltage Threshold.
 
### Fan-in

Fan-in is the number of inputs a gate has, like a two input AND gate has fan-in of two, a three input NAND gate as a fan-in of three. So a NOT gate always has a fan-in of one. The figure below shows the effect of fan-in on the delay offered by a gate for a CMOS based gate. Normally delay increases following a quadratic function of fan-in.






### ◆ Fan-out

The number of gates that each gate can drive, while providing voltage levels in the guaranteed range, is called the standard load or fan-out. The fan-out really depends on the amount of electric current a gate can source or sink while driving other gates. The effects of loading a logic gate output with more than its rated fan-out has the following effects.


- In the LOW state the output voltage  $V_{OL}$  may increase above  $V_{OLmax}$ .
- In the HIGH state the output voltage  $V_{OH}$  may decrease below  $V_{OHmin}$ .
- The operating temperature of the device may increase thereby reducing the reliability of the device and eventually causing the device failure.
- Output rise and fall times may increase beyond specifications
- The propagation delay may rise above the specified value.

 Normally as in the case of fan-in, the delay offered by a gate increases with the increase in fan-out.


 
### ◆ Gate Delay

Gate delay is the delay offered by a gate for the signal appearing at its input, before it reaches the gate output. The figure below shows a NOT gate with a delay of "Delta", where output X' changes only after a delay of "Delta". Gate delay is also known as propagation delay.



Gate delay is not the same for both transitions, i.e. gate delay will be different for low to high transition, compared to high to low transition.

Low to high transition delay is called turn-on delay and High to low transition delay is called turn-off delay.


### ✦ Wire Delay

Gates are connected together with wires and these wires do delay the signal they carry, these delays become very significant when frequency increases, say when the transistor sizes are sub-micron. Sometimes wire delay is also called flight time (i.e. signal flight time from point A to B). Wire delay is also known as transport delay.



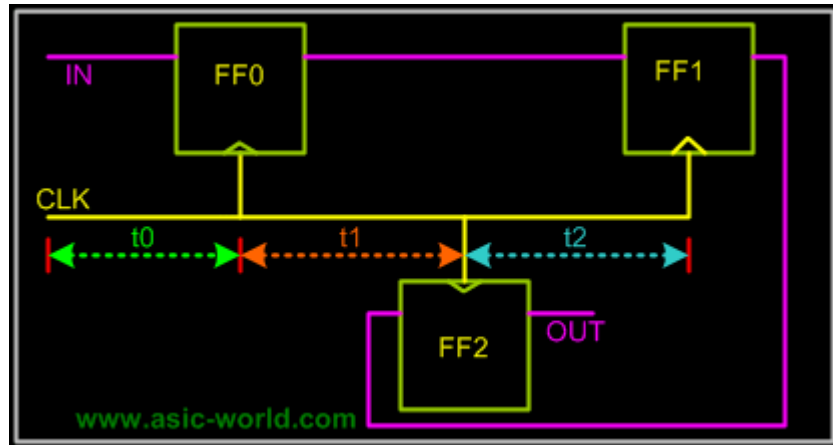
### Skew

The same signal arriving at different parts of the design with different phase is known as skew. Skew normally refers to clock signals. In the figure below, clock signal CLK reaches flip-flop FF0 at time  $t_0$ , so with respect to the clock phase at the source, it has at FF0 input a clock skew of  $t_0$  time units. Normally this is expressed in nanoseconds.



 The waveform below shows how clock looks at different parts of the design. We will discuss the effects of clock skew later.



### ◆ Logic levels

Logic levels are the voltage levels for logic high and logic low.

- **$VO_{Hmin}$**  : The minimum output voltage in HIGH state (logic '1').  $VO_{Hmin}$  is 2.4 V for TTL and 4.9 V for CMOS.
- **$VO_{Lmax}$**  : The maximum output voltage in LOW state (logic '0').  $VO_{Lmax}$  is 0.4 V for TTL and 0.1 V for CMOS.
- **$VI_{Hmin}$**  : The minimum input voltage guaranteed to be recognised as logic 1.  $VI_{Hmin}$  is 2 V for TTL and 3.5 V for CMOS.
- **$VI_{Lmax}$**  : The maximum input voltage guaranteed to be recognised as logic 0.  $VI_{Lmax}$  is 0.8 V for TTL and 1.5 V for CMOS.

### ◆ Current levels

- **$IO_{Hmin}$** : The maximum current the output can source

in HIGH state while still maintaining the output voltage above  $V_{O_{Hmin}}$ .

- $I_{O_{Lmax}}$  : The maximum current the output can sink in LOW state while still maintaining the output voltage below  $V_{O_{Lmax}}$ .
- $I_{Imax}$  : The maximum current that flows into an input in any state ( $1\mu A$  for CMOS).

### ✦ Noise Margin

Gate circuits are constructed to sustain variations in input and output voltage levels. Variations are usually the result of several different factors.

- Batteries lose their full potential, causing the supply voltage to drop
- High operating temperatures may cause a drift in transistor voltage and current characteristics
- Spurious pulses may be introduced on signal lines by normal surges of current in neighbouring supply lines.

All these undesirable voltage variations that are superimposed on normal operating voltage levels are called noise. All gates are designed to tolerate a certain amount of noise on their input and output ports. The maximum noise voltage level that is tolerated by a gate is called noise margin. It derives from I/P-O/P voltage characteristic, measured under different operating conditions. It's normally supplied from manufacturer in the gate documentation.

- **LNM (Low noise margin):** The largest noise amplitude that is guaranteed not to change the output voltage level when superimposed on the input voltage of the logic gate (when this voltage is in the LOW interval).  $LNM = V_{I_{Lmax}} - V_{O_{Lmax}}$ .
- **HNM (High noise margin):** The largest noise amplitude that is guaranteed not to change the output voltage level if superimposed on the input voltage of the logic gate (when this voltage is in the HIGH interval).  $HNM = V_{O_{Hmin}} - V_{I_{Hmin}}$

### ✦ tr (Rise time)

The time required for the output voltage to increase from  $V_{ILmax}$  to  $V_{IHmin}$ .

### ✦ tf (Fall time)

The time required for the output voltage to decrease from  $V_{IHmin}$  to  $V_{ILmax}$ .

#### ◆ **$t_p$ (Propagation delay)**

The time between the logic transition on an input and the corresponding logic transition on the output of the logic gate. The propagation delay is measured at midpoints.

#### ◆ **Power Dissipation.**

Each gate is connected to a power supply  $V_{CC}$  ( $V_{DD}$  in the case of CMOS). It draws a certain amount of current during its operation. Since each gate can be in a High, Transition or Low state, there are three different currents drawn from power supply.

- $I_{CCH}$ : Current drawn during HIGH state.
- $I_{CCT}$ : Current drawn during HIGH to LOW, LOW to HIGH transition.
- $I_{CCL}$ : Current drawn during LOW state.

For TTL,  $I_{CCT}$  the transition current is negligible, in comparison to  $I_{CCH}$  and  $I_{CCL}$ . If we assume that  $I_{CCH}$  and  $I_{CCL}$  are equal then,

$$\text{Average Power Dissipation} = V_{cc} * (I_{CCH} + I_{CCL})/2$$

For CMOS,  $I_{CCH}$  and  $I_{CCL}$  current is negligible, in comparison to  $I_{CCT}$ . So the Average power dissipation is calculated as below.

$$\text{Average Power Dissipation} = V_{cc} * I_{CCT}.$$

So for TTL like logics family, power dissipation does not depend on frequency of operation, and for CMOS the power dissipation depends on the operation frequency.

Power Dissipation is an important metric for two reasons. The amount of current and power available in a battery is nearly constant. Power dissipation of a circuit or system defines battery life: the greater the power dissipation, the shorter the battery life. Power dissipation is proportional to the heat generated by the chip or system; excessive heat dissipation may increase operating temperature and cause gate circuitry to drift out of its normal operating range; will cause gates to generate improper output values. Thus power dissipation of any gate implementation must be kept as low as possible.

Moreover, power dissipation can be classified into Static

power dissipation and Dynamic power dissipation.


- **Ps (Static Power Dissipation):** Power consumed when the output or input are not changing or rather when clock is turned off. Normally static power dissipation is caused by leakage current. (As we reduce the transistor size, i.e. below 90nm, leakage current could be as high as 40% of total power dissipation).
- **Pd (Dynamic Power Dissipation):** Power consumed during output and input transitions. So we can say Pd is the actual power consumed i.e. the power consumed by transistors + leakage current.

Thus

Total power dissipation = static power dissipation + dynamic power dissipation.
 
## Diode Logic

In DL (diode logic), all the logic is implemented using diodes and resistors. One basic thing about the diode, is that diode needs to be forward biased to conduct. Below is the example of a few DL logic circuits.



When no input is connected or driven, output Z is low, due to resistor R1. When high is applied to either X or Y, or both X and Y are driven high, the corresponding diode get forward biased and thus conducts. When any diode conducts, output Z goes high.


### Points to Ponder

- Diode Logic suffers from voltage

- degradation from one stage to the next.
- Diode Logic only permits OR and AND functions.
- Diode Logic is used extensively but not in integrated circuits.
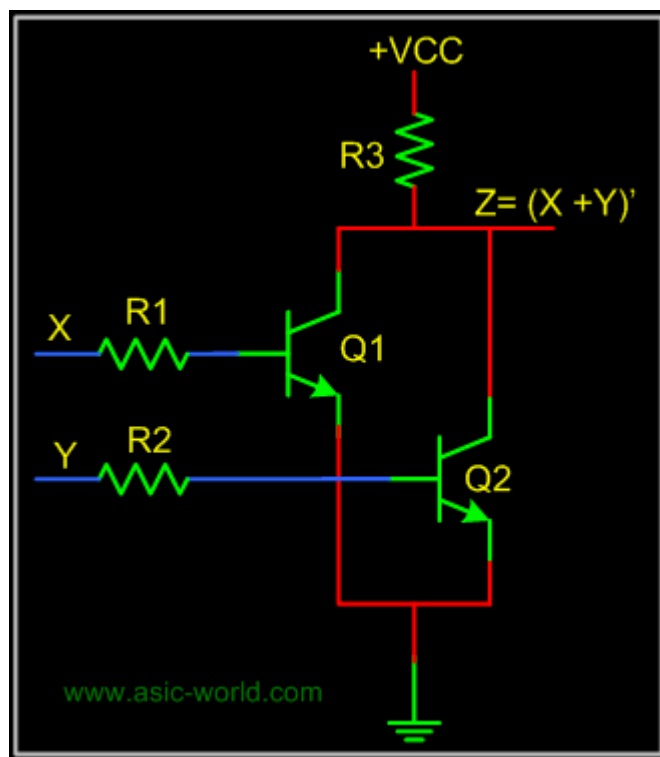
### ❖ Resistor Transistor Logic

In RTL (resistor transistor logic), all the logic are implemented using resistors and transistors. One basic thing about the transistor (NPN), is that HIGH at input causes output to be LOW (i.e. like a inverter). Below is the example of a few RTL logic circuits.




A basic circuit of an RTL NOR gate consists of two transistors Q1 and Q2, connected as shown in the figure above. When either input X or Y is driven HIGH, the corresponding transistor goes to saturation and output Z is pulled to LOW.

### ❖ Diode Transistor Logic

In DTL (Diode transistor logic), all the logic is implemented using diodes and transistors. A basic circuit in the DTL logic family is as shown in the

figure below. Each input is associated with one diode. The diodes and the 4.7K resistor form an AND gate. If input X, Y or Z is low, the corresponding diode conducts current, through the 4.7K resistor. Thus there is no current through the diodes connected in series to transistor base . Hence the transistor does not conduct, thus remains in cut-off, and output out is High.

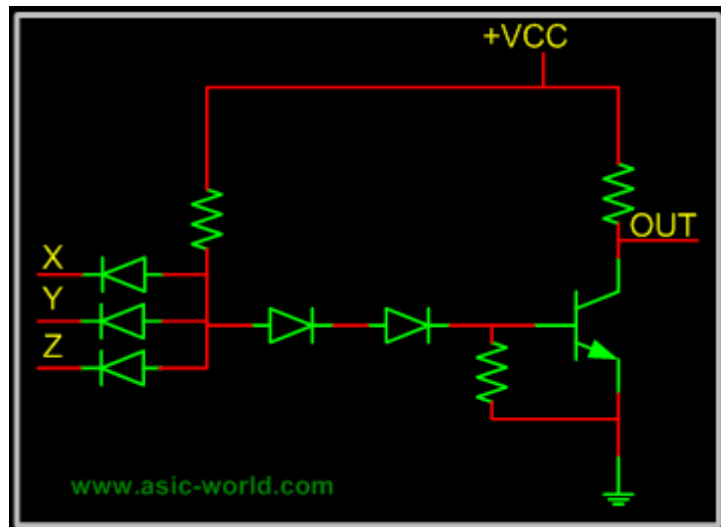If all the inputs X, Y, Z are driven high, the diodes in series conduct, driving the transistor into saturation. Thus output out is Low.



### ❖ Transistor Transistor Logic

In Transistor Transistor logic or just TTL, logic gates are built only around transistors. TTL was developed in 1965. Through the years basic TTL has been improved to meet performance requirements. There are many versions or families of TTL.

- Standard TTL.
- High Speed TTL
- Low Power TTL.
- Schottky TTL.


Here we will discuss only basic TTL as of now; maybe in the future I will add more details about other TTL versions. As such all TTL families have three configurations for outputs.

- Totem - Pole output.
- Open Collector Output.



- Tristate Output.

Before we discuss the output stage let's look at the input stage, which is used with almost all versions of TTL. This consists of an input transistor and a phase splitter transistor. Input stage consists of a multi emitter transistor as shown in the figure below. When any input is driven low, the emitter base junction is forward biased and input transistor conducts. This in turn drives the phase splitter transistor into cut-off.

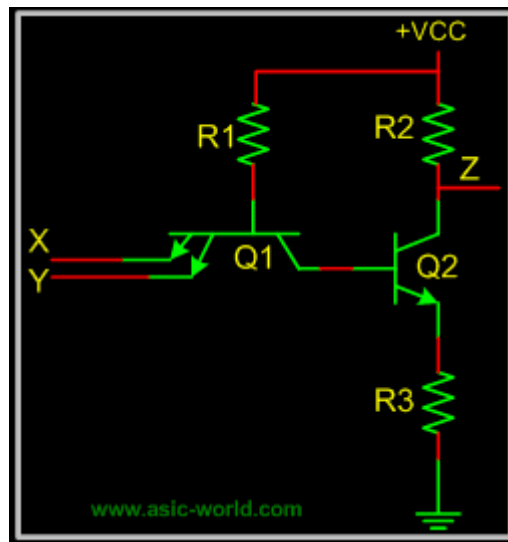

### ✦ Totem - Pole Output

Below is the circuit of a totem-pole NAND gate, which has got three stages.

- Input Stage
- Phase Splitter Stage
- Output Stage


Input stage and Phase splitter stage have already been discussed. Output stage is called Totem-Pole because transistor Q3 sits upon Q4.

Q2 provides complementary voltages for the output transistors Q3 and Q4, which stack one above the other in such a way that while one of these conducts, the other is in cut-off.

 Q4 is called pull-down transistor, as it pulls the output voltage down, when it saturates and the other is in cut-off (i.e. Q3 is in cut-off). Q3 is called

pull-up transistor, as it pulls the output voltage up, when it saturates and the other is in cut-off (i.e. Q4 is in cut-off).

Diodes in input are protection diodes which conduct when there is large negative voltage at input, shorting it to the ground.




✦ **Tristate Output.**

Normally when we have to implement shared bus systems inside an ASIC or externally to the chip, we have two options: either to use a MUX/DEMUX based system or to use a tri-state base bus system.

In the latter, when logic is not driving its output, it does not drive LOW neither HIGH, which means that logic output is floating. Well, one may ask, why not just use an open collector for shared bus systems? The problem is that open collectors are not so good for implementing wire-ANDs.

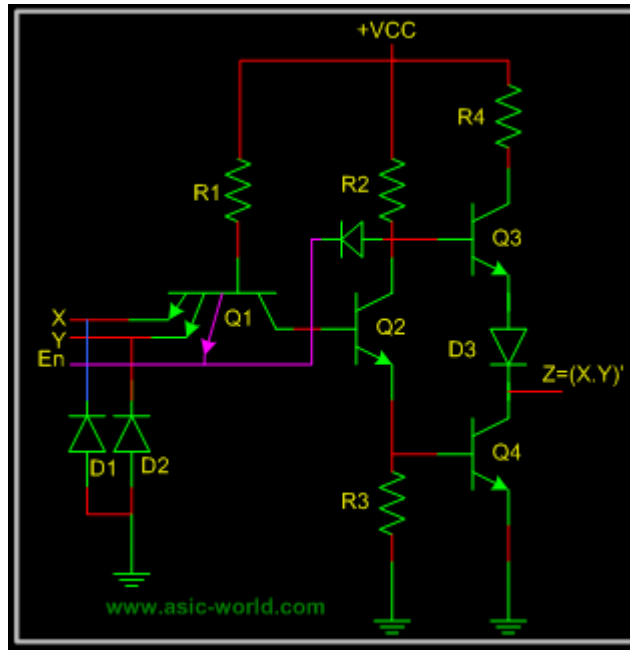
The circuit below is a tri-state NAND gate; when Enable En is HIGH, it works like any other NAND gate. But when Enable En is driven LOW, Q1 Conducts, and the diode connecting Q1 emitter and Q2 collector, conducts driving Q3 into cut-off. Since Q2 is not conducting, Q4 is also at cut-off. When both pull-up and pull-down transistors are not conducting, output Z is in high-impedance state.



Note : I will try to add more details when I find time.
 
## Diode Logic

In DL (diode logic), all the logic is implemented using diodes and resistors. One basic thing about the diode, is that diode needs to be forward biased to conduct. Below is the example of a few DL logic circuits.



When no input is connected or driven, output Z is low, due to resistor R1. When high is applied to either X or Y, or both X and Y are driven high, the corresponding diode get forward biased and thus conducts. When any diode conducts, output Z goes high.


### Points to Ponder

- Diode Logic suffers from voltage

- degradation from one stage to the next.
- Diode Logic only permits OR and AND functions.
- Diode Logic is used extensively but not in integrated circuits.
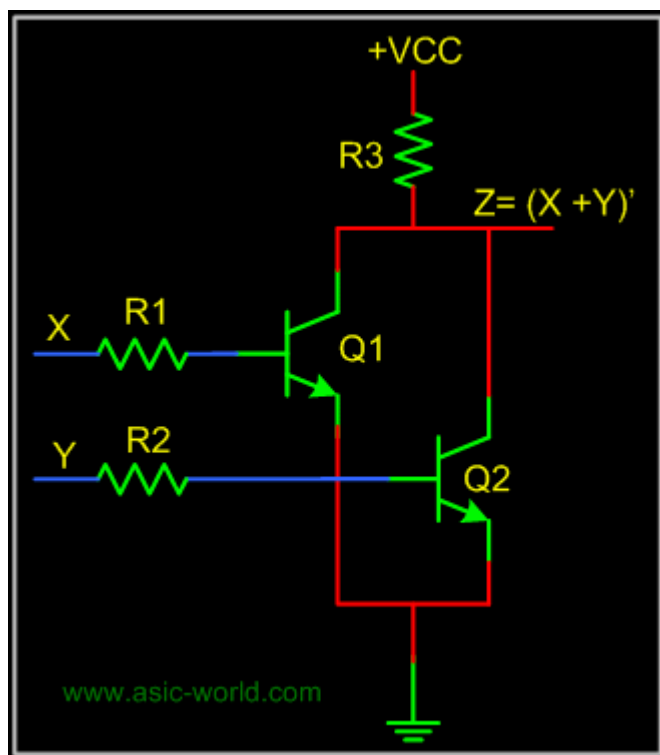
### ❖ Resistor Transistor Logic

In RTL (resistor transistor logic), all the logic are implemented using resistors and transistors. One basic thing about the transistor (NPN), is that HIGH at input causes output to be LOW (i.e. like a inverter). Below is the example of a few RTL logic circuits.




A basic circuit of an RTL NOR gate consists of two transistors Q1 and Q2, connected as shown in the figure above. When either input X or Y is driven HIGH, the corresponding transistor goes to saturation and output Z is pulled to LOW.

### Diode Transistor Logic

In DTL (Diode transistor logic), all the logic is implemented using diodes and transistors. A basic circuit in the DTL logic family is as shown in the

figure below. Each input is associated with one diode. The diodes and the 4.7K resistor form an AND gate. If input X, Y or Z is low, the corresponding diode conducts current, through the 4.7K resistor. Thus there is no current through the diodes connected in series to transistor base. Hence the transistor does not conduct, thus remains in cut-off, and output out is High.

 If all the inputs X, Y, Z are driven high, the diodes in series conduct, driving the transistor into saturation. Thus output out is Low.



### ❖ Transistor Transistor Logic

In Transistor Transistor logic or just TTL, logic gates are built only around transistors. TTL was developed in 1965. Through the years basic TTL has been improved to meet performance requirements. There are many versions or families of TTL.


- Standard TTL.
- High Speed TTL
- Low Power TTL.
- Schottky TTL.

Here we will discuss only basic TTL as of now; maybe in the future I will add more details about other TTL versions. As such all TTL families have three configurations for outputs.

- Totem - Pole output.
- Open Collector Output.

- Tristate Output.

Before we discuss the output stage let's look at the input stage, which is used with almost all versions of TTL. This consists of an input transistor and a phase splitter transistor. Input stage consists of a multi emitter transistor as shown in the figure below. When any input is driven low, the emitter base junction is forward biased and input transistor conducts. This in turn drives the phase splitter transistor into cut-off.

 

### ✦ Totem - Pole Output

Below is the circuit of a totem-pole NAND gate, which has got three stages.

- Input Stage
- Phase Splitter Stage
- Output Stage


Input stage and Phase splitter stage have already been discussed. Output stage is called Totem-Pole because transistor Q3 sits upon Q4.

Q2 provides complementary voltages for the output transistors Q3 and Q4, which stack one above the other in such a way that while one of these conducts, the other is in cut-off.

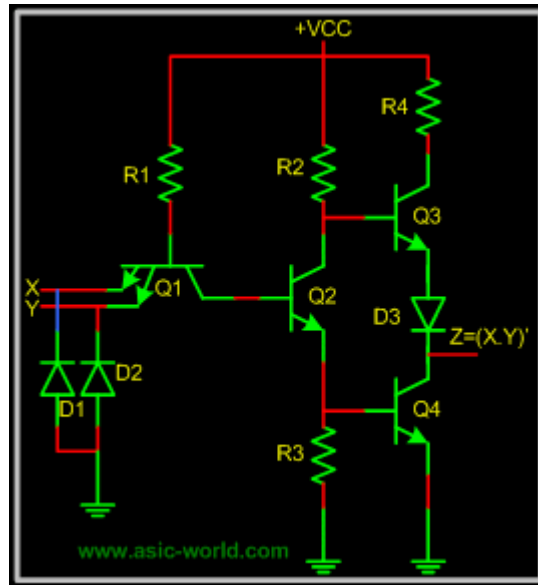Q4 is called pull-down transistor, as it pulls the output voltage down, when it saturates and the other is in cut-off (i.e. Q3 is in cut-off). Q3 is called

pull-up transistor, as it pulls the output voltage up, when it saturates and the other is in cut-off (i.e. Q4 is in cut-off).

Diodes in input are protection diodes which conduct when there is large negative voltage at input, shorting it to the ground.




### ✦ Tristate Output.

Normally when we have to implement shared bus systems inside an ASIC or externally to the chip, we have two options: either to use a MUX/DEMUX based system or to use a tri-state base bus system.

In the latter, when logic is not driving its output, it does not drive LOW neither HIGH, which means that logic output is floating. Well, one may ask, why not just use an open collector for shared bus systems? The problem is that open collectors are not so good for implementing wire-ANDs.

 The circuit below is a tri-state NAND gate; when Enable En is HIGH, it works like any other NAND gate. But when Enable En is driven LOW, Q1 Conducts, and the diode connecting Q1 emitter and Q2 collector, conducts driving Q3 into cut-off. Since Q2 is not conducting, Q4 is also at cut-off. When both pull-up and pull-down transistors are not conducting, output Z is in high-impedance state.



## Emitter coupled logic


Emitter coupled logic (ECL) is a non saturated logic, which means that transistors are prevented from going into deep saturation, thus eliminating storage delays. Preventing the transistors from going into saturation is accomplished by using logic levels whose values are so close to each other that a transistor is not driven into saturation when its input switches from low to high. In other words, the transistor is switched on, but not completely on. This logic family is faster than TTL.

Voltage level for high is -0.9 Volts and for low is -1.7V; thus biggest problem with ECL is a poor noise margin.

A typical ECL OR gate is shown below. When any input is HIGH (-0.9v), its connected transistor will conduct, and hence will make Q3 off, which in turn will make Q4 output HIGH.

 When both inputs are LOW (-1.7v), their connected transistors will not conduct, making Q3 on, which in turn will make Q4 output LOW.






 
### ❖ Metal Oxide Semiconductor Logic

MOS or Metal Oxide Semiconductor logic uses nmos and pmos to implement logic gates. One needs to know the operation of FET and MOS transistors to understand the operation of MOS logic circuits.

The basic NMOS inverter is shown below: when input is LOW, NMOS transistor does not conduct, and thus output is HIGH. But when input is HIGH, NMOS transistor conducts and thus output is LOW.



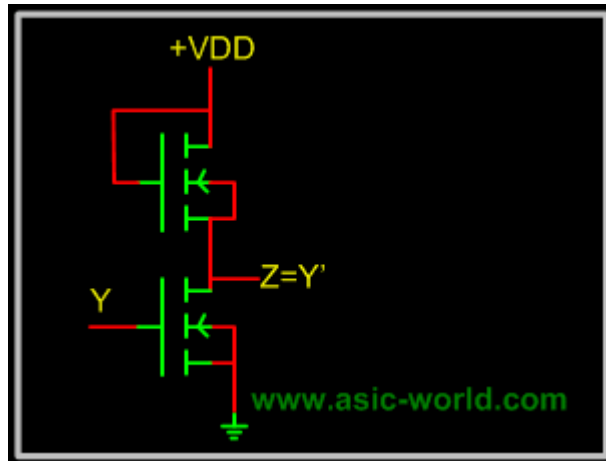Normally it is difficult to fabricate resistors inside the chips, so the resistor is replaced with an NMOS gate as shown below. This new NMOS transistor acts as resistor.




### Complementary Metal Oxide Semiconductor Logic

CMOS or Complementary Metal Oxide Semiconductor logic is built using both NMOS and PMOS. Below is the basic CMOS inverter circuit, which follows these rules:


- NMOS conducts when its input is HIGH.
- PMOS conducts when its input is LOW.

 So when input is HIGH, NMOS conducts, and thus output is LOW; when input is LOW PMOS conducts and thus output is HIGH.



 
### Introduction

Combinatorial Circuits are circuits which can be considered to have the following generic structure.



 Whenever the same set of inputs is fed in to a combinatorial circuit, the same outputs will be generated. Such circuits are said to be stateless. Some simple combinatorial logic elements that we have seen in previous sections are "Gates".



All the gates in the above figure have 2 inputs and one output; combinational elements simplest form are "not" gate and "buffer" as shown in the figure below. They have only one input and one output.



- Introduction

- Decoders

- Basic Binary Decoder
- Binary  $n$ -to- $2^n$  Decoders
  - Example - 2-to-4 Binary Decoder
  - Example - 3-to-8 Binary Decoder
- Implementing Functions Using Decoders
  - Example - Full adder

- Encoders
  - Example - Octal-to-Binary Encoder
  - Example - Decimal-to-Binary Encoder
- Priority Encoder
  - Example - 4to3 Priority Encoder
- Multiplexer
  - Mechanical Equivalent of a Multiplexer
  - Example - 2x1 MUX
    - Design of a 2:1 Mux
  - Example : 4:1 MUX
  - Larger Multiplexers
    - Example - 8-to-1 multiplexer from Smaller MUX
    - Example - 16-to-1 multiplexer from 4:1 mux
- De-multiplexers
  - Mechanical Equivalent of a De-Multiplexer
  - Example: 1-to-4 De-multiplexer
- Boolean Function Implementation
  - Implementing Functions Multiplexers
    - Example: 3-variable Function Using 8-to-1 mux
    - Example: 3-variable Function Using 4-to-1 mux
  - Example: 2 to 4 Decoder using Demux
- Mux-Demux Application Example

### ● Digital Logic Families.

- Basic Concepts
  - Fan-in
  - Fan-out
  - Gate Delay
  - Wire Delay
  - Skew
  - Logic levels
  - Current levels
  - Noise Margin
  - $t_r$  (Rise time)
  - $t_f$  (Fall time)
  - $t_p$  (Propagation delay)
  - Power Dissipation.
- Diode Logic
- Resistor
- Transistor

- Logic
- Diode
- Transistor
- Logic
- Transistor
- Transistor
- Logic
- Totem - Pole
- Output
- Tristate
- Output.
- Integrated
- Injection Logic
- Emitter coupled
- logic
- Metal Oxide
- Semiconductor
- Logic
- Complementary
- Metal Oxide
- Semiconductor
- Logic

## Numbering System

- Decimal System
- Decimal Examples
- Binary System
- Binary Counting
- Representing Binary
- Quantities
- Typical Voltage
- Assignment
- Octal System
- Octal to Decimal
- Conversion
- Hexadecimal System
- Hexadecimal to Decimal
- Conversion

### Code Conversion

- Binary-To-Decimal
- Conversion
- Decimal-To-Binary
- Conversion
- Reverse of Binary-To-
- Decimal Method
- Repeat Division-Convert
- decimal to binary
- Binary-To-Octal / Octal-To-
- Binary Conversion
- Repeat Division-Convert

- decimal to octal
- Hexadecimal to
- Decimal/Decimal to Hexadecimal Conversion
  - Repeat Division- Convert decimal to hexadecimal
- Binary-To-Hexadecimal
- /Hexadecimal-To-Binary Conversion
- Octal-To-Hexadecimal
- Hexadecimal-To-Octal Conversion

### Binary Codes

- Weighted Binary Systems
  - 8421 Code/BCD Code
  - 2421 Code
  - 5211 Code
  - Reflective Code
  - Sequential Codes
- Non Weighted Codes
  - Excess-3 Code
  - Gray Code

### Error Detecting and Correction Codes


- Error Detecting Codes
  - Parity
  - Check Sums
- Error-Correcting Codes
  - Hamming Code
- Alphanumeric Codes
  - ASCII Code
  - EBCDIC Code

### Floating Point Numbers

- Binary Representation of Floating Point Numbers
  - Example

 
## Basic Logic Gates

All digital systems can be constructed by only three basic logic gates. These basic gates are called the AND gate, the OR gate, and the NOT gate. Some textbooks also include the NAND gate, the NOR gate and the EOR gate as the members of the family of basic logic gates. The description of the operations of these gates are listed below [Ref.2]:



 
**AND gate**

The AND gate is a circuit which gives a high output (logic 1) if all its inputs are high. A dot (•) is used to indicate the AND operation. In practice, however, the dot is *usually omitted*.



 **OR gate**

The OR gate is a circuit which gives a high output if one or more of its inputs are high. A plus sign (+) is used to indicate the OR operation.



**NOT gate**

The NOT gate is a circuit which produces at its output the negated (inverted) version of its input logic. The circuit is also known as an *inverter*. If the input variable is A, the inverted output is written as  $\bar{A}$ .



**NAND gate**

The NAND gate is a NOT-AND circuit which is equivalent to an AND circuit followed by a NOT circuit. The output of the NAND gate is high if any of its inputs is low.



**NOR gate**

The NOR gate is a NOT-OR circuit which is equivalent to an OR circuit followed by a NOT circuit. The output of the NOR gate is low if any of its inputs is high.



**EOR gate**


The Exclusive-OR gate is a circuit which gives a high output if either of its two inputs is high, but not both. A encircled plus sign ( $\oplus$ ) is used to indicate the EOR operation

A NAND gate can be used as a NOT gate by the following wiring:



**Figure 1.2 Wiring the NAND gate as an inverter**

## Symbols for logic gates

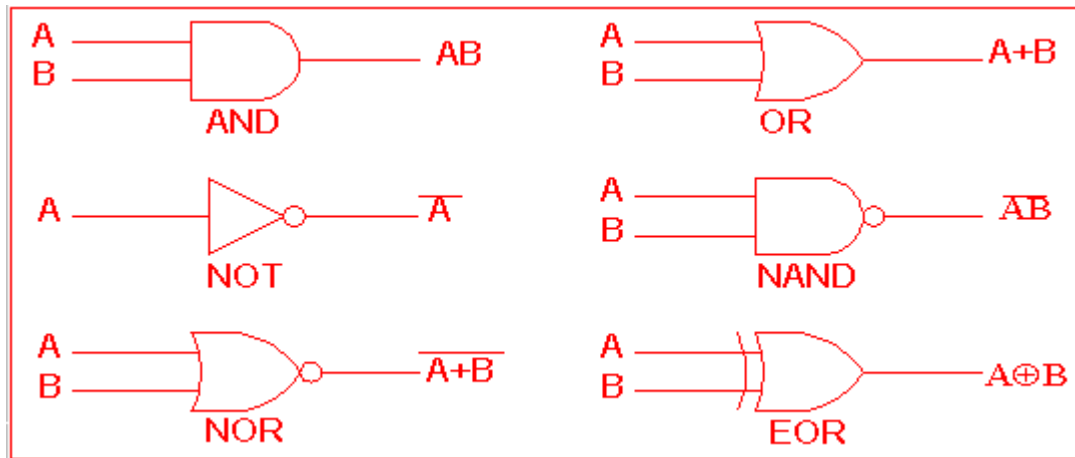

## Truth table representation of logic gates

The functions of these basic building blocks are summarized by means of a *Truth Table* as shown in Table 1.1. The table shows *all possible* input/output combinations for two inputs. A truth table with  $n$  inputs (logic variables) has  $2^n$  rows.

### Not Gate

Input $A$	Output $\bar{A}$
0	1
1	0

Inputs		Outputs				
$A$	$B$	$AND$	$OR$	$NAND$	$NOR$	$EOR$
0	0	0	0	1	1	0
0	1	0	1	1	0	1
1	0	0	1	1	0	1
1	1	1	1	0	0	0



**Table 1.1** Truth table representation of logic gates

## Digital Signals and Logic Gates

Engineers know that it is easier to design **two-state** devices than multi-state devices. In logic systems, variables, circuits, statements, etc., can be treated in one of two distinct states: true or false, yes or no, on or off, present or absent, energized or not energized, conducting or non-conducting, high voltage or low voltage, and so on.



In digital electronics, we distinguish two distinct values of voltage,  $V_H$  corresponding to the higher of the two voltages and  $V_L$  corresponding to the lower of the two voltages. There are three ways in which we can assign binary values to these voltages :

1. *Positive logic assignment* : True [ 1 ] :  $V_H$   
False [ 0 ] :  $V_L$
2. *Negative logic assignment* : True [ 1 ] :  $V_L$   
False [ 0 ] :  $V_H$
3. *Mixed logic assignment* : Allow the designers to use positive or negative logic at any point in their design, as they desire.

### ● Introduction

- Asynchronous sequential circuit
- Synchronous sequential circuits

### ● Concept of Sequential Logic

### ● Latches and Flip-Flops

- RS Latch
- RS Latch with Clock
- Setup and Hold Time
- D Latch
- JK Latch
- T Latch
- JK Master Slave Flip-Flop

### ● Sequential Circuits Design

- State Diagram
- State Table
- K-map
- Circuit