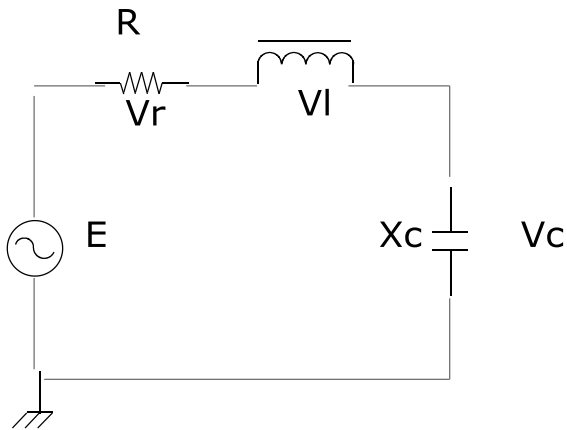


E025 Online Test

Ref 17

For the given series resonance circuitry, find I , V_r , V_l and V_c . If the resonance frequency is 4000Hz, Find the bandwidth . What power dissipated in circuit.




$$E = 10 \angle 0^\circ \text{ V} \quad R = 2 \text{ Ohm}, \quad X_l = 10 \text{ ohm}, \quad X_c = 10 \text{ ohm}$$

A	$I = 5 \text{ Angle } 0 \text{ amp}, V_r = 10\text{V},$ $V_l = 10 \text{ Angle } 90\text{V}, V_c = 50 \text{ Angle } -90 \text{ V}$	B	$I = 10 \text{ Angle } 0 \text{ amp}, V_r = 5\text{V},$ $V_l = 5 \text{ Angle } 90\text{V}, V_c = 50 \text{ Angle } +90 \text{ V}$
C	$I = 10 \text{ Angle } -90 \text{ amp}, V_r = 10\text{V},$ $V_l = 10 \text{ Angle } 0\text{V}, V_c = 50 \text{ Angle } +90 \text{ V}$	D	$I = 10 \text{ Angle } 0 \text{ amp}, V_r = 10\text{V},$ $V_l = 10 \text{ Angle } 90\text{V}, V_c = 50 \text{ Angle } -90 \text{ V}$
Answer			

Ref 18

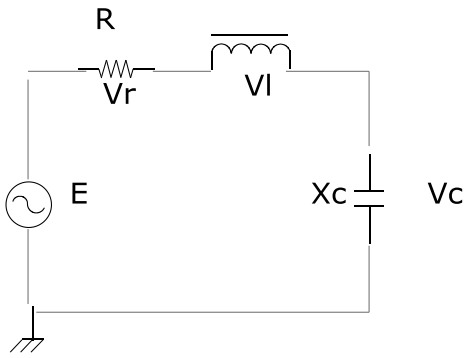In the given circuit, Quality factor (Q), Bandwidth of resonant frequency 5000HZ and power dissipated at half power frequency are




$$R = 2 \text{ ohm}, X_L = 10 \text{ ohm}, X_C = 10 \text{ ohm} \quad E = 10 \angle 0^\circ \text{ V}$$

A	Q= 10, BW= 2000HZ, P (HPF)= 50W	B	Q= 5, BW= 1000HZ, P (HPF)= 25W
C	Q= 15, BW= 2000HZ, P (HPF)= 50W	D	Q= 20, BW= 3000HZ, P (HPF)= 25W
Answer			

Ref 19

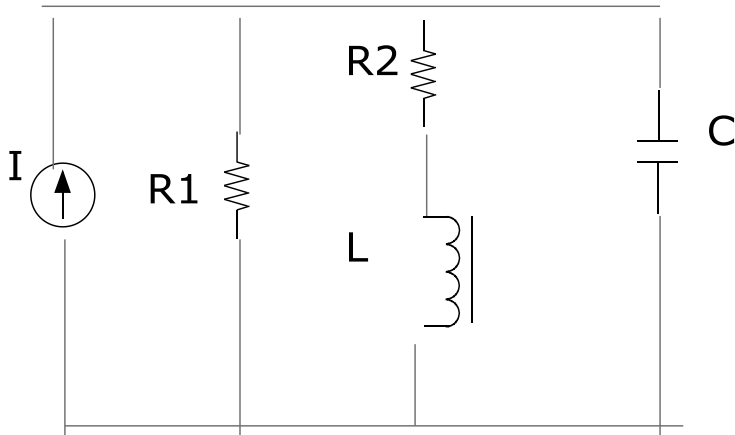Q9. For the given network with f_p provided.




$$R_1 = 40 \text{ K}\Omega, R_2 = 10 \Omega, L = 1 \text{ mH}, f_p = 0.04 \text{ MHz}$$

- (a) Determine Q_l
- (b) Determine R_p
- (c) Calculate Z_{tp}
- (d) Find C at resonance
- (e) Find Q_p
- (f) Calculate BW

A	Q= 25.12, Rp= 6.31 KΩ, Ztp= 5.45 KΩ C = 15.9 nF, Qp= 21.68, BW= 1.85 KHz	B	Q= 100, Rp= 10 KΩ, Ztp= 10KΩ C = 20 nF, Qp= 50, BW= 1KHz
C	Q= 50, Rp= 12 KΩ, Ztp= 7 KΩ C = 20 μF, Qp= 30, BW= 2KHz	D	Q= 25.12, Rp= 6.31 KΩ, Ztp= 5.45 KΩ C = 15.9 μF, Qp= 21.68, BW= 1.85 KHz
Answer			


Ref 20

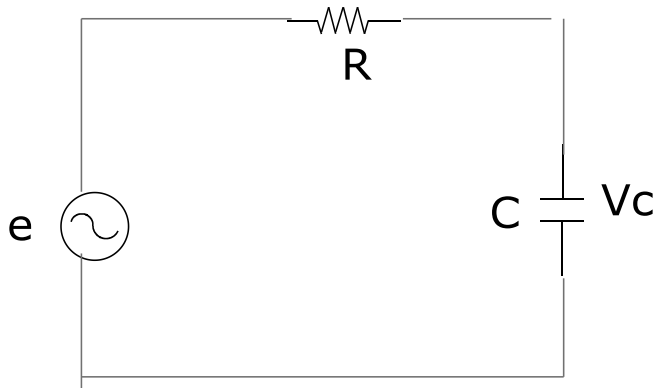The input voltage to the given circuit is $e = 12 + 10 \sin 2 t$  $R = 3 \Omega$, $C = 1/8 \text{ F}$ The effective value of current (I), V_c and the power dissipated in the circuit are

A	$I = 3 \text{ amp}$, $V_c = 13.67 \text{ V}$, $P_{\text{eff}} = 6 \text{ w}$	B	$I = 1.4142 \text{ amp}$, $V_c = 20 \text{ V}$, $P_{\text{eff}} = 12 \text{ w}$
C	$I = 1.4142 \text{ amp}$, $V_c = 13.67 \text{ V}$, $P_{\text{eff}} = 6 \text{ w}$	D	$I = 2 \text{ amp}$, $V_c = 20 \text{ V}$, $P_{\text{eff}} = 12 \text{ w}$
Answer			

Ref 21

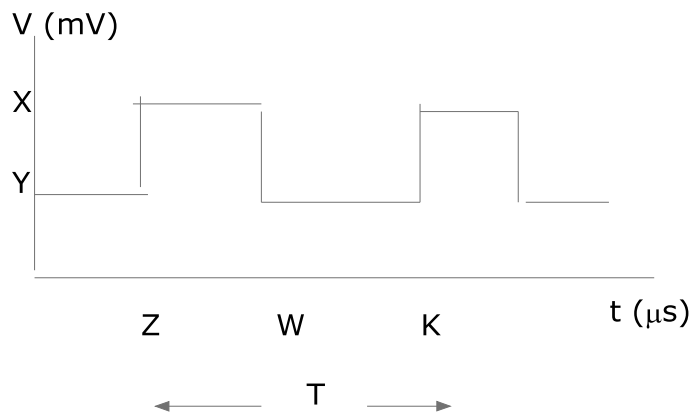
Determine the average value for given periodic pulse waveform.



$$X = 8, Y = 2, Z = 2, W = 6, K = 12$$

A	4.4 mV, 0.4 sec	B	8 mV, 1 sec
C	3 mV, 10 sec	D	8 mV, 0.4 sec
Answer			

Ref 22

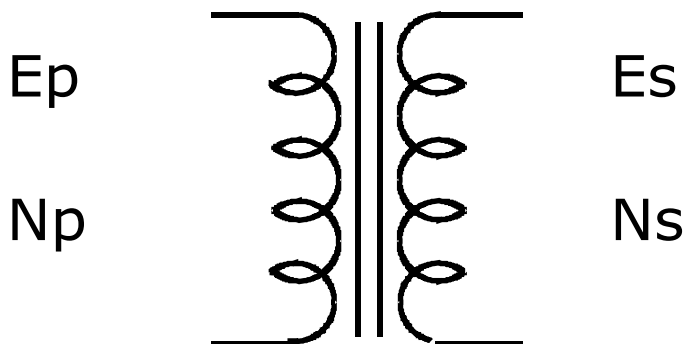


$$E_p = 200 \text{ V}, N_p = 50, E_s = 240 \text{ V}, N_s = ?$$

In the given transformer, maximum flux and secondary turn are

A	30mwb, 300 Turns	B	15mwb, 1000 Turns
C	70mwb, 300 Turns	D	15.02mwb, 600 Turns
Answer			

Ref 23

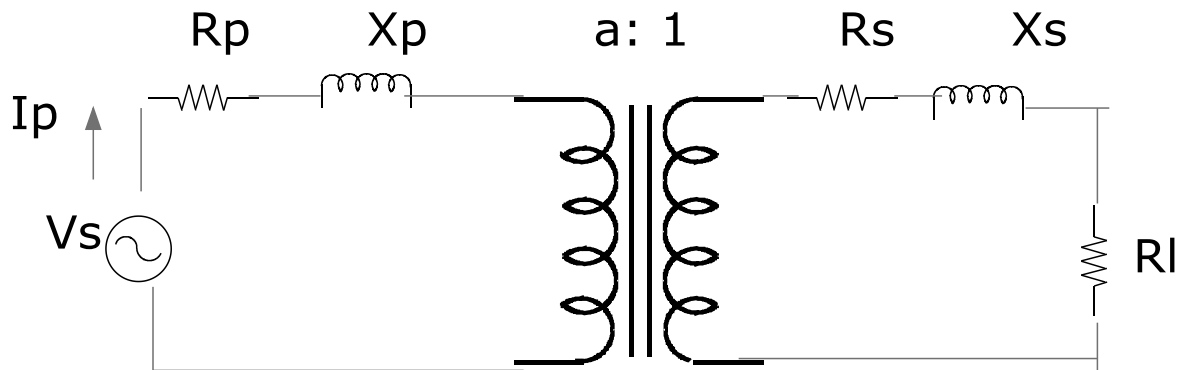

$I_p = 10\text{A}$, $R_p = 1\ \Omega$, $X_p = 2\ \Omega$, $a = 2$, $R_s = 1\ \Omega$, $X_s = 2\ \Omega$, $R_l = 50\ \Omega$

In above circuit, the voltage V_s is


A	2452V	B	1000V
C	300V	D	5000V
Answer			

Ref 24

If the system has a voltage gain of 36dB and output voltage 6.8V, the input voltage is

A	3V	B	10V
C	0.8V	D	0.107V
Answer			

Ref 25

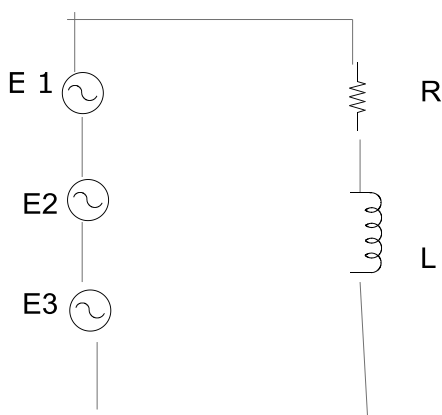


$E_1 = 25\text{V}$, $E_2 = 80 \sin \omega t$, $E_3 = 20 \sin 3\omega t$, $R = 20\ \Omega$, $L = 0.2\text{H}$

Total power dissipated in the given circuit is

A	53.5W	B	100W
C	200W	D	0.1W
Answer			

Ref 26

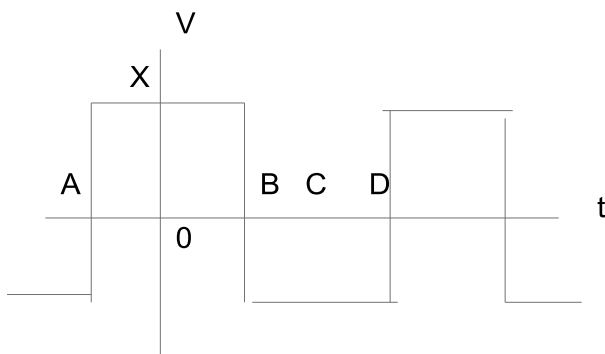

$$V = 100V, A = -\pi/4, B = \pi/2, C = \pi, D = 3\pi/2$$

The first four terms of the given trigonometric Fourier series are

A	$0 + \frac{400}{\pi} \cos \theta + 0 - \frac{400}{\pi} \cos 3 \theta$	B	$\frac{400}{\pi} + \frac{400}{\pi} \cos \theta +$ $\frac{400}{2\pi} \cos 2 \theta - \frac{400}{3\pi} \cos 3 \theta$
C	$0 + 0 + 0 - \frac{400}{3\pi} \cos 3 \theta$	D	$\frac{400}{\pi} + 0 + 0 + \frac{400}{3\pi} \cos 3 \theta$
Answer			