

SERIES RESONANT CIRCUIT

- **Circuit configuration– Resistor, Inductor and capacitor are connected in series**
- **$Z = R + jX_L - jX_C$**
- **Resonance occur when $X_L = X_C$**
- **$X_L = 2\pi f L$ $X_L =$ Inductive Reactance (Ω)**
- **$f =$ frequency (HZ)**
- **$L =$ Inductance (Henry)**

SERIES RESONANT CIRCUIT

1

- $X_c = \text{-----}$

$$2 \pi f C$$

Where $X_c =$ Capacitive reactance (Ω)

$f =$ Frequency (HZ)

$C =$ Capacitance (Farad)

Resonant Frequency & Quality Factor

- Resonant frequency (f_r) = $\frac{1}{2\pi \sqrt{LC}}$
-
- $\frac{\text{Reactive Power}}{\text{Active Power}} = \frac{X_L}{R}$
- Quality Factor (Q) = $\frac{\text{Reactive Power}}{\text{Active Power}} = \frac{X_L}{R}$
-

Band Width


-
- Bandwidth (BW) = $f_2 - f_1 = \frac{f_r}{Q}$

F1- Lower cut off frequency,

F2= Upper cut off frequency

Phf = Half power frequency = $\frac{1}{2}$ P max

① SERIES RESONANT CIRCUIT

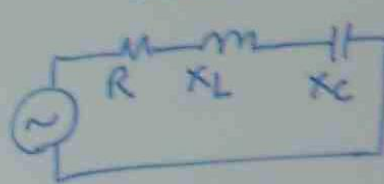

$$Z = R + jX_L - jX_C$$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fc}$$

AT RESONANCE, $X_L = X_C \rightarrow Z = R$



$$I = \frac{E}{Z} = \frac{E}{R} \quad (\text{MAXIMUM CURRENT})$$

$$2\pi fL = \frac{1}{2\pi fc}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$\rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

\hat{f} RESONANT FREQUENCY

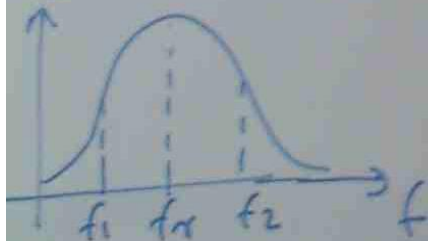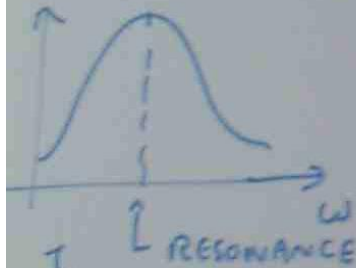

QUALITY FACTOR

$$Q = \frac{\text{REACTIVE POWER}}{\text{AVERAGE POWER}} = \frac{X_L}{R}$$

$$BW = f_2 - f_1 = \frac{f_r}{Q}$$

$$P_{HPF} (\text{HALF POWER FREQUENCY}) = \frac{1}{2} P_{MAX}$$

RLC Series Connection

- RLC Series connection

- $Z = R + j Xl - j Xc$

E

- $I = \text{-----}$

Z

Calculation of series RLC circuit


- $V = I \times X$

- $V_c = I \times X_c$

- $BW = f_2 - f_1 = \frac{f_r}{Q}$

- $P_{\text{avg}} = \frac{1}{2} P_{\text{max}} = \frac{1}{2} I_{\text{max}}^2 R$

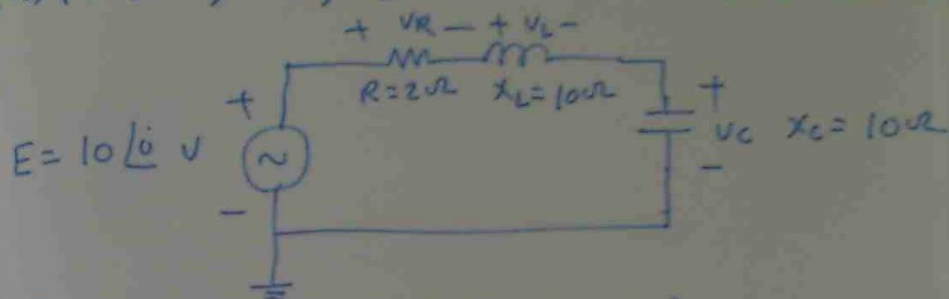Pb FOR THE GIVEN SERIES RESONANT CIRCUIT,
 (a) FIND I , V_R , V_L AND V_C AT RESONANCE.



(b) WHAT IS Q OF THE CIRCUIT?

(c) IF RESONANT FREQUENCY IS 5000 HZ, FIND BAND WIDTH

(d) WHAT IS POWER DISSIPATED IN CIRCUIT AT HALF POWER FREQUENCY?

$$(a) Z = R + jX_L - jX_C = 2 + j10 - j10 = 2\Omega$$

$$I = \frac{E}{Z} = \frac{10\angle 0}{2\angle 0} = 5\angle 0 \text{ Amp}, V_R = 5 \times 2 = 10\text{V}$$

$$V_L = I X_L = 5\angle 0 \times 10\angle 90 = 50\angle 90\text{V}$$

$$V_C = I X_C = 5\angle 0 \times 10\angle -90 = 50\angle -90\text{V}$$

$$(b) Q = \frac{X_L}{R} = \frac{10}{2} = 5$$

$$(c) BW = f_2 - f_1 = \frac{f_r}{Q} = \frac{5000}{5} = 1000 \text{ Hz}$$

$$(d) P_{HPF} = \frac{1}{2} P_{MAX} = \frac{1}{2} I_{MAX}^2 R$$


$$= \frac{1}{2} \times 5^2 \times 2 = 25 \text{ W}$$

Parallel Resonant Circuit

- $R_p = \frac{L}{Rl \times C}$
- $Z_{tp} = R_s$ parallel with $R_p = R_s$ parallel with $Ql^2 Rl$

- $F_p = f_s$ $\left[1 - \frac{1}{Ql^2} \right]$, $Bw = \frac{Rl}{2 \pi fL}$

PARALLEL RESONANT CIRCUIT

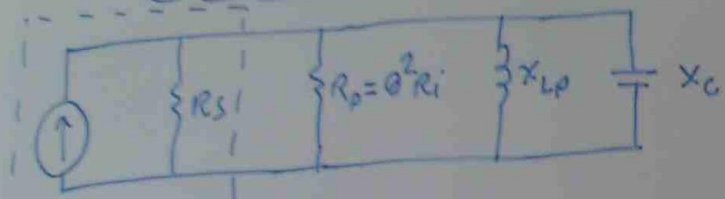

source

$$R_p = \frac{L}{R_L C}, \quad Z_{TP} = R_s \parallel R_p = R_s \parallel Q_i^2 R_L$$

$$f_p = f_s \sqrt{1 - \frac{1}{Q_i^2}}, \quad BW = \frac{R_L}{2\pi f L}$$

10/ FOR THE GIVEN NETWORK WITH f_p

PROVIDED,

(a) DETERMINE Q_i


(b) DETERMINE R_p

(c) CALCULATE Z_{TP}

(d) FIND 'C' AT RESONANCE

(e) FIND Q_p

(f) CALCULATE BW

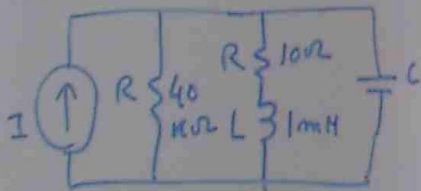

$$f_p = 0.04 \text{ MHz}$$

$$(a) Q_L = \frac{X_L}{R_L} = \frac{2\pi f_p L}{R_L} = \frac{2 \times 3.14 \times 0.04 \times 10^6 \times 1 \times 10^{-3}}{10} = 25.12$$

$$(b) R_p = Q_L^2 R_L = (25.12)^2 \times 10 = 6.31 \text{ k}\Omega$$

$$(c) Z_{TP} = R_s \parallel R_p = \frac{R_s R_p}{R_s + R_p} = \frac{40 \times 6.31}{40 + 6.31} = 5.45 \text{ k}\Omega$$

$$(d) C = \frac{1}{4\pi^2 f^2 L} = \frac{1}{4 \times 3.14^2 \times (0.04 \times 10^6)^2 \times 1 \times 10^{-3}} = 15.9 \times 10^{-9} \text{ F} = 15.9 \text{ nF}$$

$$(e) Q_p = \frac{Z_{TP}}{X_L} = \frac{5.45 \times 10^3}{2 \times 3.14 \times 0.04 \times 10^6 \times 1 \times 10^{-3}} = 21.68$$


$$(f) BW = \frac{f_p}{Q_p} = \frac{0.04 \times 10^6}{21.68} = 1.85 \text{ kHz}$$

STUDY EG25 / 2 / SLIDE 2 → 4

DO EXERCISES

Non sinusoidal circuits & Fourier Series
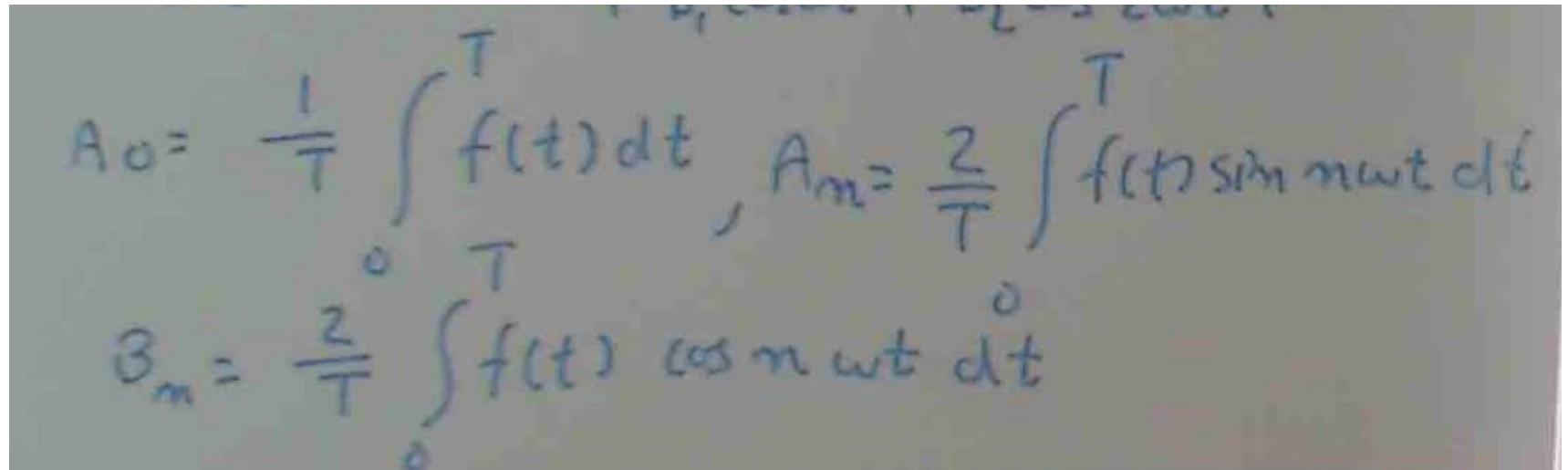
$$F(t) = A_0 + A_1 \sin \omega t + A_2 \sin 2\omega t + \dots + B_1 \cos \omega t + B_2 \cos 2\omega t + \dots$$



Handwritten formulas for Fourier coefficients:

$$A_0 = \frac{1}{T} \int_0^T f(t) dt, \quad A_m = \frac{2}{T} \int_0^T f(t) \sin m\omega t dt$$
$$B_m = \frac{2}{T} \int_0^T f(t) \cos m\omega t dt$$

Calculation of effective voltage

- $V_{\text{eff}} = V_o^2 + \sqrt{\frac{V_{m1}^2 + V_{m2}^2 + \dots}{2}}$

- $V_{\text{eff}} = V_o^2 + \sqrt{V_{1\text{eff}}^2 + V_{2\text{eff}}^2 + \dots}$

Total power

- $P_t = V_o I_o + V_1 I_1 \cos \Theta_1 + V_2 I_2 \cos \Theta_1 + \dots$
----- $+ V_n I_n \cos \Theta_n$

② NON SINUSOIDAL CIRCUITS



FOURIER SERIES


$$f(t) = A_0 + A_1 \sin \omega t + A_2 \sin 2\omega t + \dots$$

DC (OR)
AVERAGE VALUE

$$+ B_1 \cos \omega t + B_2 \cos 2\omega t + \dots$$

$$A_0 = \frac{1}{T} \int_0^T f(t) dt, \quad A_m = \frac{2}{T} \int_0^T f(t) \sin m\omega t dt$$
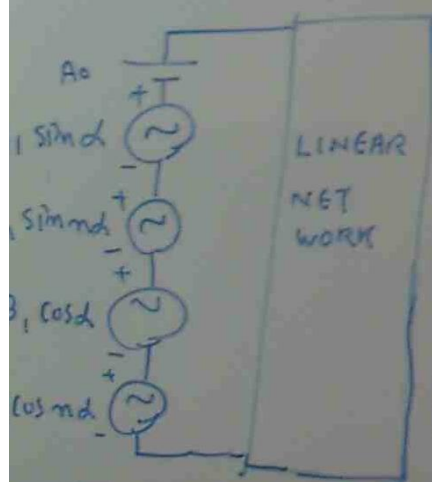
$$B_m = \frac{2}{T} \int_0^T f(t) \cos m\omega t dt$$




$$V_{\text{eff}} = \sqrt{V_0^2 + \frac{V_{m1}^2 + V_{m2}^2 + \dots}{2}}$$

$$V_{\text{eff}} = \sqrt{V_0^2 + V_{\text{eff}1}^2 + V_{\text{eff}2}^2 + \dots}$$

SIMILAR FOR I_{eff}
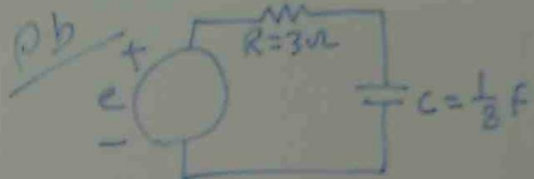
$$P_T = V_0 I_0 + V_1 I_1 \cos \phi_1 + \dots + V_m I_m \cos \phi_m$$



THE INPUT TO THE CIRCUIT IS


$$e = 12 + 10 \sin 2t$$

(a) FIND THE CURRENT i AND VOLTAGE V_R & V_C

(b) THE EFFECTIVE VALUE OF i , V_R , V_C

(c) FIND THE POWER DELIVERED TO THE CIRCUIT

FOR DC SUPPLY

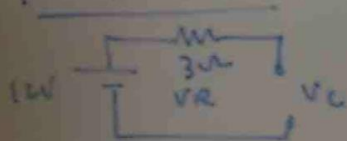


$$V_R = 0, I = 0, V_C = 12V$$

FOR $10 \sin 2t$ SUPPLY

$$\sin 2t$$

$$\omega = 2$$

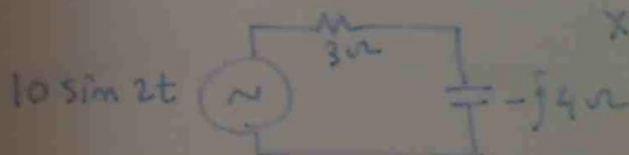

$$X_C = \frac{1}{\omega C} = \frac{1}{2 \times \frac{1}{2}} = 1 \Omega$$

$$Z = \sqrt{R^2 + X_C^2} \angle -\tan^{-1} \frac{X_C}{R} = \sqrt{3^2 + 1^2} \angle -\tan^{-1} \frac{1}{3}$$

$$I = \frac{E}{Z} = \frac{10/\sqrt{2} \angle 0}{5 \angle -53.2} = 1.4142/\sqrt{2} \angle 53.2 \text{ A}$$

$$V_R = I \times R = 1.4142/\sqrt{2} \times 3 \angle 0 = 4.24/\sqrt{2} \text{ V}$$

$$V_{C \text{ eff}} = I \times X_C = 1.4142/\sqrt{2} \times 1 \angle -90 = 1.4142/\sqrt{2} \angle -90 \text{ V}$$

$$I_{\text{eff}} = \sqrt{0^2 + 1.414^2} = 1.414 \text{ AMP} \quad P_{\text{eff}} = I_{\text{eff}}^2 R = 1.414^2 \times 3 = 6 \text{ W} \quad V_{C \text{ eff}} = \sqrt{12^2 + 5.64^2} = 13.67 \text{ V}$$



PULSE WAVEFORM & RC RESPONSE

- $\% \text{ Tilt} = \frac{V_1 - V_2}{V} \times 100$
- $V = \frac{V_1 + V_2}{2}$

DUTY CYCLE

- **Duty cycle** = $\frac{\text{Pulse width}}{\text{Period}}$ = $\frac{tp}{T}$
- **Frequency** = $\frac{1}{\text{Period}}$, $f = \frac{1}{T}$

③ PULSE WAVE FORMS AND RC RESPONSE

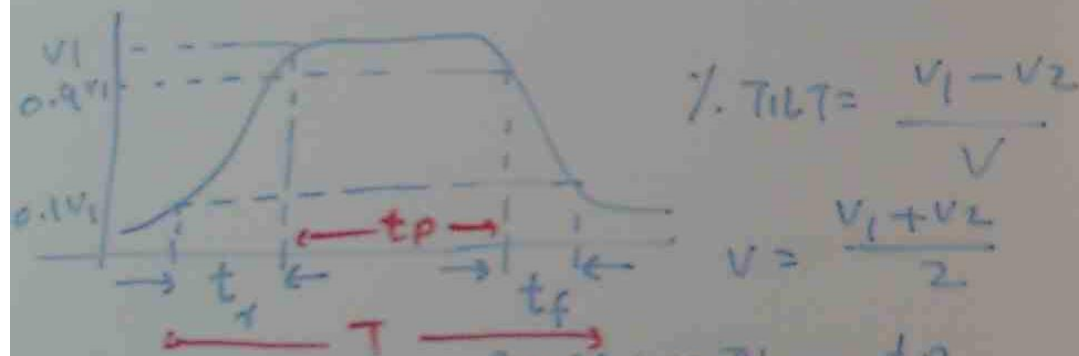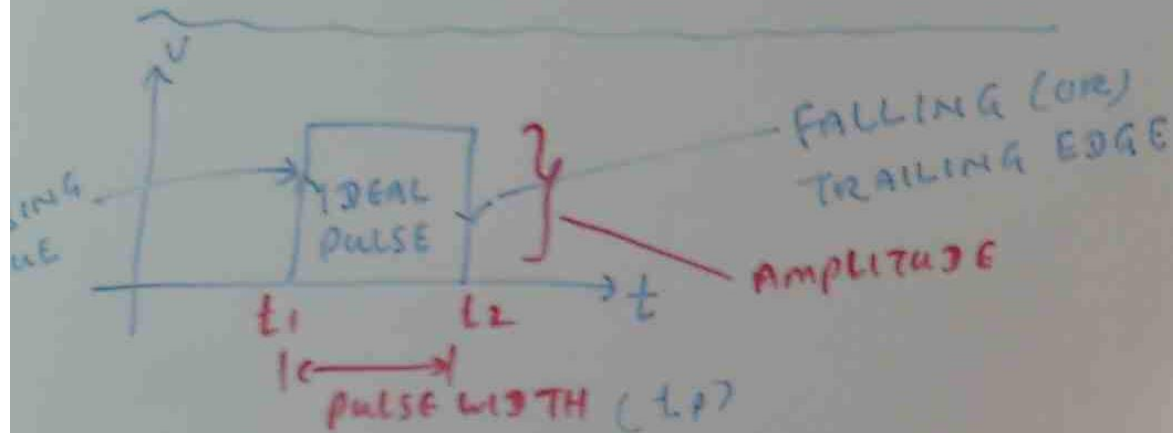


$$\% \text{ TILT} = \frac{V_1 - V_2}{V}$$

$$V = \frac{V_1 + V_2}{2}$$

$$\text{DUTY CYCLE} = \frac{\text{PULSE WIDTH}}{\text{PERIOD}} = \frac{t_p}{T}$$

$$\text{FREQUENCY} = \frac{1}{\text{PERIOD}}, f = \frac{1}{T}$$

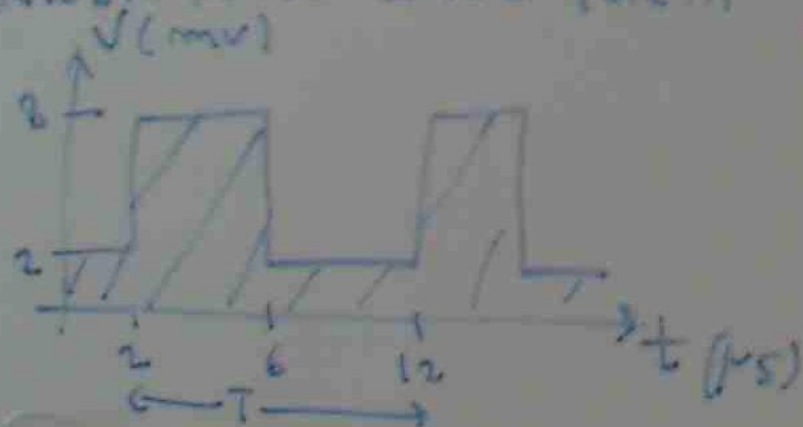Q. DETERMINE THE AVERAGE VALUE FOR PERIODIC PULSE WAVE FORM




$$\text{AVERAGE VALUE} = \frac{\text{AREA UNDER CURVE}}{T}$$

$$a = \frac{8(6-2) + 2(12-6)}{12-2} = \frac{8 \times 4 + 2 \times 6}{10}$$

$$= \frac{44}{10} = 4.4 \text{ mv}$$

$$\text{DUTY CYCLE} = \frac{t_p}{T} = \frac{6-2}{12-2} = \frac{4}{10} = 0.4$$



④ TRANSFORMER

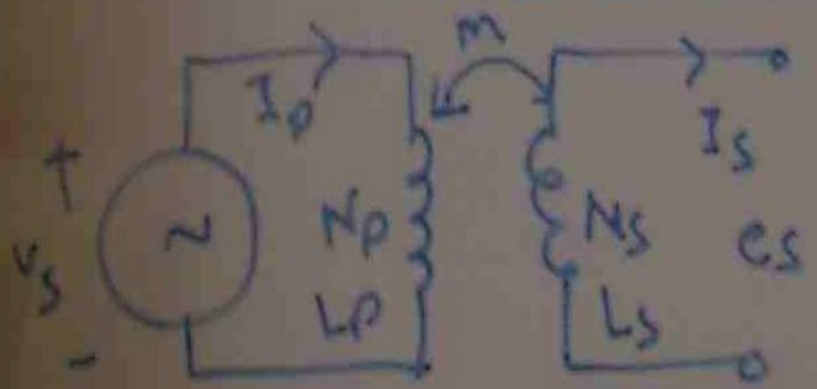


$$e_p = L_p \frac{dI_p}{dt}$$

$$e_p = N_p \frac{d\phi_p}{dt}$$
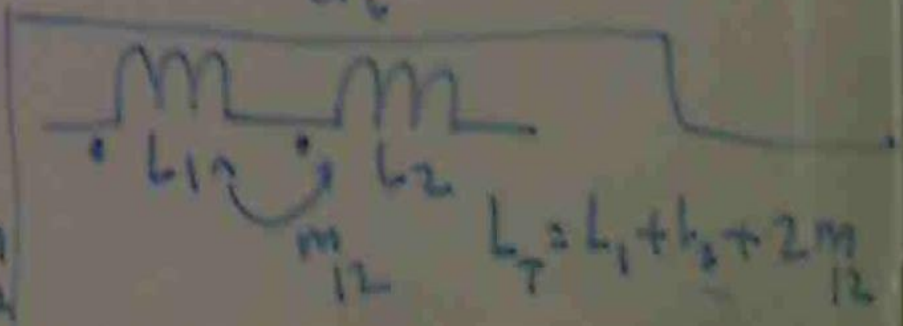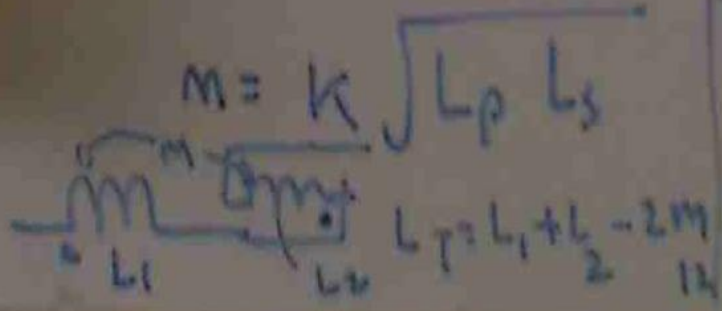
$$e_s = L_s \frac{dI_s}{dt}, \quad e_s = N_s \frac{d\phi_s}{dt}$$



TRANSFORMER

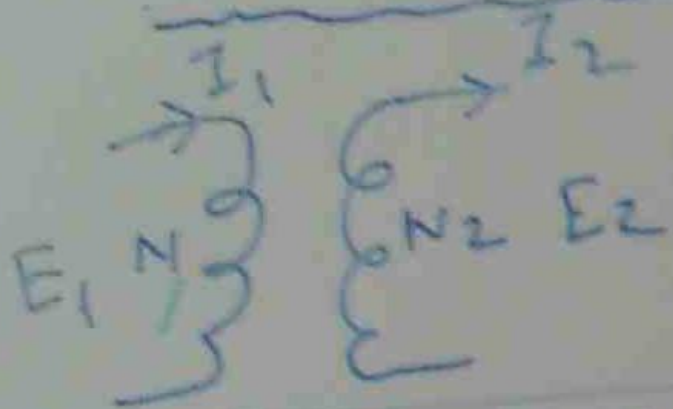

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$\phi_{\text{m}} = \text{FLUX}$

$$E_1 = 4.44 f N_1 \phi_{\text{m}}$$

$f = \text{FREQUENCY}$

$E_1 = \text{PRIMARY VOLTAGE}$ } $N_1 = \text{PRIMARY TURN}$

$E_2 = \text{SECONDARY VOLTAGE}$ } $N_2 = \text{SECONDARY TURN}$


$I_1 = \text{PRIMARY CURRENT}$

$I_2 = \text{SECONDARY CURRENT}$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = a$$

$a = \text{TURN RATIO}$

Pb
 $E_p = 200V$
 $N_p = 50$

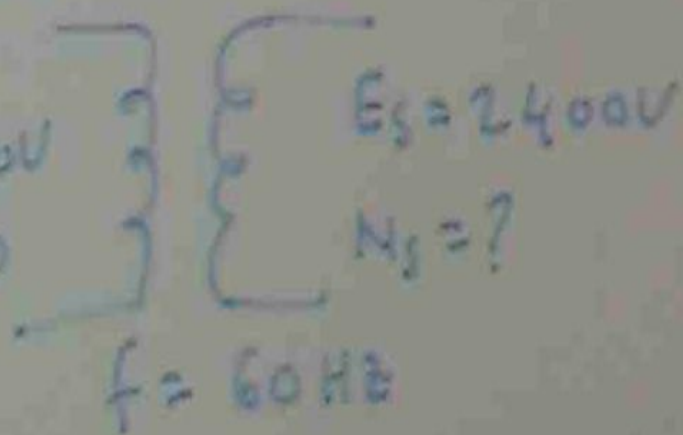

CALCULATE

(a) MAXIMUM FLUX

ϕ_m

(b) SECONDARY TURNS


N_s

$$E_p = 4.44 N_p f \phi_m$$

$$\phi_m = \frac{E_p}{4.44 \times N_p \times f} = \frac{200}{4.44 \times 50 \times 60} = 15.02 \times 10^{-3} \text{ wb}$$


$$\frac{E_p}{E_s} = \frac{N_p}{N_s} \rightarrow N_s = \frac{E_s N_p}{E_p} = \frac{2400 \times 50}{200} = 600 \text{ TURNS}$$

REFLECTED IMPEDANCE & POWER

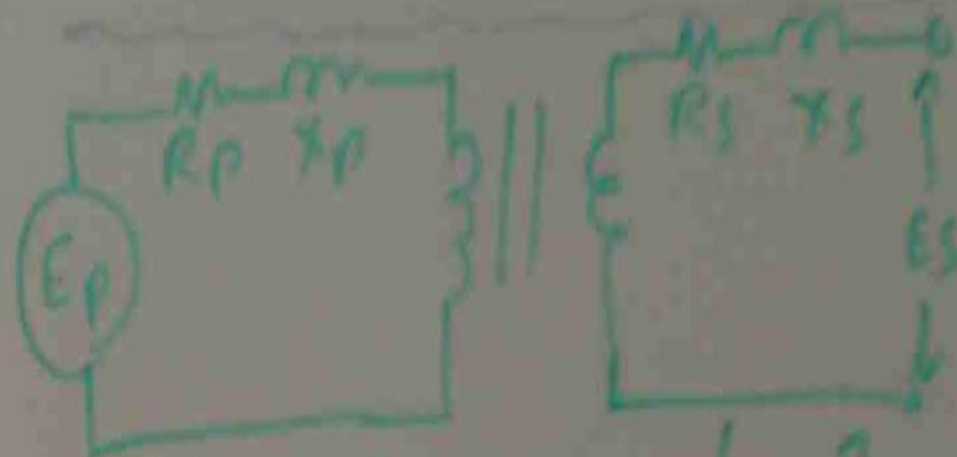

$$R_s' = a^2 R_s, \quad X_s' = a^2 X_s, \quad Z_s' = a^2 Z_s$$

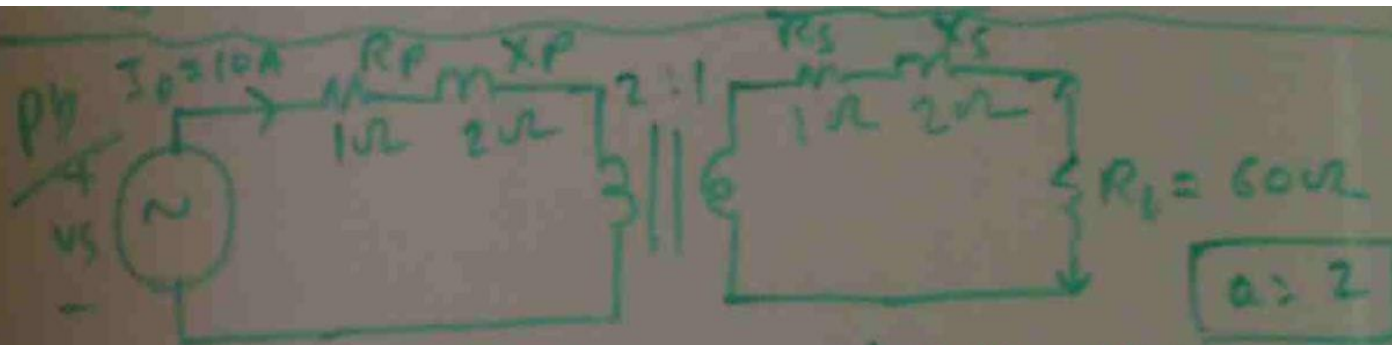- R_s' = SECONDARY RESISTANCE REFER TO PRIMARY
- X_s' = SECONDARY REACTANCE REFER TO PRIMARY
- Z_s' = SECONDARY IMPEDANCE REFER TO PRIMARY



DETERMINE (a) R_e , X_e , (b) V_L , V_s

$$(a) R_e = R_p + a^2 R_s = 1 + 2^2 \times 1 = 5\Omega$$

$$X_e = X_p + a^2 X_s = 2 + 2^2 \times 2 = 10\Omega$$

$$(b) a V_L = I_p \times a^2 R_L = 10 \times 2^2 \times 60 = 2400V$$

$$V_L = \frac{2400}{a} = \frac{2400}{2} = 1200V$$

$$V_s = I_p (R_e + a^2 R_L + j X_e)$$

$$= 10 (5 + 2^2 \times 60 + j 10)$$

$$= 10 (245 + j 10) = 10 \sqrt{245^2 + 10^2} = 2452.04V$$

⑥ DECIBEL, FILTERS, BODE PLOTS



$$\text{VOLTAGE GAIN} = \frac{V_2}{V_1} \quad \text{POWER GAIN} = \frac{P_2}{P_1}$$
$$\text{CURRENT GAIN} = \frac{I_2}{I_1}$$

DECIBEL

$$\text{dB POWER GAIN} = 10 \log_{10} \frac{P_2}{P_1}$$

$$\text{dB VOLTAGE GAIN} = 20 \log_{10} \frac{V_2}{V_1}$$

$$\text{dB CURRENT GAIN} = 20 \log_{10} \frac{I_2}{I_1}$$

pb IF A SYSTEM HAS A VOLTAGE GAIN OF 36 dB, FIND THE APPLIED VOLTAGE IF OUTPUT VOLTAGE IS 6.8V

$$\text{dB VOLTAGE} = 20 \log_{10} \frac{V_o}{V_i}$$

$$36 = 20 \log_{10} \frac{6.8}{V_i}$$

$$\frac{36}{20} = \log_{10} \frac{6.8}{V_i} \rightarrow$$

$$1.8 = \log_{10} \frac{6.8}{V_i}$$


$$\frac{6.8}{V_i} = 10^{1.8}$$

$$V_i = \frac{6.8}{10^{1.8}}$$

$$= 0.109V$$


FILTERS

RC LOW PASS FILTER

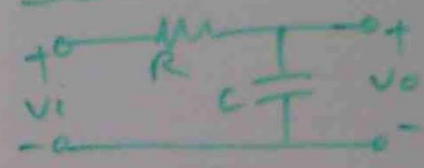




$$V_o = \frac{V_i}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}}$$

RC HIGH PASS FILTER

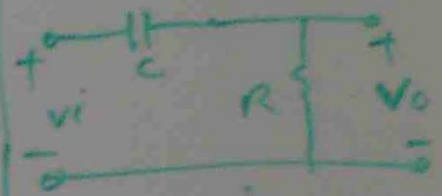




$$V_o = \frac{V_i}{\sqrt{\left(\frac{X_C}{R}\right)^2 + 1}}$$

BAND PASS FILTER

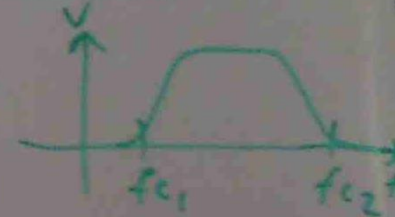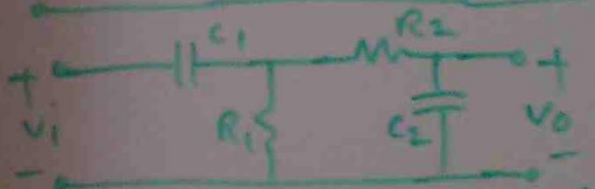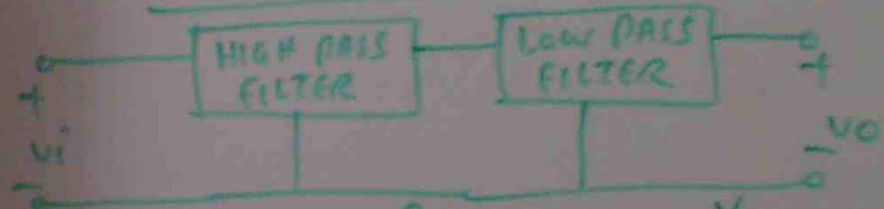


$$f_{c1} = \frac{1}{2\pi R_1 C_1}, \quad f_{c2} = \frac{1}{2\pi R_2 C_2}$$

BAND STOP FILTER

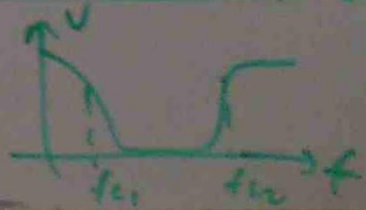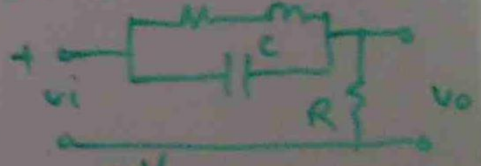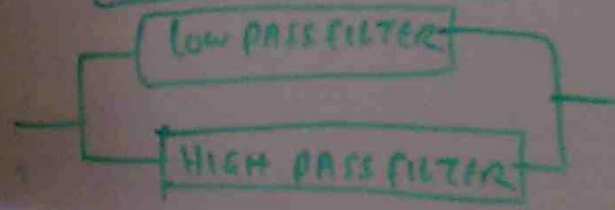

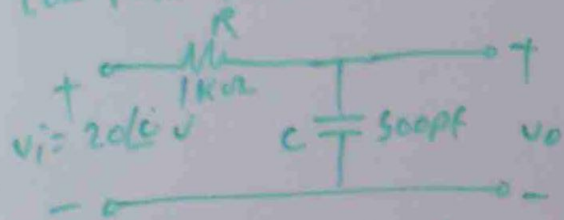Pb SKETCH THE OUTPUT VOLTAGE V_o VERSUS FREQUENCY FOR GIVEN LOW PASS FILTER



$$f_c = \frac{1}{2\pi RC} = \frac{1}{2 \times 3.1416 \times 1 \times 10^3 \times 500 \times 10^{-12}} = 318.31 \text{ kHz}$$


$$V_o = \frac{V_i}{\sqrt{\left(\frac{R}{X_c}\right)^2 + 1}} = \frac{V_i}{\sqrt{(2\pi f C R)^2 + 1}}$$

$$f = 10 \text{ kHz} \rightarrow 100 \text{ kHz} \rightarrow 1 \text{ MHz} \rightarrow 10 \text{ MHz}$$


$$f = 10 \text{ kHz} (V_o) = \frac{20}{\sqrt{(2 \times 3.14 \times 10 \times 10^3 \times 500 \times 10^{-12} \times 1 \times 10^3)^2 + 1}} \approx 20 \text{ V}$$

$$f = 100 \text{ kHz} \rightarrow V_o = 19.08 \text{ V} \quad f = 1 \text{ MHz} \rightarrow V_o = 6.1 \text{ V}$$
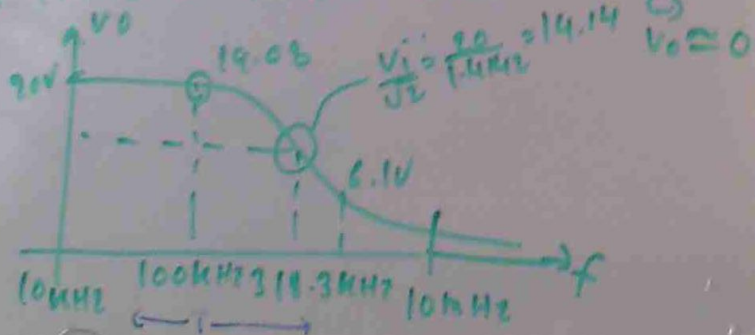
$$f = 1 \text{ MHz} \rightarrow V_o = 6.1 \text{ V} \quad f = 10 \text{ MHz} \rightarrow V_o \approx 0$$



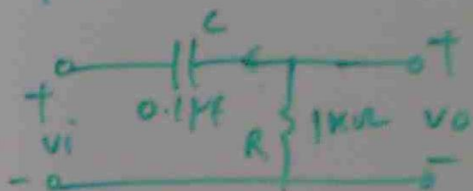P6 SKETCH $A_{v,dB}$ FOR GIVEN HIGH PASS FILTER CIRCUIT



$$f_c = \frac{1}{2\pi RC}$$


$$= \frac{1}{2\pi \times 10^3 \times 0.1 \times 10^{-6}}$$

$$= 1592.36 \text{ Hz}$$

$$|A_{v,dB}| = 20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f_c}{f}\right)^2}}$$

f 100 Hz → 200 Hz → 1 kHz → 1.59 kHz → 10 kHz


f	$A_{v,dB}$	dB
100 Hz	$20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{1592}{100}\right)^2}}$	-24
200	$20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{1592}{200}\right)^2}}$	-20
1 kHz / 1000	$20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{1592}{1000}\right)^2}}$	-6
1.59 kHz	$20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{1592}{1592}\right)^2}}$	-3
10 kHz	$20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{1592}{10000}\right)^2}}$	0

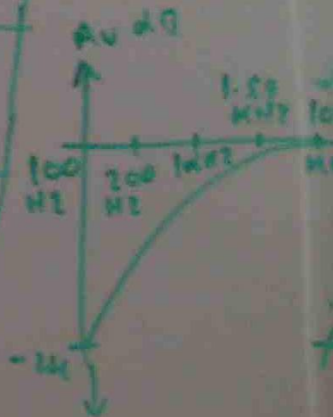

80 sin wt

$$X_L = 27fL$$

$$= 250 \times 0.2 = 50 \Omega$$

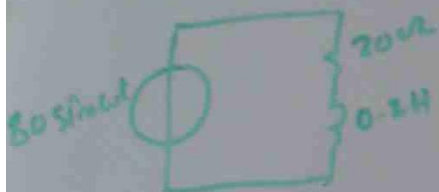

$$\omega = 250 \text{ rad/sec}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{20^2 + 50^2}$$

$$= 53.85 \Omega$$

$$\theta = \tan^{-1} \frac{50}{20} = 68.2^\circ$$

$$I = \frac{E}{Z} = \frac{80}{53.85} = 1.49, \quad I = \frac{1.49}{\sqrt{2}} \sin(250t - 68.2^\circ)$$

$$= 1.05 \sin(250t - 68.2^\circ)$$

20 sin 3wt

$$X_L = 3\omega L = 3 \times 250 \times 0.2$$

$$= 150 \Omega$$



$$Z = \sqrt{20^2 + 150^2} = 151.3 \Omega$$

$$\theta = \tan^{-1} \frac{150}{20} = 82.4^\circ$$

$$I = \frac{E}{Z} = \frac{20}{151.3} = 0.132, \quad I = \frac{0.132}{\sqrt{2}} \sin(750t - 82.4^\circ)$$

$$I = 0.093 \sin(750t - 82.4^\circ)$$

$$E_{\text{rms}} = \sqrt{25^2 + \left(\frac{80}{\sqrt{2}}\right)^2 + \left(\frac{20}{\sqrt{2}}\right)^2} = 63.5 \text{ V}$$

$$I_{\text{rms}} = \sqrt{1.25^2 + \left(\frac{1.44}{\sqrt{2}}\right)^2 + \left(\frac{0.192}{\sqrt{2}}\right)^2} = 1.64 \text{ A}$$

$$\begin{aligned} \text{TOTAL POWER} &= 1.25^2 \times 20 + 1.05^2 \times 20 + 0.093^2 \times 20 \\ &= 53.5 \text{ WATT} \end{aligned}$$
