

50A

小野
SHOYANG
中国
YIAC

STATUS
DATE
TEST

3-140

500V

 **AMPROBE®**

MODEL: PF1050

VOLT/AMP/POWER FACTOR

ELECTRICAL ENGINEERING
CERTIFICATE

PLANT NO. B72720.


LEADING P.F.
INDICATOR 

VOLTS/AMPS RANGE

0-999  0-999

AMPS  PF
VOLTS

00.9

434996

AMPROBE®

MODEL: PF1050

VOLT/AMP/POWER FACTOR

ELECTRICAL ENGINEERING
CERTIFICATE

PLANT NO. 372720.

LEADING P.F.
INDICATOR

VOLTS/AMPS RANGE
0-999 - 0-999

AMPS - PF
VOLTS

23.3

134996

FOR FACTORY SERVICE: AMPROBE INSTRUMENT, LYNBROOK, N.Y. 11563
Part No. 981670 Rev. A
4/83

1. Connect the power cord to the power line being measured. The power factor is displayed in the display window. The power factor is 1.00 when the load is purely resistive. The power factor is less than 1.00 when the load is inductive. The power factor is greater than 1.00 when the load is capacitive.

2. Set "VOLTS-VOLTS-PF" switch to "VOLTS".

3. Set "VOLTS-VOLTS-PF" switch to "AMPS".


4. Connect the current transducer to the conductor to be measured. The current is displayed in the display window. The current is 0.00 when the conductor is not connected. The current is greater than 0.00 when the conductor is connected.

5. If the current transducer is connected to the conductor, the current is displayed in the display window. The current is 0.00 when the conductor is not connected. The current is greater than 0.00 when the conductor is connected.

6. A blinking display indicates that the current being measured is in excess of the range setting.


7. A blinking display indicates that the current being measured is in excess of the range setting.

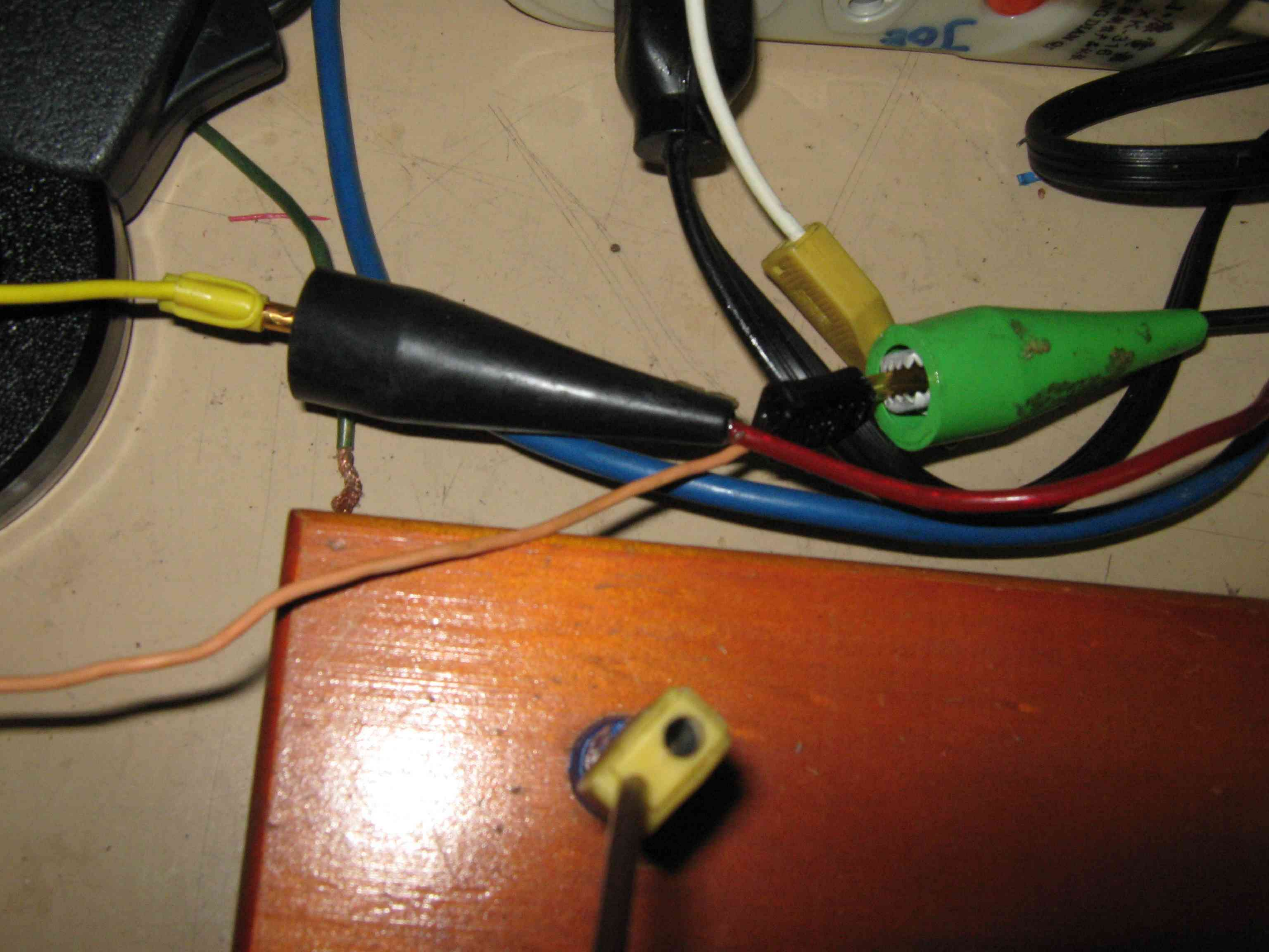8. A blinking display indicates that the current being measured is in excess of the range setting.




3 ϕ 4 WIRE / 3 WIRE BALANCED & UNBALANCED LOAD


CONNECT THE CIRCUIT

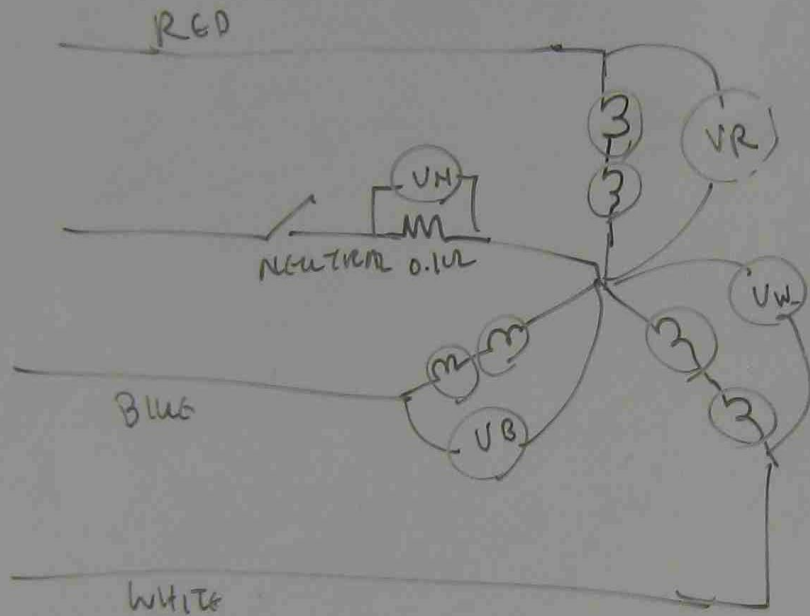

CONDITION	NEUTRAL WIRE
ALL LAMPS	ON
ONE LAMP IN BLUE PHASE IS OFF	ON
ONE LAMP IN BLUE PHASE IS OFF	OFF


Condition	NEUTRAL WIRE	V_R	V_W	V_B	V_N	$I = \frac{V_N}{0.1\Omega} =$
ALL LAMPS	ON					
ONE LAMP IN BLUE PHASE IS OFF	ON					
ONE LAMP IN BLUE PHASE IS OFF	OFF					

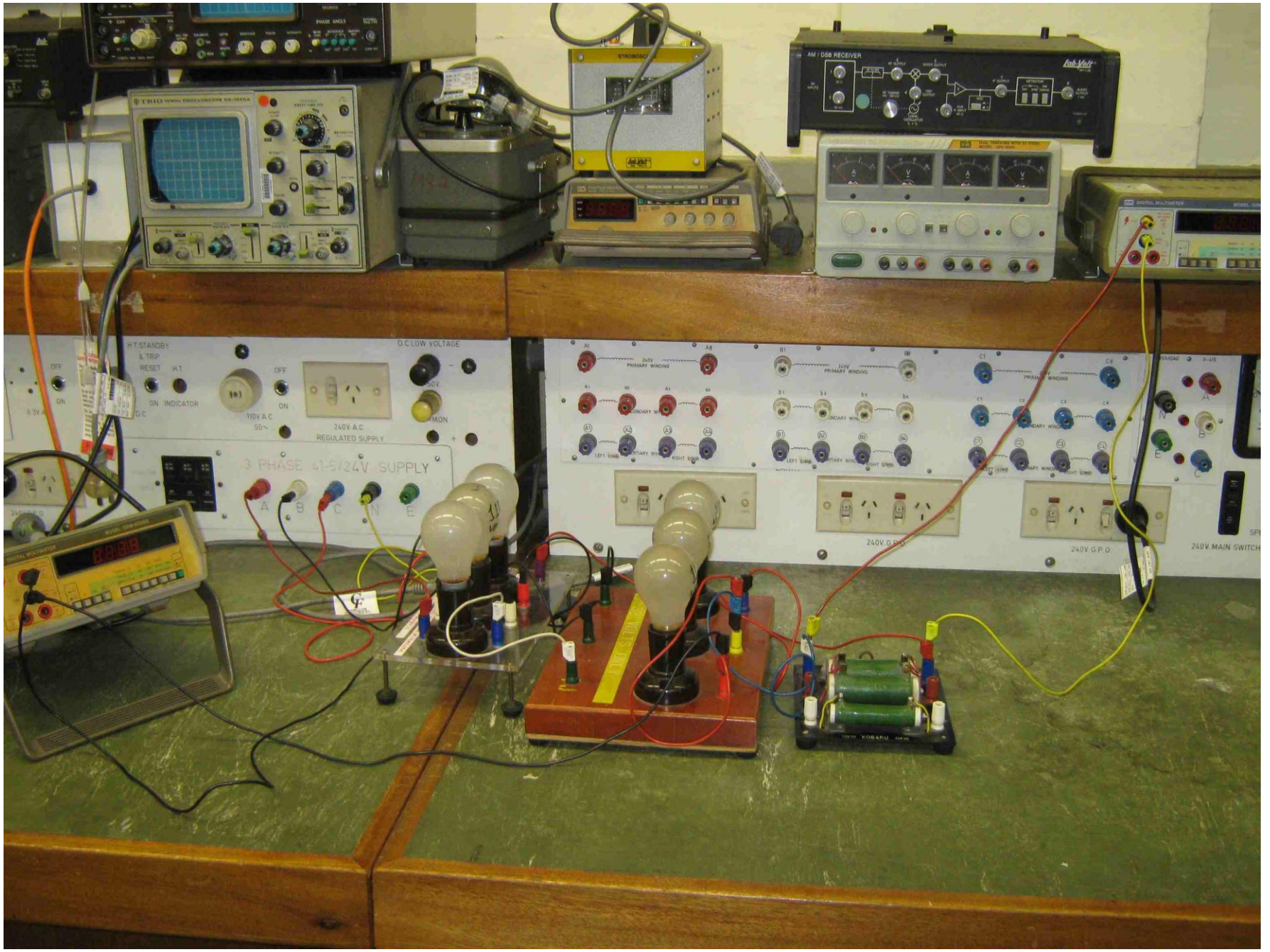


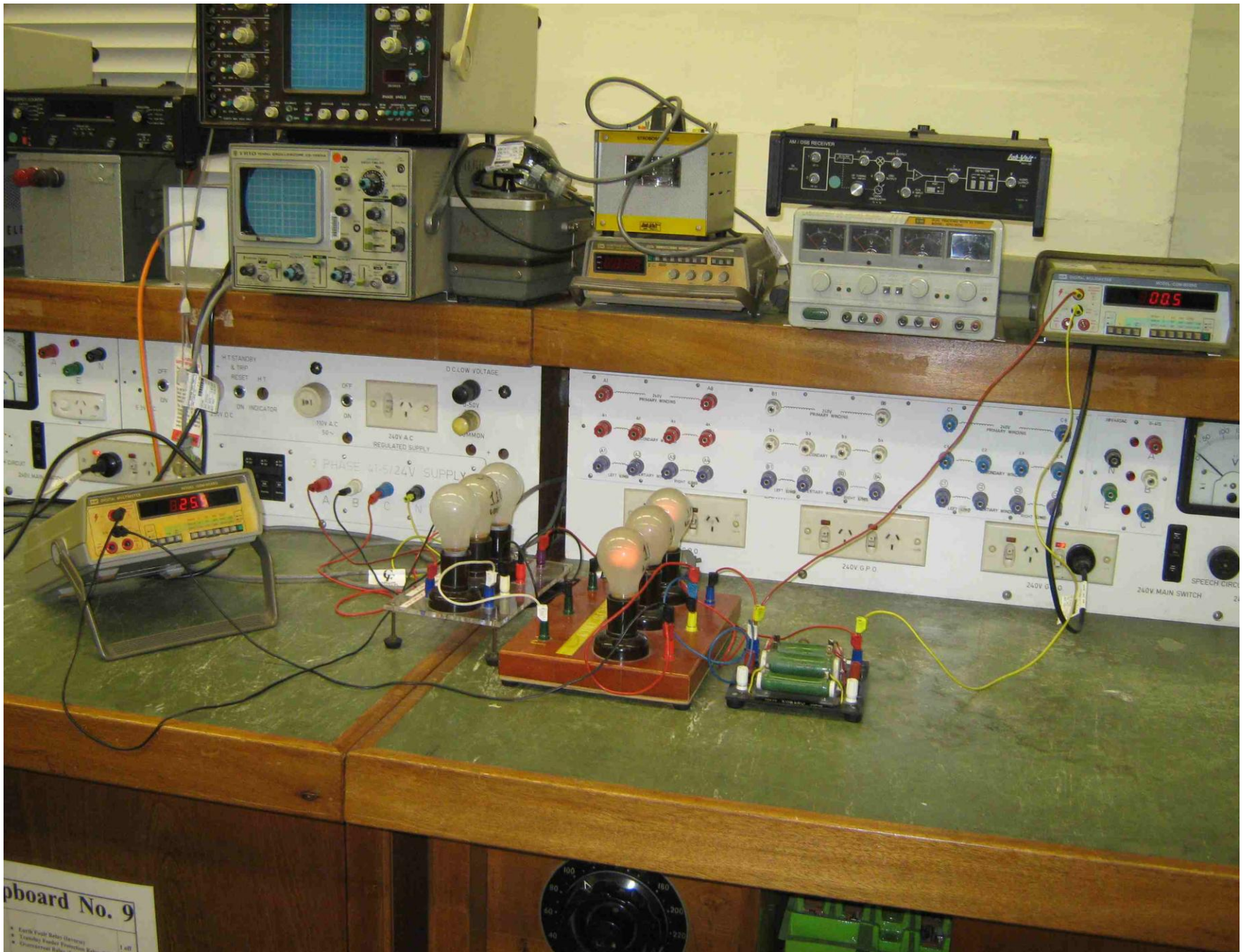

board No. 9

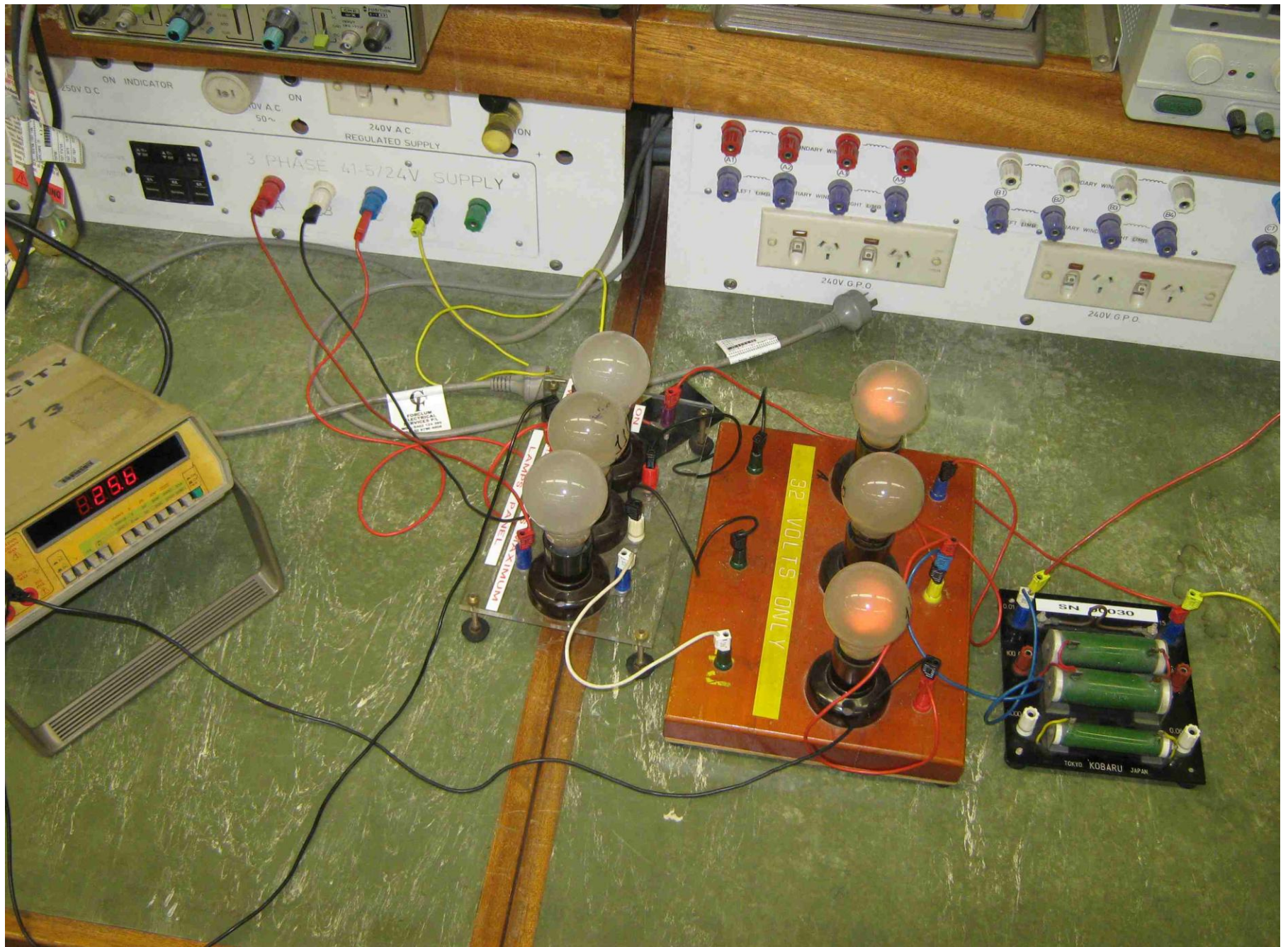- Earth Fault Relay (Electrical)
- Transformer (Electrical)
- Capacitor Bank (Electrical)



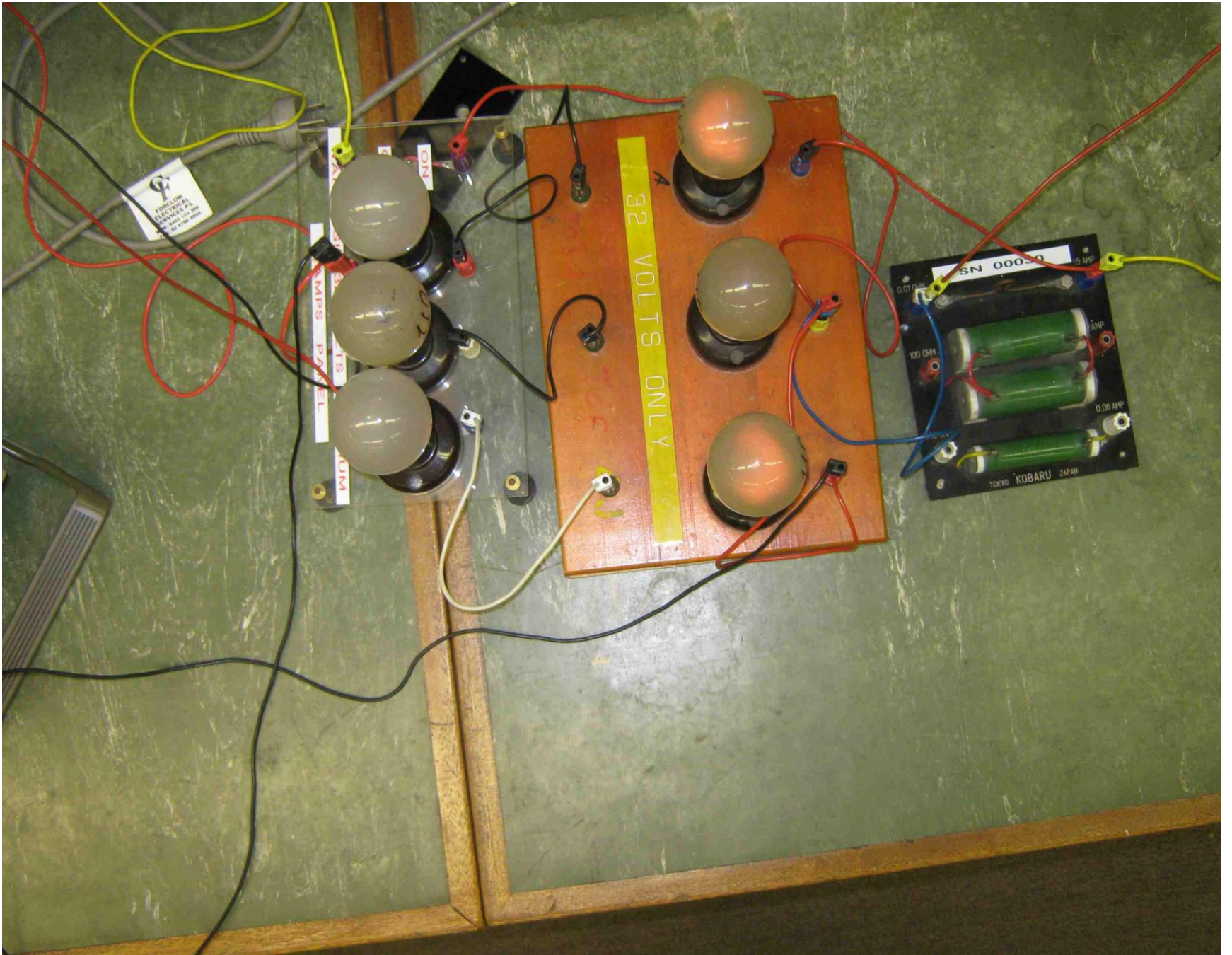





MAXIMUM POWER TRANSFER THEOREM

WHEN LOAD RESISTANCE IS EQUAL TO SOURCE RESISTANCE, MAXIMUM POWER IS TRANSFERRED


CONSIDER THE CIRCUIT

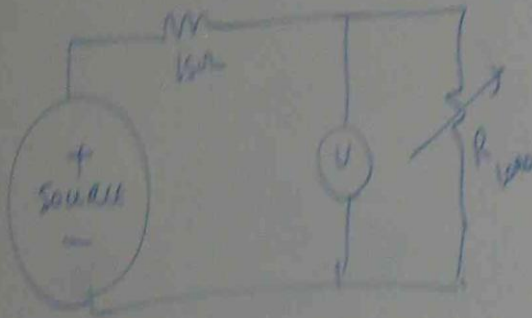

STEP	V	R_{LOAD}	Power $\frac{V^2}{R_{LOAD}}$
1	-	10Ω	Power 1
2	-	11Ω	Power 2
3	-	12Ω	
4	-	13Ω	
5	-	14Ω	
6	-	15Ω	
7	-	16Ω	
8		17Ω	
9		18Ω	
10		19Ω	
11		20Ω	

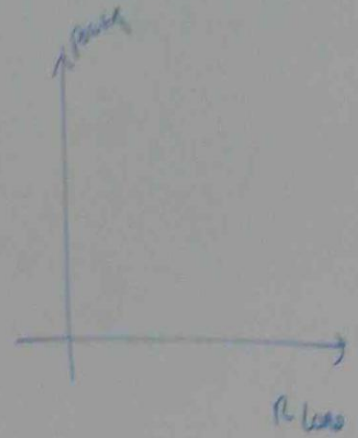

DRAW THE GRAPH

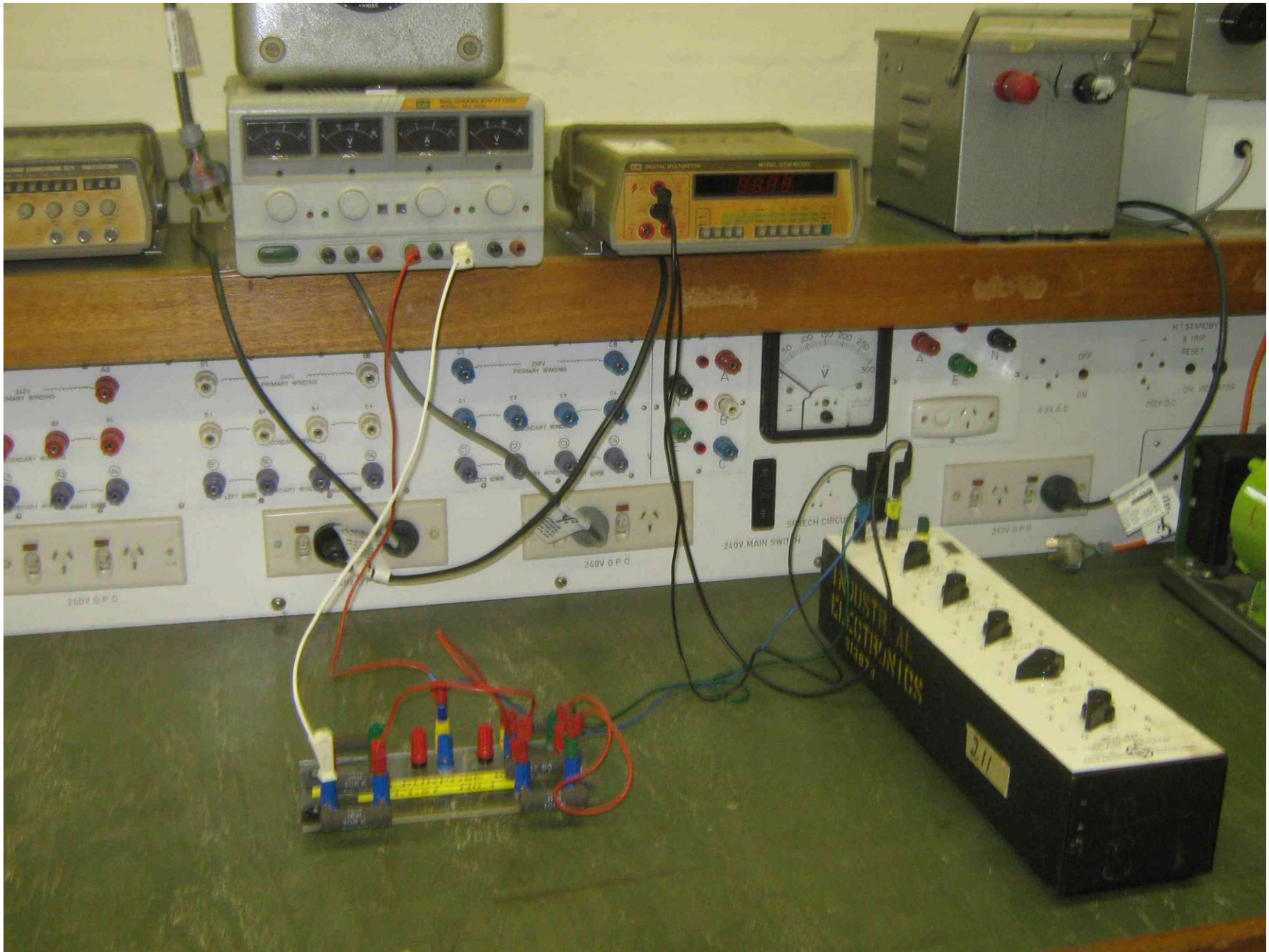


PRACTICAL

MAXIMUM POWER TRANSFER THEOREM

MAXIMUM POWER IS TRANSFERRED WHEN SOURCE IMPEDANCE IS EQUAL TO LOAD IMPEDANCE

CONNECT THE GIVEN CIRCUIT

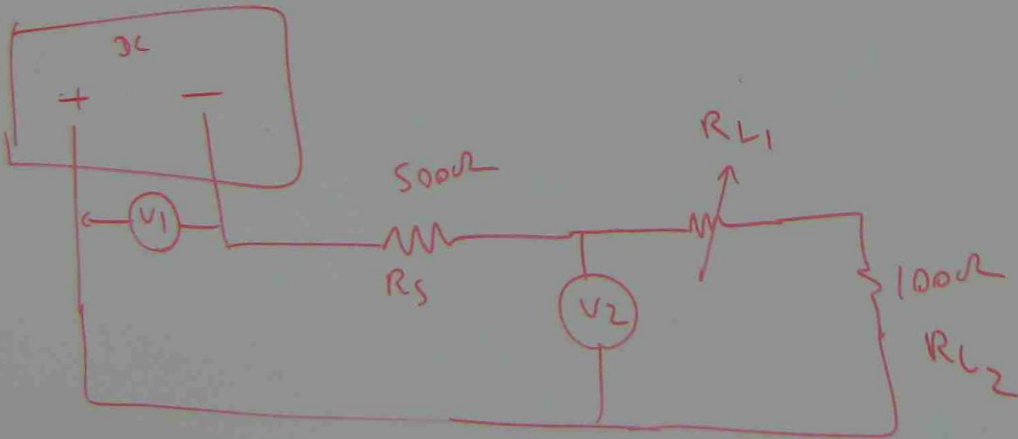

VARY R_{L1} & NOTE V_2

R_{L1}	R_{L2}	R_{L1}
0	100Ω	
100	100	
200	100	
300	100	
400	100	
500	100	
600	100	
700	100	
800	100	

DRAW THE GRAP

VARY R_{L1} & NOTE V_2

R_{L1}	R_{L2}	$R_{LT} = R_{L1} + R_{L2}$	V_2	$P = \frac{V_2^2}{R_{LT}}$ WATT
0	100Ω			
100	100			
200	100			
300	100			
400	100			
500	100			
600	100			
700	100			
800	100			

1000Ω
} R_{L2}




EQUAL TO LOAD

BY R_{L1} & NOTE V_2

R_{L1}	R_{L2}	$R_{LT} = R_{L1} + R_{L2}$	V_2	$P = \frac{V_2^2}{R_{LT}}$ WATT
0	100 Ω			
100	100			
200	100			
300	100			
400	100			
500	100			
600	100			
700	100			
800	100			


DRAW THE GRAPH

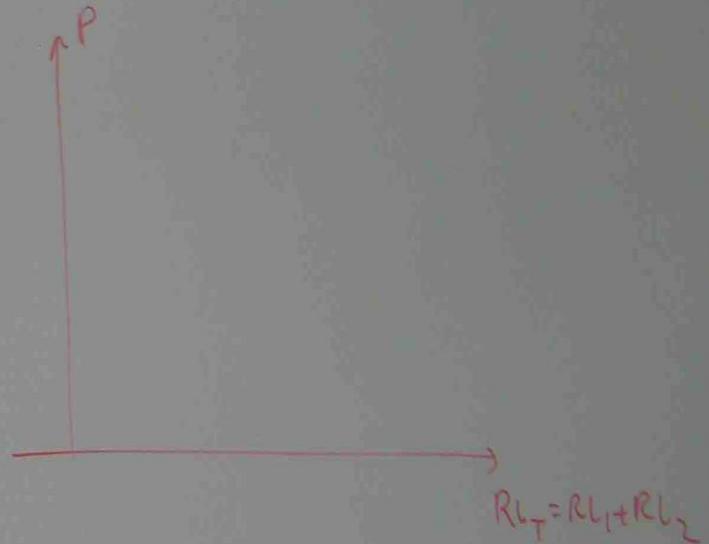

SERIES RLC CIRCUIT

TO STUDY THE BEHAVIOUR OF RLC CIRCUIT

(I) CONNECT THE CIRCUIT

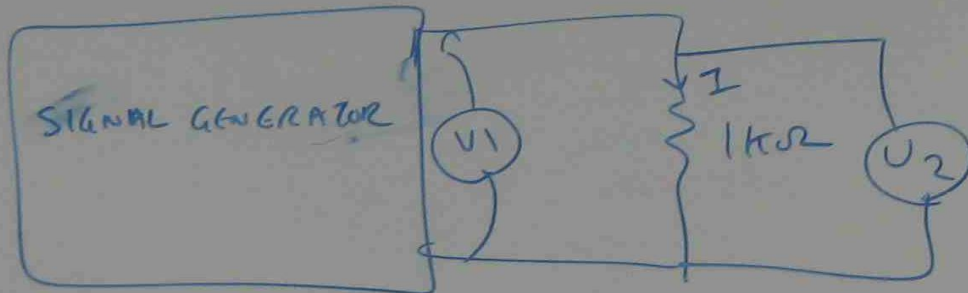

$$I = \frac{V}{R}$$


INCREASE FREQUENCY 10 TO 100 Hz,

fff	V ₂	$I_R = \frac{V_2}{1000\Omega}$
10 Hz 20 Hz		
50 Hz 70 Hz 100 Hz		

COMMENT = ?

II

CONNECT THE CIRCUIT

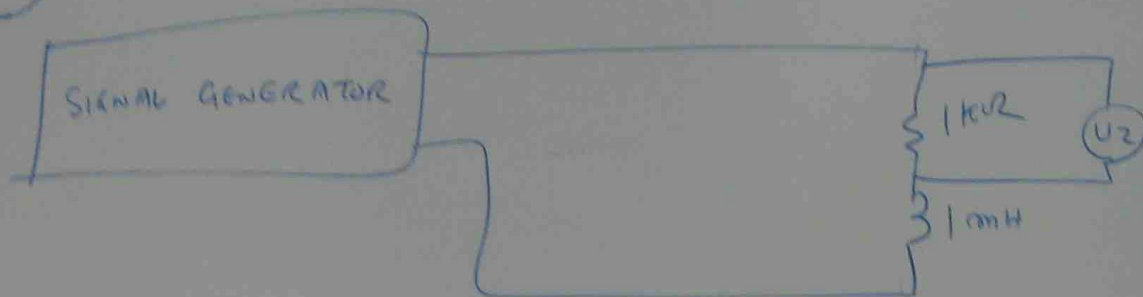


INCREASE FREQUENCY, MAKE COMMENT

f	U_2	$I = \frac{U_2}{1k\Omega}$
10		
20		
50		
70		
100 Hz		

$$I = \frac{U}{\sqrt{R^2 + X_L^2}}$$
$$= \frac{U}{\sqrt{R^2 + (2\pi fL)^2}}$$

MAKE COMMENT = ?

CONNECT THE CIRCUIT

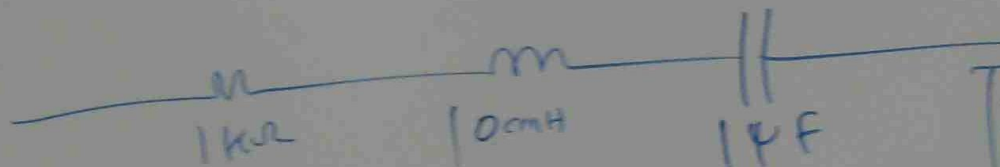

$$Z = R + jX_L + (-jX_C)$$
$$= R + j(X_L - X_C)$$

CALCULATE RESONANT FREQUENCY

$$X_L = X_C \Rightarrow 2\pi fL = \frac{1}{2\pi fC}$$

$$2\pi^2 f^2 LC = 1$$

$$f = \sqrt{\frac{1}{2\pi^2 LC}} = \frac{1}{2\pi\sqrt{LC}}$$


$$= \frac{1}{2 \times 3.1416 \sqrt{10 \times 10^{-3} \times 1 \times 10^{-6}}}$$

$$= 50 \text{ Hz}$$



CONNECT THE CIRCUIT

AT RESONANT POINT

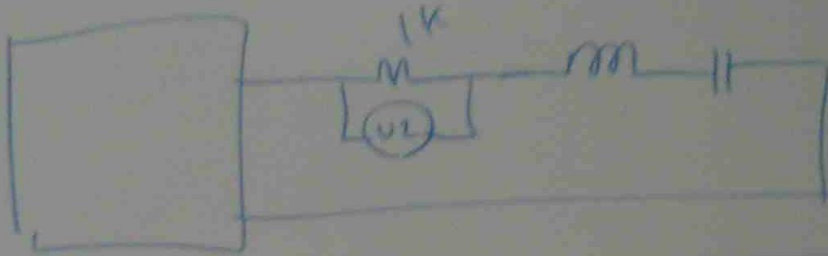



$$I = \frac{V}{R + j(\omega L - \frac{1}{\omega C})}$$

↑
CANCEL

f	V2	$I = \frac{V2}{1k}$
10		
20		
30		
40		
50		
60		
70		
80		
90		
100		

How HAPPENS
TO CURRENT?

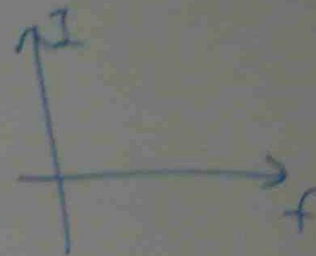

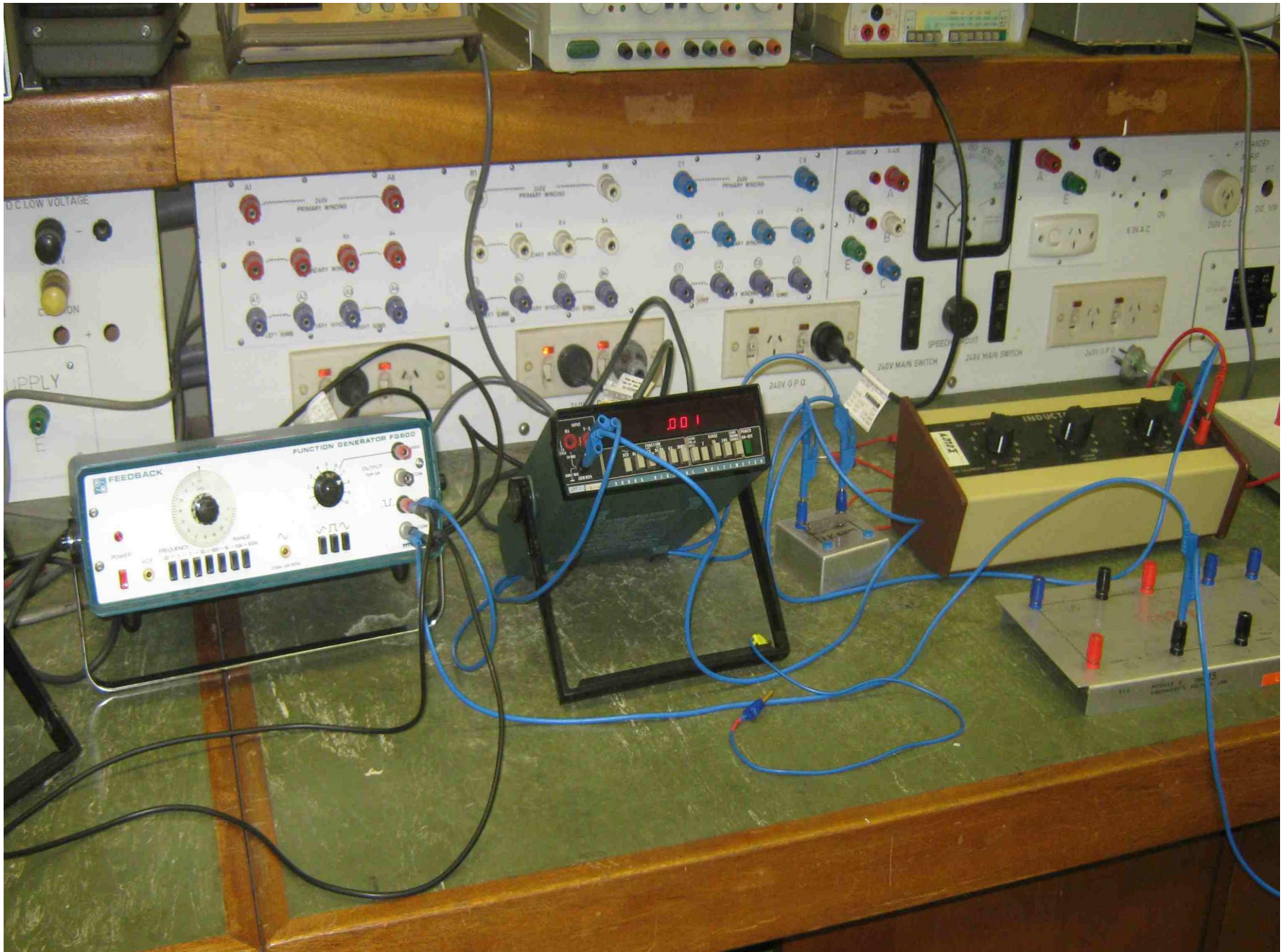



INDUCTANCE

MODEL : SVL 33

AIR CORED

0 1 2 3 4 5 6 7 8 9 10

x100mH
35 mA

0 1 2 3 4 5 6

x10mH
60mA

0 1 2 3 4 5 6 7 8 9 10

x1 mH
75 mA

ELECTRICAL ENGINEERING
CERTIFICATE
70107
PLANT NO.

5% TOLERANCE

200V
2000mA
2000KΩ

POWER
ON-OFF

I M E T E R

1K OHM


AIR CORED


ELECTRICAL ENGINEERING
CERTIFICATE
PLANT NO. E0107


4 5
3
2
1
0

±5% TOLERANCE

x100 mH
35 mA

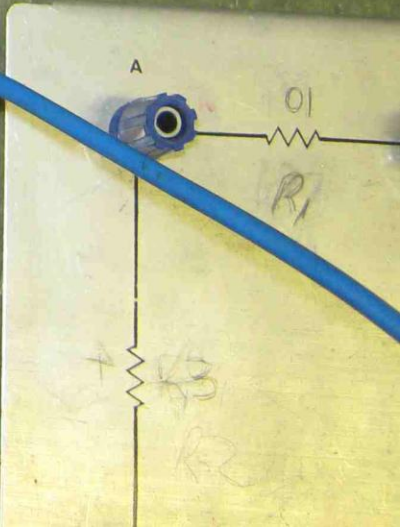


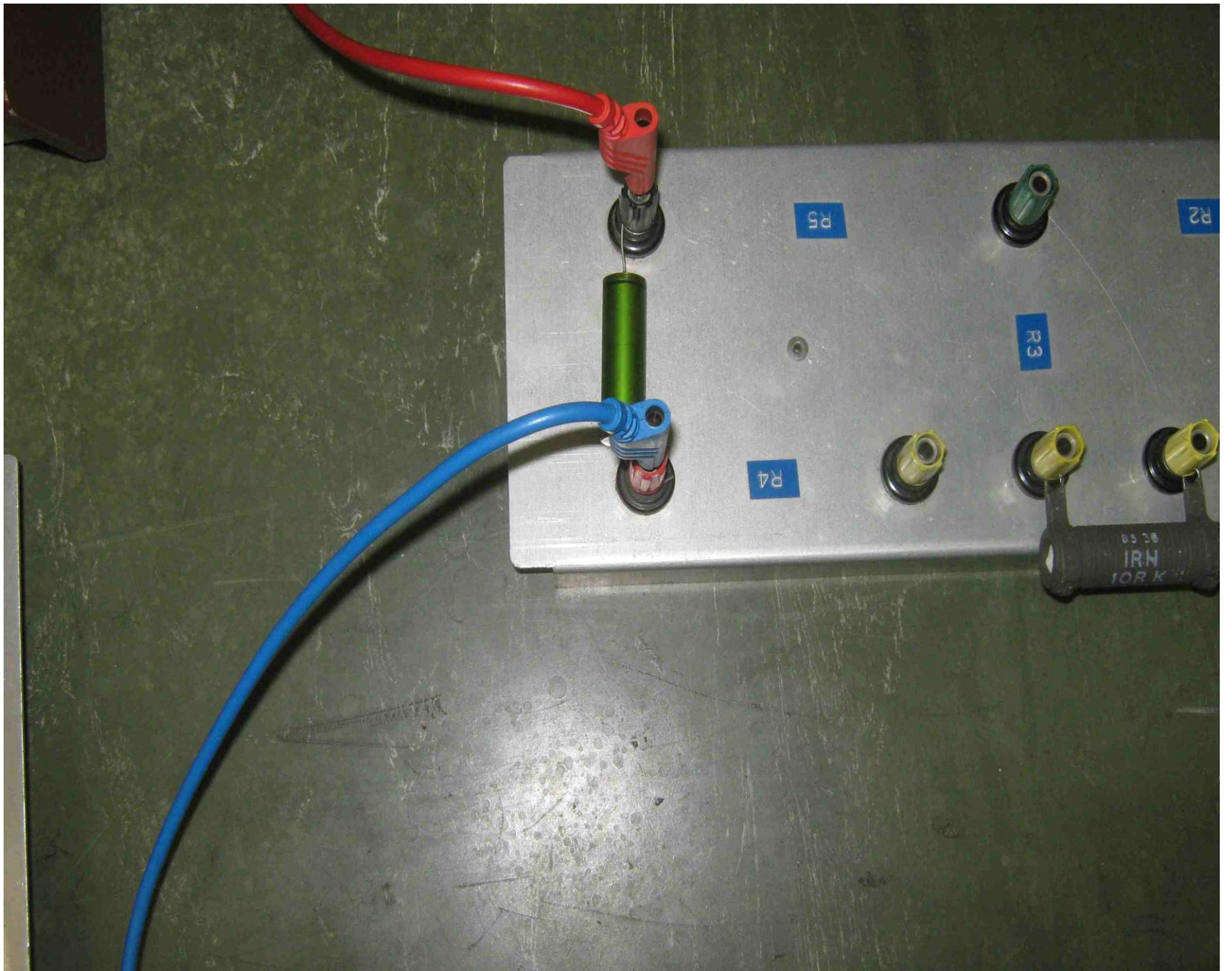

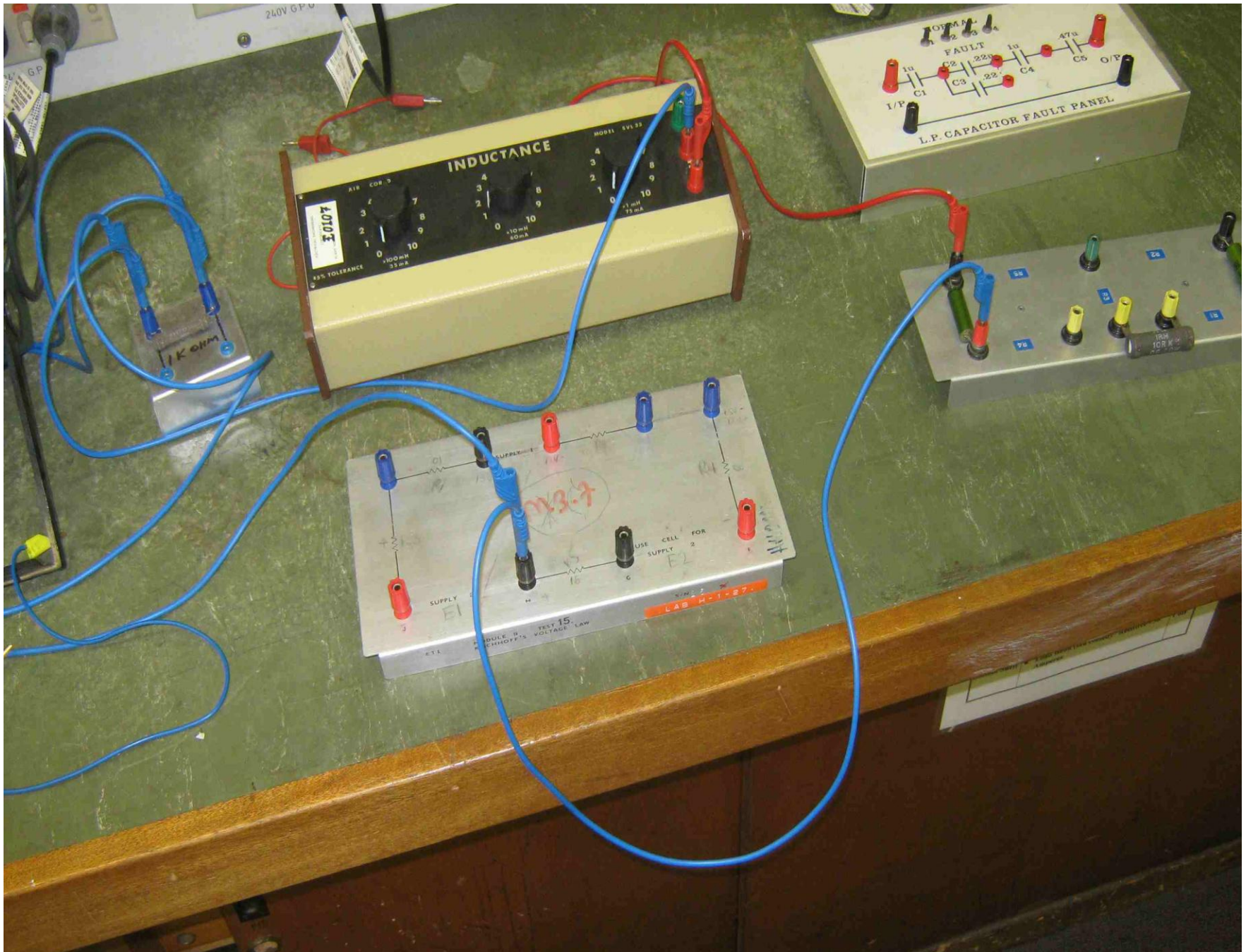


SUPER POSITION THEOREM

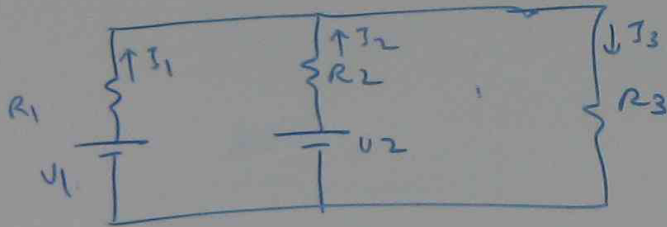THE CURRENTS FLOWS IN A CIRCUIT CAN BE DETERMINED BY KILLING THE SOURCES ALTERNATIVELY AND VECTORIALLY ADDING THE CURRENTS.



KILL V_1 , FIND I_1, I_2, I_3

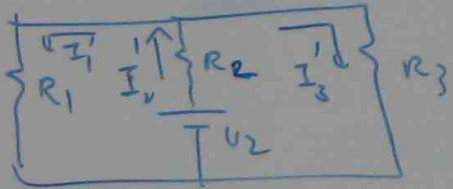


$$I_2' = \frac{V_2}{\frac{R_1 \times R_3}{R_1 + R_3} + R_2}$$

$$I_1' = I_2' \times \frac{R_3}{R_1 + R_3} \quad \downarrow$$

$$I_3' = I_2' \times \frac{R_1}{R_1 + R_3} \quad \downarrow$$

KILL V_2 FIND I_1, I_2, I_3

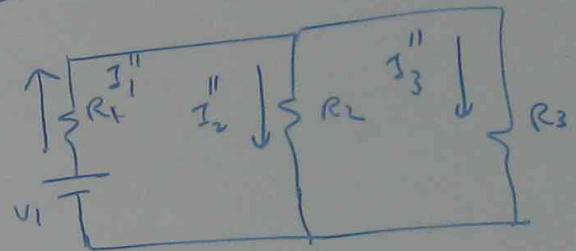

$$I_1'' = \frac{V_1}{R_1 + \frac{R_2 \times R_3}{R_2 + R_3}} \quad \uparrow$$

$$I_2'' = I_1'' \times \frac{R_3}{R_2 + R_3} \quad \downarrow$$


$$I_3'' = I_1'' \times \frac{R_2}{R_2 + R_3} \quad \downarrow$$

$$I_1 = I_1^I + I_1^II = I_2^I \times \frac{R_3}{R_1 + R_3} \downarrow - \frac{V_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} \uparrow$$

$$I_2 = I_2^I + I_2^II = \frac{V_2}{\frac{R_1 \times R_3}{R_1 + R_3} + R_2} \uparrow - I_1^II \times \frac{R_3}{R_2 + R_3} \downarrow$$

$$I_3 = I_3^I + I_3^II = I_2^I \times \frac{R_1}{R_1 + R_3} \downarrow + I_1^II \times \frac{R_2}{R_2 + R_3} \downarrow$$

PRACTICAL (i) CONNECT THE GIVEN CIRCUIT

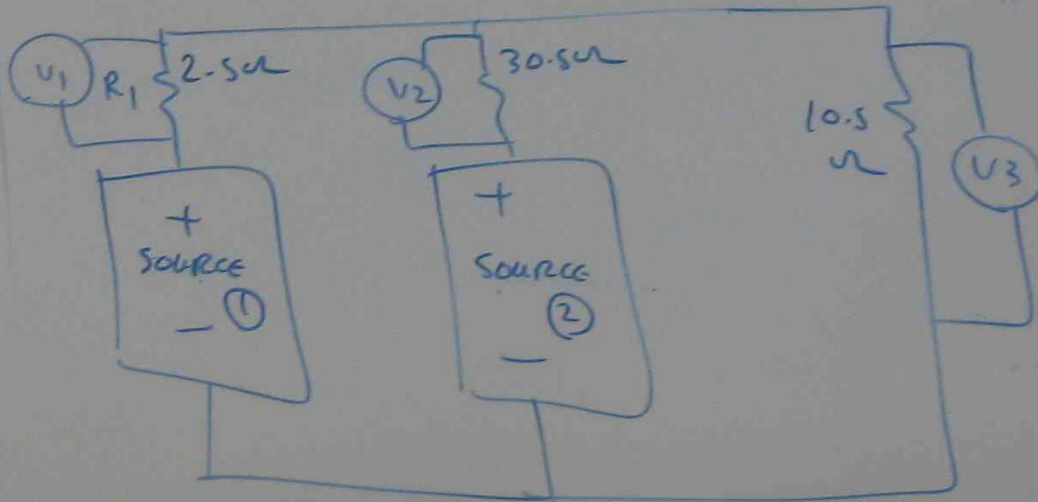

SWITCH ON SOURCE ①, TAKE V_1, V_2, V_3

V_1	$I_1 = \frac{V_1}{R_1}$	V_2	$I_2 = \frac{V_2}{R_2}$	V_3	$I_3 = \frac{V_3}{R_3}$

SWITCH OFF SOURCE ①, SWITCH ON SOURCE ②, TAKE V_1, V_2, V_3

V_1	$I_1'' = \frac{V_1}{R_1}$	V_2	$I_2'' = \frac{V_2}{R_2}$	V_3	$I_3'' = \frac{V_3}{R_3}$



THEN ADD I_1' & I_1'' , I_2' & I_2'' , I_3' & I_3''

$$I_1 = I_1' + I_1'' \quad \left| \quad I_2 = I_2' + I_2'' = \quad \left| \quad I_3 = I_3' + I_3'' \right. \right.$$

SWITCH ON BOTH SOURCE ① & ② TAKE V_1, V_2, V_3

V_1	$I_1 = \frac{V_1}{R_1}$	V_2	$I_2 = \frac{V_2}{R_2}$	V_3	$I_3 = \frac{V_3}{R_3}$

3 ϕ POWER MEASUREMENT

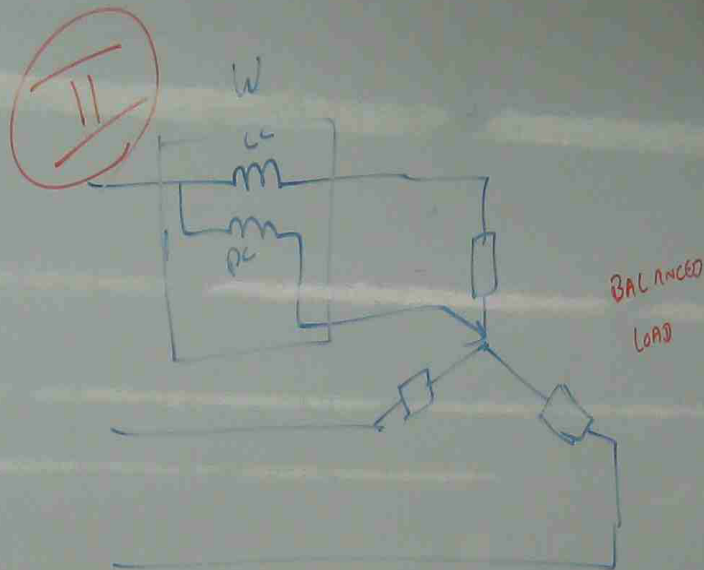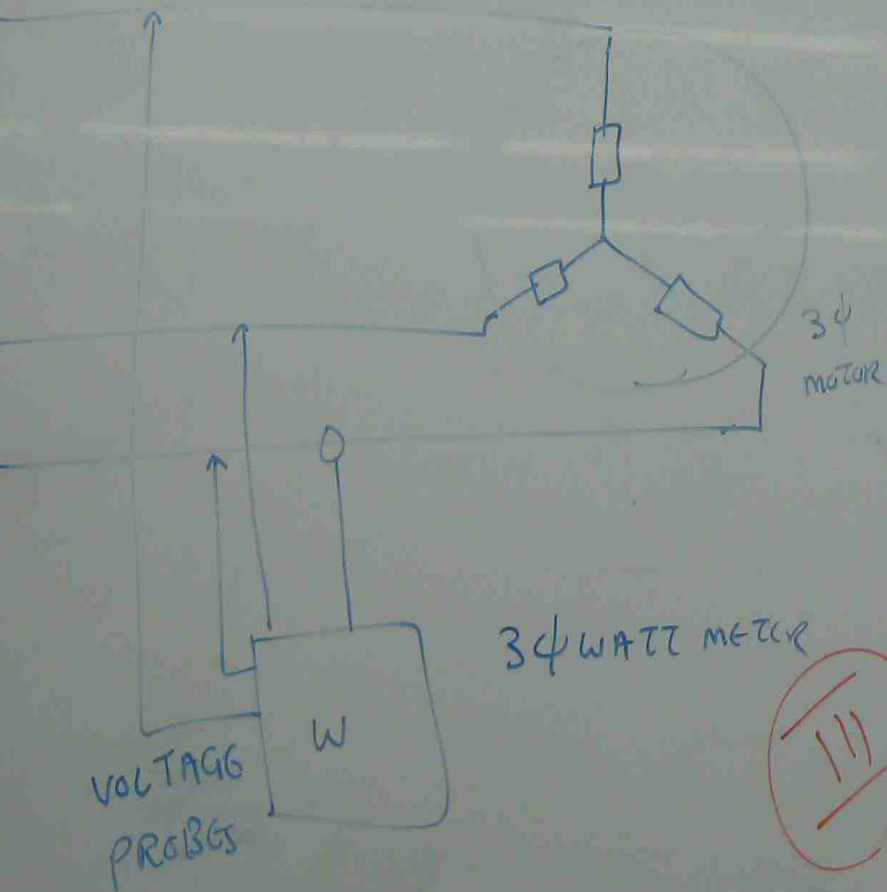


$$3\phi \text{ POWER} = 3 \times \text{WATT METER READING}$$

FOR 1 ϕ



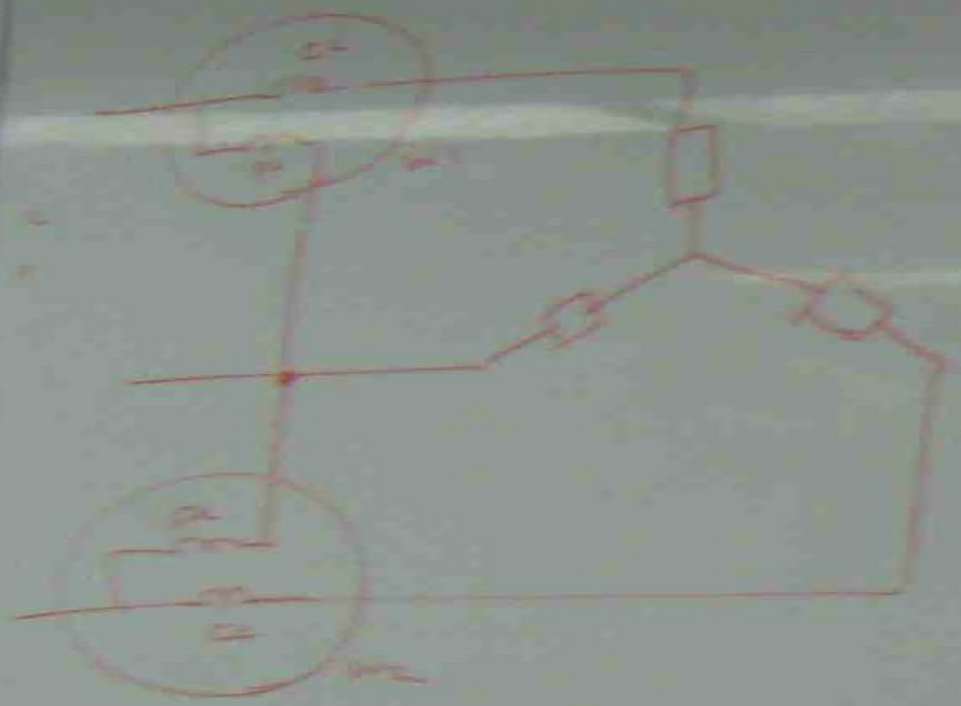TWO WATT METER METHOD FOR 3 ϕ UNBALANCED LOAD




Total power = $3 \times \frac{415}{\sqrt{3}} \times 7$

(I)

3φ power = $3 \times \frac{415}{\sqrt{3}} \times 7$


CONNECT THE CIRCUIT

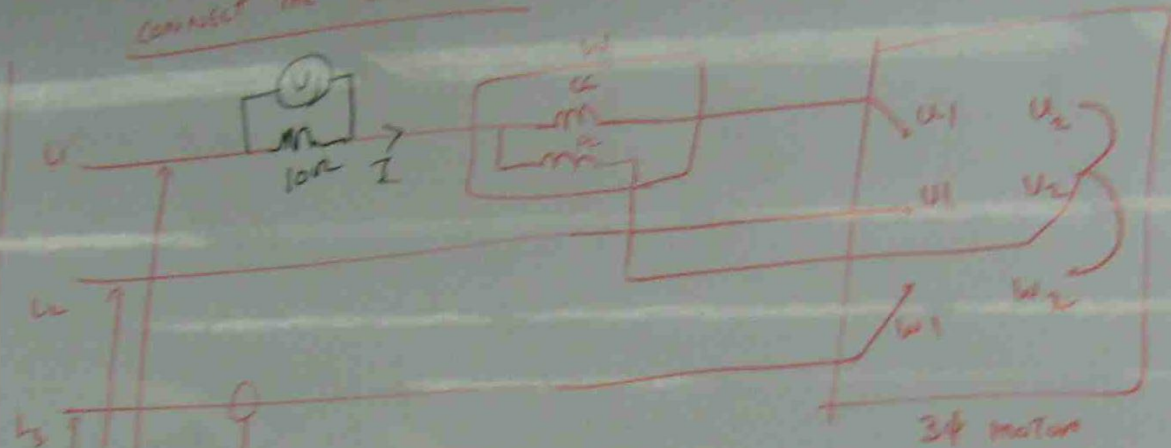

II TAKE VOLTAGE, CURRENT & P.F. READINGS OF POWER ANALYZER.
 $W = V \times I \times PF$

III TAKE ANALOG WATT METER READING, CONSIDER SCALE FACTOR.

EX IF 50V I = 5A SETTINGS

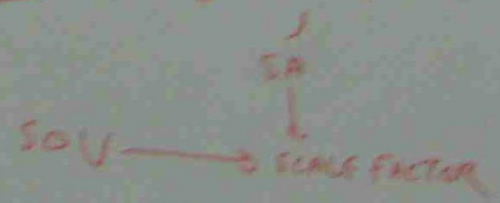

ACTUAL WATT = READING X SCALE FACTOR



3φ motor WATT = 3 X ACTUAL WATT

I $I = \frac{V_1}{10R}$ Amp

3φ power = 3 V I
 (APPROXIMATE)

Customer Service
Centre

TAFE

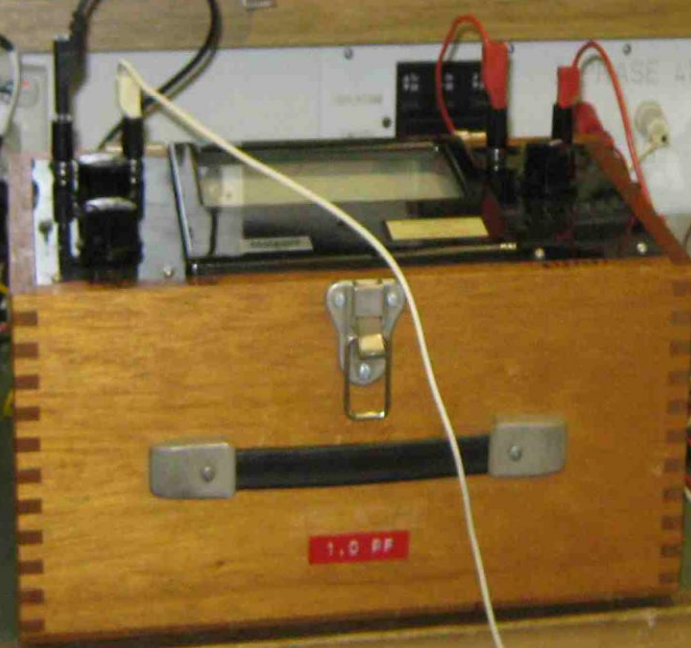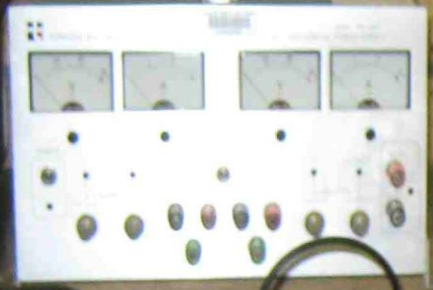

BASE 41-5/24V SUPPLY





CURRENT SWITCH

SCALE FACTORS					
WATTS	25	50	100	250	500
1-25	0.375	0.625	1.25	3.125	6.25
2-5	0.625	1.25	2.5	6.25	12.5
5	1.25	2.5	5.0	12.5	25.0


TO OBTAIN WATTS MULTIPLY READING BY SCALE FACTORS ACCORDING TO POTENTIAL & CURRENT SWITCH SETTINGS

ELECTRICAL ENGINEERING
CERTIFICATE
PLANT NO. 864991

PATON

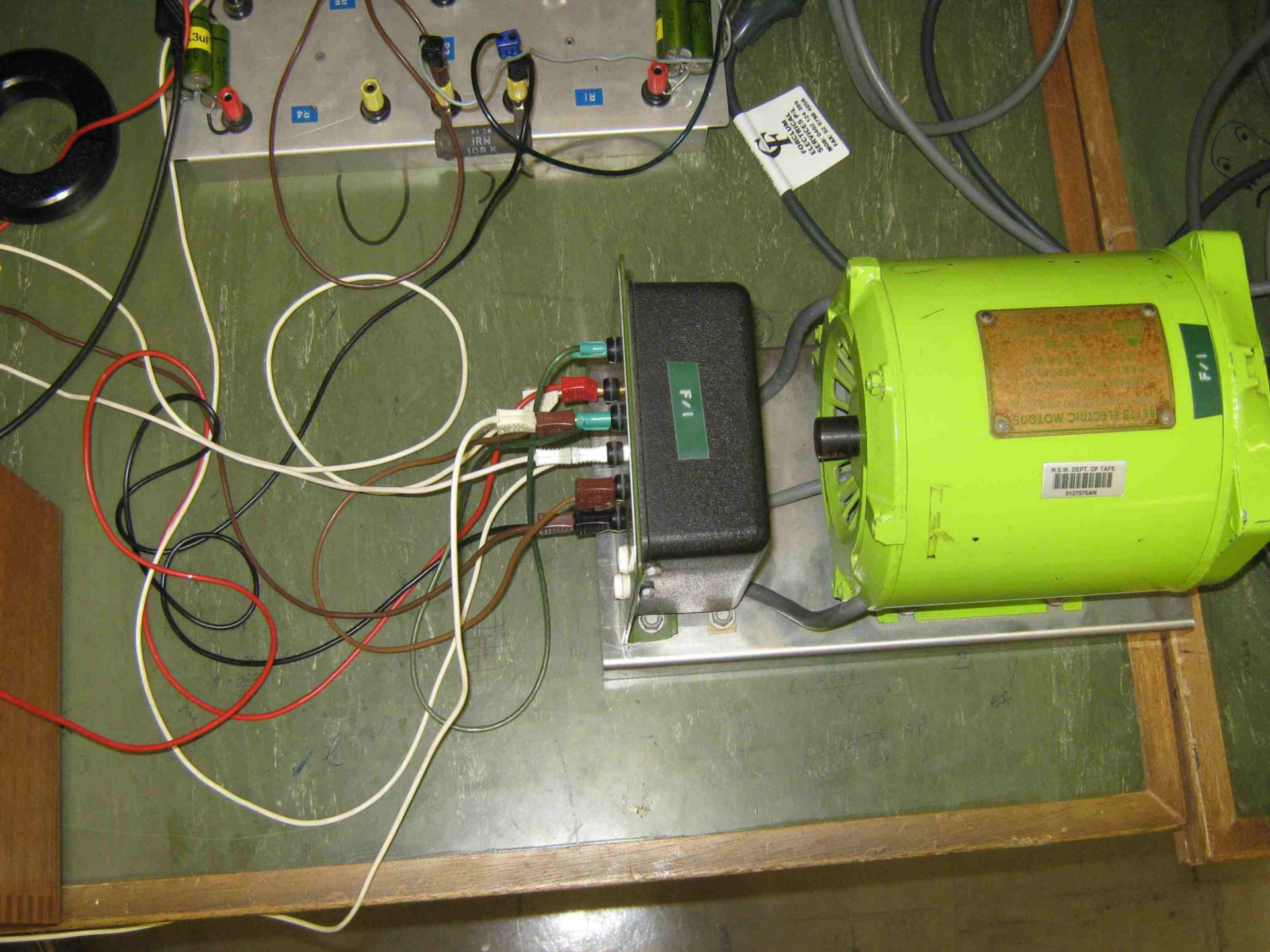STONEY INSTITUTE TECHNOLOGY
ELECTROTECHNOLOGY





FORBES
ELECTRICAL SERVICES
151A
TAFE NSW
151A
TAFE NSW

R4

R1

IRN
10R K

F/1



F/1

BETTS ELECTRIC MOTORS
F/1
MOTOR

N.S.W. DEPT. OF TAFE
0127576AN




C/A SERIES A.C. CIRCUITS

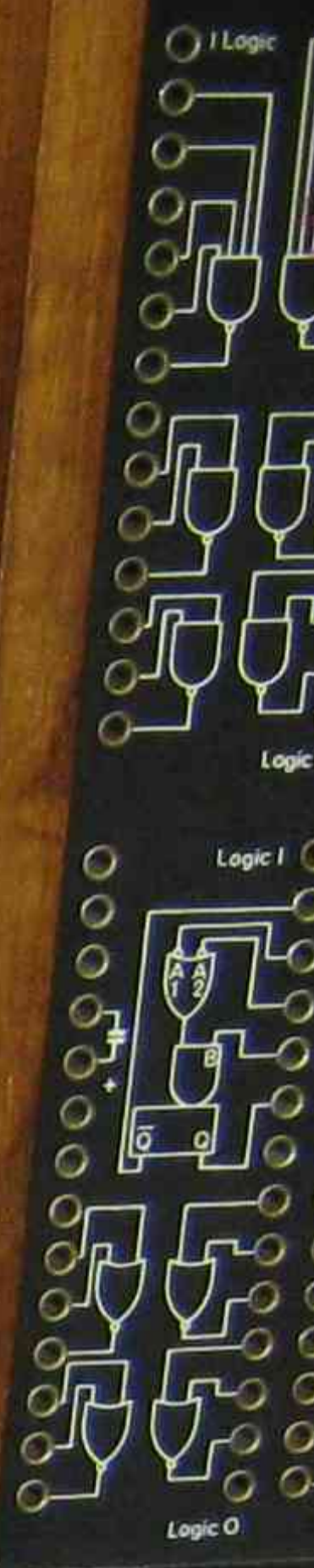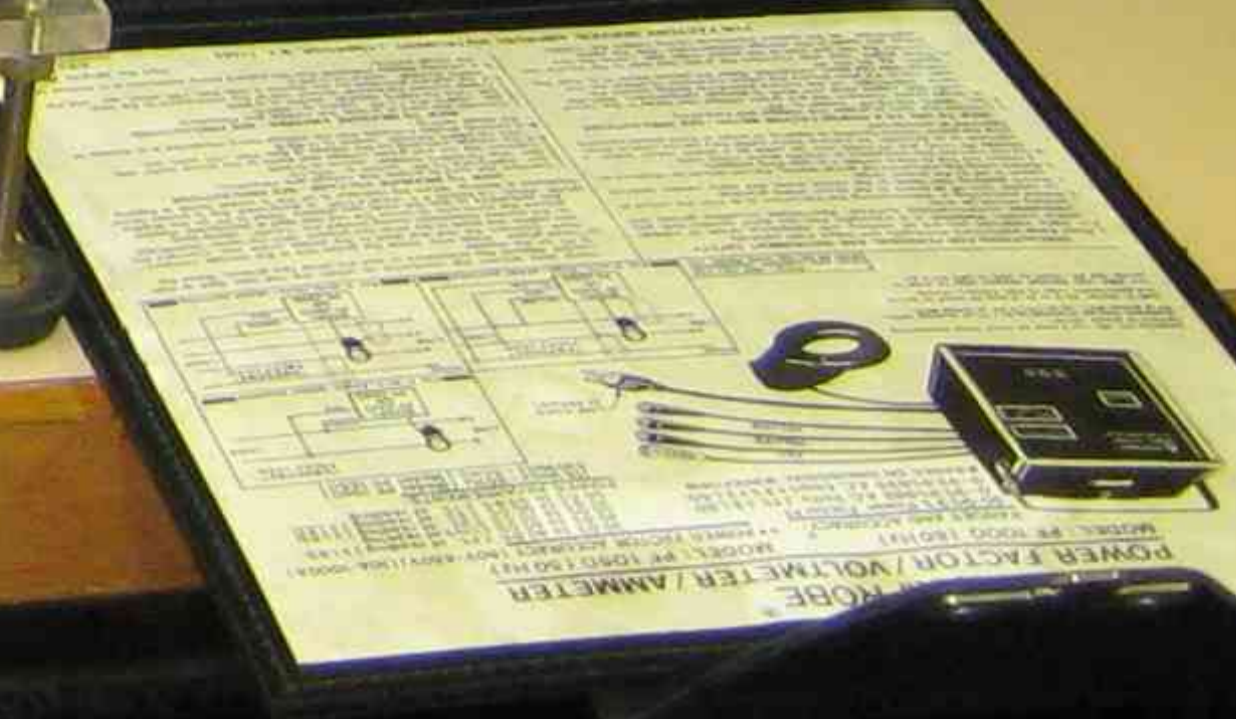

POWER SYSTEM ANALYSIS 3ϕ BALANCED λ & Δ CONNECTION (LAB-2)

CONNECT THE GIVEN CIRCUIT

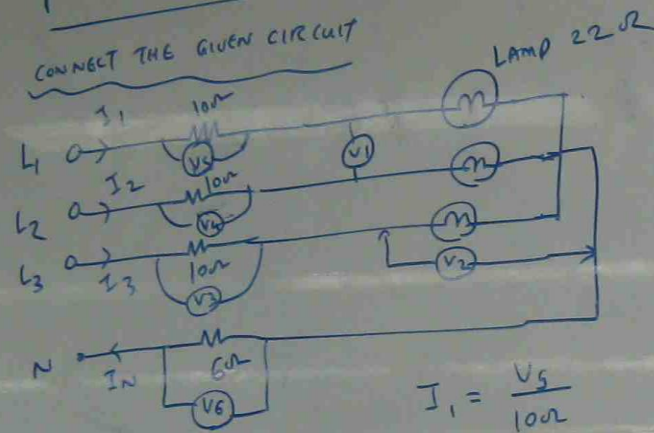

TAKING $V_1, V_2, V_3, V_4, V_5, V_6$

$V_1 =$ LINE VOLTAGE

$V_2 =$ PHASE VOLTAGE

$V_5, V_6, V_7 =$ SERIES RESISTOR VOLTAGE

($I_1, I_2, I_3 =$ LINE CURRENT)

$$I_1 = \frac{V_5}{100\Omega}$$


$$I_2 = \frac{V_4}{100\Omega}, \quad I_3 = \frac{V_3}{100\Omega}$$

$$I_N = \frac{V_6}{6\Omega}$$

COMPARE I_1, I_2, I_3
COMMENT ON I_N

$$\text{LINE TO PHASE VOLTAGE RATIO} = \frac{V_1}{V_2} =$$

CHANGE THE CONNECTION TO Δ

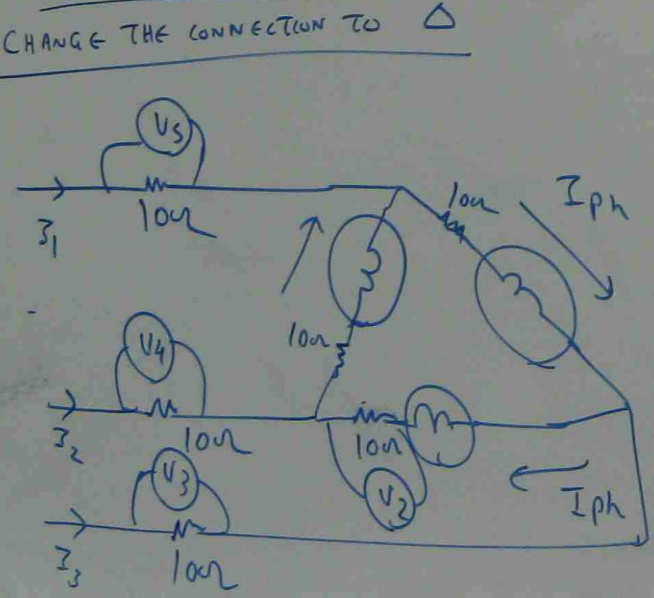



$$I_1 = \frac{V_5}{100\Omega}, \quad I_2 = \frac{V_4}{100\Omega}, \quad I_3 = \frac{V_3}{100\Omega}$$

$$I_{ph} = \frac{V_2}{100\Omega}$$

CALCULATE $\frac{I_1}{I_{ph}}, \frac{I_2}{I_{ph}}, \frac{I_3}{I_{ph}}$

PROVIDE COMMENT.

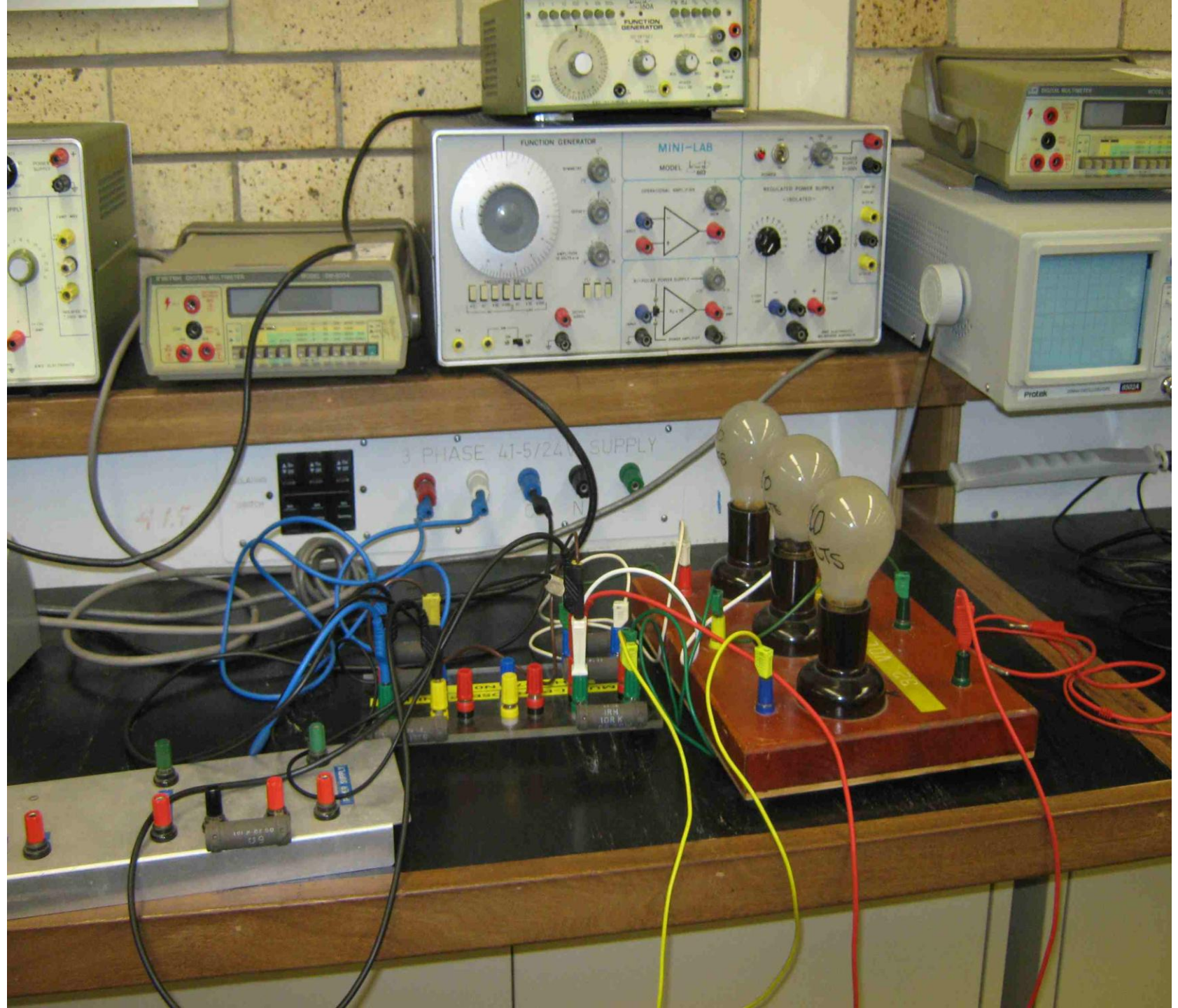

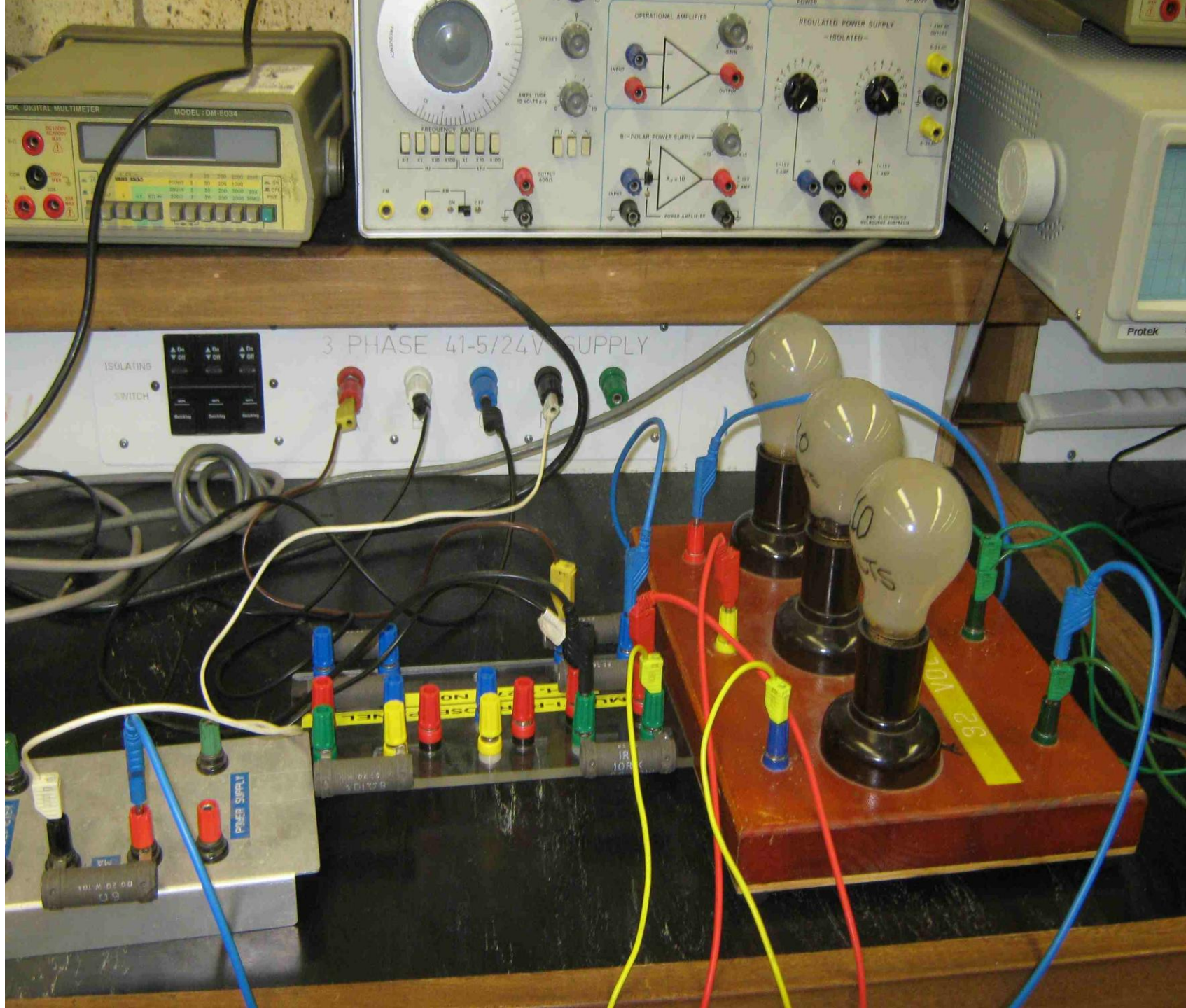

DIGITAL MULTIMETER
MODEL: DM-8034

OPERATIONAL AMPLIFIER
REGULATED POWER SUPPLY
BI-POLAR POWER SUPPLY

ISOLATING SWITCH

3 PHASE 415/240V SUPPLY

ON OFF


POWER SUPPLY

100V 3S

MAXIMUM POWER TRANSFER THEOREM


THEORY

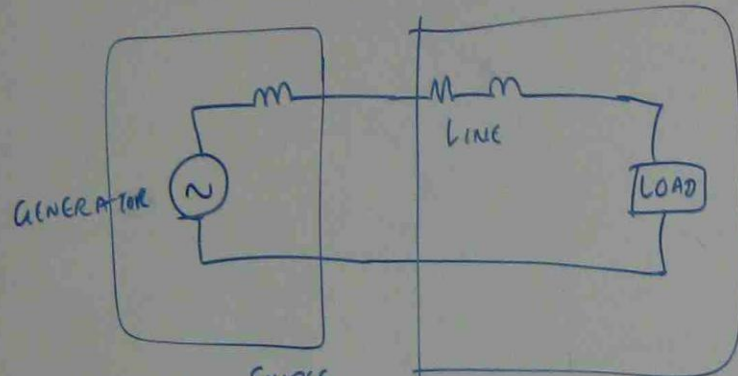MAXIMUM POWER IS TRANSFERRED FROM THE SOURCE WHEN SOURCE IMPEDANCE IS EQUAL TO LINE + LOAD IMPEDANCE



SOURCE IMPEDANCE = LOAD IMPEDANCE → MAXIMUM POWER IS TRANSFERRED.

(1) CONNECT THE GIVEN CIRCUIT

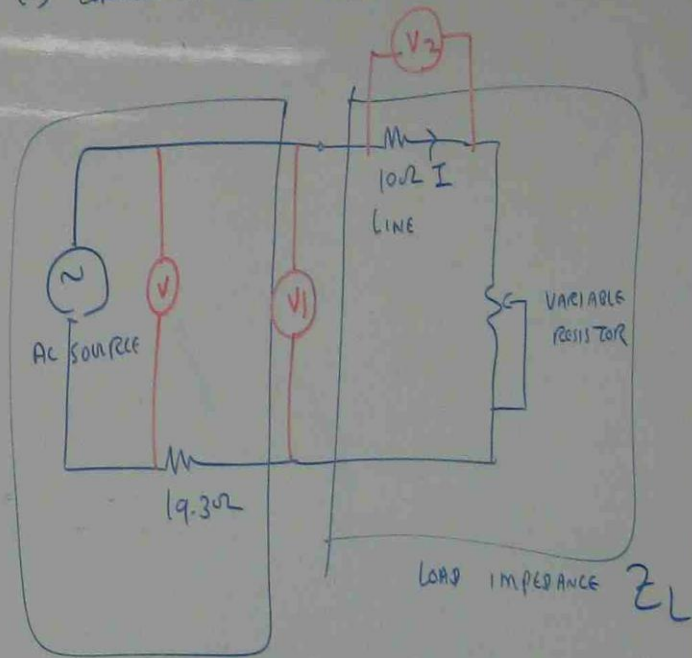

SOURCE IMPEDANCE

$$Z_s = 19.3 \Omega$$

SWITCH, ADJUST THE VARIABLE RESISTOR

NOTE V , V_1 , V_2

FILL IN TABLE

Source	V_1	V_2	$I = \frac{V_2}{Z_{out}}$	Power = $V_1 \times I$
6.2	2.4			-
	3.6			-
	4.2			-
	4.7			
	5.5			
	6			
	6.2			

— WHEN POWER REACHES THE MAXIMUM POINT,
 MEASURE, LINE + LOAD IMPEDANCE (Z_L)
 AND THEN COMPARE WITH SOURCE RESISTANCE

Z_L & Z_S COMPARISON

FUNCTION GENERATOR
MINI-LAB
MODEL 800

OPERATIONAL AMPLIFIERS
REGULATED POWER SUPPLY - ISOLATED -
BI-POLAR POWER SUPPLY

DIGITAL MULTIMETER
MODEL GDM-8034

Prottek 20MHz OSCILLOSCOPE 6502A

DIGITAL MULTIMETER

DIGITAL MULTIMETER

ETI MODULE 3
MAXIMUM POWER TRANSFER

42.11

