

### **G002 Online Test**

Ref149

A sine wave voltage of 240V RMS is applied to a resistive circuit of  $60\Omega$ . Calculate(a) RMS value of current (b) Maximum value of current.

A	2A, 4A	B	4A, 5.65A
C	2A, 2.8A	D	1A, 2A
<b>Answer</b>			

Ref150

A coil of negligible resistance draws a current of 0.2A (RMS) when connected to 240V, 50Hz.

(a) Determine inductive reactance (b) Coil inductance.

A	600 $\Omega$ , 3.8 H	B	1200 $\Omega$ , 1.9 H
C	1200 $\Omega$ , 3.8 H	D	1800 $\Omega$ , 7.6 H
<b>Answer</b>			

Ref151

A 64 mH inductor is connected in series with a  $300\Omega$  resistor to a 1000HZ AC supply voltage of 10V rms. Find (a) the impedance (b) The phase angle (c) The current (d) the potential drop across resistor.

A	500 $\Omega$ ,( 53.2 Deg), 0.002A (-53.2Deg), 6V,8V	B	500 $\Omega$ ,( 36.8 Deg), 0.001A (+53.2Deg), 8V,6V
C	500 $\Omega$ ,( 0 Deg), 0.002A (-0 Deg), 6V,8V	D	500 $\Omega$ ,( 90 Deg), 0.002A (-90 Deg), 6V,8V
<b>Answer</b>			

Ref152

Find the current in the circuit when an AC voltage 10V rms at 1000HZ is applied to 2  $\mu\text{F}$  capacitor.

A	0.375A	B	0.25A
C	0.125A	D	0.5A
<b>Answer</b>			

Ref153

A 1  $\mu\text{F}$  capacitor is connected in series with 200  $\Omega$  resistor to 10V rms. 1600HZ supply. Find (a) the impedance (b) The phase angle (c) The current (d) Potential drop across resistor (e) Potential drop across capacitor.

A	111.3 $\Omega$ ,(-26.5 Deg), 0.0224A (-26.5Deg), 4.5V,2.24V	B	222.6 $\Omega$ ,( +26.5 Deg), 0.0224A (-26.5Deg), 9V ,4.48V
C	222.6 $\Omega$ ,( 0 Deg), 0.0224A (0 Deg), 9V ,4.48V	D	222.6 $\Omega$ ,(-26.5 Deg), 0.0448A (+26.5Deg), 9V ,4.48V
<b>Answer</b>			

Ref154


A series circuit is connected to a 10V rms AC supply. The circuit has resistance 100  $\Omega$ , inductive reactance 300  $\Omega$ , capacitive reactance 400  $\Omega$ . Find (a) Impedance (b) Current (c) Phase angle (d) Voltage drop across resistor (e) Voltage drop across inductor (f) Voltage drop across capacitor.

A	141 $\Omega$ (Angle -45 Deg), 0.071A, 45 Deg, 7.1V, 21.3V,28.4V	B	70.7 $\Omega$ (Angle +45 Deg), 0.035A, 45 Deg, 3.35V, 10.65V,14.2V
C	141 $\Omega$ (Angle 45 Deg), 0.071A,-45 Deg 7.1V, 28.4V, 21.3V	D	141 $\Omega$ (Angle 0 Deg),0.071A, 0 Deg, 7.1V, 21.3V, 28.4V
<b>Answer</b>			

### Ref155

The following is a diagram of a parallel circuit with a supply voltage 100V rms at 50Hz. Determine the followings.

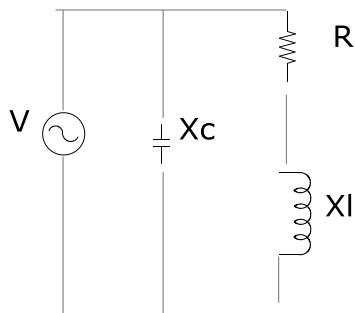- (a) Total circuit current
- (b) Total circuit impedance
- (c) Phase angle between circuit current and applied voltage
- (d) Power factor of circuit.



$$X_c = 318.5 \Omega, R = 100 \Omega, X_I = 94.2 \Omega, V = 100 \text{ V}, 50\text{Hz}$$

A	1.8A (Angle -36.8 Deg), 206 $\Omega$ , 56.86 Deg, 0.8	B	0.97A (Angle +36.8 Deg), 103 $\Omega$ , 36.8 Deg 0.59
C	0.97A (Angle -36.8 Deg), 103 $\Omega$ , 36.8 Deg 0.59	D	0.97A (Angle +53.2 Deg), 206 $\Omega$ , 53.2 Deg 0.59
<b>Answer</b>			

### Ref156

A capacitor draws 0.971 Amp at PF 0.34 from 100V supply. Total power is

A	36.8W	B	100W
C	52.43W	D	70.7 W
<b>Answer</b>			

### Ref157

The phase voltage and current in 3 phase star connected current are 240V and 50A. Find the line voltage and line current.

A	415V rms, 50A	B	240V rms, 50A
C	415V rms, 86.5A	D	240V rms, 86.5A
<b>Answer</b>			

Ref158

A delta connected load takes a line current 40A and line voltage 415V. Find (a) Phase current (b) Phase voltage

A	40A, 415V	B	23.1A, 415V
C	40A, 240V	D	23.1A. 240V
	Answer		

Ref159

Three phase 415V, 37.3 KW, Delta connected alternator has efficiency 90% and PF 0.88 Lagging. Find (a) Line current (b) Phase current.

A	130A, 75.6A	B	65.5 A, 75.6A
C	65.5A, 37.8A	D	130A, 37.8A
	Answer		

Ref160

The force produced in three phase winding of AC machine is

A	$\frac{3 \text{ Im } N e^{j\omega t}}{2}$	B	$\frac{\text{Im } N e^{j\omega t}}{2}$
C	$\frac{\sqrt{3} \text{ Im } N e^{j\omega t}}{2}$	D	$\sqrt{3} \text{ Im } N e^{j\omega t}$
	Answer		