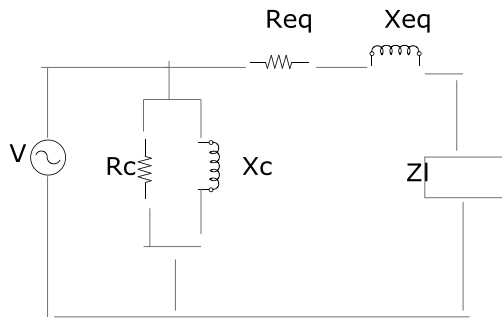


G040 Online Test

Ref339



$Req = 0.3\Omega$, $Xeq = 0.4\Omega$, $Rc = 200\Omega$, $Xc = 400\Omega$, $V = 200\text{ V}$, $Zl = 2.7 + j 3.6\Omega$

Find efficiency

A	47%	B	86.4%
C	99%	D	35%
Answer			

Ref340

200/400V Transformer

Open circuit test— $I_o = 0.7\text{A}$, $P_o = 60\text{W}$ Short circuit test--- $V_{sc} = 9\text{V}$, $I_{sc} = 6\text{A}$, $P_{sc} = 26\text{ w}$. Find Re' , Xe' , Rc and Xc

A	0.12Ω , 0.4Ω , 666.7Ω , 317.8Ω	B	0.06Ω , 0.2Ω , 333.35Ω , 156Ω
C	1Ω , 4Ω , 666.7Ω , 317.8Ω	D	2Ω , 8Ω , 500Ω , 400Ω
Answer			

Ref341

KVA = 500, Copper loss = 4 KW, Iron loss = 2.4 KW. Find $\frac{1}{2}$ load efficiency at 0.8 PF lagging.

A	66%	B	98.1%
C	75%	D	40%
Answer			

Ref342

$$\%Reg = \% Req \cos\theta + / - \%X_{eq} \sin\theta$$

+ for

A	Leading	B	Lagging
C	Unity	D	
Answer			

Ref343

Dy, Yd connection is suitable for

A	Small HV transformer	B	Large LV transformer
C	Power supply transformer	D	Earthing transformer
Answer			

Ref344

10MVA Star/ Star connected transformer. 33KV/ 11KV

No load test Line voltage = 11KV, Line current = 15A, Power = 75KWShort circuit test Line voltage = 1650V L-L, Line current = rated current, Power = 90KW

Find Req, Xeq, Ro', Xo'

A	0.98Ω, 5.3 Ω, 14.5KΩ, 2.93 KΩ	B	2Ω, 10 Ω, 20KΩ, 5KΩ
C	4Ω, 20 Ω, 40KΩ, 15 KΩ	D	1Ω, 5 Ω, 30KΩ, 15 KΩ
Answer			

Ref345

Find the load at maximum efficiency of the following single phase transformer. KVA = 5000, Voltage ratio = 6600/440, Iron loss = 2.9 KW, Full load copper loss = 4KW, Maximum efficiency is achieved at 0.8 PF lagging. Find maximum efficiency.

A	0.7 , 90%	B	0.851, 98.38%
C	0.35, 75%	D	0.45, 85%
Answer			

Ref346

Find all day efficiency of the following transformer 100 KVA, single phase, Iron loss=750W Full load copper loss = 750W 24 hr load cycle.

Time	Power factor	Output
8 hr	0.8 Lag	80KW
6hr	0.9 lag	50 KVA
4hr	25KVA & 20 KW	
3hr	Energized with no load	
The rest of time	De-energized	

Calculate all day efficiency.

A	98.1%	B	75%
C	60%	D	50%
Answer			

Ref347

To operate two transformers in parallel , it needs

A	Same voltage ratio	B	Same % impedance
C	Like polarity	D	All above
Answer			

Ref348

2700KVA load PF 0.9 lagging is supplied by two transformers connected in parallel.

Tr A = 2000KVA $Z = 3 + j2$ ohm

TrB = 1000KVA $X = 3 + j5$ ohm

Find load A transformer load share, B load share.

A	1350, 1350 KVA	B	900, 1800 KVA
C	1000KVA, 1700KVA	D	721KVA, 2332KVA
Answer			

Ref349

Which winding can not take away harmonic ?

A	Star/Star without neutral	B	Star/Star with neutral
C	Delta/Delta	D	Star/Delta
Answer			

Ref350

400/200 V , 50VA transformer needs to supply 600/200V. Find the rating.

A	The same rating	B	100VA
C	33.3VA	D	11VA
Answer			

Ref351

ONAF is

A	Oil is naturally cooled by force air	B	Forced oil is cooled by forced air
C	Oil is naturally cooled by force oil	D	Oil is naturally cooled by natural air
Answer			