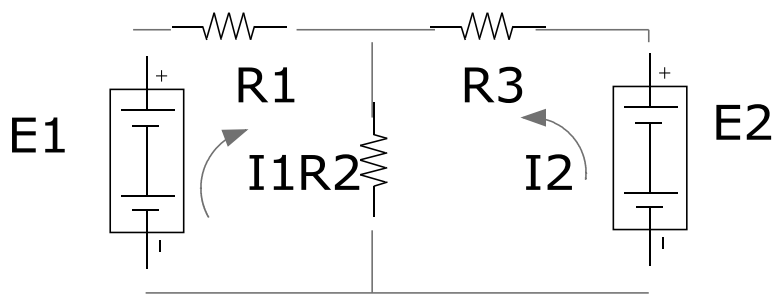


G048 Online Test

Ref418




$R1 = 2 \Omega$ ,  $R2 = 4 \Omega$ ,  $R3 = 1 \Omega$ ,  $E1 = 2V$ ,  $E2 = 6V$

Find  $I1$  and  $I2$  by using Kirchoff's voltage law.

A	-1A, -2A	B	0.5A, 1A
C	1A, 2A	D	-3A, -4A
<b>Answer</b>			

Ref419

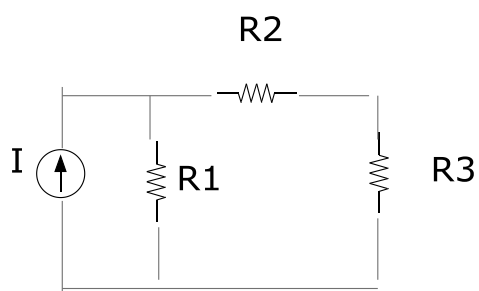


$I = 2A$ ,  $R1 = 4 \Omega$ ,  $R2 = 2 \Omega$ ,  $R3 = 7 \Omega$

Thevenin's equivalent resistance and voltage of the given circuit are

A	24 $\Omega$ , 32V	B	3 $\Omega$ , 4V
C	12 $\Omega$ , 16V	D	6 $\Omega$ , 8V
<b>Answer</b>			

Ref420

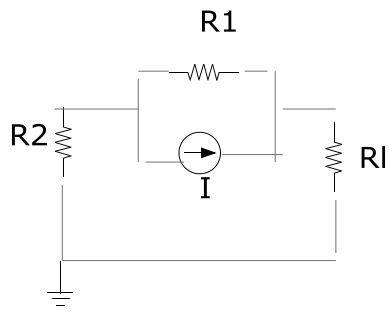


$R1 = 5 \Omega, R2 = 4 \Omega, R1 = 9 \Omega, I = 10A$

Norton equivalent current of the given circuit is

A	22A	B	11A
C	5.55A	D	2.75A
<b>Answer</b>			

Ref421

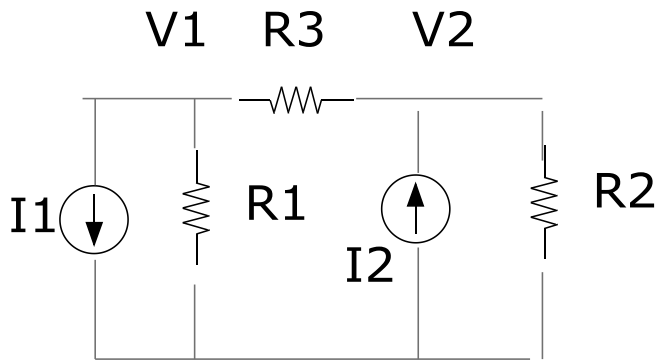


$I1 = 2A, R1 = 6 \Omega, R2 = 4 \Omega, R3 = 3 \Omega, I2 = 3A$

The voltages  $V1$  &  $V2$  solved by Nodal analysis are

A	$2V1 = 1V, V2 = 4V$	B	$V1 = -0.92V, V2 = 4.615V$
C	$V1 = 2V, V2 = 8V$	D	$V1 = 3V, V2 = 7V$
<b>Answer</b>			

Ref422

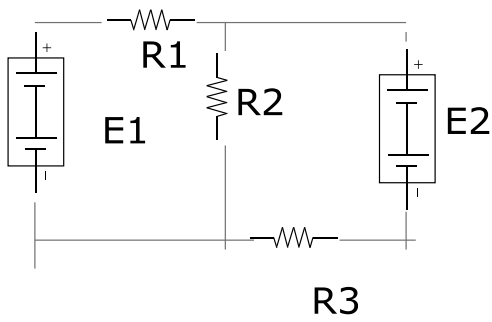


$E1 = 54V, R1 = 24 \Omega, R2 = 12 \Omega, R3 = 4 \Omega, E2 = 48V$

The current passing through R3 calculated by Superposition Theorem is

A	5A	B	7A
C	1.25A	D	2.5A
<b>Answer</b>			

Ref423

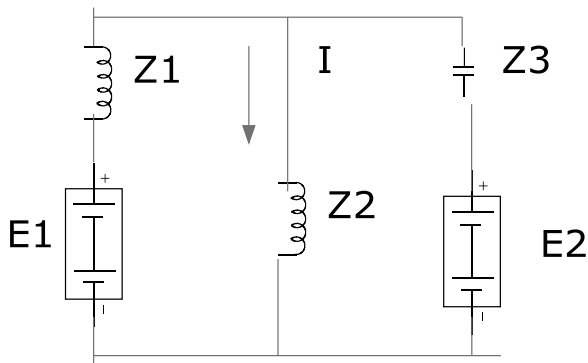

$E1 = 10 \angle 0^\circ V$


$E2 = 5 \angle 0^\circ V$

$Z1 = j4 \Omega, Z2 = j4 \Omega, Z3 = -j3 \Omega$

The value of the current calculated by Superposition theorem is

A	6.25 120 Deg	B	6.25 Angle 0 Deg
C	6.25 Angle - 90 Deg	D	6.25 Angle 90 Deg
<b>Answer</b>			

Ref424

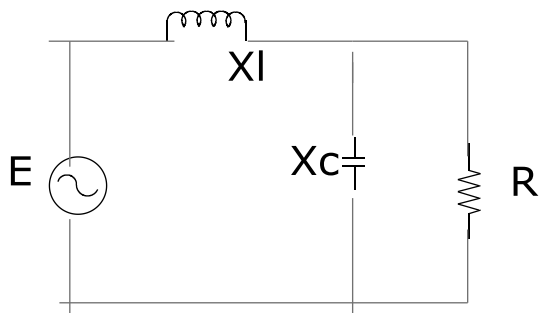

$E = 10(\text{Angle } 0) \text{ V}$ ,  $XI = j 8 \Omega$   $Xc = -j 8 \Omega$

Thevenin's equivalent voltage and impedance of the given network are

A	Vth= 3.33 (Angle -120)V, Zth = 2.67 (Angle -90) $\Omega$	B	Vth= 3.33 (Angle -80)V, Zth = 1.35 (Angle 0) $\Omega$
C	Vth= 3.33 (Angle 0)V, Zth = 2.67 (Angle 0) $\Omega$	D	Vth= 3.33 (Angle -180)V, Zth = 2.67 (Angle -90) $\Omega$
Answer			