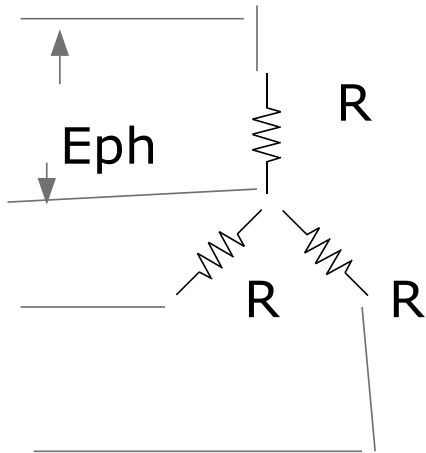


G049 Online Test

Ref425




$R = 100 \Omega$  each,  $E_{ph} = 173.2V$

The neutral current flow in the given circuit is

A	$I_n = 0A$	B	$I_n = 8.66 - j0.5A$
C	$I_n = -0.5 + j 0.866 A$	D	$I_n = 8.66 + j0.5A$
<b>Answer</b>			

Ref426

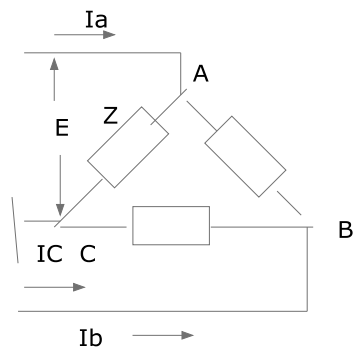

$Z = 50 (\text{Angle } 0) \Omega$   $E = 400V$ . The currents in A,B, C lines are


A	$I_a = 13.9 \angle -30 A, I_b = 13.9 \angle -150A$ $I_c = 13.9 \angle 90 A$	B	$I_a = 13.9 \angle -30 A, I_b = 13.9 \angle -150A$ $I_c = 13.9 \angle 90 A$
C	$I_a = 13.9 \angle 0 A, I_b = 13.9 \angle 120A$ $I_c = 13.9 \angle -120 A$	D	$I_a = 13.9 \angle 0 A, I_b = 13.9 \angle -120A$ $I_c = 13.9 \angle 120 A$
<b>Answer</b>			

Ref427

Three phase power and power factor angle measured by 2 watts meters method can be calculated by

A	$W_t = W_1 = W_2$ $\Phi = \tan^{-1} (W_1 - W_2) / (W_1 + W_2)$	B	$W_t = W_1 = W_2$ $\Phi = \tan^{-1} (W_1 + W_2) / (W_1 - W_2)$
C	$W_t = W_1 - W_2$ $\Phi = \tan^{-1} \sqrt{3} (W_1 - W_2) / (W_1 + W_2)$	D	$W_t = W_1 + W_2$ $\Phi = \tan^{-1} \sqrt{3} (W_1 - W_2) / (W_1 + W_2)$
<b>Answer</b>			


Ref 428

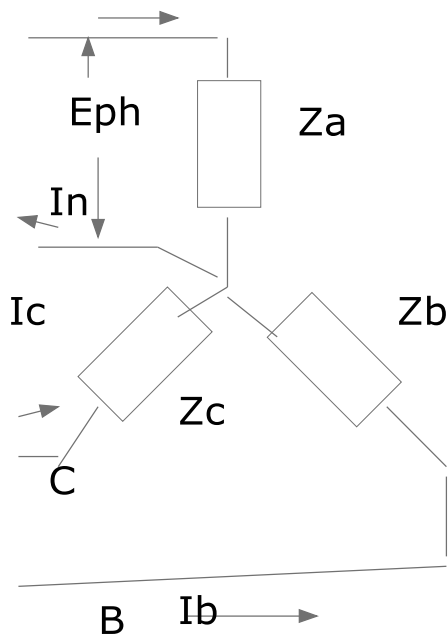

$E_{ph} = 100V$ ,  $Z_a = 100\Omega$ ,  $Z_b = 100\Omega$  in series with  $66.3\mu F$ ,  $Z_c = 100\Omega$  in series with  $139.2mH$   $f = 50HZ$ .  
Calculate the current in neutral wire ( $I_n$ )

A	$I_n = 0.878 \angle 0^\circ$ A	B	$I_n = 0.878 \angle 0.978^\circ$ A
C	$I_n = 0.878 \angle 30^\circ$ A	D	$I_n = 0$ A
<b>Answer</b>			

Ref429

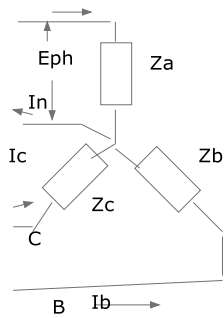

If the above star connection is converted to delta,  $Z_{ab}$  is equal to

A	$(Z_a Z_b + Z_b Z_c + Z_c Z_a) / Z_c$	B	$(Z_a + Z_b + Z_c) / Z_a Z_b Z_c$
C	$(Z_a + Z_b + Z_c) / Z_a$	D	$(Z_a + Z_b + Z_c) / Z_c$
<b>Answer</b>			

Ref430

A three phase 415V system's neutral wire is broken. The following line currents are flowing.

$$Z_a = 50 \angle 0^\circ \Omega, I_a = 1.55 \angle -8.5^\circ \text{ A}$$

$$Z_b = 50 \angle 0^\circ \Omega, I_b = 2.47 \angle -170^\circ \text{ A}$$

$$Z_c = 158 \angle 0^\circ \Omega, I_c = 1.03 \angle -30^\circ \text{ A}$$

(a) What is the voltage between new star point and original star point

(b) Which phase got over voltage?

A	A, $20 \angle 90^\circ \text{ V}$	B	No line, 0V
C	B, $40 \angle 0^\circ \text{ V}$	D	C, $40 \angle 16.59^\circ \text{ V}$
<b>Answer</b>			

Ref431

For one line to ground fault

A	$I_a = I_b = \sqrt{3} I_1$	B	$I_a = I_b = 2 I_1$
C	$I_a = I_b = 3 I_1$	D	$I_a = I_b = I_1$
<b>Answer</b>			

Ref432

$Z_1 = 65\%$   $Z_2 = 69\%$   $Z_0 = 40\%$  Base MVA = 100 MVA  $E = 132\text{KV}$  2 Line to ground fault. Calculate fault current.

A	1830 (Angle 0 Degree)Amp	B	918 (Angle 0 Degree)Amp
C	918 (Angle -60Degree)Amp	D	456 (Angle -60Degree)Amp
<b>Answer</b>			

Ref433


$I_a = 100 \angle 0^\circ$  Amp       $I_b = 100 \angle 180^\circ$  Amp       $I_c = 0$  Amp

Find  $I_{a1}$ ,  $I_{b1}$  and  $I_{c1}$ 

A	$I_{a1} = 57.7 \angle 0^\circ$ A, $I_{b1} = 57.7 \angle 0^\circ$ A, $I_{c1} = 57.7 \angle 0^\circ$ A	B	$I_{a1} = 57.7 \angle 0^\circ$ A, $I_{b1} = 57.7 \angle -120^\circ$ A, $I_{c1} = 57.7 \angle 120^\circ$ A
C	$I_{a1} = 57.7 \angle -30^\circ$ A, $I_{b1} = 57.7 \angle -150^\circ$ A, $I_{c1} = 57.7 \angle 90^\circ$ A	D	$I_{a1} = 57.7 \angle 120^\circ$ A, $I_{b1} = 57.7 \angle 120^\circ$ A, $I_{c1} = 57.7 \angle 120^\circ$ A
<b>Answer</b>			

Ref434

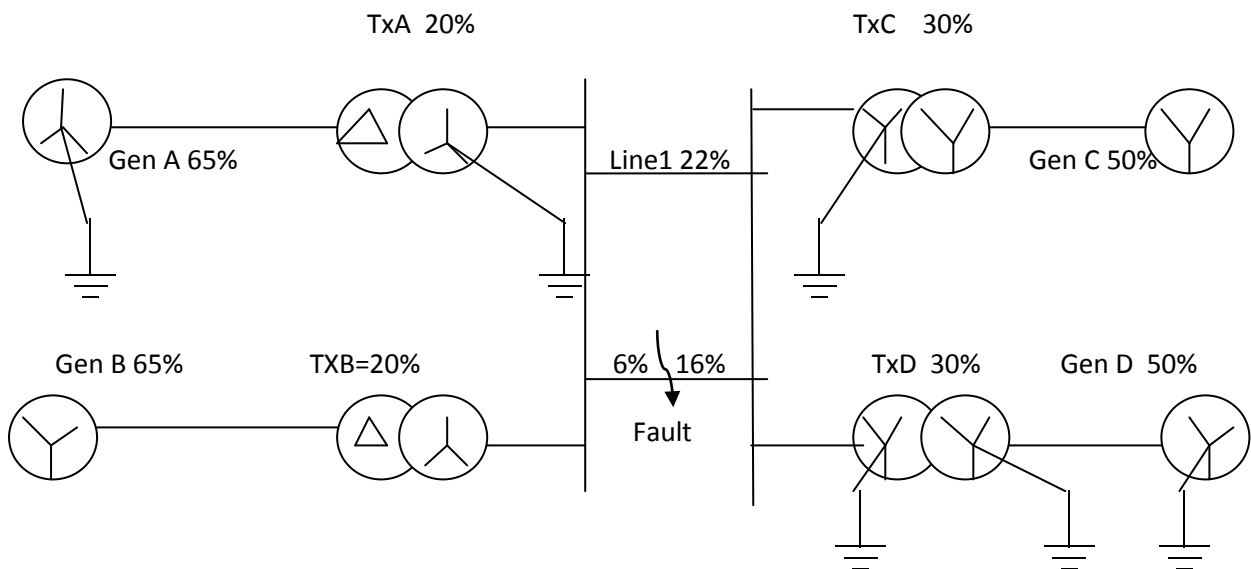Calculate the positive, negative and zero sequence equivalent diagram for the given power system.



A	10%,10%,10%	B	25.5%. 25.5%, 25.5%
C	50%,50%,50%	D	25.5%. 25.5%, 15.1%
Answer			