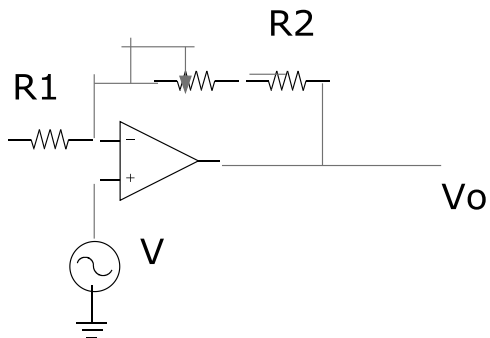


**H045 Online Test**

Ref489



$R1=1\text{ K}\Omega$ ,  $R2=10\text{ K}\Omega$   $V = 10\text{ mV}$

In given inverting amplifier, what is minimum voltage gain?

A	10	B	9
C	12	D	11
<b>Answer</b>			


Ref490

Non inverting amplifier , voltage gain is 20. Input 10mV P-P, 10% to 90% rise time. 3.5 $\mu$ s. Input is increased to 1V, out put is increased from 10 to 90% & rise time is increased to 12.8 $\mu$ s.

Calculate (a) Bandwidth (b) Rise time (c) Gain bandwidth product.

A	100 KHZ, 0.625 $\mu$ S, 1 MHZ	B	200 KHZ, 1.25 $\mu$ S, 2 MHZ
C	300 KHZ, 2.5 $\mu$ S, 3 MHZ	D	
<b>Answer</b>			

Ref491

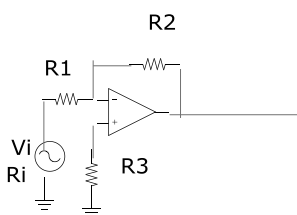

$R1=1\text{ K}\Omega$  ,  $R2=100\text{ K}\Omega$ ,  $R3=1.57\text{ K}\Omega$   $Ri = 600\ \Omega$ . Offset current is 2 mA

Out put dc voltage is

A	1 mV	B	0.5 mV
C	3 mV	D	2 mV
Answer			

Ref492

Bias compensated Op-Amp,  $R_f = 100 \text{ K } \Omega$  ,  $R_i = 1600 \text{ } \Omega$  , Drift  $V_{IO} = 30 \text{ } \mu\text{V/ } ^\circ\text{C}$ . Drift  $I_o = 300 \text{ PA/ Z}$ . Null at  $20^\circ\text{C}$  . Find dc offset at  $80^\circ\text{C}$ .

A	118mV	B	236 mV
C	59 mV	D	30mV
Answer			

Ref493

Calculate the full power bandwidth of an Op-amp which has a slew rate  $0.2 \text{ V/}\mu\text{S}$  and works with  $\pm 15 \text{ V}$  power supply.

A	4 KHZ	B	18 KHZ
C	27 KHZ	D	9.1 KHZ
Answer			

Ref494

Noise density  $15 \text{ nV/ } \sqrt{\text{HZ}}$  . Find noise voltage over a bandwidth  $30\text{KHz}$ .

A	$1.3 \text{ } \mu\text{V rms}$	B	$2.6 \text{ } \mu\text{V rms}$
C	$3.9 \text{ } \mu\text{V rms}$	D	$5.2 \text{ } \mu\text{V rms}$
Answer			


Ref495

Op-amp circuit. The source resistance is  $30\text{ K}\Omega$ . The thermal noise due to the source resistance is  $2.8\text{ }\mu\text{V}$ . The internal noise current of op-amp is  $60\text{ pA}$  and the internal noise voltage of the op-amp is  $4.1\text{ }\mu\text{V}$ .

- (a) What is the total equivalent input noise voltage?  
 (b) What will be the new value if bandwidth is tripled?

A	$5.3\text{ }\mu\text{V}, 9.6\text{ }\mu\text{V}$	B	$10.6\text{ }\mu\text{V}, 4.8\text{ }\mu\text{V}$
C	$2.7\text{ }\mu\text{V}, 3.2\text{ }\mu\text{V}$	D	
<b>Answer</b>			

Ref496

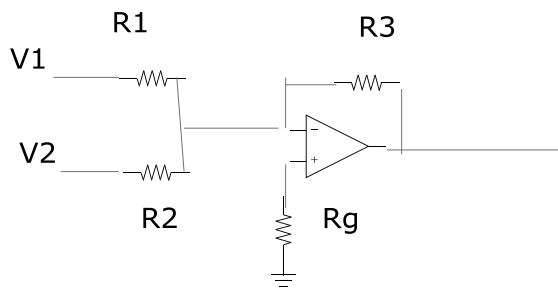

$R1 = 10\text{ K}\Omega$ ,  $R2 = 4.7\text{ K}\Omega$ ,  $R3 = 100\text{ K}\Omega$ ,  $Rg = 3.3\text{ K}\Omega$

$R_s$  value is


A	$12.8\text{ K}\Omega$	B	$3.2\text{ K}\Omega$
C	$4\text{ K}\Omega$	D	$6.4\text{ K}\Omega$
<b>Answer</b>			

Ref497

The noise voltage equation is

A	$E_r = \sqrt{4\text{ K T } R_s B}$	B	$E_r = \sqrt{\text{K T } R_s B}$
C	$E_r = \sqrt{2\text{ K T } R_s B}$	D	$E_r = \sqrt{1.5\text{ K T } R_s B}$
<b>Answer</b>			

Ref498

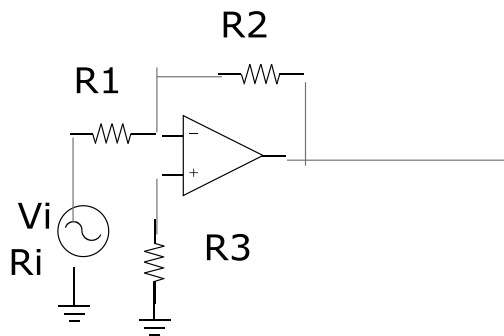

$R1 = 4.7 \text{ K}\Omega$ ,  $R2 = 100 \text{ K}\Omega$ ,  $R3 = 3.3 \text{ K}\Omega$

Calculate (a) Input signal to noise ratio (b) Output signal to noise ratio

A	33.4 dB, 19 dB	B	10 dB, 25 dB
C	66dB, 38 dB	D	66.8 dB, 57.1 dB
<b>Answer</b>			

Ref499

When the phase angle is less than  $-180^\circ$ , the amplifier is

A	Stable	B	Unstable
C		D	
<b>Answer</b>			

Ref500

If phase margin is less than  $45^\circ$ , the system is

A	Critical damp	B	Over damp
C	Underdamp	D	
<b>Answer</b>			