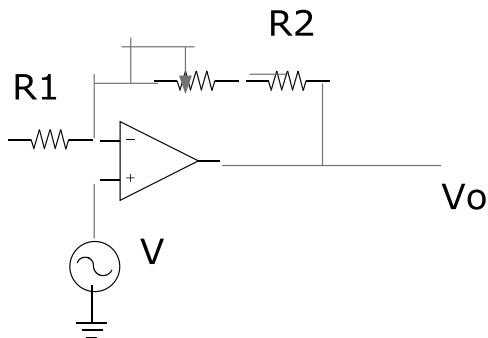


H045 Online Test

Ref489



$R1=1\text{ K}\Omega$, $R2= 10\text{K}\Omega$ $V = 10\text{ mV}$

In given inverting amplifier, what is minimum voltage gain?

A	11	B	9
C	12	D	10
Answer			


Ref490

Non inverting amplifier , voltage gain is 20. Input 10mV P-P, 10% to 90% rise time. $3.5\mu\text{s}$. Input is increased to 1V, out put is increased from 10 to 90% & rise time is increased to $12.8\mu\text{s}$.

Calculate (a) Bandwidth (b) Rise time (c) Gain bandwidth product.

A	200 KHZ, $1.25\mu\text{s}$, 2 MHZ	B	100 KHZ, $0.625\mu\text{s}$, 1 MHZ
C	300 KHZ, $2.5\mu\text{s}$, 3 MHZ	D	
Answer			

Ref491

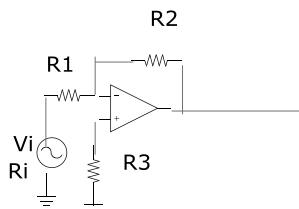

$R1= 1\text{ K}\Omega$, $R2=100\text{ K}\Omega$, $R3= 1.57\text{ K}\Omega$ $Ri = 600\ \Omega$. Offset current is 2 mA

Out put dc voltage is

A	2 mV	B	0.5 mV
C	3 mV	D	1 mV
Answer			

Ref492

Bias compensated Op-Amp, $R_f = 100 \text{ K } \Omega$, $R_i = 1600 \text{ } \Omega$, Drift $V_{i0} = 30 \text{ } \mu\text{V/ } ^\circ\text{C}$. Drift $I_o = 300 \text{ PA/ } Z$. Null at 20°C . Find dc offset at 80°C .

A	236 mV	B	118mV
C	59 mV	D	30mV
Answer			

Ref493

Calculate the full power bandwidth of an Op-amp which has a slew rate $0.2 \text{ V/}\mu\text{S}$ and works with $\pm 15 \text{ V}$ power supply.

A	9.1 KHZ	B	18 KHZ
C	27 KHZ	D	4 KHZ
Answer			

Ref494

Noise density $15 \text{ nV/ } \sqrt{\text{HZ}}$. Find noise voltage over a bandwidth 30KHz .

A	$2.6 \text{ } \mu\text{V rms}$	B	$1.3 \text{ } \mu\text{V rms}$
C	$3.9 \text{ } \mu\text{V rms}$	D	$5.2 \text{ } \mu\text{V rms}$
Answer			


Ref495

Op-amp circuit. The source resistance is $30 \text{ K}\Omega$. The thermal noise due to the source resistance is $2.8 \text{ } \mu\text{V}$. The internal noise current of op-amp is 60 PA and the internal noise voltage of the op-amp is $4.1 \text{ } \mu\text{V}$.

- What is the total equivalent input noise voltage?
- What will be the new value if bandwidth is tripled?

A	2.7 μV , 3.2 μV	B	10.6 μV , 4.8 μV
C	5.3 μV , 9.6 μV	D	
Answer			

Ref496

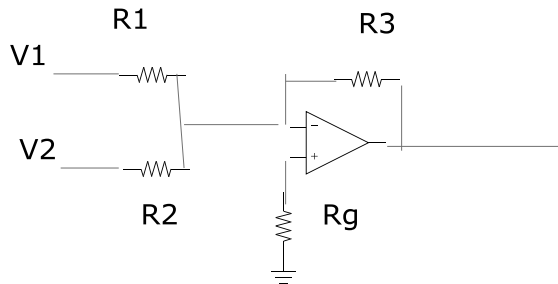

$R1 = 10 \text{ K}\Omega$, $R2 = 4.7 \text{ K}\Omega$, $R3 = 100 \text{ K}\Omega$, $Rg = 3.3 \text{ K}\Omega$

R_s value is


A	4 $\text{K}\Omega$	B	3.2 $\text{K}\Omega$
C	12.8 $\text{K}\Omega$	D	6.4 $\text{K}\Omega$
Answer			

Ref497

The noise voltage equation is

A	$E_r = \sqrt{4KT R_s B}$	B	$E_r = \sqrt{2KT R_s B}$
C	$E_r = \sqrt{KT R_s B}$	D	$E_r = \sqrt{1.5KT R_s B}$
Answer			

Ref498

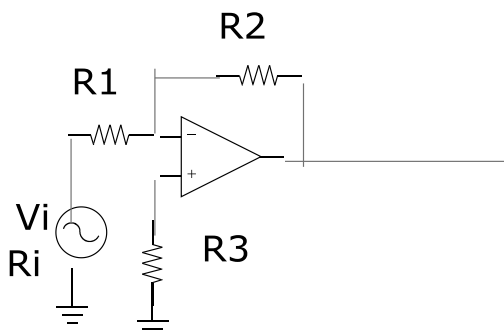

$R1 = 4.7 \text{ K}\Omega$, $R2 = 100 \text{ K}\Omega$, $R3 = 3.3 \text{ K}\Omega$

Calculate (a) Input signal to noise ratio (b) Output signal to noise ratio

A	66.8 dB, 57.1 dB	B	10 dB, 25 dB
C	66dB, 38 dB	D	33.4 dB, 19 dB
Answer			

Ref499

When the phase angle is less than -180° , the amplifier is

A	Unstable	B	Stable
C		D	
Answer			

Ref500

If phase margin is less than 45° , the system is

A	Critical damp	B	Underdamp
C	Over damp	D	
Answer			