


**I006+ H012 Online Test**

Ref502

Wheatstone bridge is \_\_\_\_\_ basic signal conditioner.

A	Active	B	Passive
C		D	
Answer			

Ref503

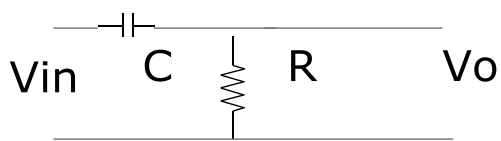

This circuit is

A	Low pass filter	B	High pass filter
C	Band pass filter	D	Band stop filter
Answer			

Ref506

The equation  $F_1/A_1 = F_2/A_2$  belongs to

A	Boyle's law	B	Charle's law
C	Bernaulli's law	D	Pascal's law
Answer			

Ref509

4 bits ripple counter has a modulus of \_\_\_\_\_ outputs.


A	4	B	8
C	12	D	16
Answer			

Ref512

To interface with high noise immunity industrial control system, which of device is to be used?

A	TTL	B	DTL
C	HTL	D	ECL
Answer			

Ref515

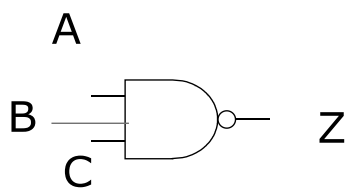

A	$Z = A B C$	B	$Z = A+B +C$
C	$Z = \overline{A B C}$	D	
Answer			

Ref518

1101- 0110 =

A	0111	B	0101
C	0110	D	0100
Answer			

Ref521

In SR flipflop, when the signal presence at S, not presence at R, Q is 1 and  $\overline{Q}$  is 0 result

A	No change	B	Set
C	Reset	D	Invalid
Answer			

Ref524

A shift register, moving data to left is

A	Divider	B	Multiplier
C	Multiplexer	D	De-multiplexer
Answer			

Ref527

What is the output voltage of A 10 bit ADC with 10 V reference . If input is (a) 0010110101 (b) 20FH

A	1.762528 V, 5.14 V	B	3.47288 V, 10.283 V
C	5.22789 V, 20.261 V	D	
Answer			

Ref530

The input to a 10 bit ADC with a 2.5V reference is 1.45V. What is the HEX output?. Suppose that the output was found to be 1B4H. What is the output voltage?

A	$V_{in} = 1.06445 \text{ V}$	B	$V_{in} = 1.12282 \text{ V}$
C	$V_{in} = 2.22412 \text{ V}$	D	$V_{in} = 3.22162 \text{ V}$
Answer			

Ref533

Dual slope ADC  $R = 100\text{K}\Omega$ ,  $C = 0.01\mu\text{F}$   $V_{ref} = 1\text{V}$ . Conversion time = 10 ms. Find the conversion time for 6.8 V input

A	6.8 ms	B	6.8 sec
C	6.8 $\mu\text{S}$	D	68 ms
Answer			

Ref536

Thermistor is

A	Temperature dependent resistor	B	Resistance temperature detector
C		D	
Answer			

Ref539

Proportional mode

A	Stabilizes the process	B	Resets the process
C	Compensates time lag in control loop	D	
Answer			

