

# Electrical Distribution

EP20

HT Line Design

Refer web site

---

## Power system Fundamentals

EP45 Trade reference study Power Equipments

---

Use Google search & find out 5 difference  
trade reference for


(1) Switch boards

(2) Busbars

(3) Insulators

(4) Circuit Breakers

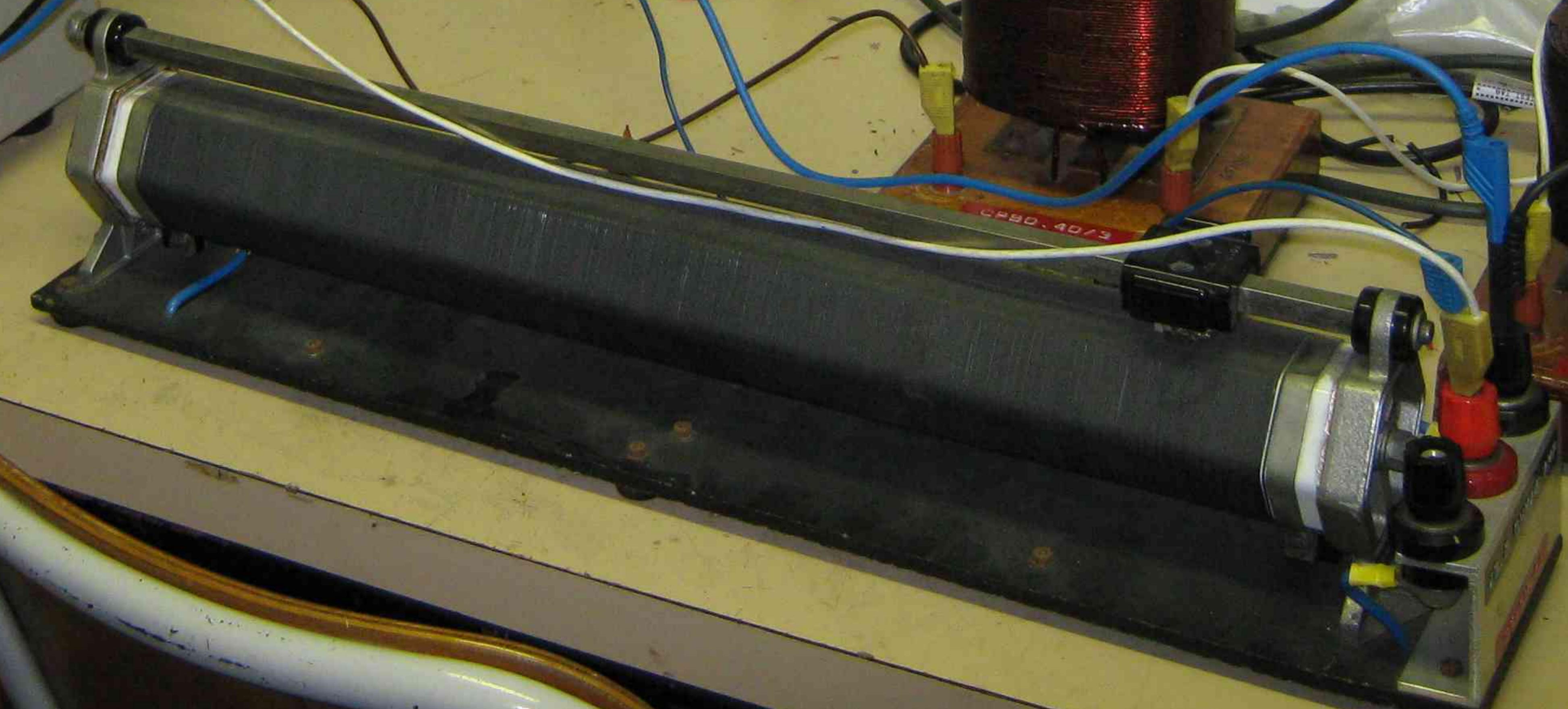(5) Other Power equipments such as  
Surge absorber, Line Trap, Lightning Arresters








240 V MAIN SWITCH No 2

FORCLUM ELECTRICAL SERVICES P/L  
11/10/159

FORCLUM ELECTRICAL SERVICES P/L  
11/10/159

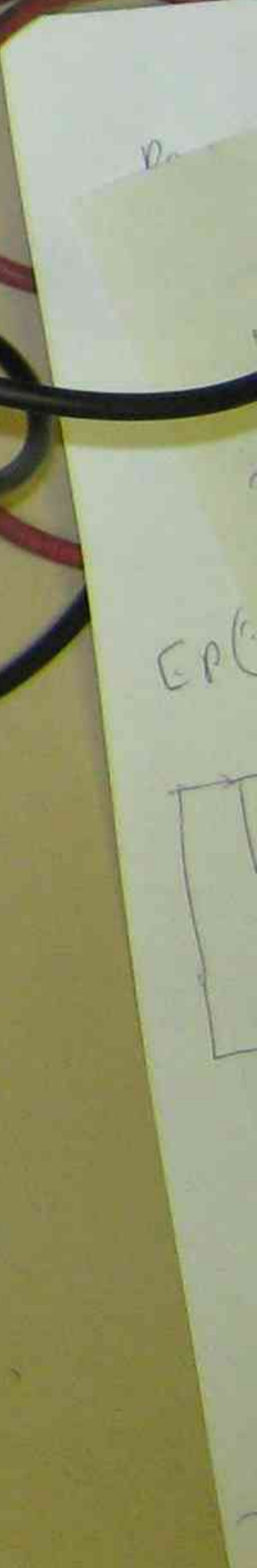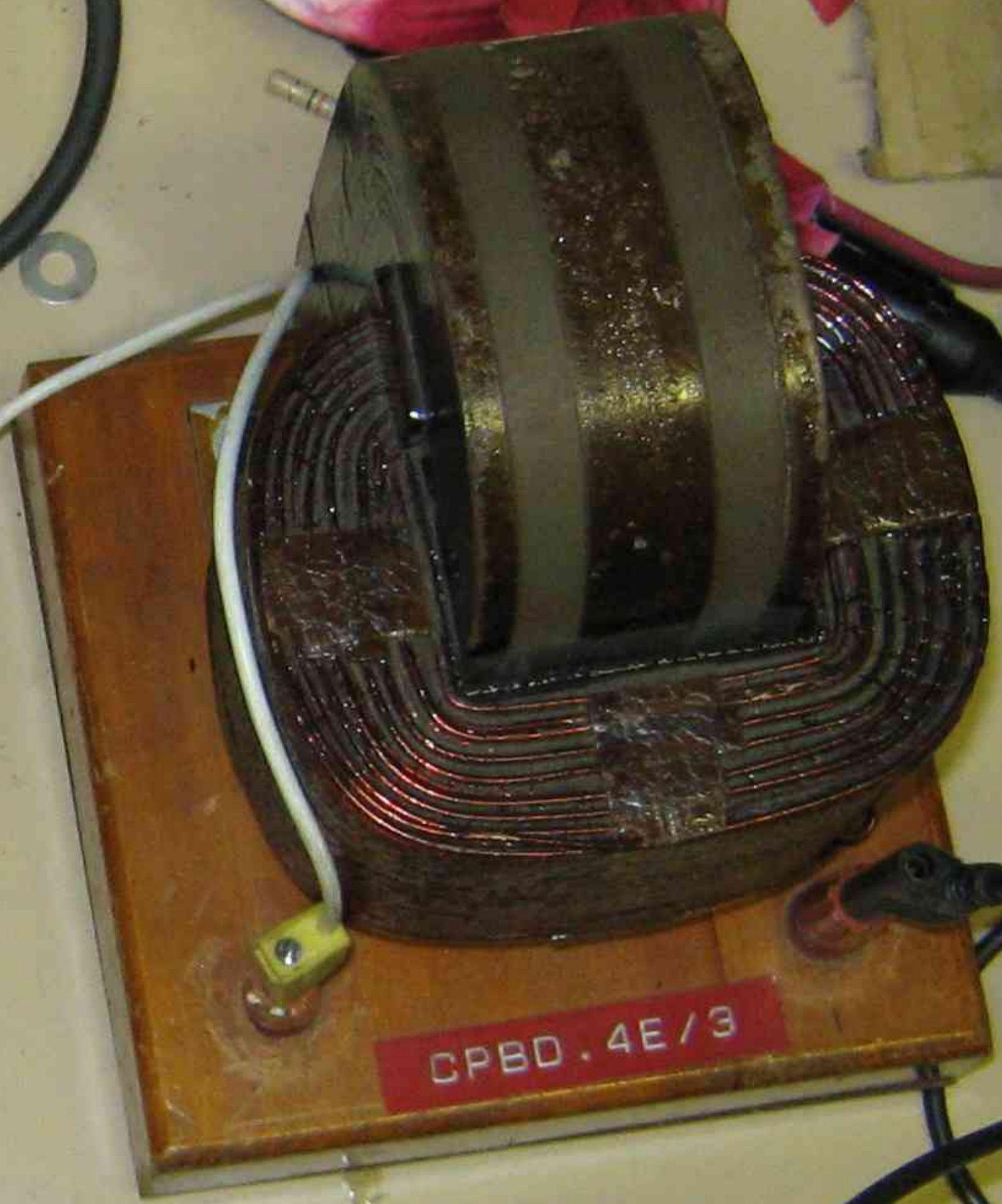FORCLUM ELECTRICAL SERVICES P/L  
11/10/159



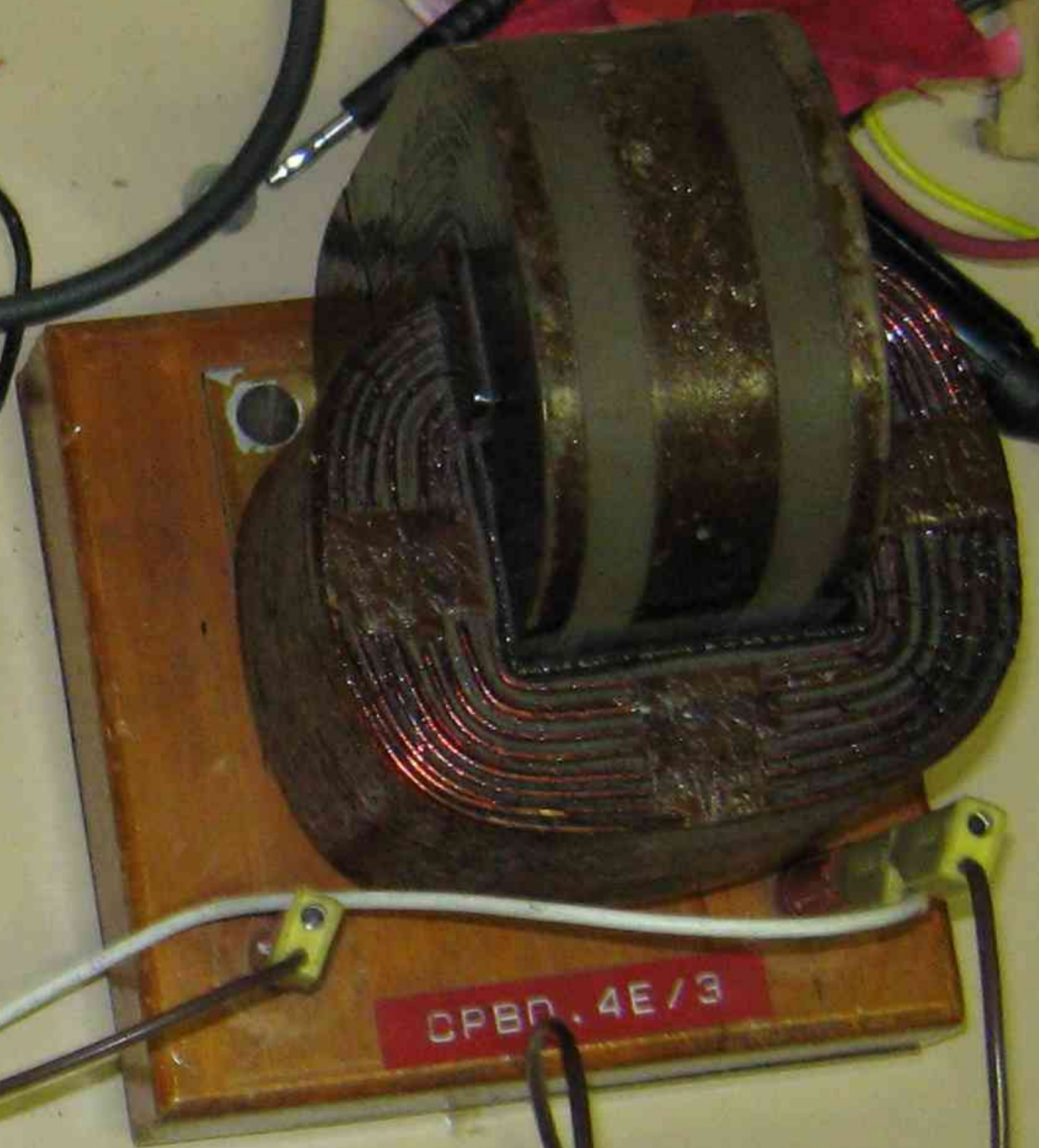

FORCLUM  
ELECTRICAL  
SERVICES P/L  
4000 GARD 124 300  
WARR. NSW 2324  
FAX: 02 5710 0000

FORCLUM  
ELECTRICAL  
SERVICES P/L  
4000 GARD 124 300  
WARR. NSW 2324  
FAX: 02 5710 0000

FORCLUM  
ELECTRICAL  
SERVICES P/L  
4000 GARD 124 300  
WARR. NSW 2324  
FAX: 02 5710 0000





DANGER 300 VOLTS

MAIN SWITCH N°1

NEUTRAL

EARTH



240 V MAIN SWITCH N°2

240 V G.P.O




70.2 OHM/4 AMP

BENCH 4A

CONTROL


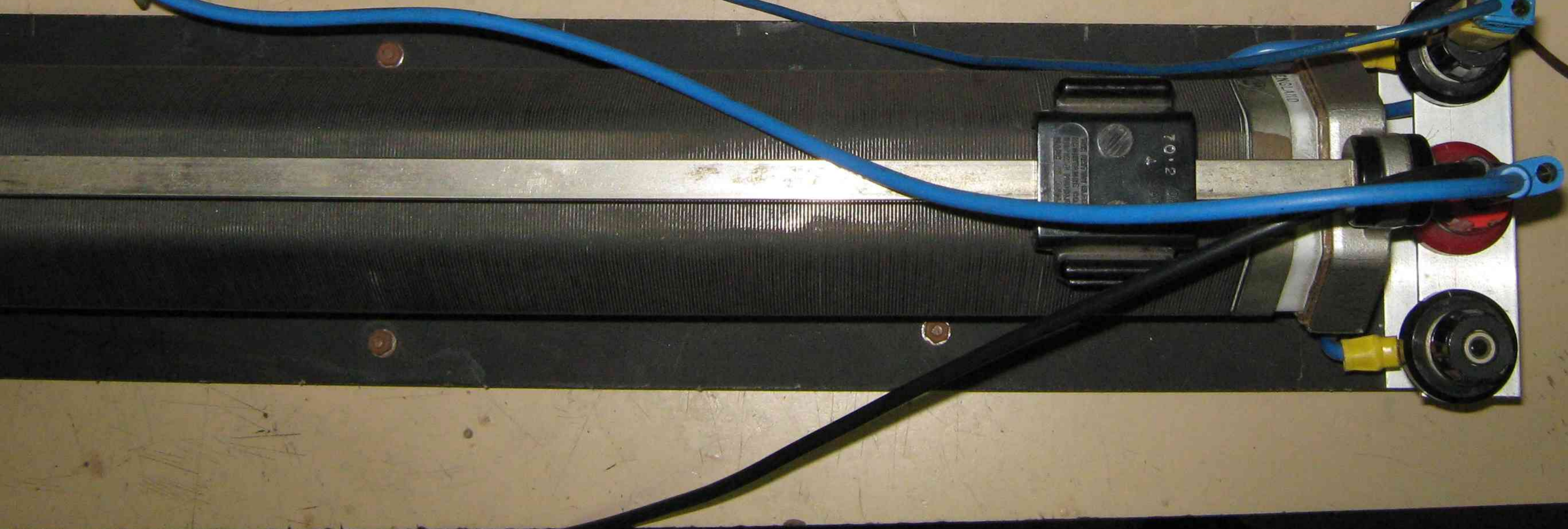
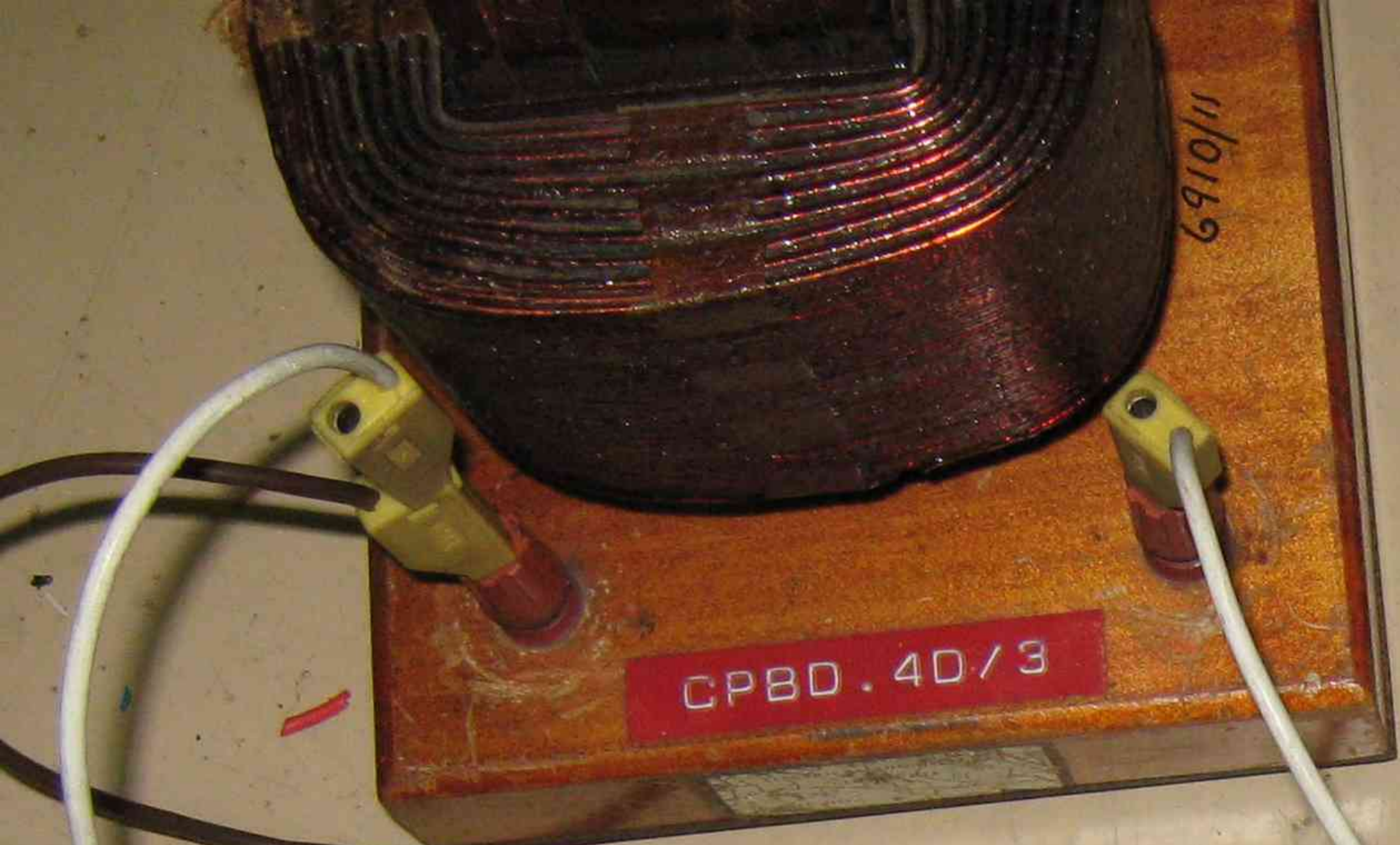




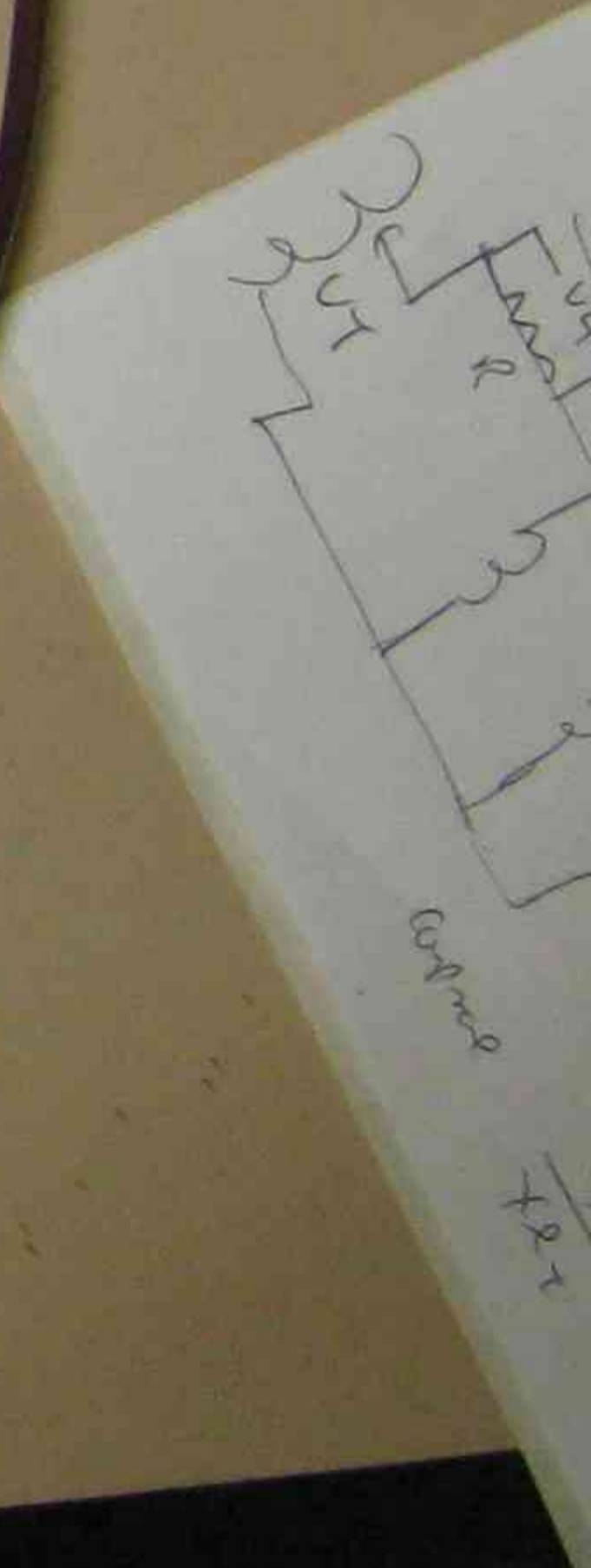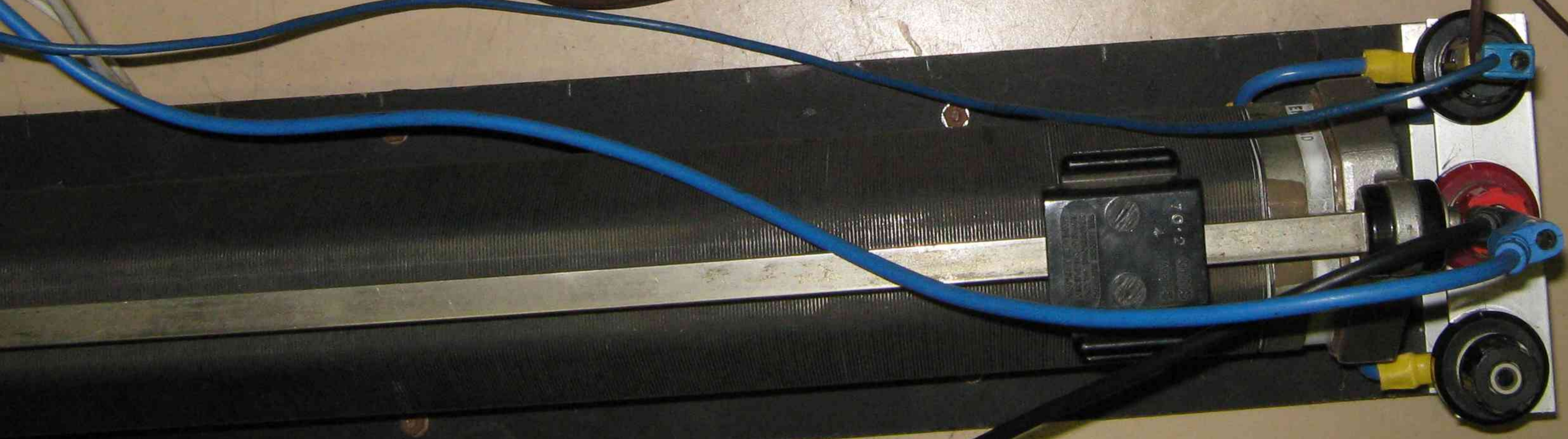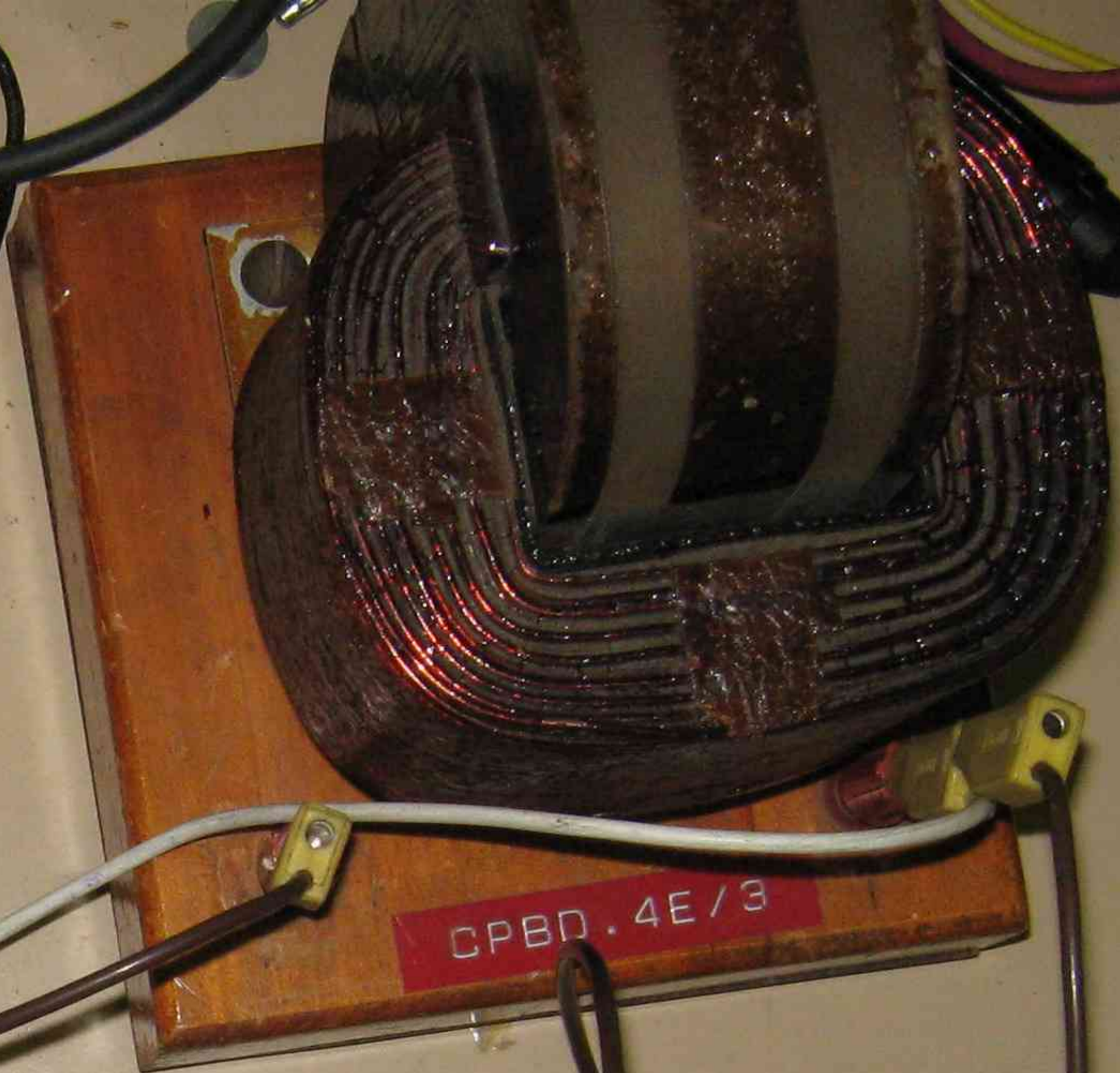

**FORCLUM**  
ELECTRICAL  
SERVICES P/L  
MOB: 0402 124 399  
FAX: 02 9798 4056

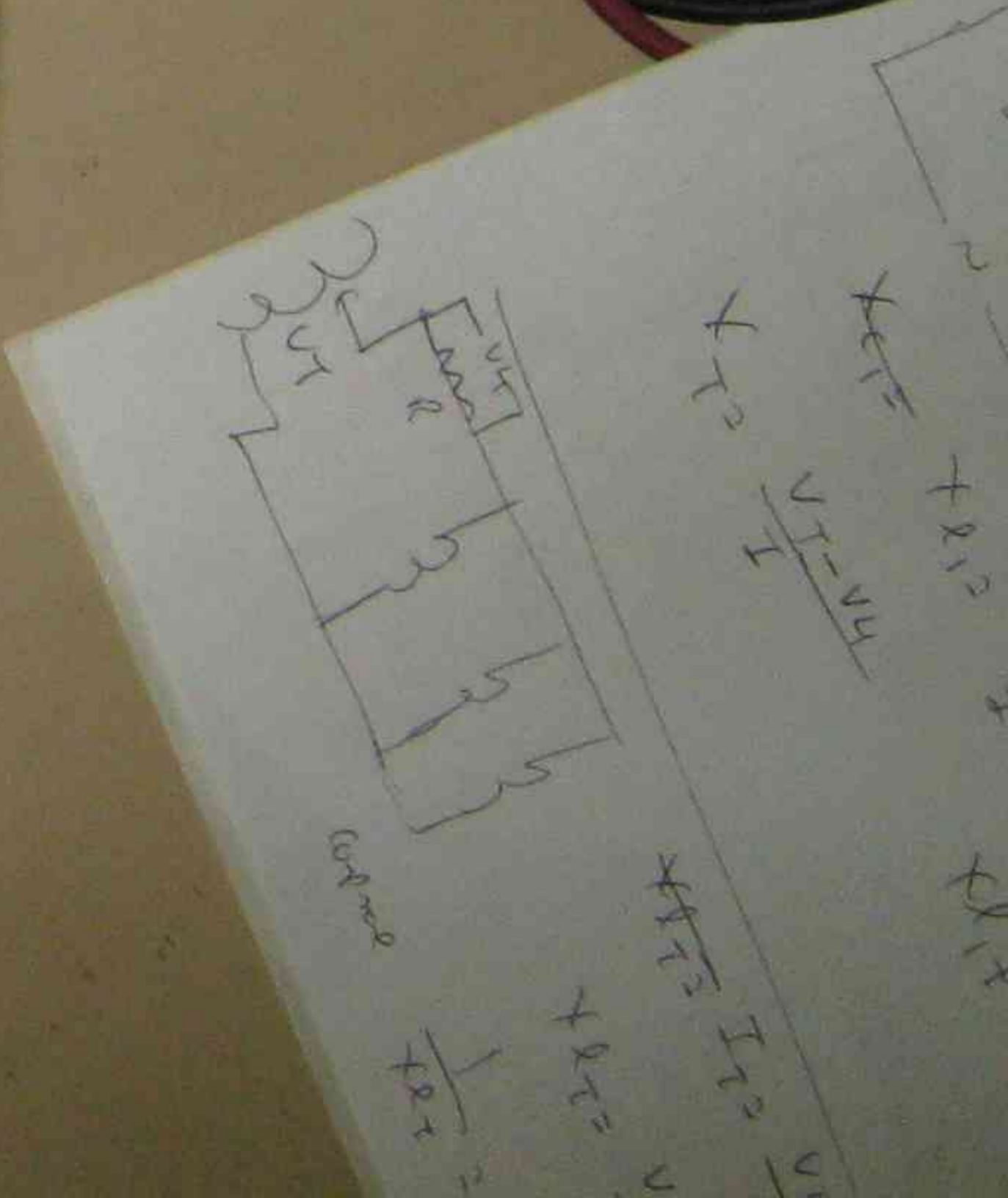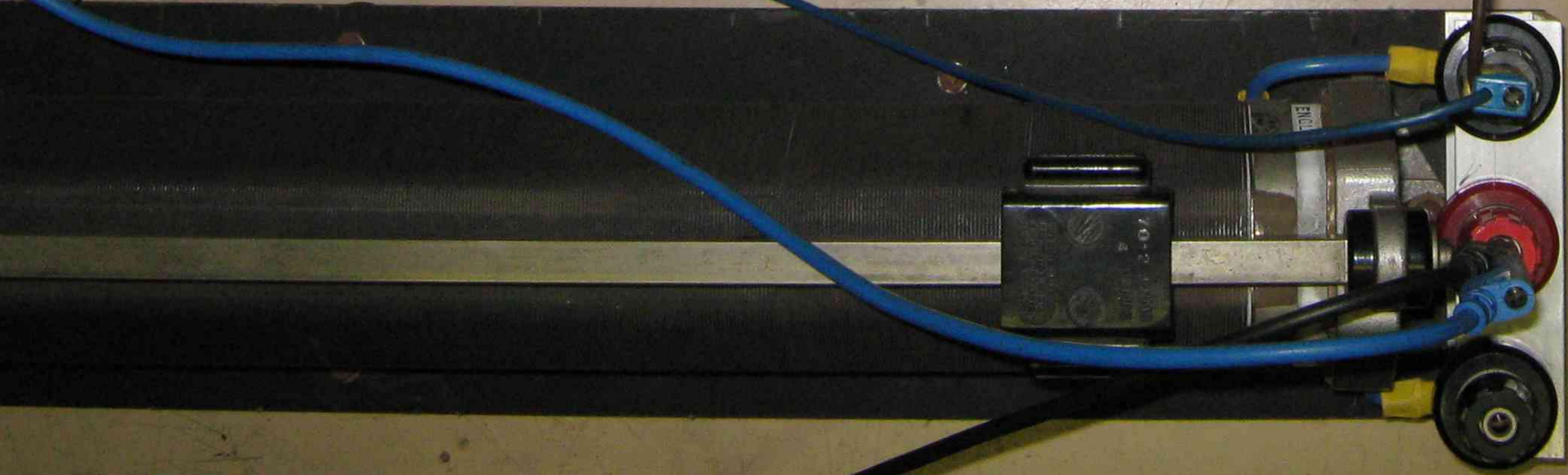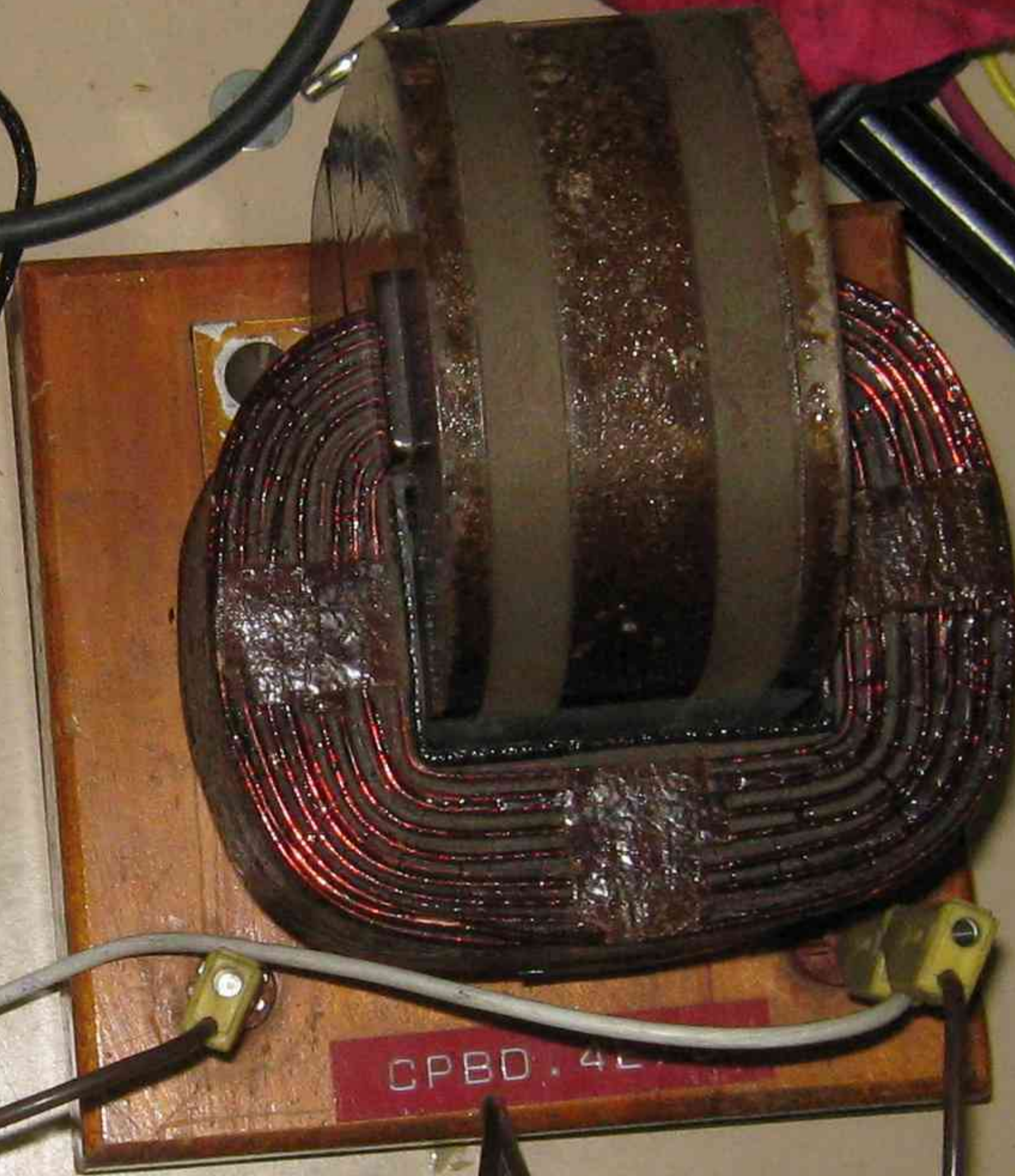**FORCLUM**  
ELECTRICAL  
SERVICES P/L  
MOB: 0402 124 399  
FAX: 02 9798 4056





Digital Multimeter (DMM) with a red LED display showing "00.0". It has various function buttons and a rotary selector switch.

EMTEK 520 Oscilloscope. Features a grid screen, "POWER" switch, "INTENSITY" knob, "TRACE ROTATION" knob, "FOCUS" knob, "CAL" knob, "POSITION" knobs, "VERTICAL" section with "VOLTS/DIV" and "VARIABLE" knobs, "INPUT AC" knob, "COUP" knob, "TEST" knob, "INPUT BO" knob, "TRIGGER" section with "SOURCE" knob, "COUPLING" knob, "LEVEL" knob, "EXT INPUT" knob, and "TRIGGER" level knob.

Grey Power Supply Unit (PSU) with a red warning label "DANGER 500 VOLTS". It has a large circular dial on the front and several output terminals on top.

White Bench Panel with two "240 V MAIN SWITCH" (Nº1 and Nº2) and two "240 V G.P.O." outlets. It also has "NEUTRAL" and "EARTH" terminals. A warning sign reads "PLEASE DO NOT PUT ANY RUBBER ON TOP OF THIS BENCH".

Two large toroidal transformers mounted on wooden blocks. The transformer on the left is labeled "CP80-4073" and the one on the right is labeled "CP80-4E73". They are connected to various cables and components on the bench.



000

000

TF 75730

EMTEK 520

DANGER 300 VOLTS

CONTROLLED BY MAIN SWITCH N°1

240V G.P.O.

240V G.P.O.

240V MAIN SWITCH N°1

NEUTRAL

EARTH

240V MAIN SWITCH N°2

240V G.P.O.

Handwritten note on the power supply.

Small label on the control panel.

Small label on the control panel.

BP 1488



Required  $L = ?$


Part 1a

Part 2

Calculate  $M$

Test

Exp (33)

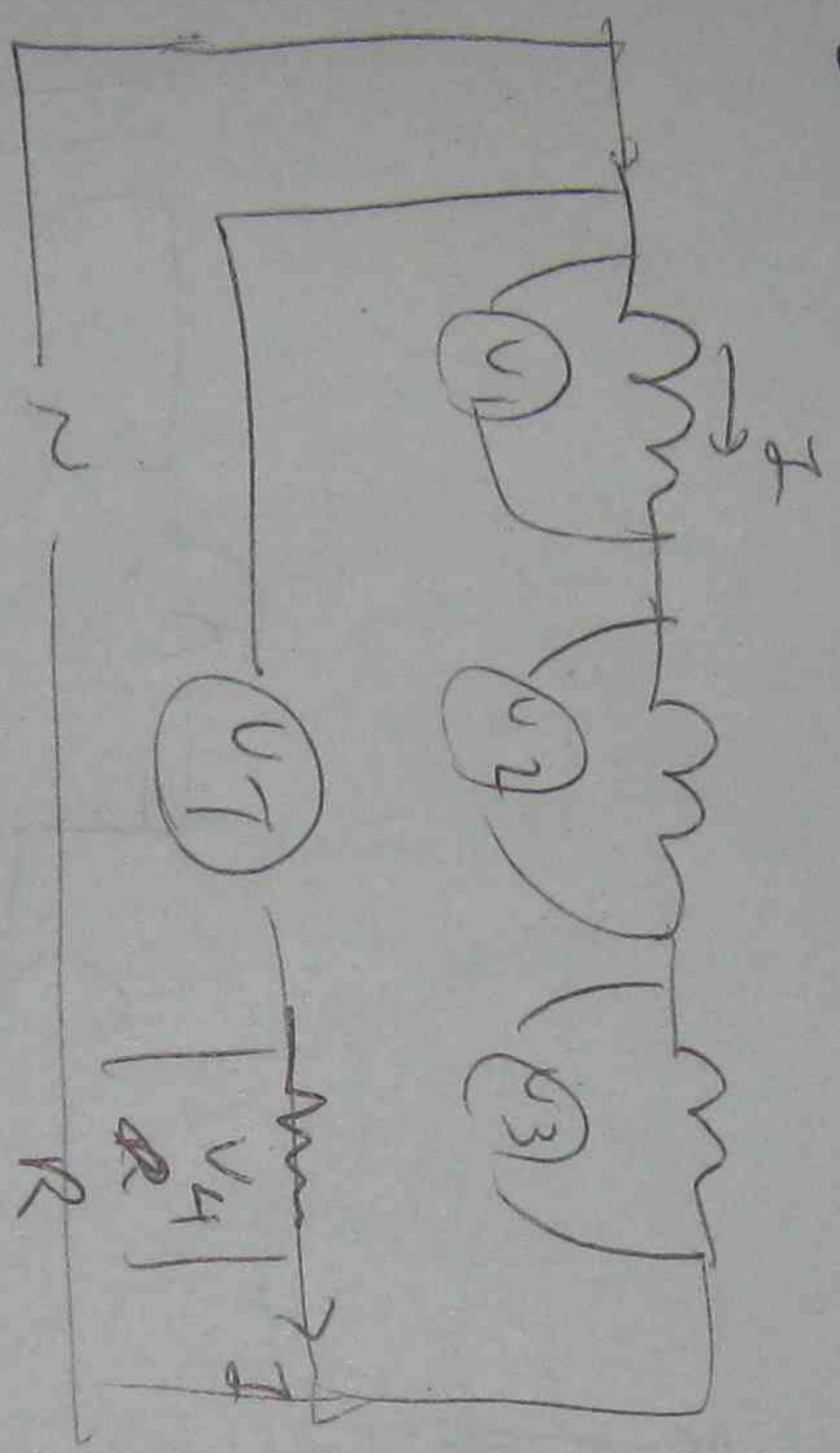

$$I = \frac{V_4}{R}$$

~~$$X_{R1} = X_{R12} = \frac{V_1}{I}$$~~

$$X_{R1} = \frac{V_2}{I}$$

$$X_{R3} = \frac{V_3}{I}$$

$$X_{R1} + X_{R2} + X_{R3} = X_{RT}$$

$$X_{RT} = \frac{V_T - V_4}{I}$$


(or)  
NOT

~~$$X_{RT} = I_{T2} = \frac{V_4}{R}$$~~

$$X_{RT} = \frac{V_T - V_4}{I_T}$$

$$\frac{1}{X_{RT}} = \frac{1}{X_{R1}} + \frac{1}{X_{R2}} + \frac{1}{X_{R3}}$$

Compare

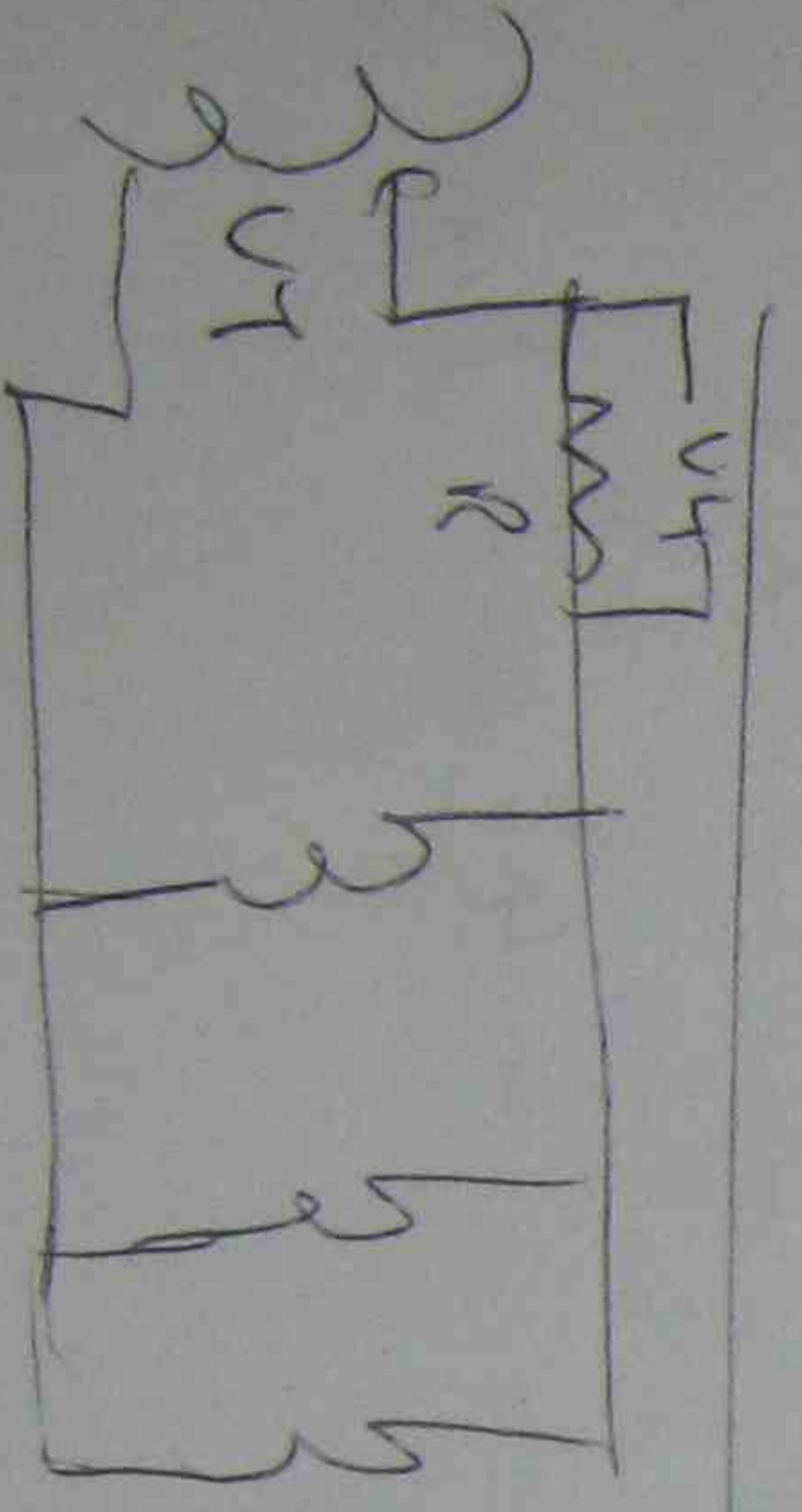


Exp (31)

$$HL = NI$$

$\uparrow$  magnetic field strength  
 $\uparrow$  length of coil  
 $\uparrow$  no. of turns  
 $\uparrow$  current

$$L = \frac{N^2 \mu_0 \mu_r A c}{l}$$

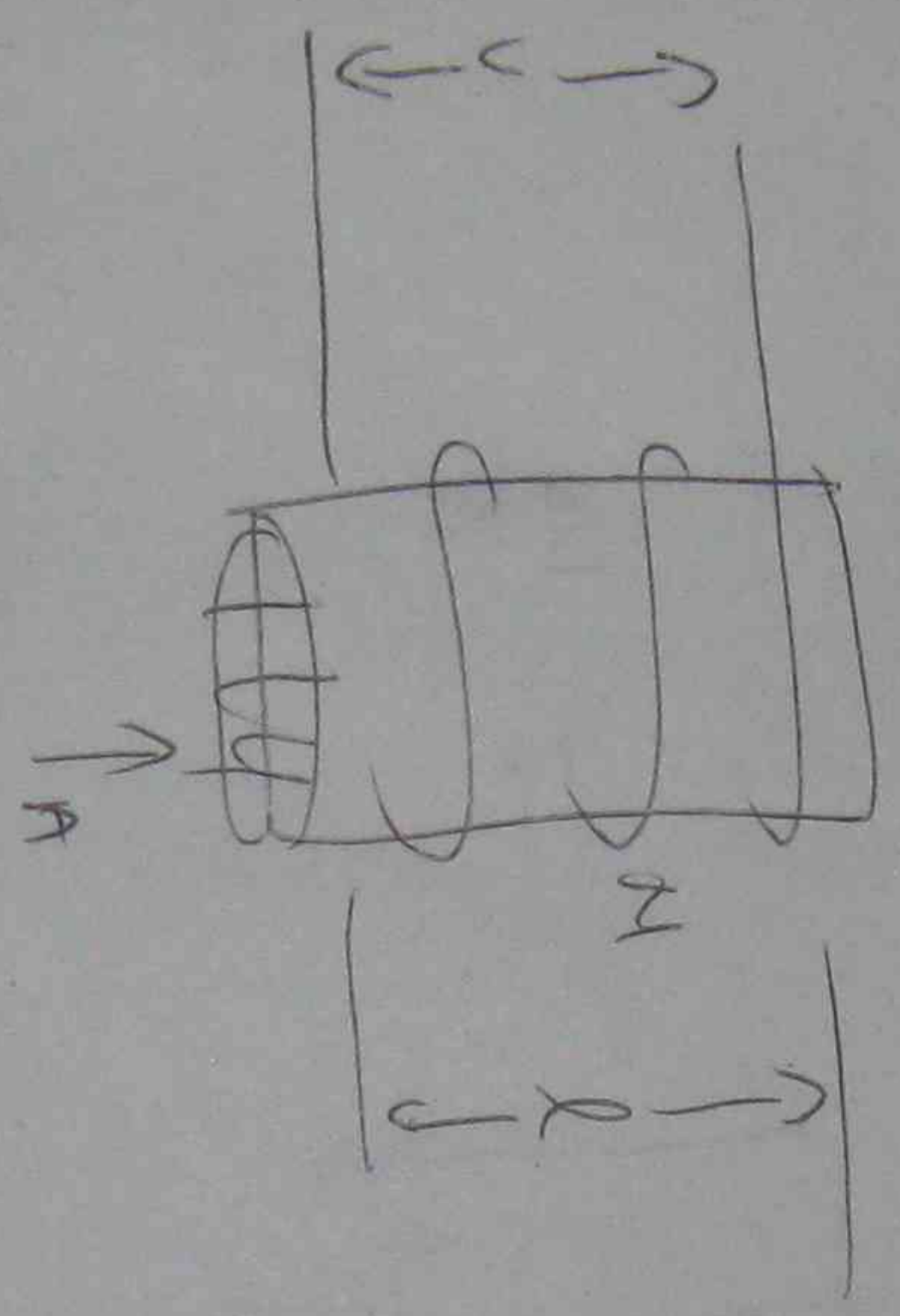
$\uparrow$  Inductance  
 $\uparrow$  no. of turns  
 $\uparrow$  length of coil  
 $\uparrow$   $\mu_r$  permeability of core  
 $\uparrow$  area of cross-section



$$2\pi f L_2 = \frac{V}{I} = XL$$

$$\therefore L = \frac{V}{2\pi f I}$$

Then find  $\mu_r$  constant

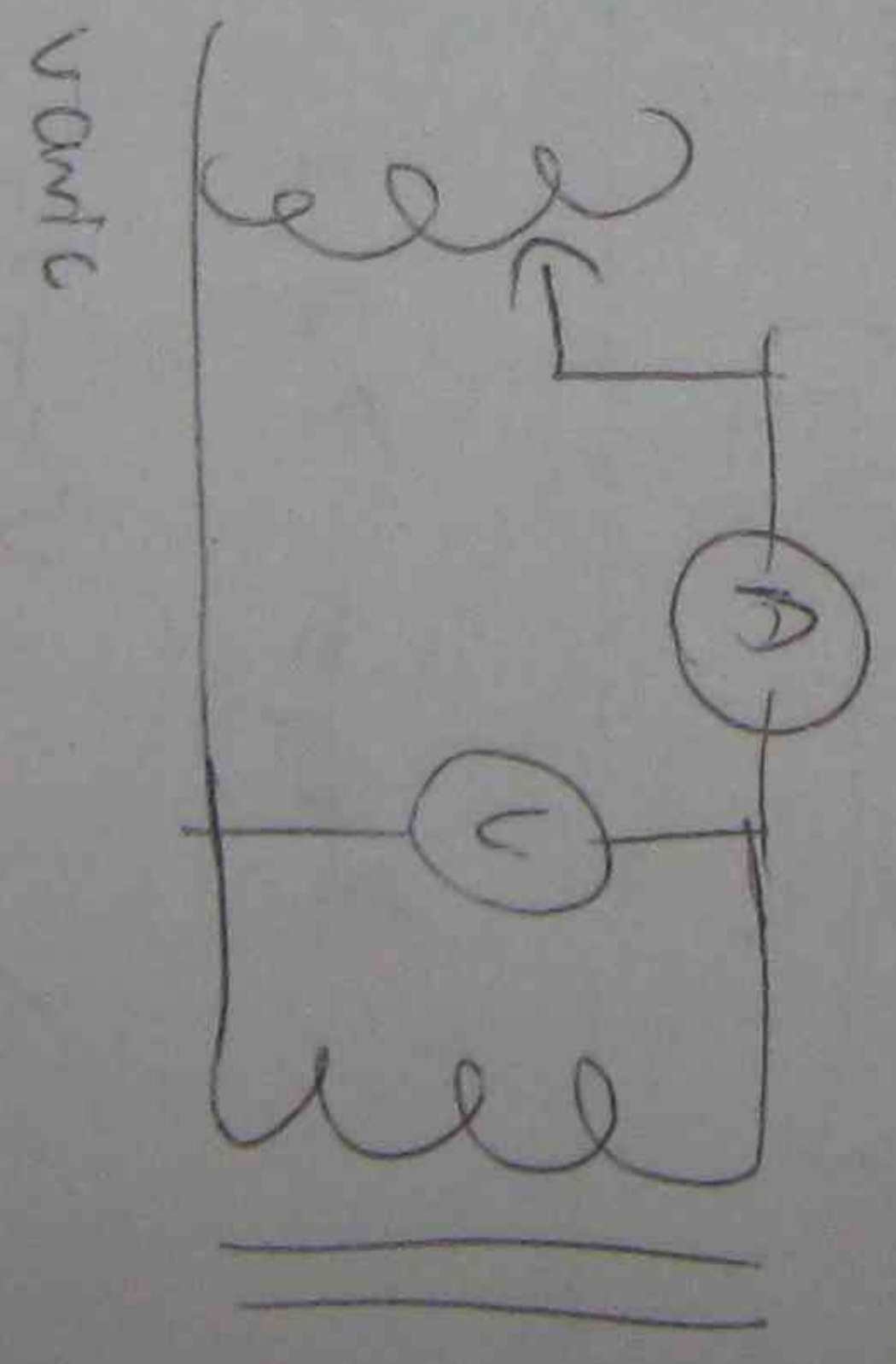

$$\mu_r = \frac{L}{\mu_0} \frac{l}{N^2 A}$$

$$= 4\pi \times 10^{-7} \frac{l}{N^2 A}$$

Required  $L = ?$


Part PA

Part 2

Calculate  $M$

Test

Exp (33)

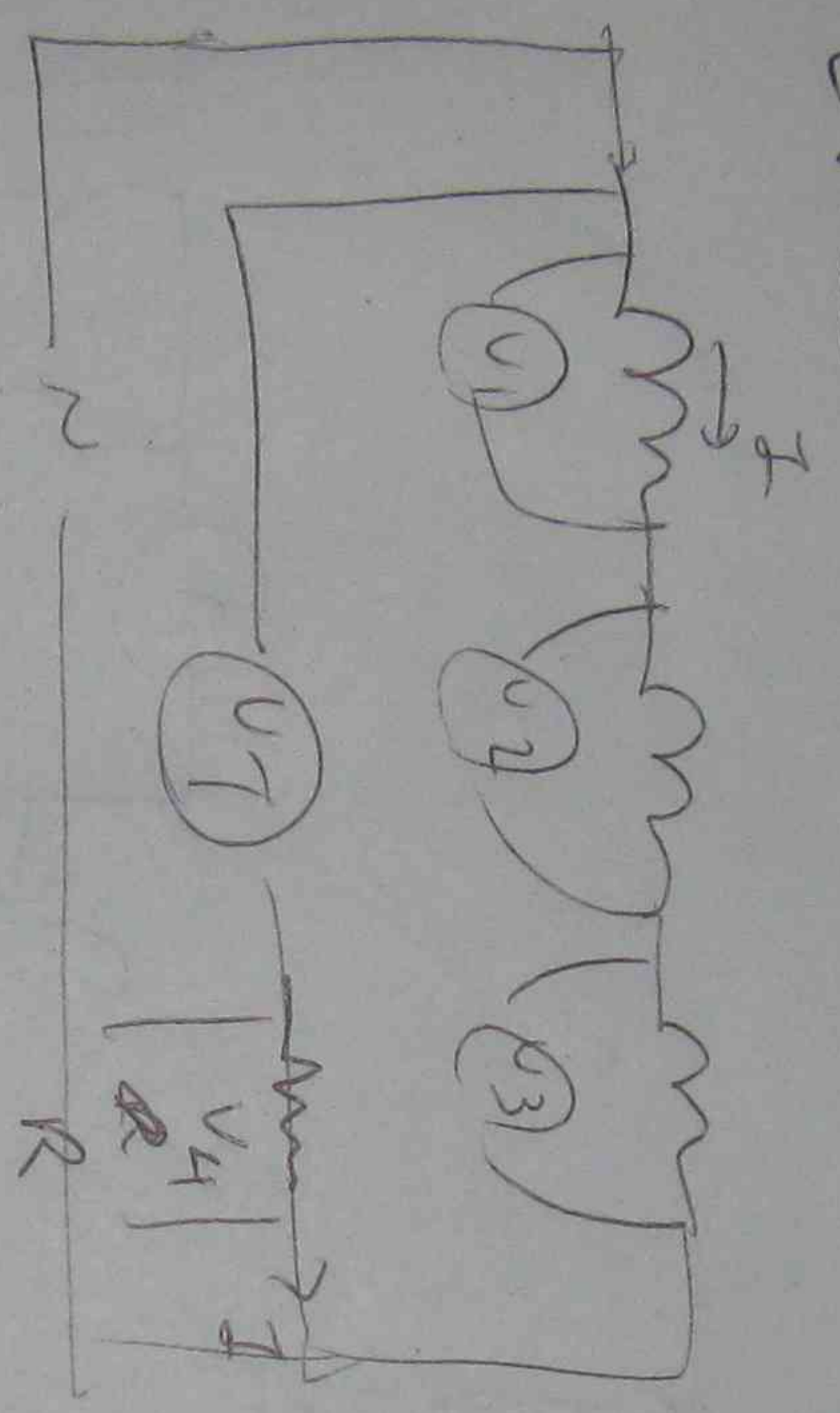

$$I = \frac{V_4}{R}$$

~~$$X_{e1} = X_{R12} = \frac{V_1}{I}$$~~


$$X_{R12} = \frac{V_2}{I}$$

$$X_{R3} = \frac{V_3}{I}$$

$$X_{T2} = \frac{V_T - V_4}{I}$$

$$X_{R1} + X_{R2} + X_{R3} = X_{RT}$$

(or)  $N_{PT}$

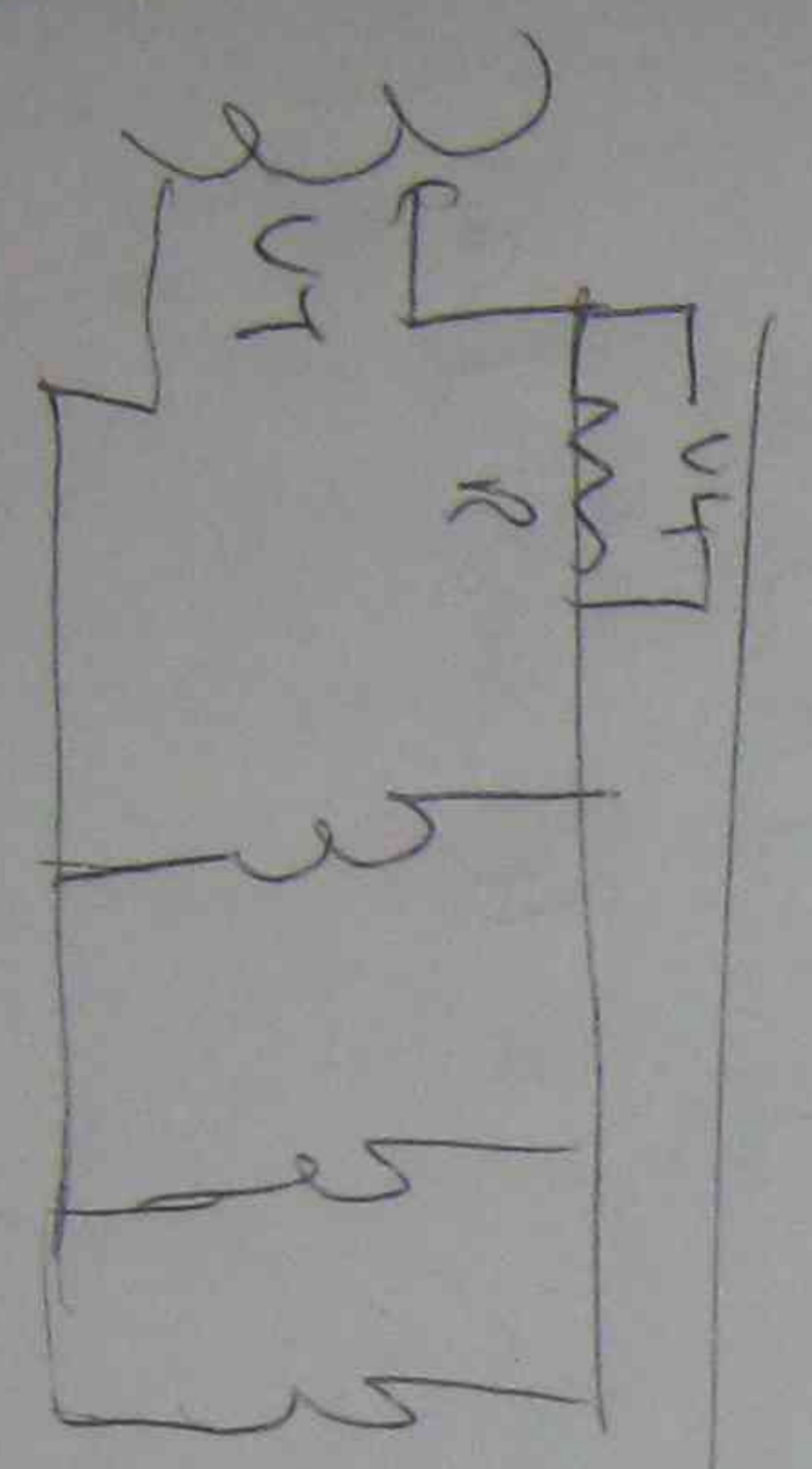

Compare


$$X_{RT2} = I_{T2} = \frac{V_4}{R}$$

$$X_{RT} = \frac{V_T - V_4}{I_T}$$

$$\frac{1}{X_{RT}} = \frac{1}{X_{R1}} + \frac{1}{X_{R2}} + \frac{1}{X_{R3}}$$




EP 33

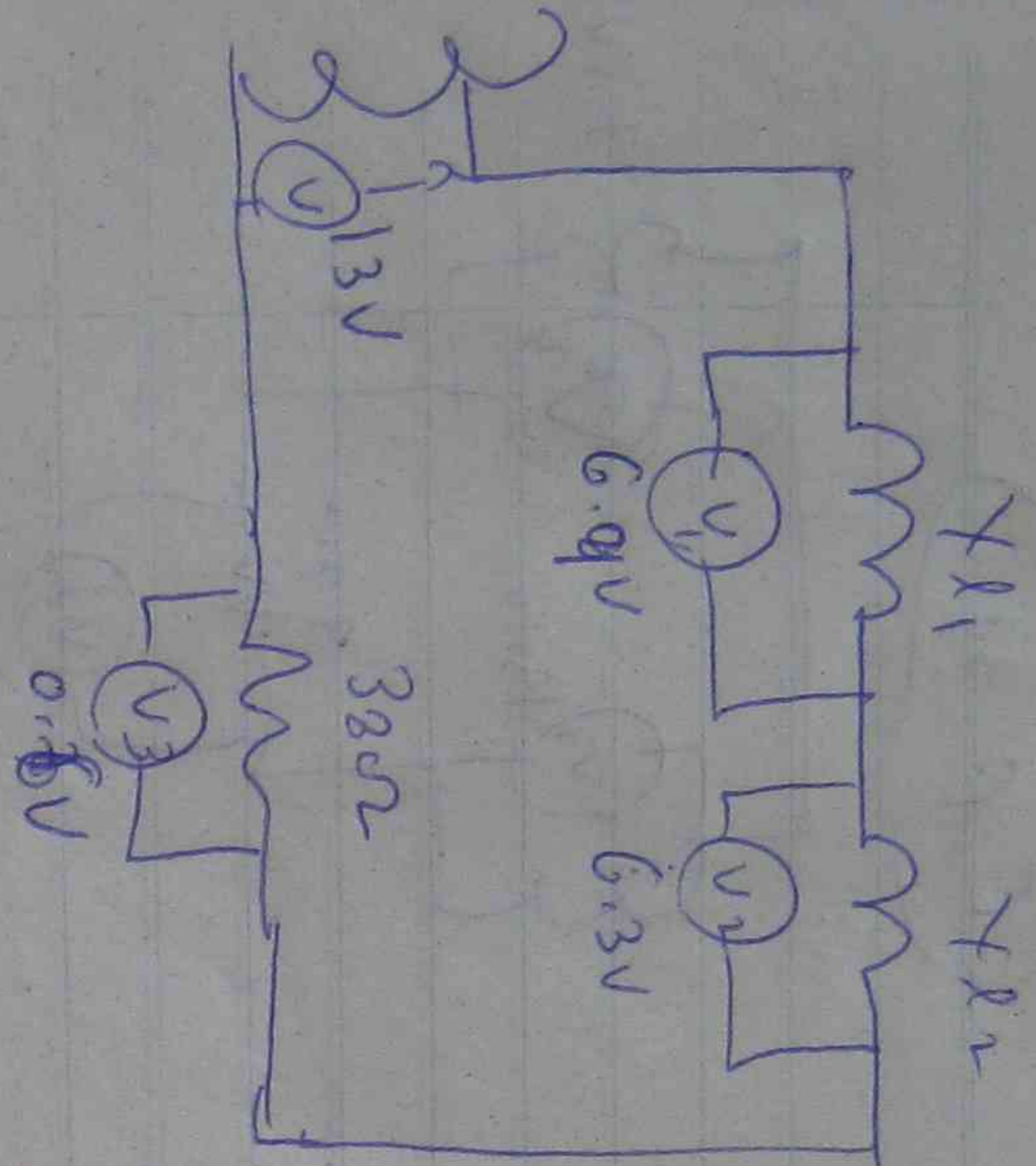

$$I = \frac{0.6}{39 \Omega} \approx 1$$
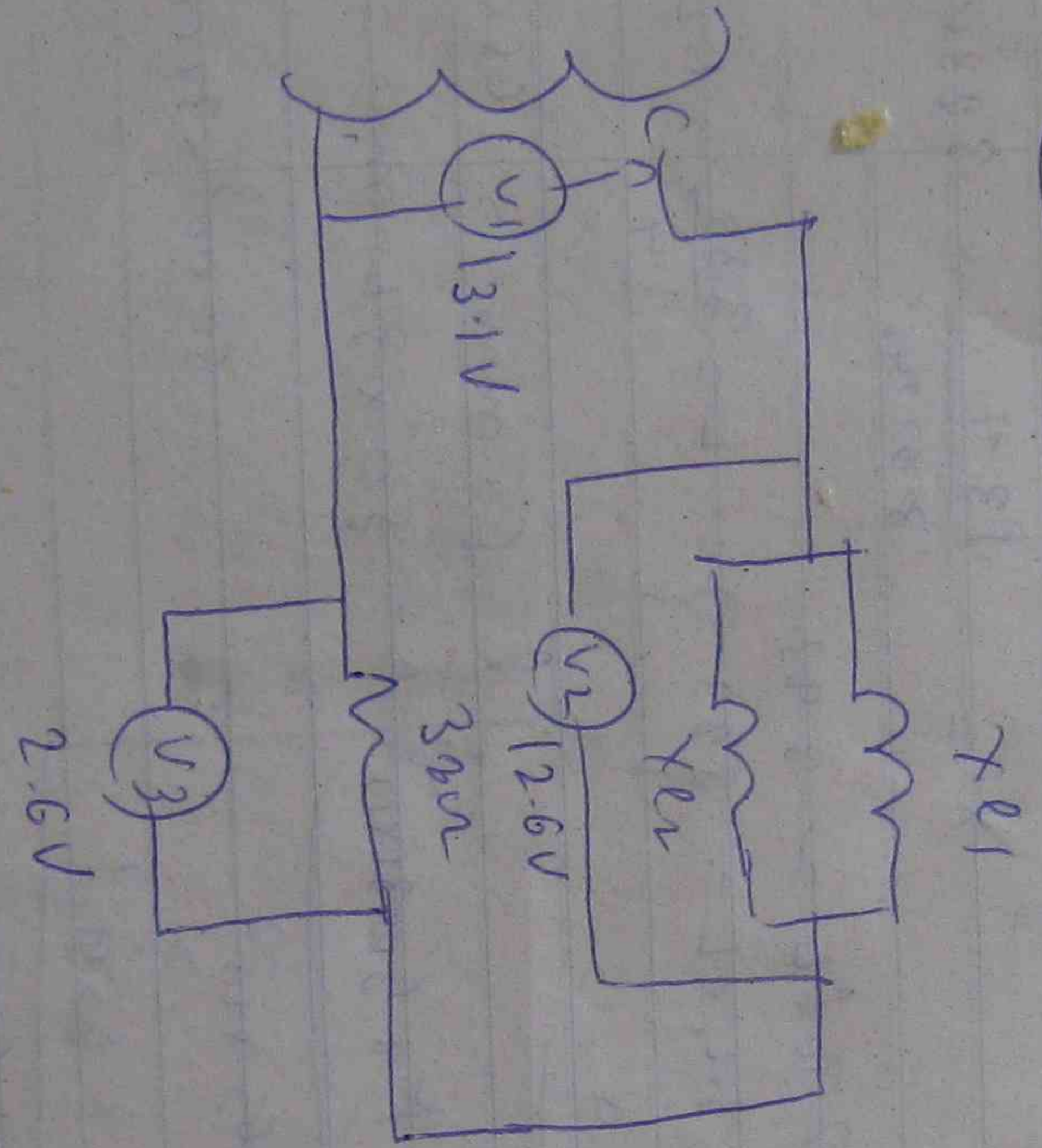
$$X_{R1} = \frac{V_1}{I}, \quad X_{R2} = \frac{V_2}{I}$$



$$I = \frac{2.6V}{39 \Omega}$$


$$X_{R2} = \frac{V_1 - V_3}{\frac{2.6}{39}}$$





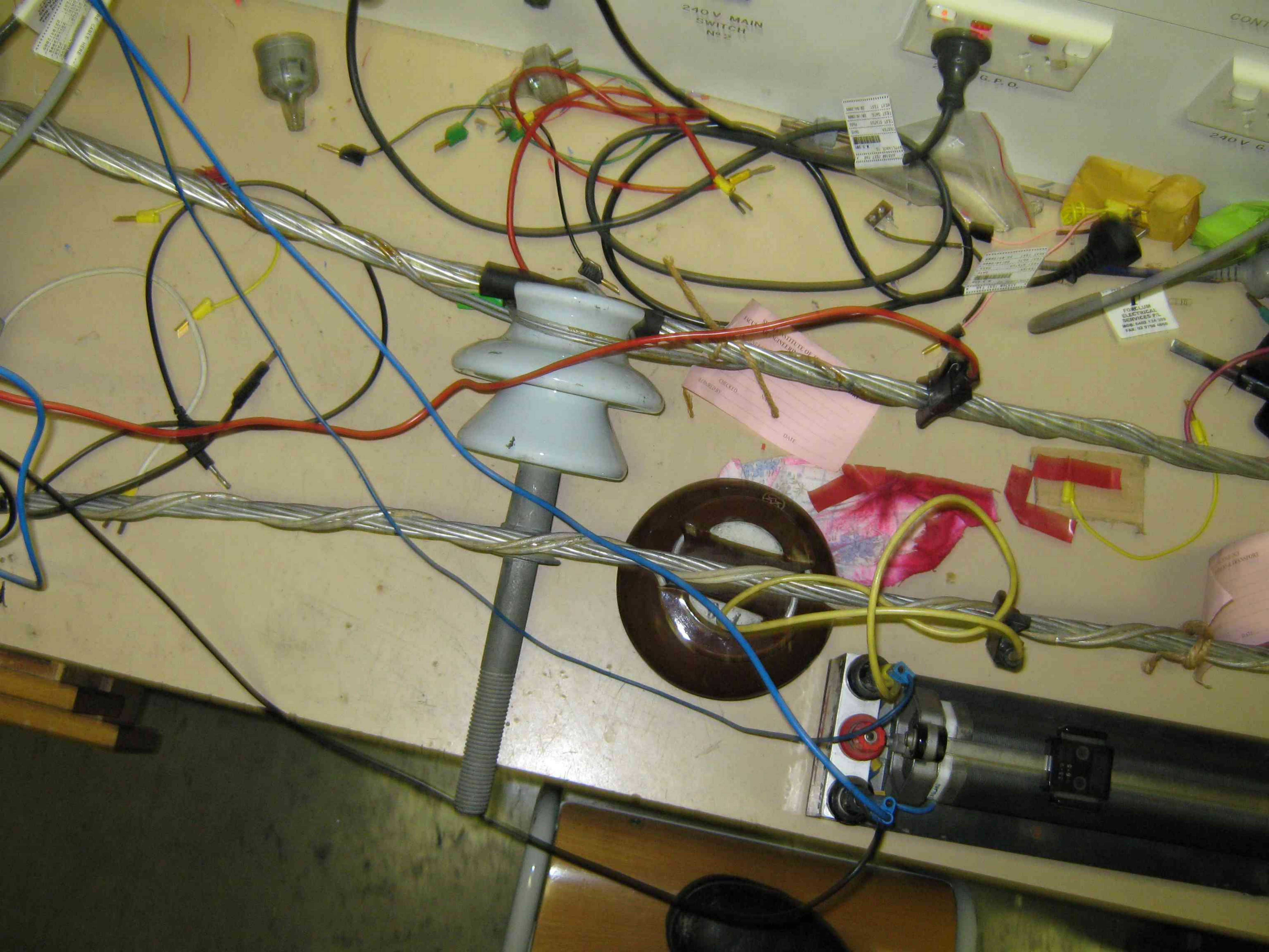Handwritten label on the front of the multimeter, possibly reading "100.6".





240V MAIN SWITCH No 2

G.P.O.


240V G

WARRANTY NO: 1001 1000  
SERIAL NO: 1001 1000  
DATE: 01/01/2010  
BY: [Signature]

INSTITUTE OF  
ELECTRICAL ENGINEERS  
CHECKED  
DATE

FORCLUM ELECTRICAL SERVICES P/L  
NO. 6485 124 200  
TEL: 02 9706 4800

WARRANTY NO: 1001 1000  
SERIAL NO: 1001 1000  
DATE

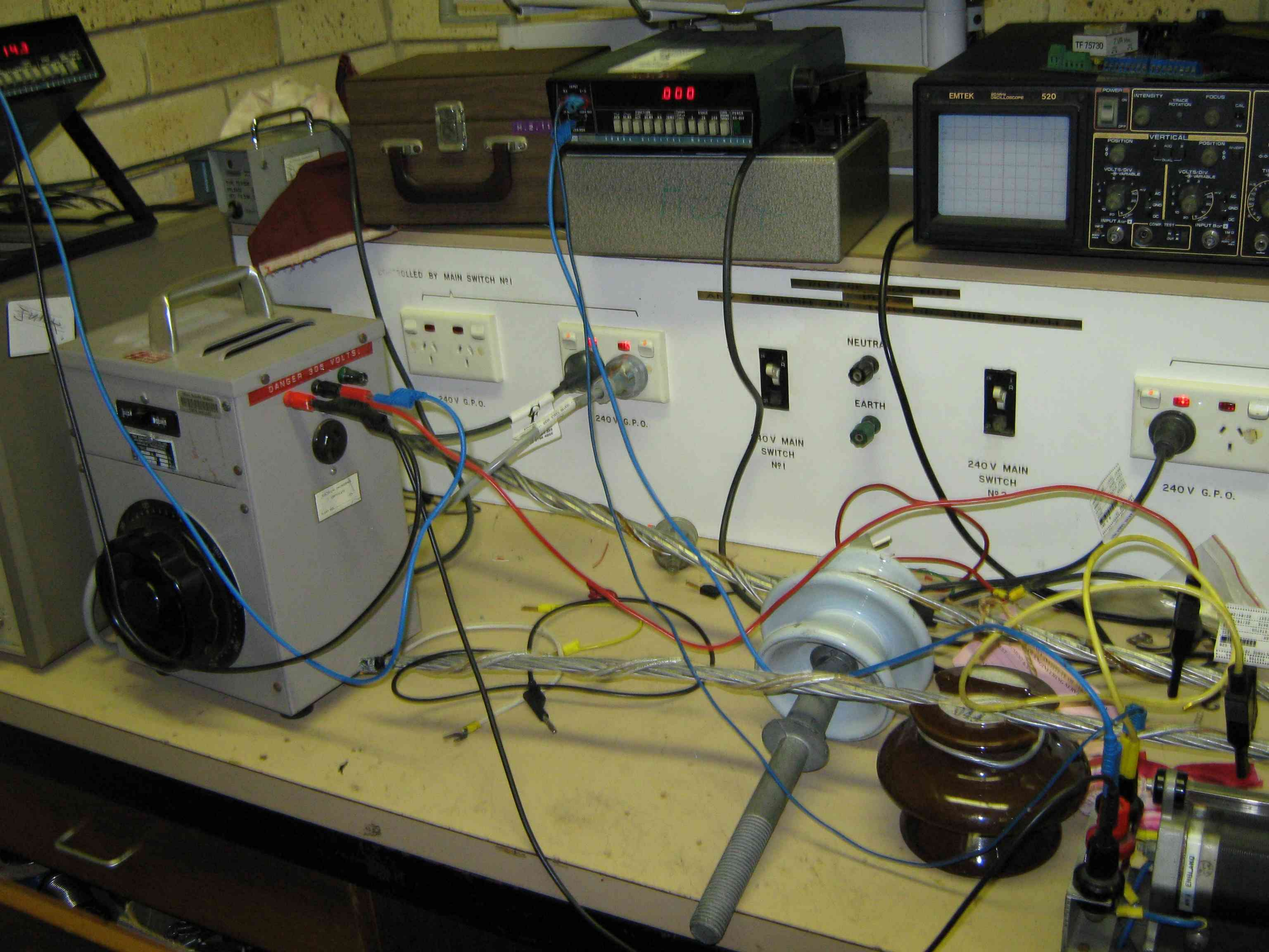

TF 75730

EMTEK 520

000

CONTROLLED BY MAIN SWITCH No1

240 V G.P.O.

240 V G.P.O.

NEUTRA

EARTH


240 V MAIN SWITCH No1

240 V MAIN SWITCH No2

240 V G.P.O.

DANGER 300 VOLTS

ENGLAND

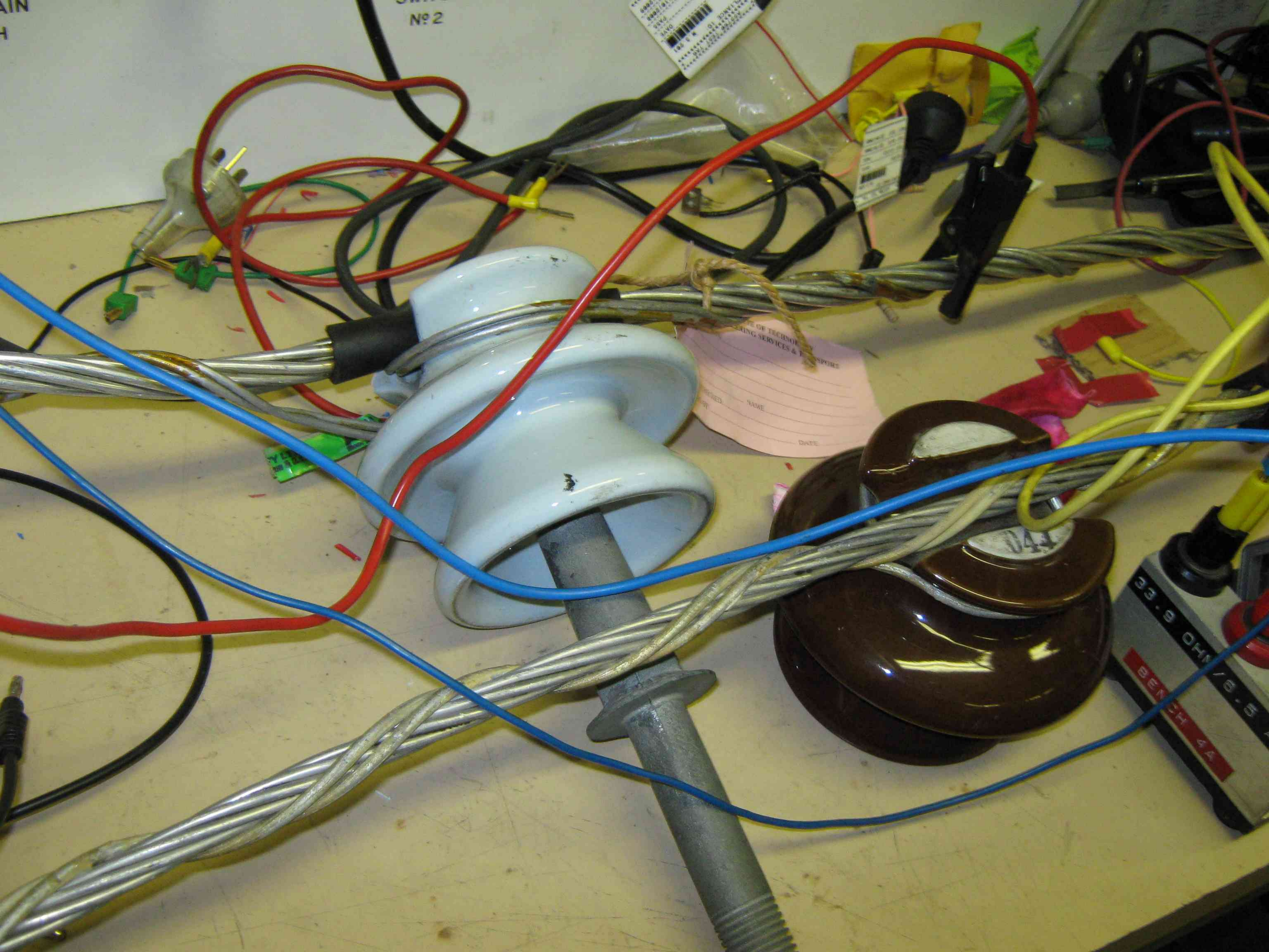

№2

STATE OF TECHNOLOGY  
ENGINEERING SERVICES & EQUIPMENT  
DATE  
NAME  
DATE

STATE OF TECHNOLOGY  
ENGINEERING SERVICES & EQUIPMENT  
DATE  
NAME  
DATE

BENCH 44  
33-9 OHM 76-5



240V G.P.O.  
 ESTN: 45328  
 TEST STATUS: PASS  
 TEST DATE: 20/10/2008  
 NEXT TEST: 20/04/2009  
 APPLIANCE ID: M 3 201  
 DATE: 20/10/2008  
 NAME: DAVE  
 MANUFACTURER:



MAIN  
 CH  
 2




TEST TAG  
ASS3760 TEST TAG  
DATE: 22/10/2008  
PASS  
TESTER: DAVE  
TEST STATUS: PASS  
TEST DATE: 22/10/2008  
NEXT TEST: 22/04/2009

FORCLUM  
ELECTRICAL  
SERVICES PT. LTD.  
111-113, 115-117, 119-121, 123-125  
TAN. ST. ST. 1000  
1-1-084


NEY INSTITUTE OF  
ENGINEERS

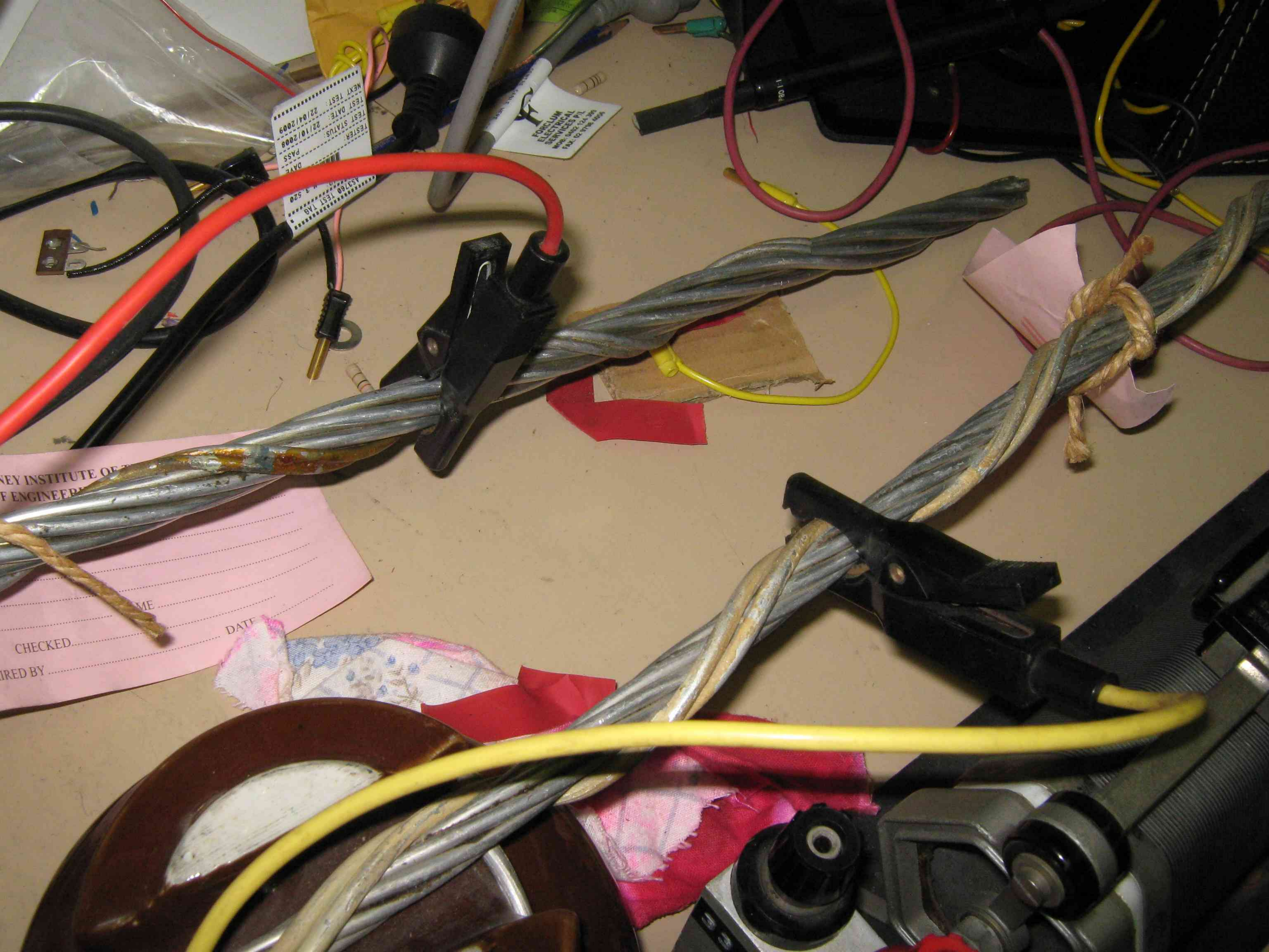NAME \_\_\_\_\_  
DATE \_\_\_\_\_  
CHECKED \_\_\_\_\_  
REQUIRED BY \_\_\_\_\_





ACR capacitance

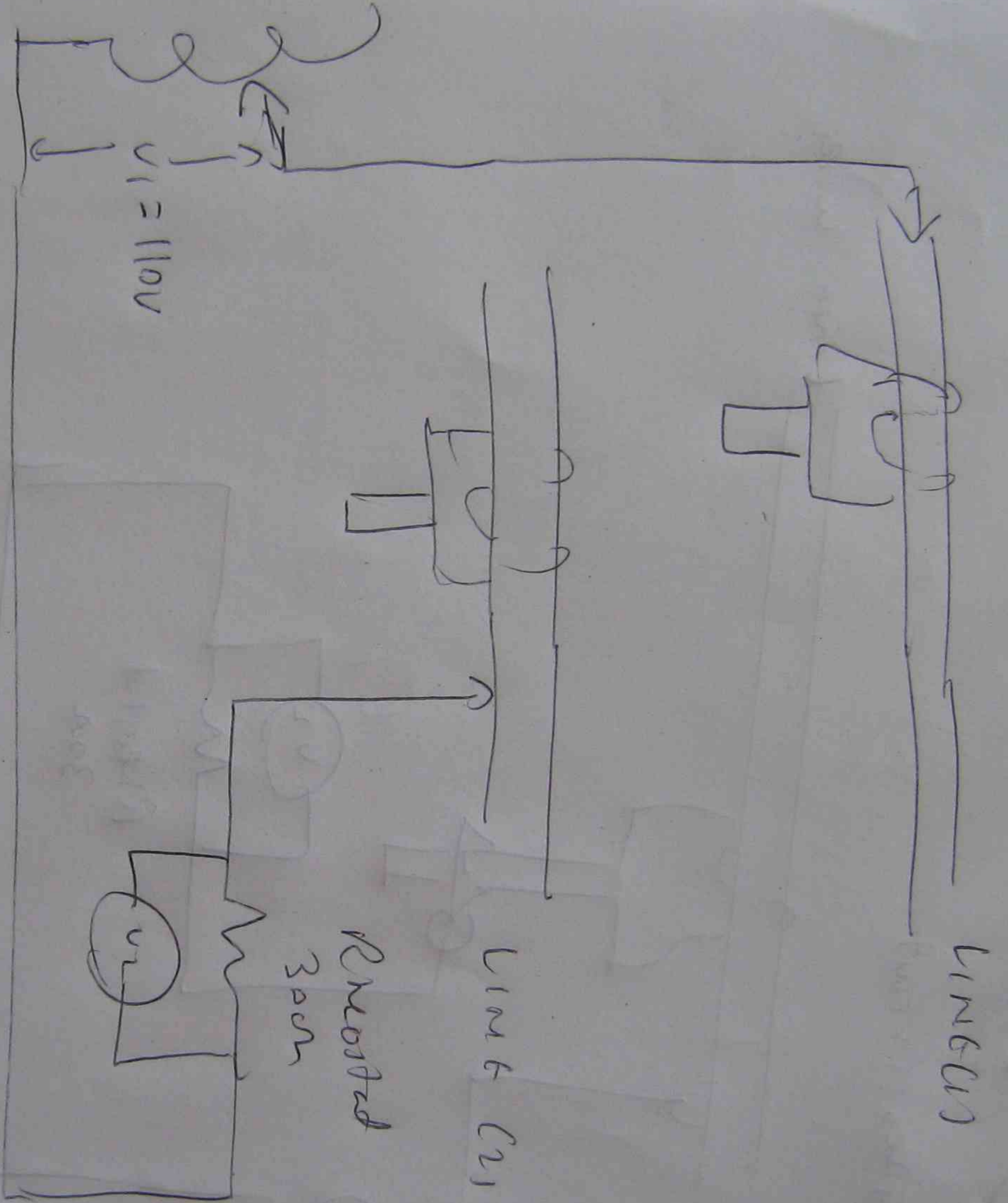


Set  $V_1 = 110V$


Measure  $V_2$ ,  $I_2$

$$R_{meas} = \frac{V_2}{I_2}$$

$$X_{C2} = \frac{110 - V_2}{I}$$

$$C_2 = \frac{1}{2\pi f X_{C2}}$$

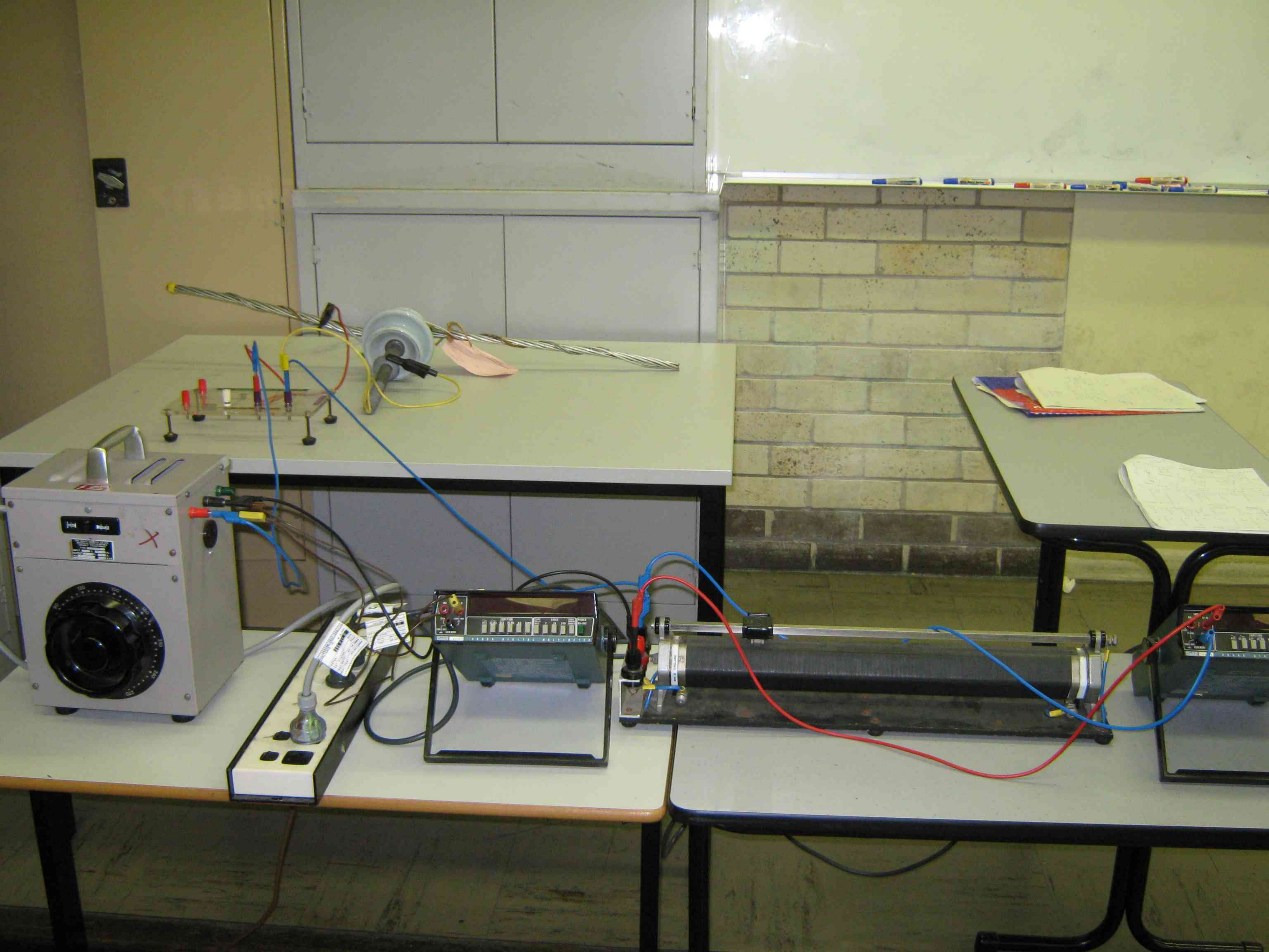

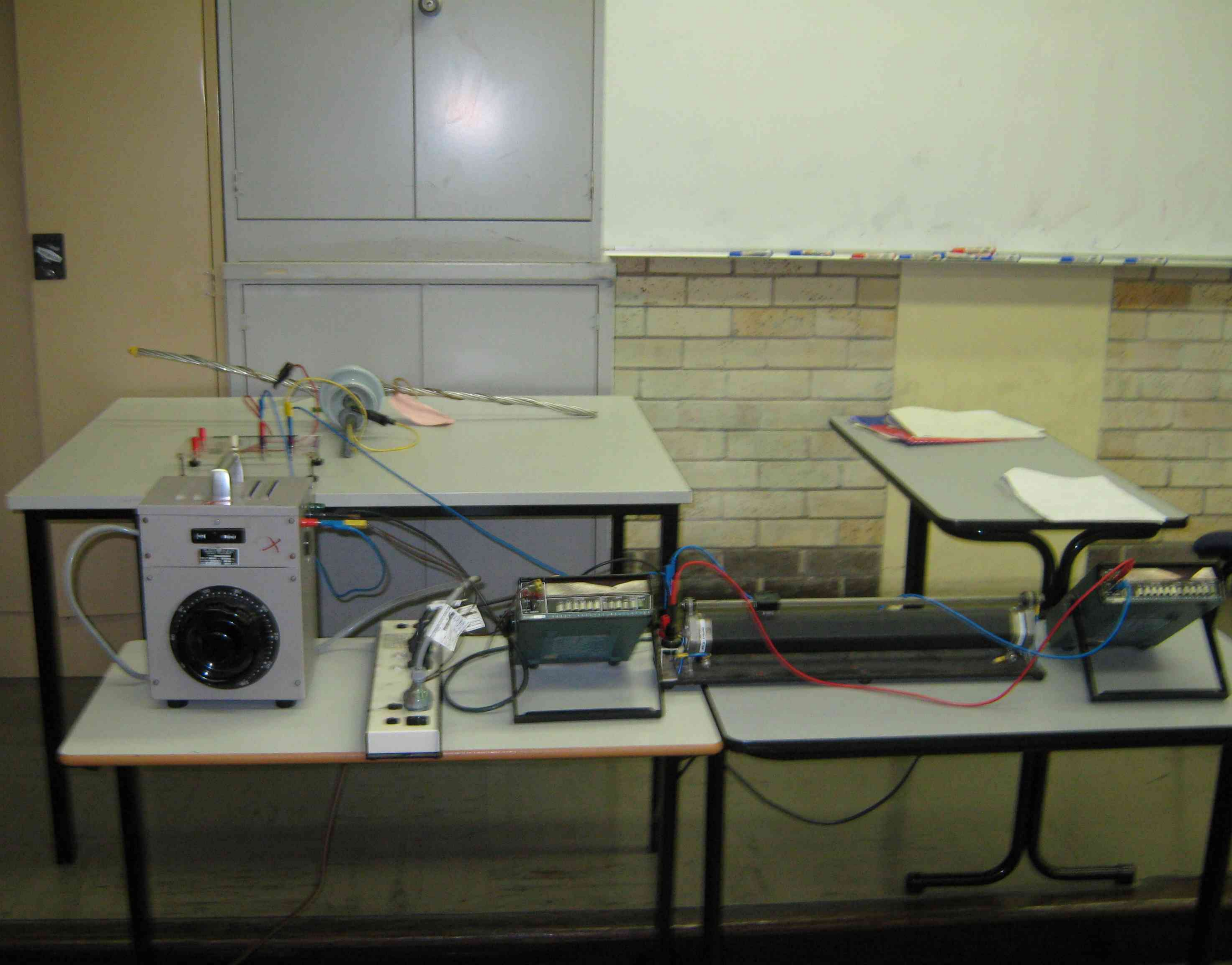


up = 18 chairs desks



# TRANSMISSION LINE PRACTICAL

## ① LINE INSULATOR TEST

(1) CONNECT THE GIVEN CIRCUIT

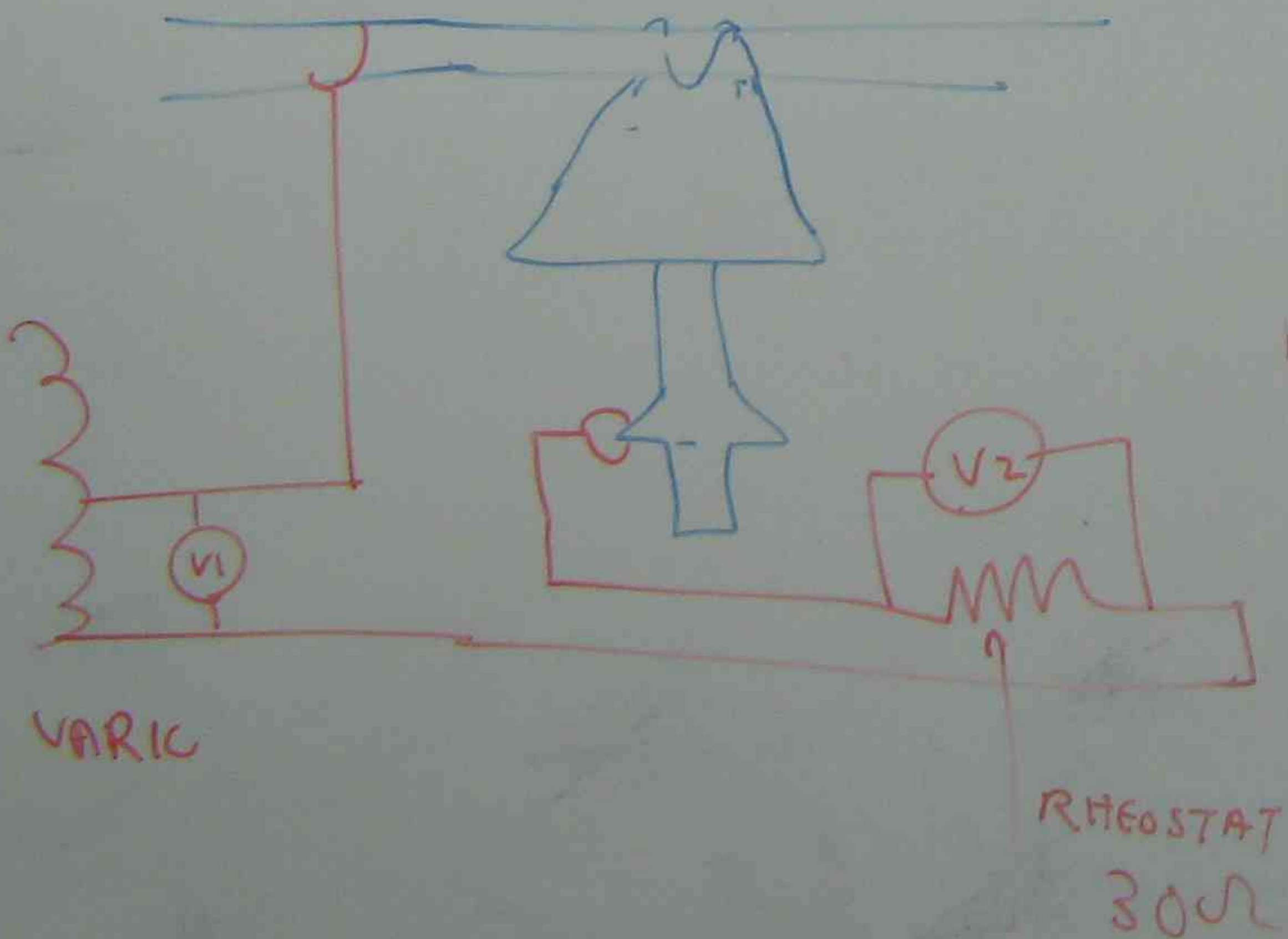

(2) INJECT  $V_1$  80V

(3) MEASURE  $V_2$

(4) CALCULATE  $I = \frac{V_2}{\text{RHEOSTAT RESISTANCE (30}\Omega\text{)}}$


(5)  $X_c = \frac{V_1 - V_2}{I}$


(6)  $C_{80V} = \frac{1}{2\pi f X_c}$  WHERE  $f = 50\text{ Hz}$

REPEAT THE ABOVE STEP FOR 90V & 100V

$C = \frac{C_{80V} + C_{90V} + C_{100V}}{3}$  F

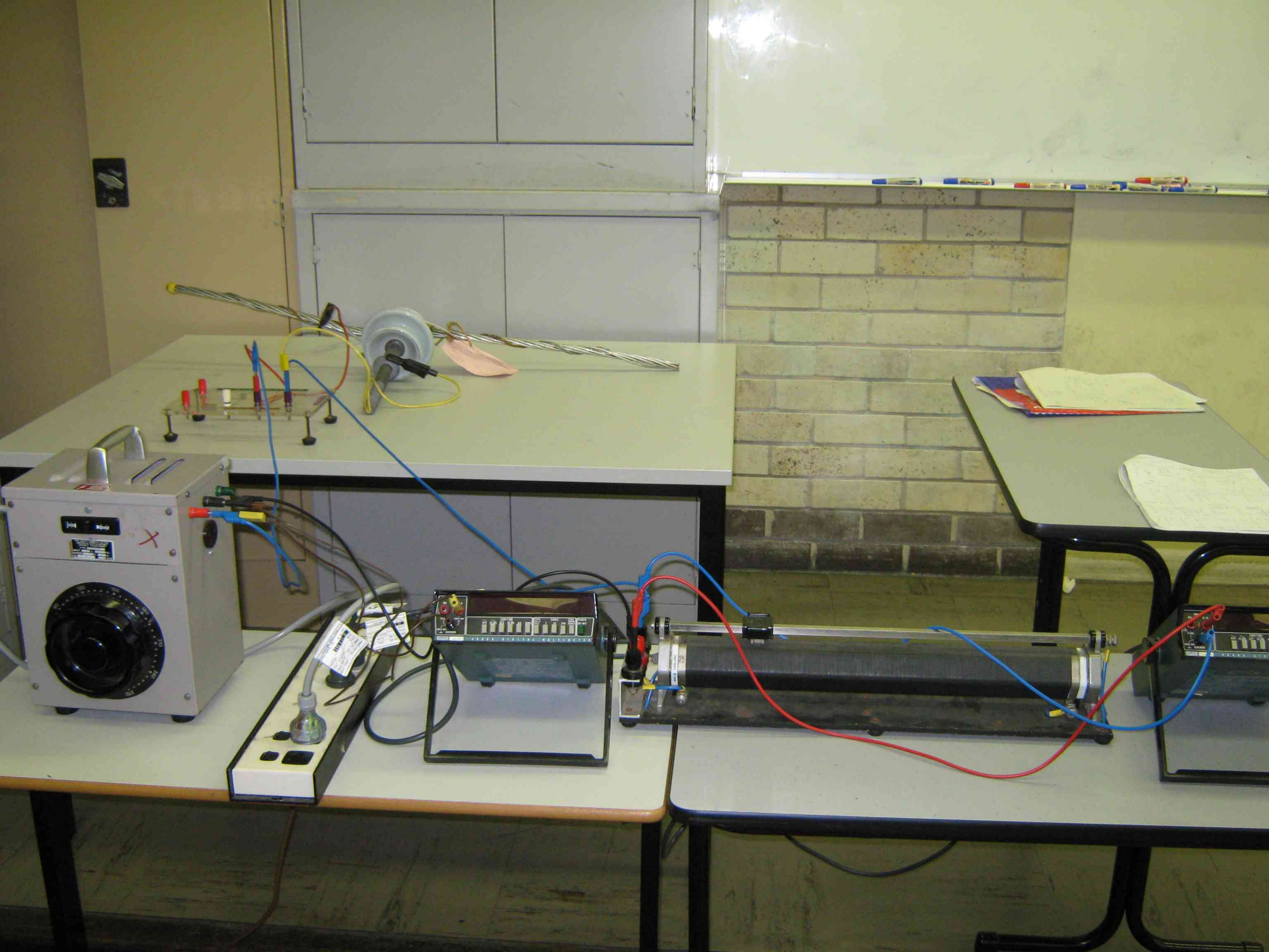(7) THEN SWITCH OFF THE SUPPLY & OBSERVE WHAT HAPPENS TO  $V_1$



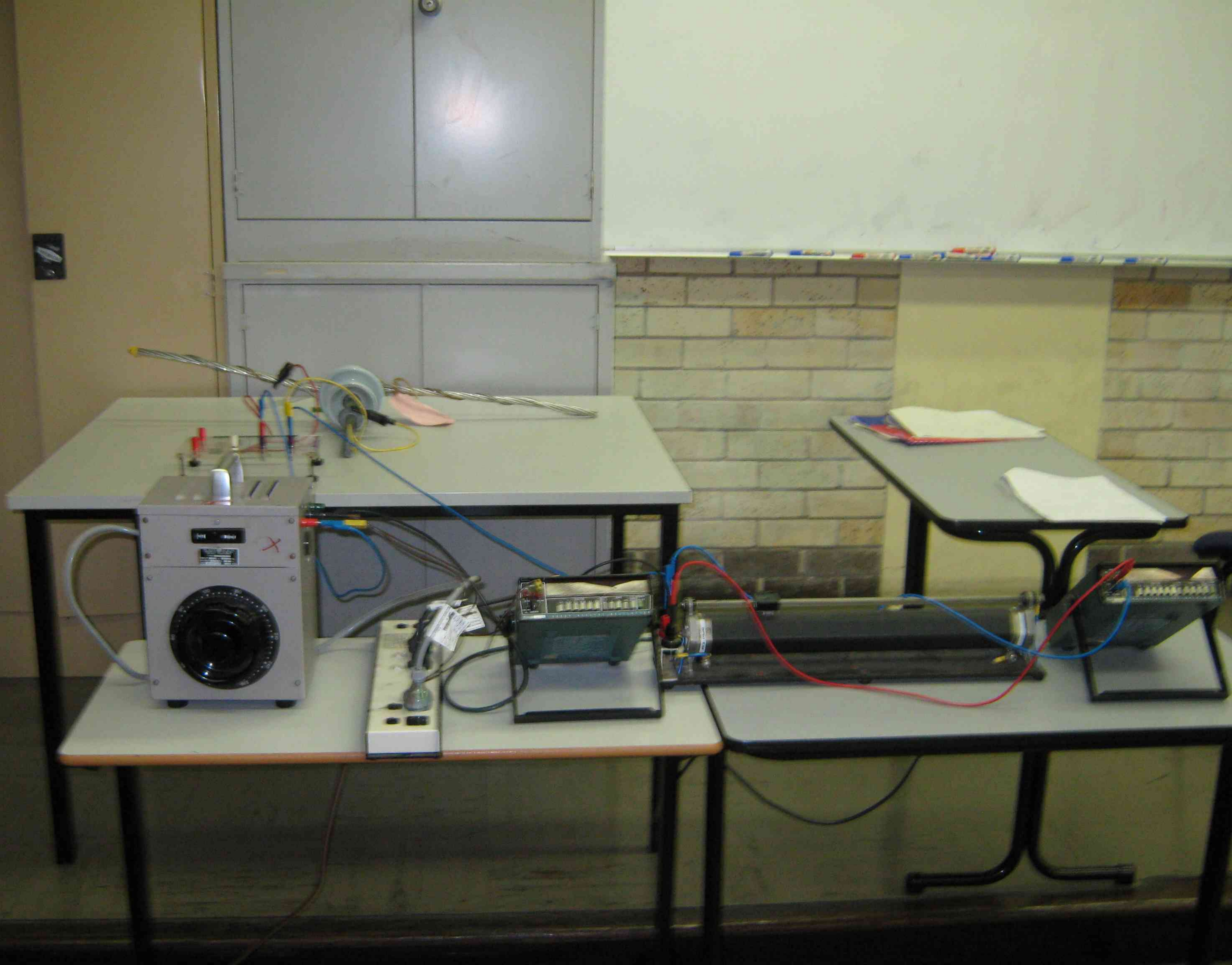


up = 18 chairs desks



# TRANSMISSION LINE PRACTICAL

## ① LINE INSULATOR TEST

(1) CONNECT THE GIVEN CIRCUIT

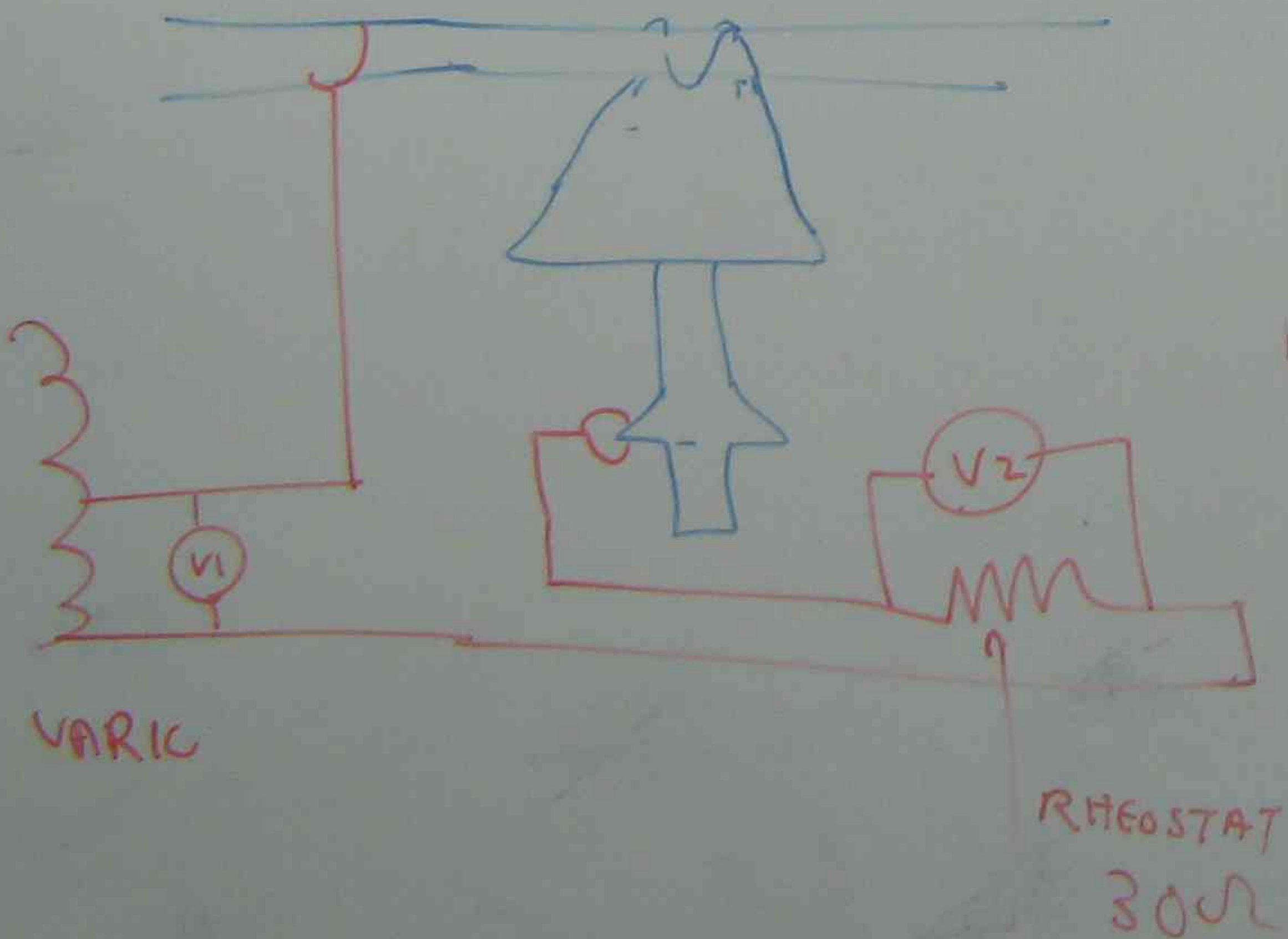

(2) INJECT  $V_1$  80V

(3) MEASURE  $V_2$

(4) CALCULATE  $I = \frac{V_2}{\text{RHEOSTAT RESISTANCE (30}\Omega)}$


$$(5) X_c = \frac{V_1 - V_2}{I}$$

$$(6) C_{80V} = \frac{1}{2\pi f X_c} \quad \text{WHERE } f = 50 \text{ Hz}$$

REPEAT THE ABOVE STEP FOR 90V & 100V

$$C = \frac{C_{80V} + C_{90V} + C_{100V}}{3} \quad \text{F}$$

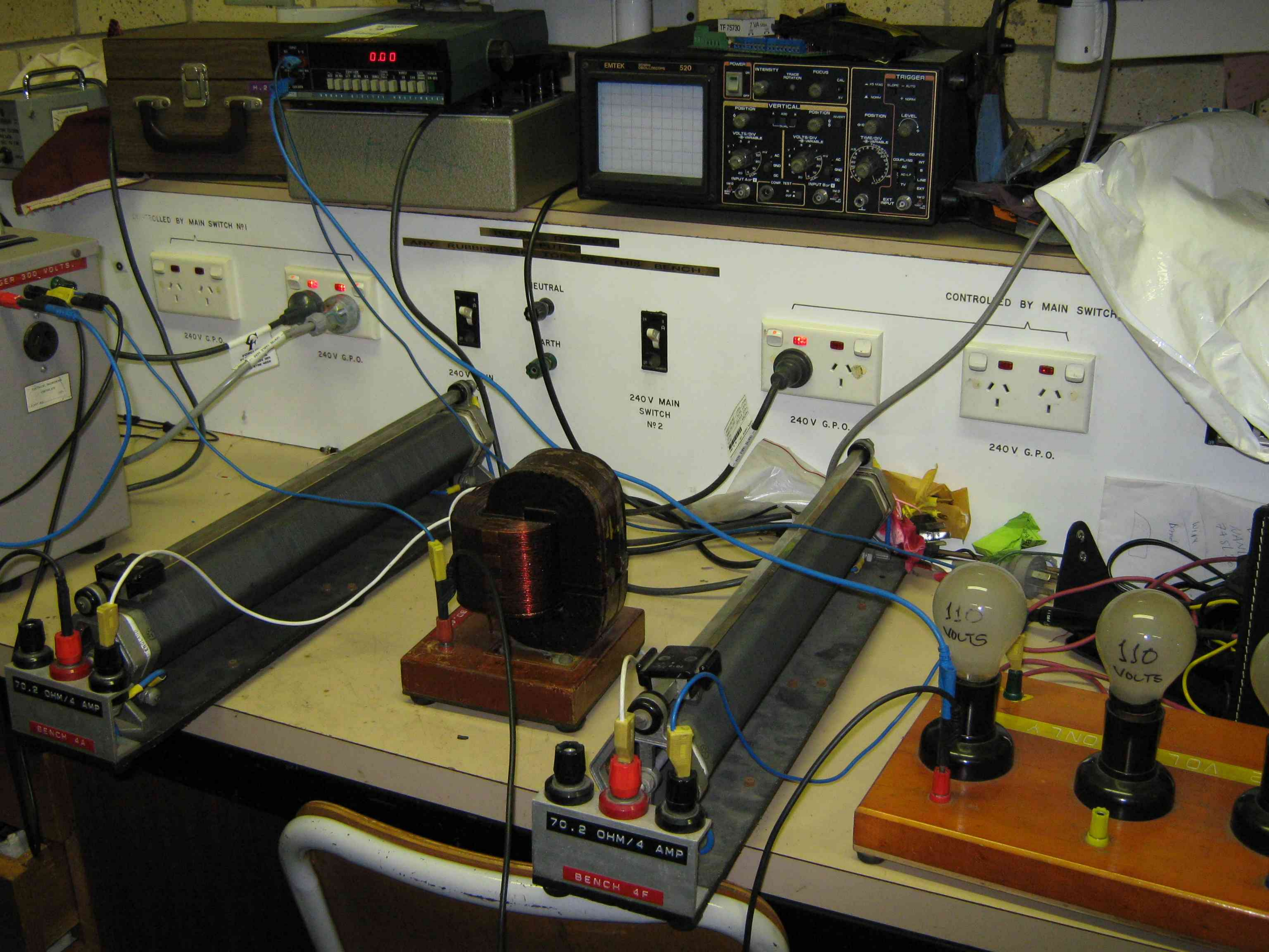(7) THEN SWITCH OFF THE SUPPLY & OBSERVE WHAT HAPPENS TO  $V_1$



0.00

EMTEK 520

CONTROLLED BY MAIN SWITCH N°1

240V G.P.O.

240V G.P.O.

NEUTRAL

EARTH

240V MAIN SWITCH N°2

240V G.P.O.

CONTROLLED BY MAIN SWITCH

240V G.P.O.

70.2 OHM/4 AMP

BENCH 4A

70.2 OHM/4 AMP

BENCH 4F

110 VOLTS

110 VOLTS






SWITCH No 2

AMERICAN  
DATE  
MOB: 0402 12  
FAX: 02 976

FORGL  
ELECTR  
SERVICE  
MOB: 0402 12  
FAX: 02 976

100-500  
11C

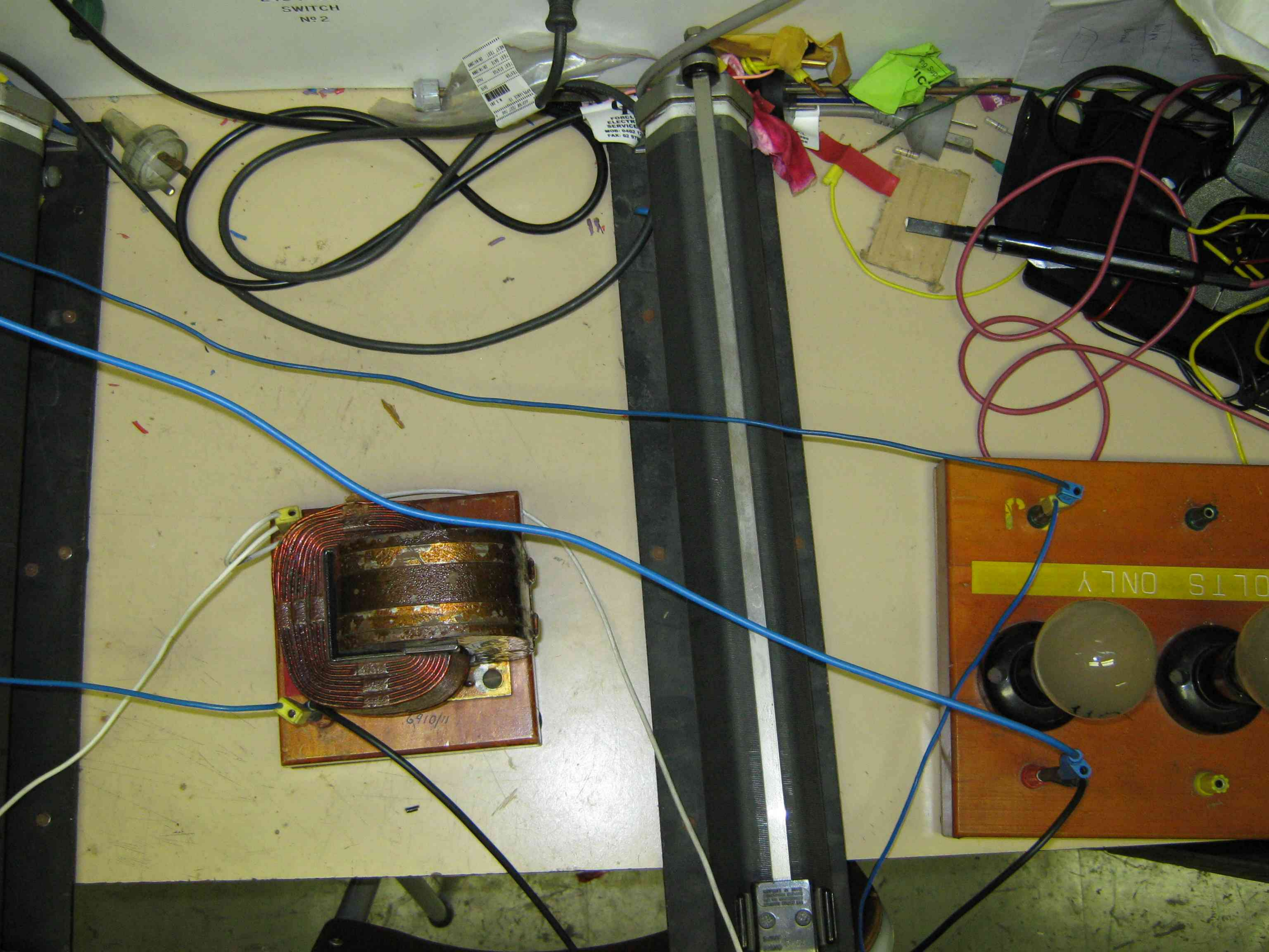



EMTEK 520

POWER INTENSITY TRACE ROTATION FOCUS CAL. TRIGGER

POSITION A POSITION B POSITION C

VOLTS/DIV VARIABLE AC DC

TIME/DIV VARIABLE

LEVEL

SOURCE COUPLING INT. LINE EXT. TV EXT. INPUT

CONTROLLED BY MAIN SWITCH No 1

CONTROLLED BY MAIN SWITCH No 2

NEUTRAL  
EARTH

240V MAIN SWITCH No 2

240V G.P.O.

240V G.P.O.

70.2 OHM/4 AMP

BENCH 4A

70.2 OHM/4 AMP

BENCH 4A

110 VOLTS

DO NOT  
ON TOP OF THIS BENCH

CONTROLLED BY MAIN SWITCH N°1

NEUTRAL  
240 V MAIN SWITCH N°1





240 V MAIN SWITCH N°2

240 V P.O.

240 V G.P.O.

FORCLER ELECTRIC SERVICES  
MOR: 5402 134  
FAX: 02 9798 4

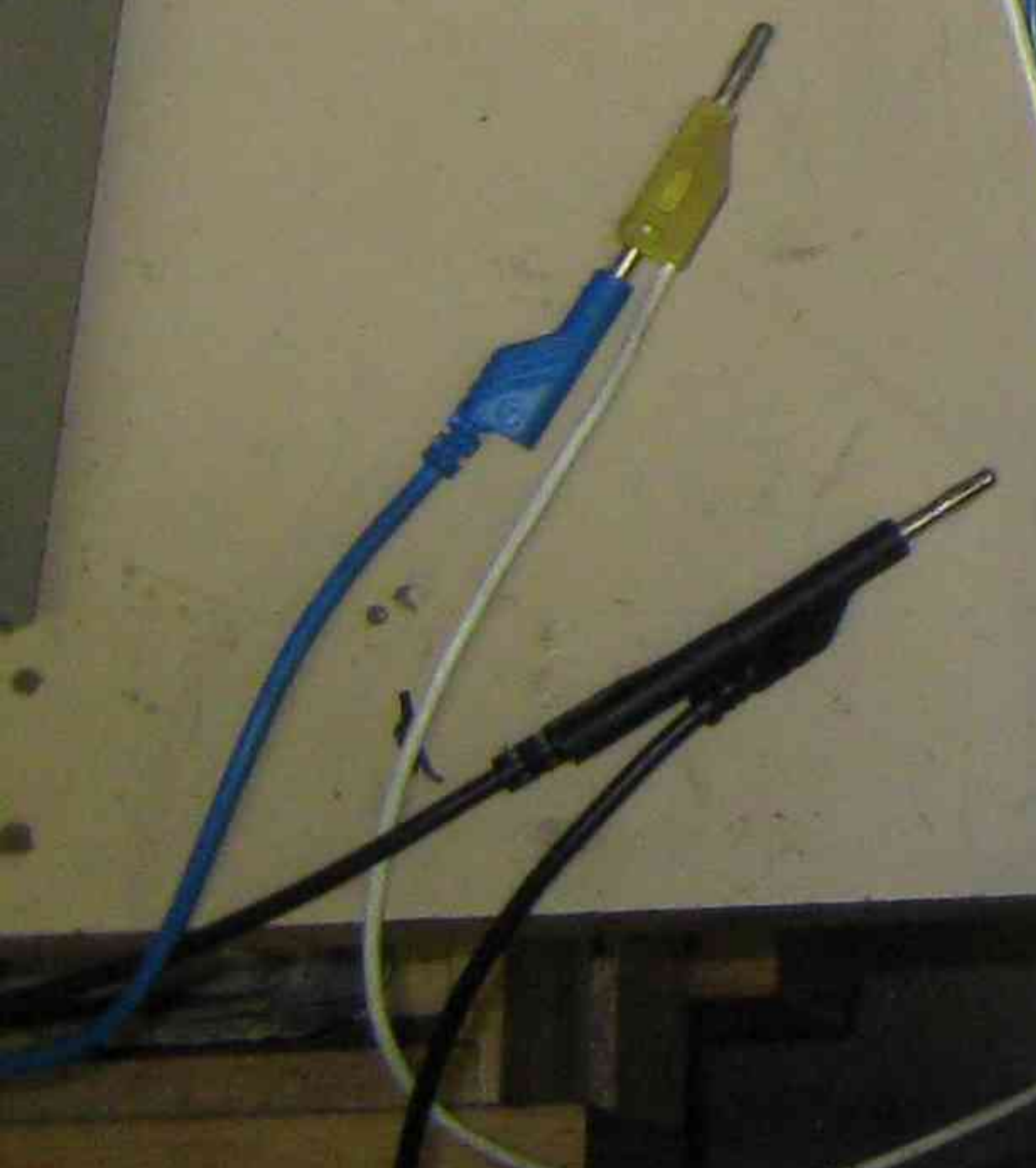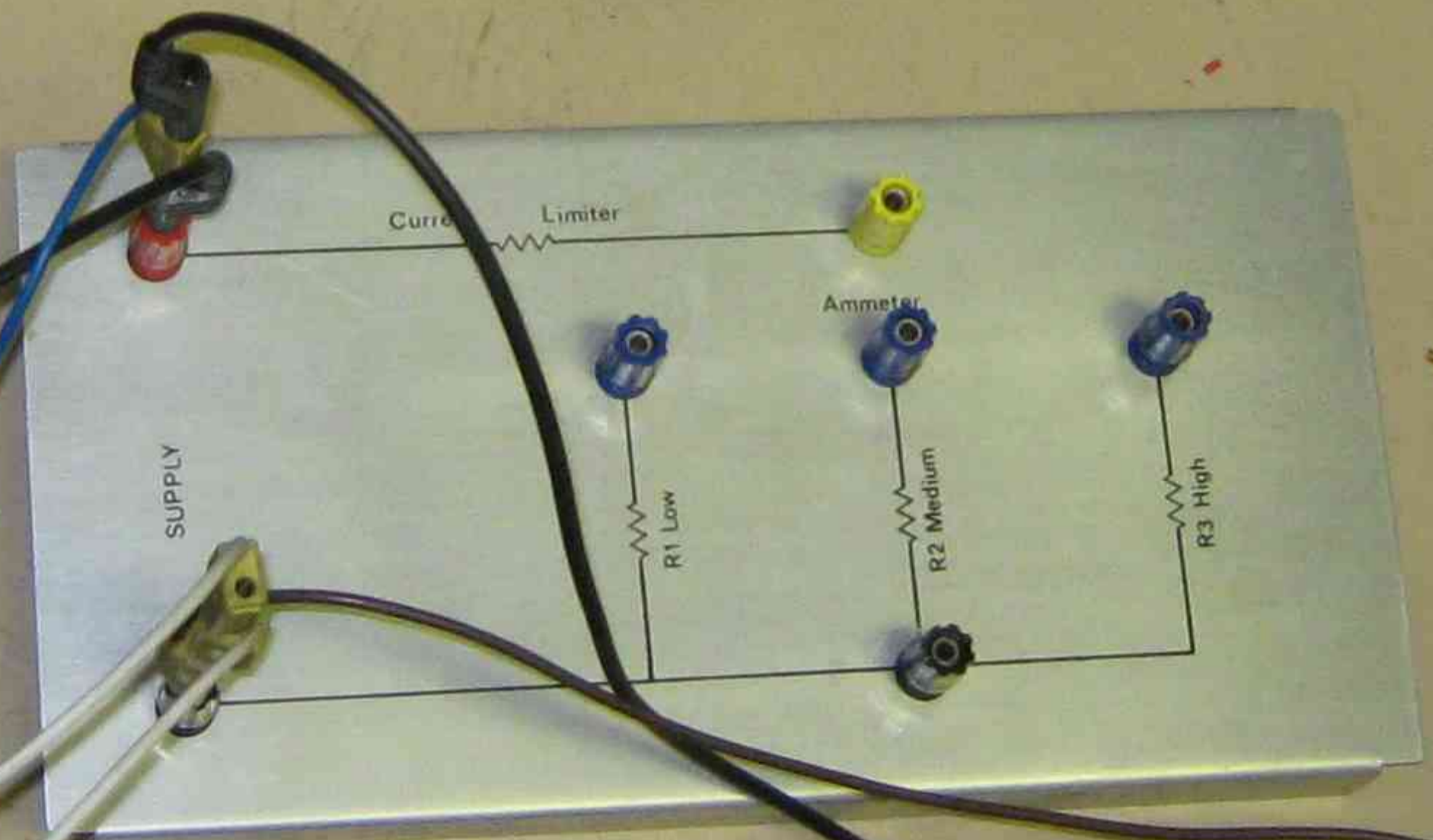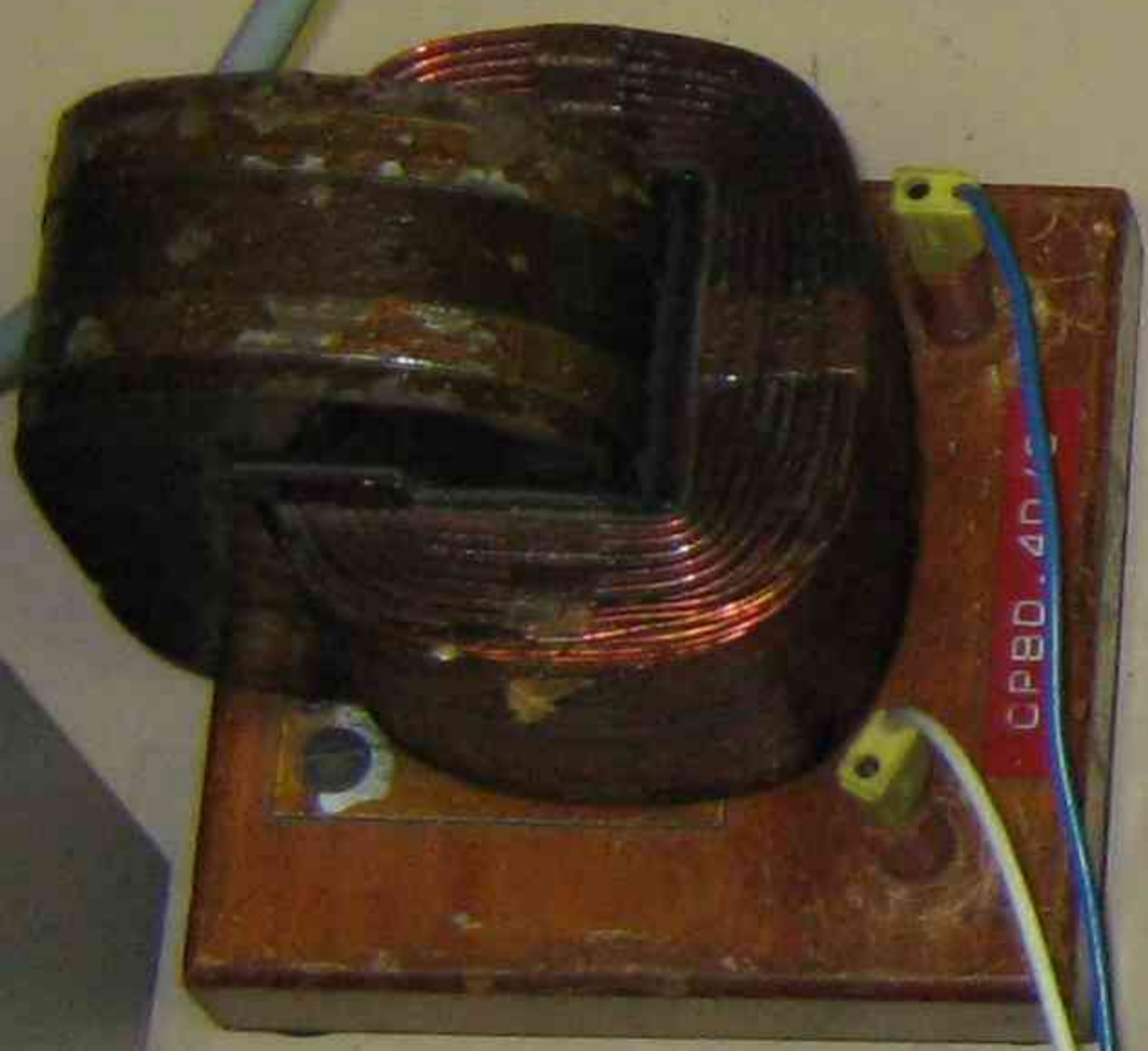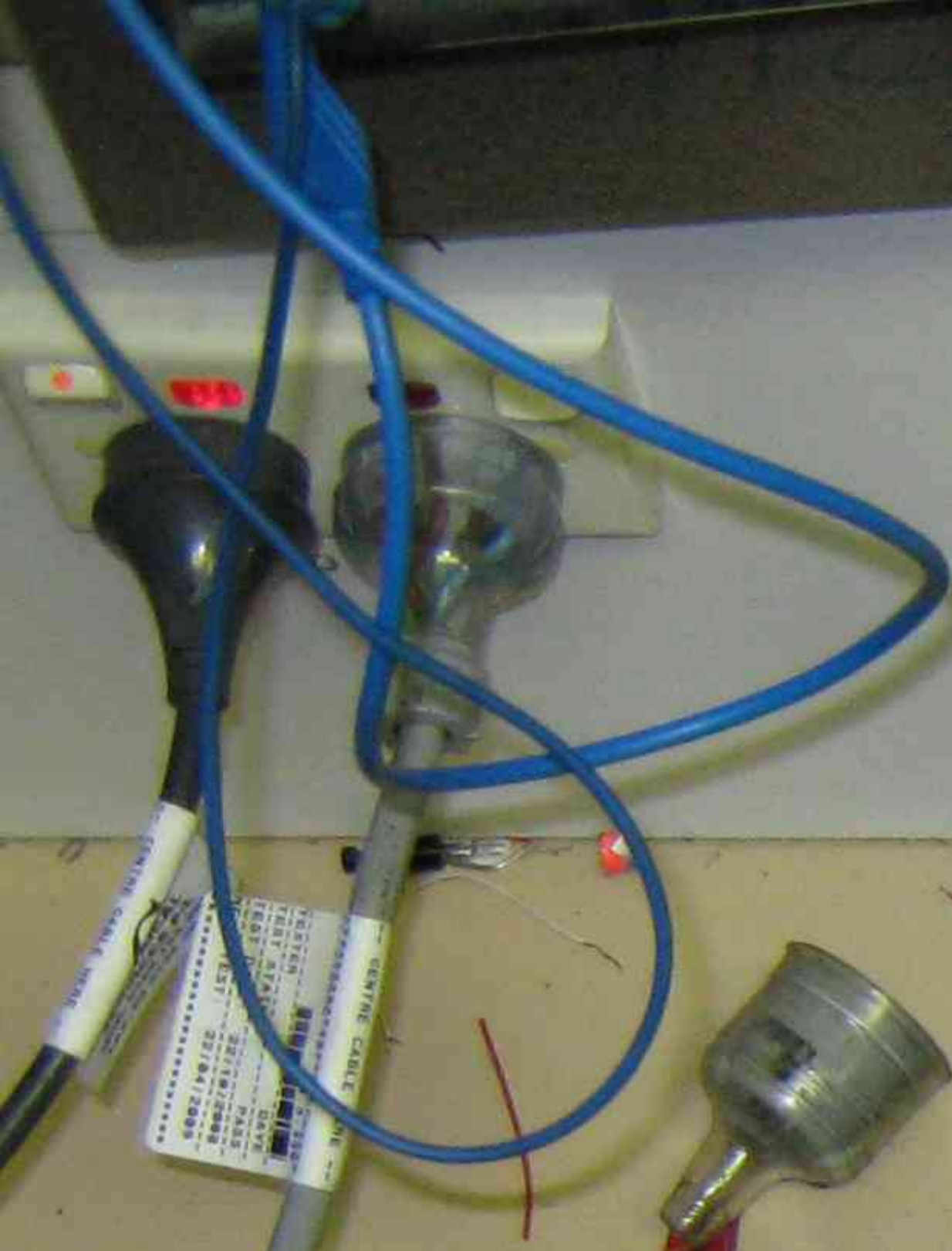FORCLER ELECTRIC SERVICES  
MOR: 5402 134  
FAX: 02 9798 4





CONTROLLED BY MAIN SWITCH No 1

240V G.P.O.

**ISOLATE BEFORE OPENING**


CPBD-40/3

TESTER: DAVE  
TEST STATUS: PASS  
TEST DATE: 20/10/2008  
NEXT TEST: 20/04/2009

H. 1

240V MAIN SWITCH

SUPPLY

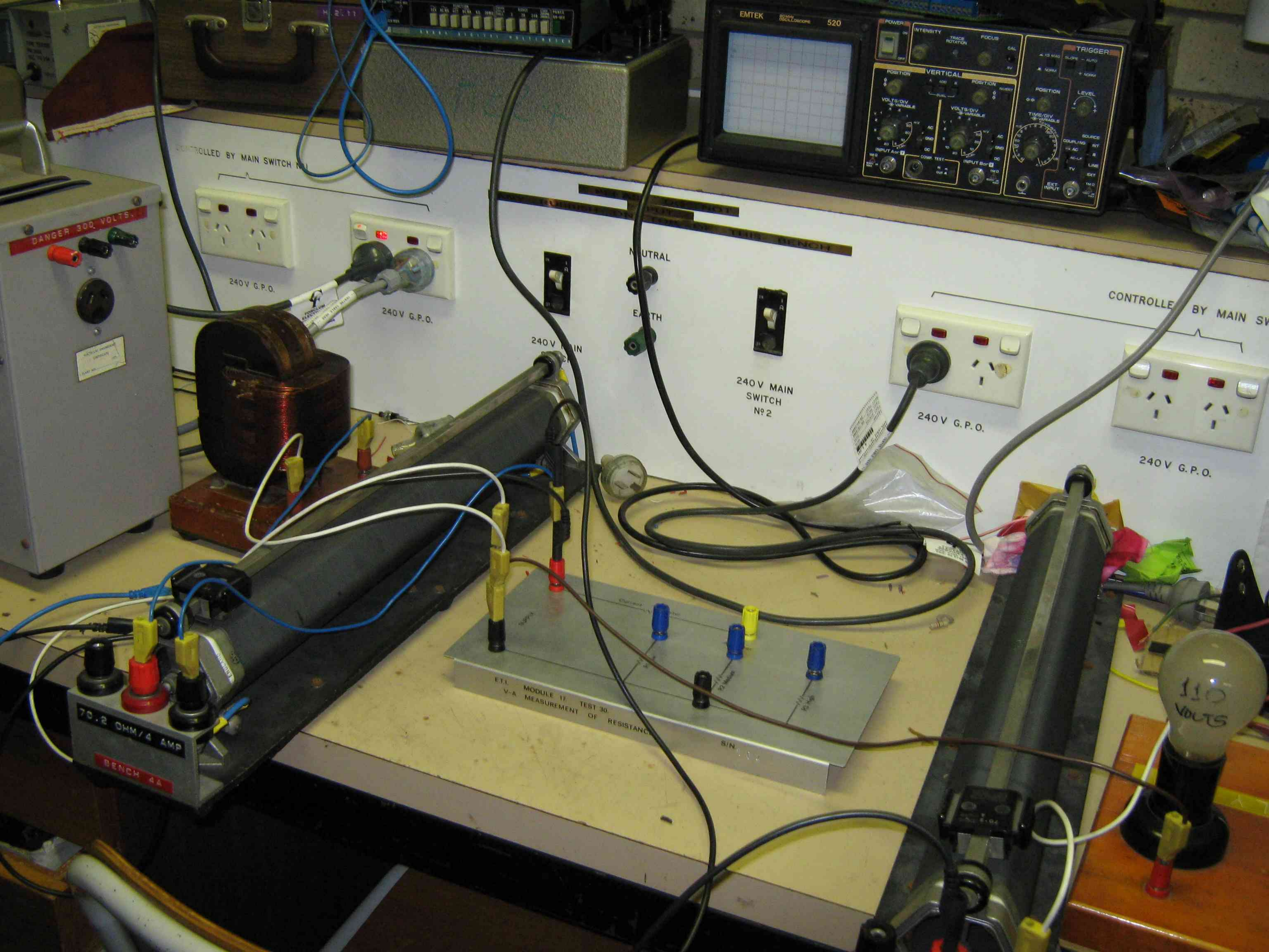

CONTROLLED BY MAIN SWITCH

240V G.P.O.

240V G.P.O.

240V MAIN

NEUTRAL  
EARTH

240V MAIN  
SWITCH  
No 2

240V G.P.O.

CONTROLLED BY MAIN SW

240V G.P.O.

240V G.P.O.

EMTEK  
OSCILLOSCOPE  
520

POWER  
INTENSITY  
TRACE ROTATION  
FOCUS  
CAL.  
3V

POSITION  
VERTICAL  
POSITION  
INVERT

VOLTS/DIV  
VARIABLE

VOLTS/DIV  
VARIABLE

TRIGGER  
SLOPE - AUTO  
NORM  
+ NORM

POSITION  
LEVEL

TIME/DIV  
VARIABLE

COPYING  
SOURCE  
COUPLING  
INT  
AC-DC  
LINE  
EXT  
TV  
EXT INPUT

E.T.I. MODULE 17 TEST 30  
V-A MEASUREMENT OF RESISTANCE

S/N

110  
VOLTS



12.28

1.195

EMTEK 520

DANGER 300 VOLTS.

CONTROLLED BY MAIN SWITCH No 1

240 V G.P.O.

240 V G.P.O.

240 V MAIN

NEUTRAL


EARTH

240 V MAIN SWITCH No 2

240 V G.P.O.

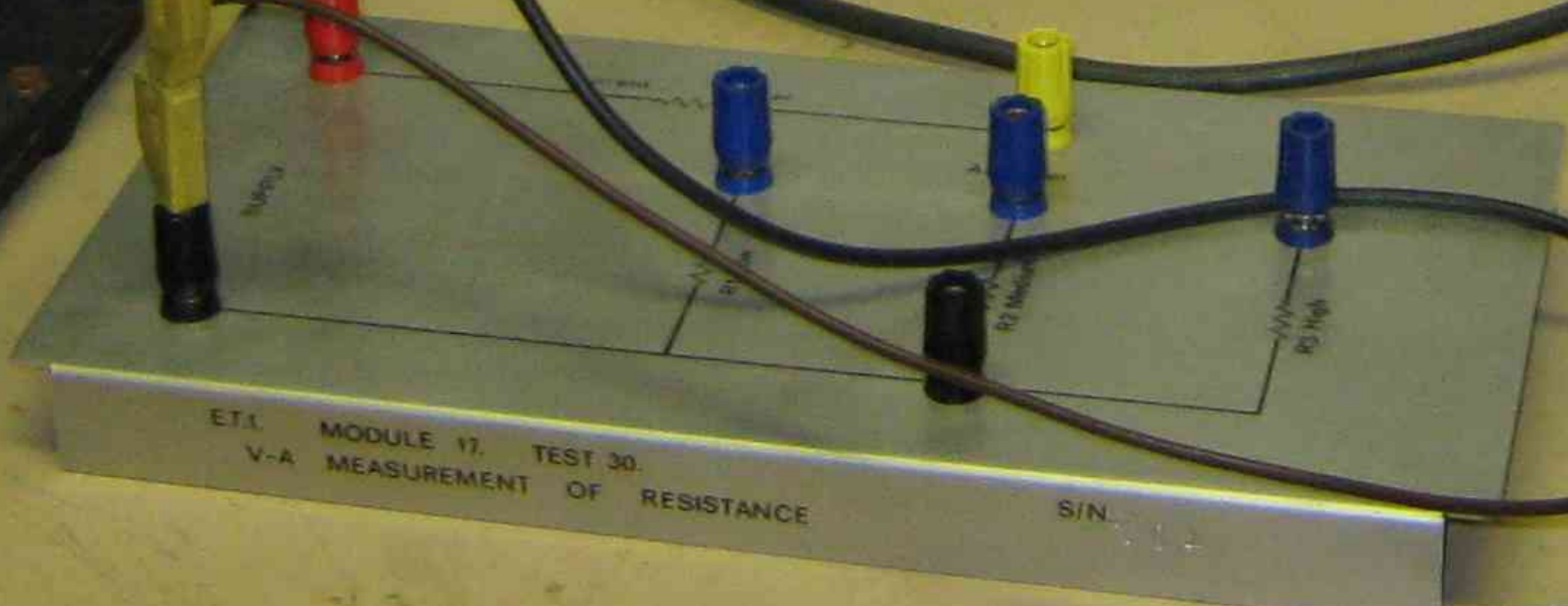70.2 OHM / 4 AMP

MODULE 11 TEST 20 MEASUREMENT OF RESISTANCE



A TNO




# ELECTRICAL DISTRIBUTION

EP 23


Load Centre

(1) Connect the given circuit

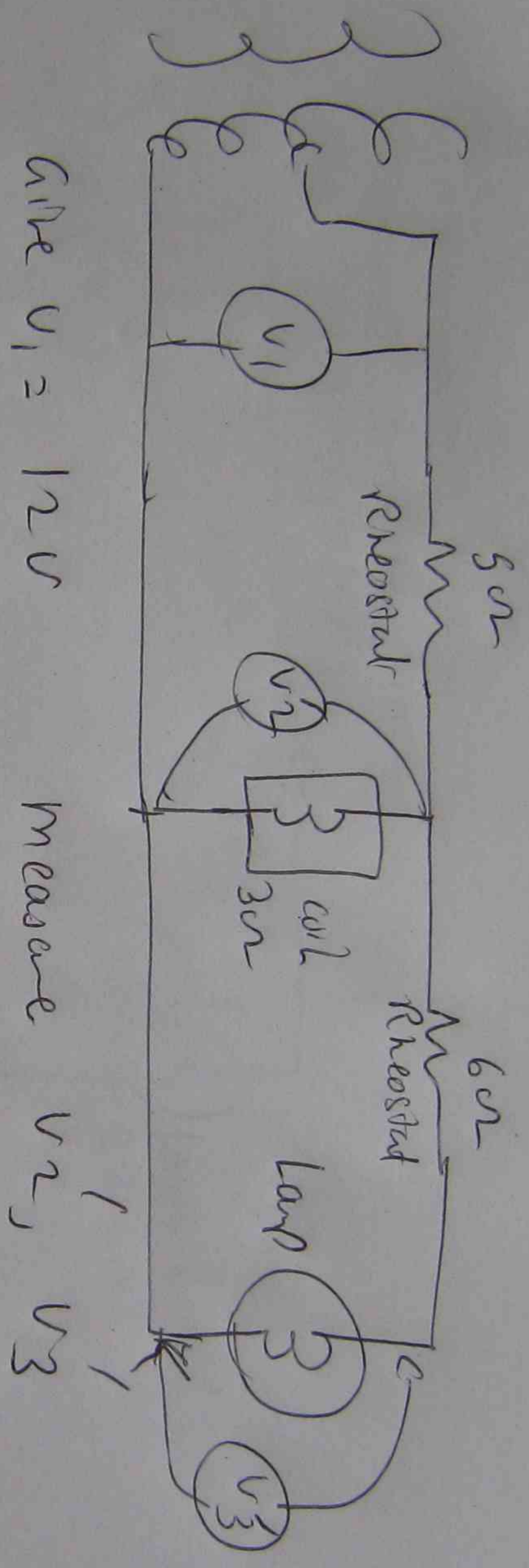

Give  $V_1 = 12V$  measure  $V_2, V_3$

(2) connect the given circuit

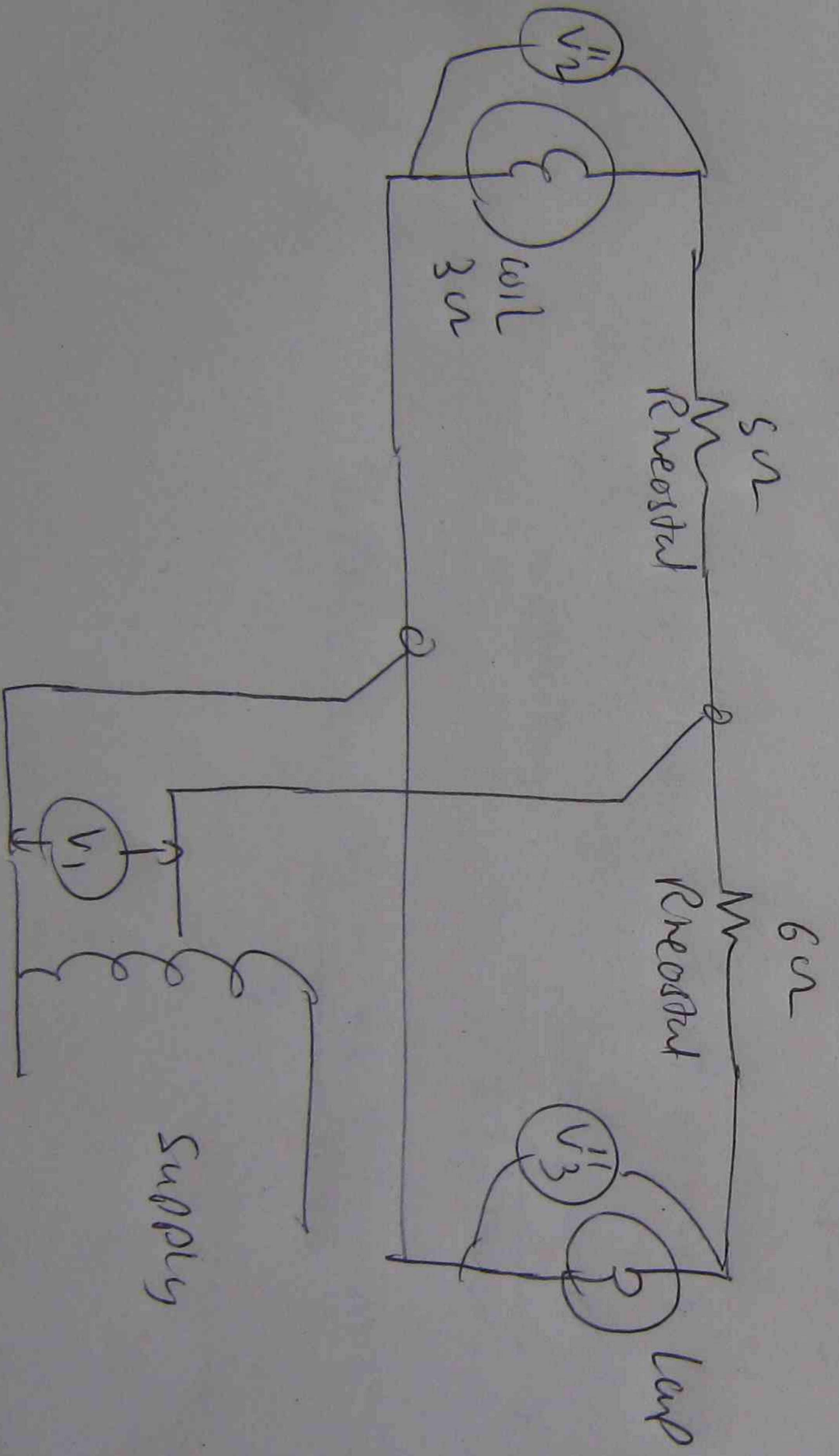


Give  $V_1 = 12V$ , measure  $V_2, V_3$

(3) Compare  $V_2$  &  $V_2'$  &  $V_3$  &  $V_3'$

(4) make comment & find out the reason.

# POWER SYSTEM PROTECTION PRACTICAL (2)


## CURRENT TRANSFORMER RATIO

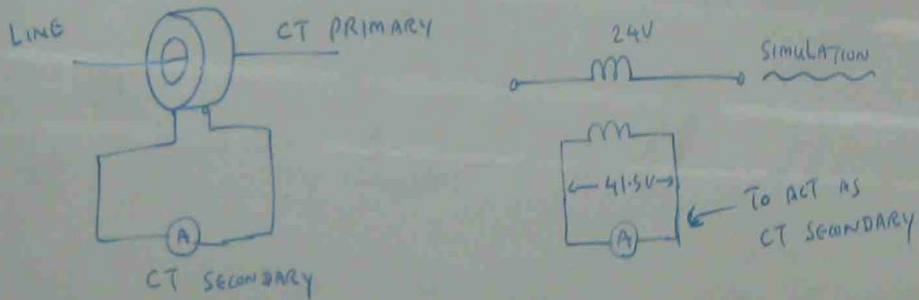

TAKE THE READINGS & FILL IN THE TABLE

$V_1$	$V_2$	$I_1 = \frac{V_2}{10\Omega}$	$V_3$	$I_2 = \frac{V_3}{6\Omega}$	CT RATIO $\frac{I_1}{I_2} = a$
4V					$a_1 =$
5V					$a_2 =$
6V					$a_3 =$
7V					$a_4 =$

CONNECT THE GIVEN CIRCUIT

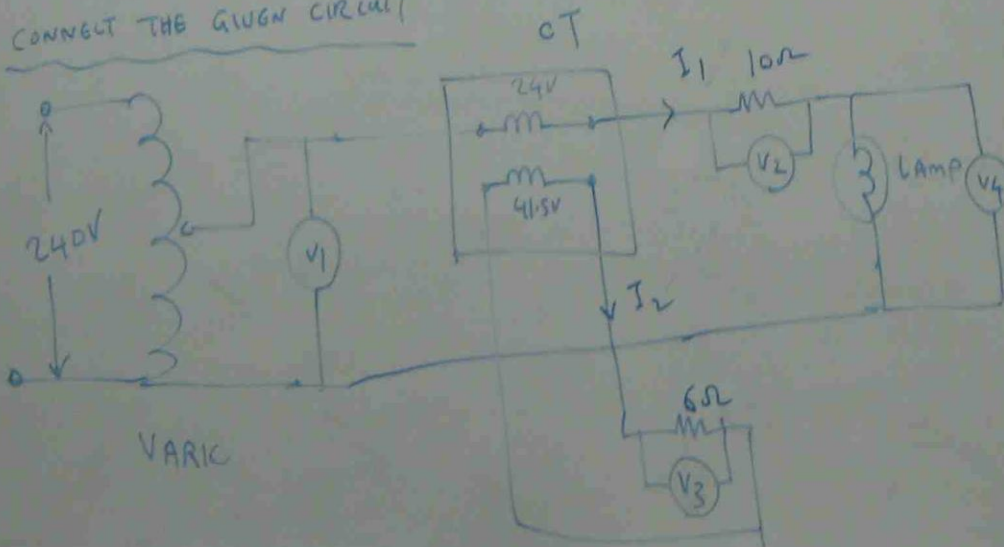

AVERAGE CT RATIO =  $\frac{a_1 + a_2 + a_3 + a_4}{4}$

THEN ADJUST

$$V_3 = 0.3 \text{ V (OR)} \quad I_2 = \frac{0.3}{6} = 0.05 \text{ A}$$

USE CT RATIO AND CALCULATE

PRIMARY CURRENT  $I_1$


$$I_1 = \text{AVERAGE CT RATIO} \times 0.5 \text{ AMP}$$


=


THEN MEASURE  $V_2$  AND FIND

$$I_1 = \frac{V_2}{10 \Omega}$$

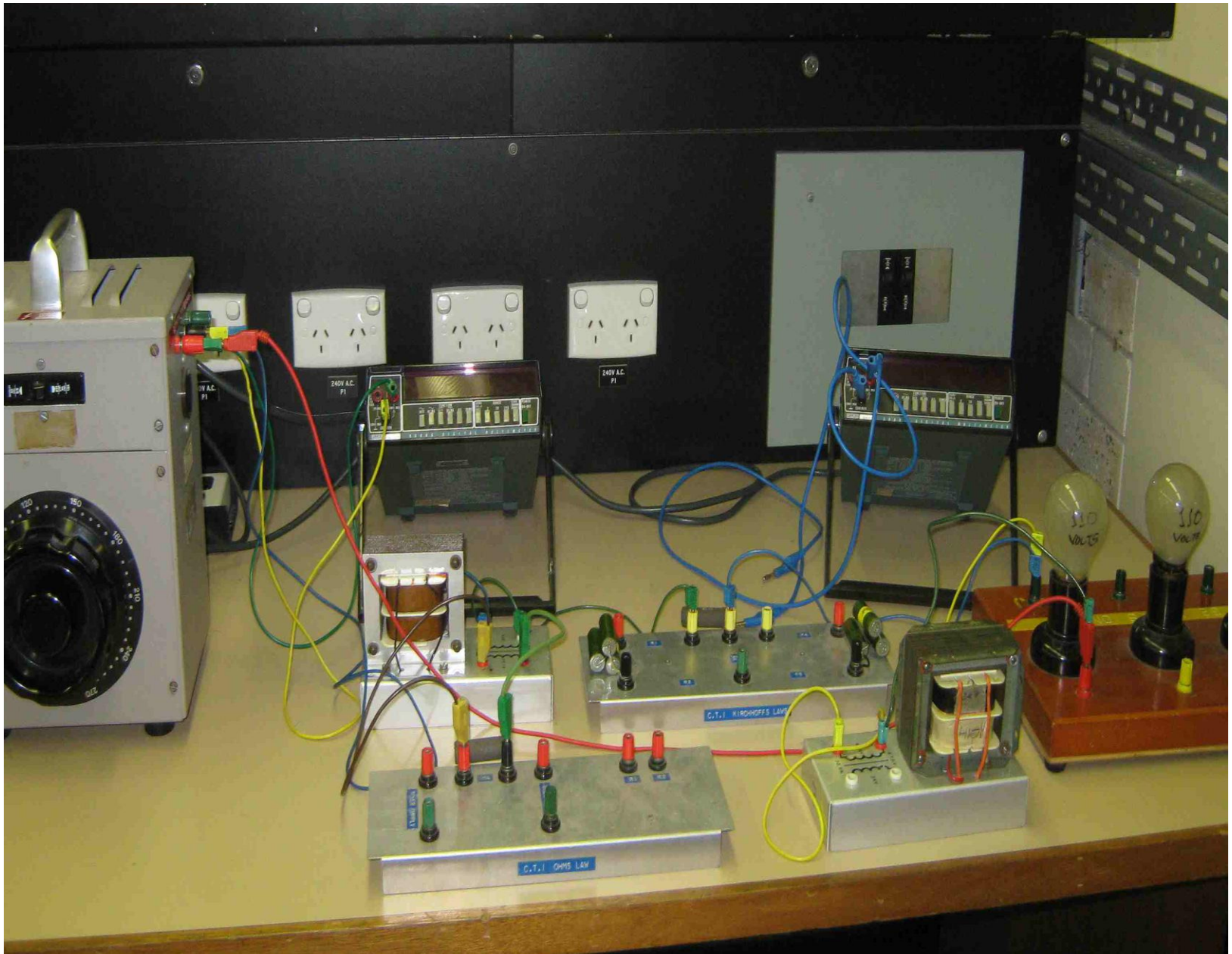COMPARE CALCULATED RESULT AND MEASURED RESULT.



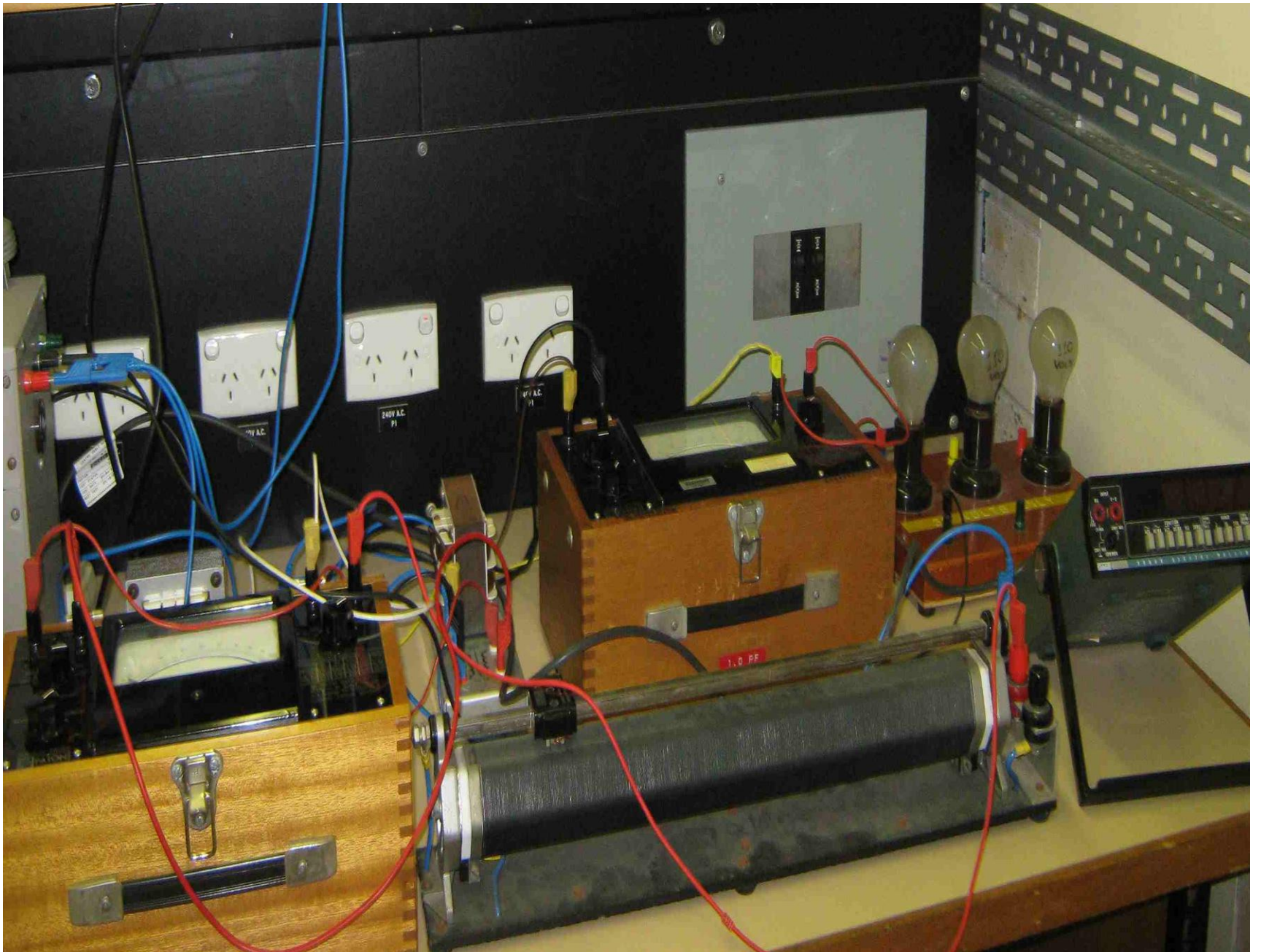

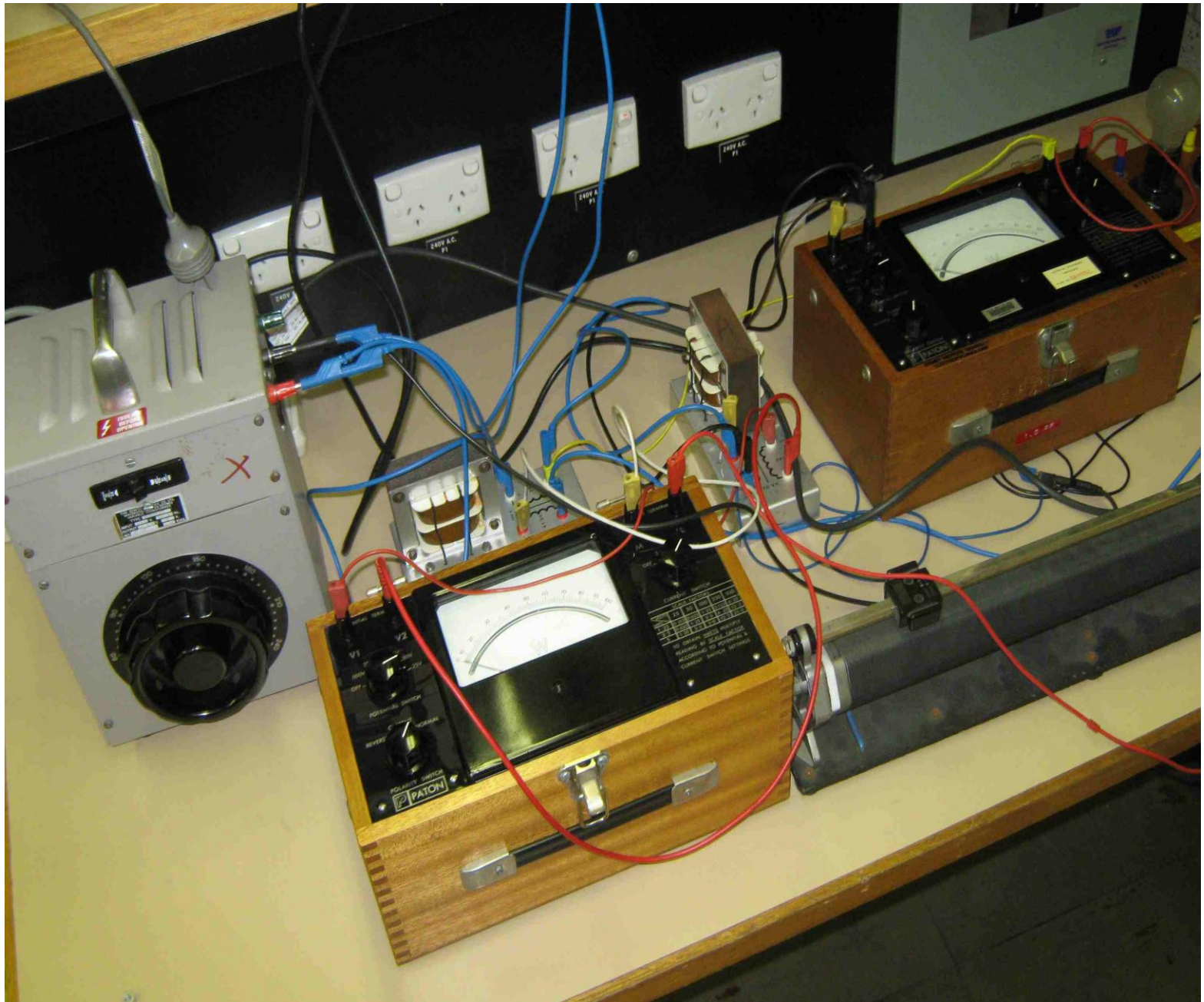












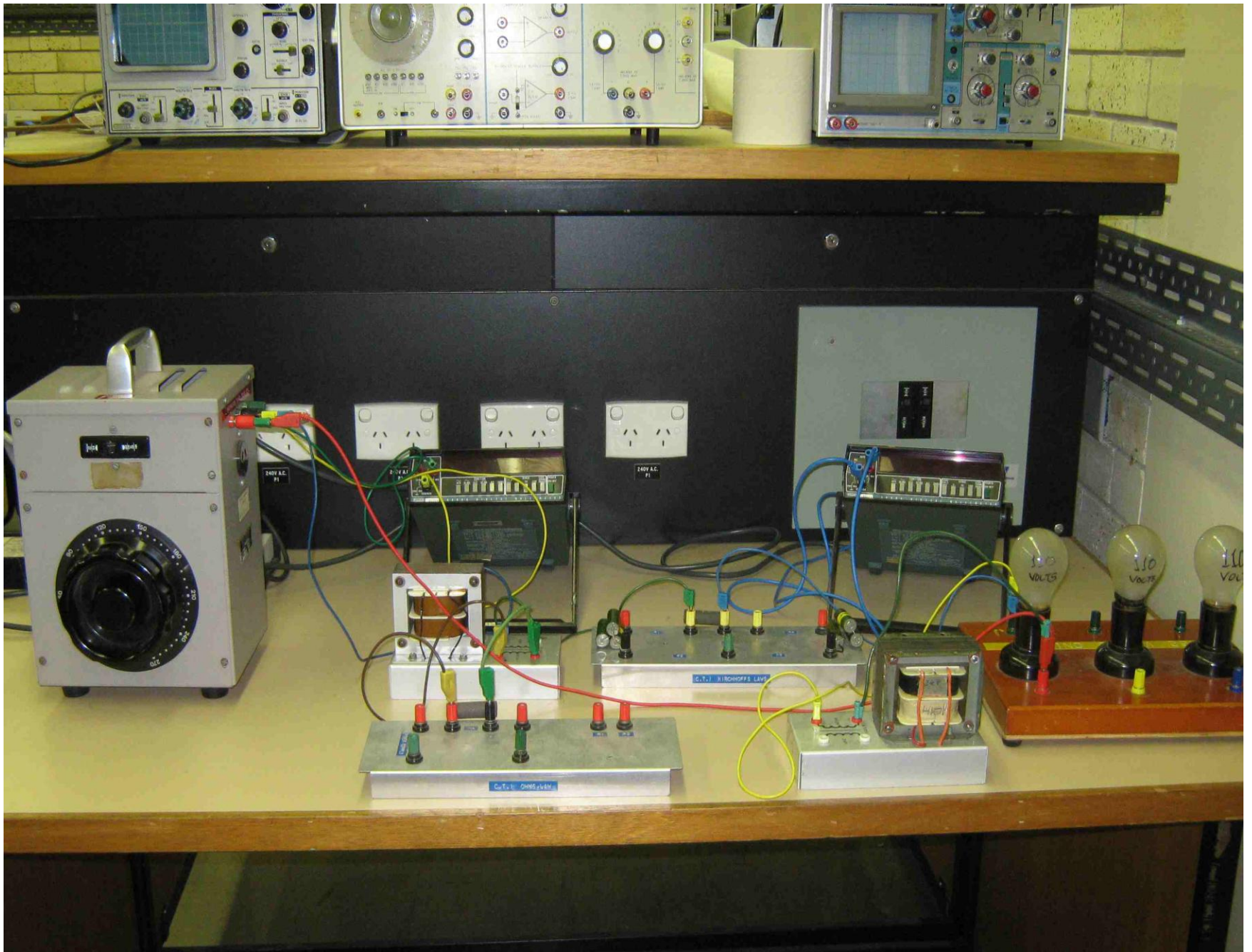



# POWER SYSTEM PROTECTION PRACTICAL (2)


## CURRENT TRANSFORMER RATIO

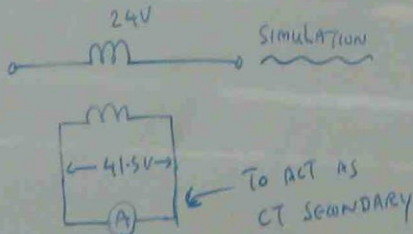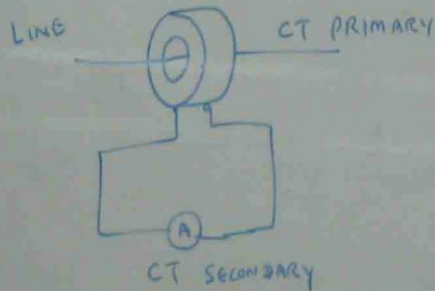

TAKE THE READINGS & FILL IN THE TABLE

$V_1$	$V_2$	$I_1 = \frac{V_2}{10\Omega}$	$V_3$	$I_2 = \frac{V_3}{6\Omega}$	CT RATIO $\frac{I_1}{I_2} = a$
4V					$a_1 =$
5V					$a_2 =$
6V					$a_3 =$
7V					$a_4 =$

CONNECT THE GIVEN CIRCUIT

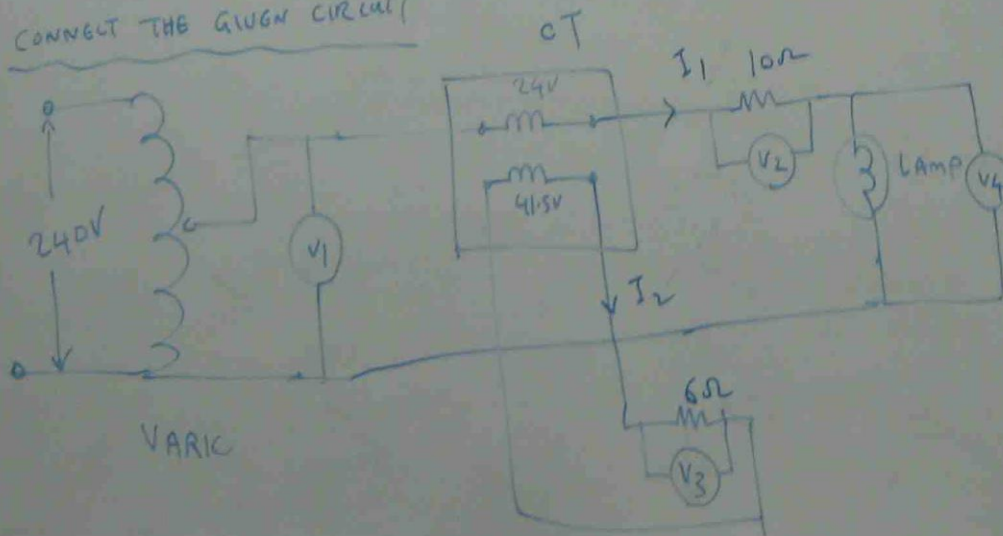

AVERAGE CT RATIO =  $\frac{a_1 + a_2 + a_3 + a_4}{4}$

CT RATIO

$$\frac{I_1}{I_2} = a$$

$$a_1 =$$

$$a_2 =$$

$$a_3 =$$

$$a_4 =$$



THEN ADJUST

$$V_3 = 0.3 \text{ V (OR)} I_2 = \frac{0.3}{6} = 0.05 \text{ A}$$

USE CT RATIO AND CALCULATE

PRIMARY CURRENT  $I_1$


$$I_1 = \text{AVERAGE CT RATIO} \times 0.5 \text{ AMP}$$

=

THEN MEASURE  $V_2$  AND FIND

$$I_1 = \frac{V_2}{10 \Omega}$$

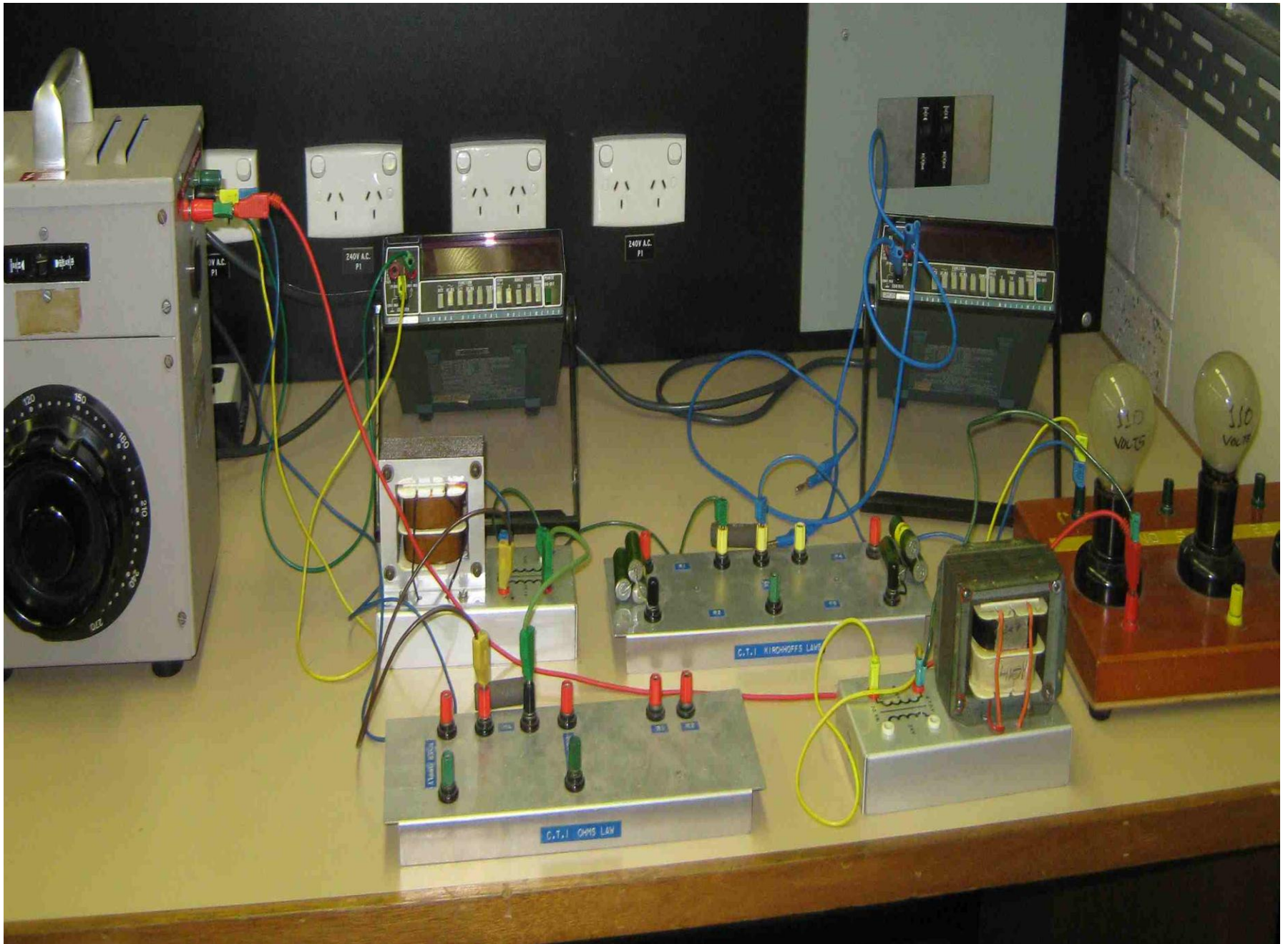COMPARE CALCULATED RESULT AND MEASURED RESULT.





# PROTECTIVE TRANSFORMERS

CT - CURRENT TRANSFORMER } PROTECTIVE TRANSFORMER  
PT - POTENTIAL TRANSFORMER }



PROTECTIVE TRANSFORMERS ARE UTILIZED TO REDUCE THE SYSTEM LEVEL HIGH VOLTAGE AND CURRENT TO RELAY LEVEL / INSTRUMENT LEVEL LOW VOLTAGE AND CURRENT.

## CONNECTION (PT)

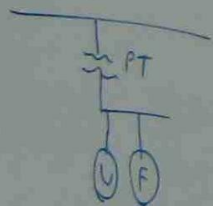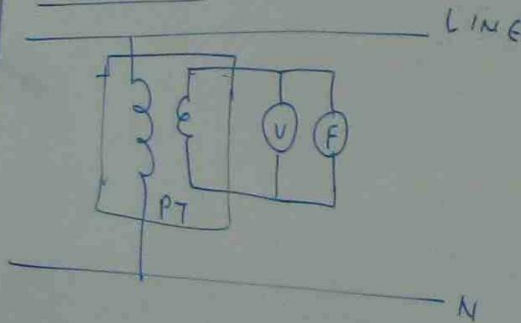



PT REDUCES HIGH VOLTAGE TO LOW VOLTAGE

## LT CONNECTION

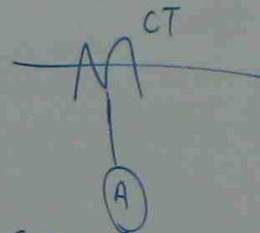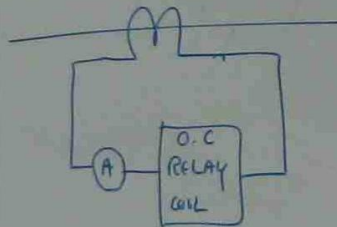

CT - REDUCES HIGH CURRENT TO LOW CURRENT
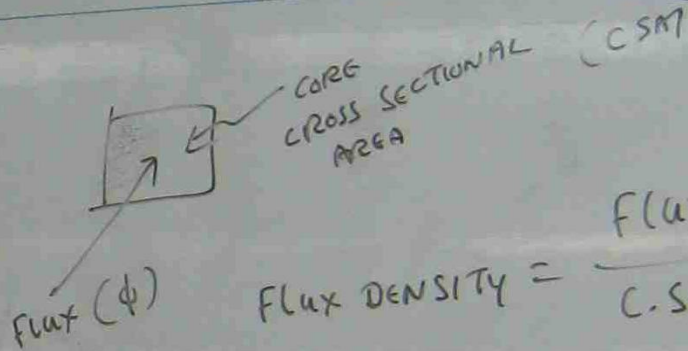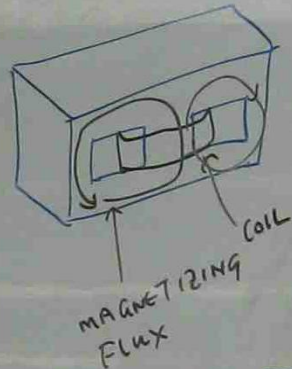
## DIFFERENCE BETWEEN POWER TRANSFORMER & INSTRUMENT TRANSFORMER



$$\text{FLUX DENSITY} = \frac{\text{FLUX}}{\text{C.S.A}} \quad (\text{wb})$$

IN POWER TRANSFORMER, CORE FLUX DENSITY IS CONSTANT REGARDLESS OF THE LOAD.


BUT IN CURRENT TRANSFORMER, CORE FLUX DENSITY DEPENDS ON (1) MAGNITUDE OF PRIMARY CURRENT (2) IMPEDANCE OF SECONDARY CIRCUIT.

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2}$$



# REAL POWER | REACTIVE POWER AND APPARENT POWER

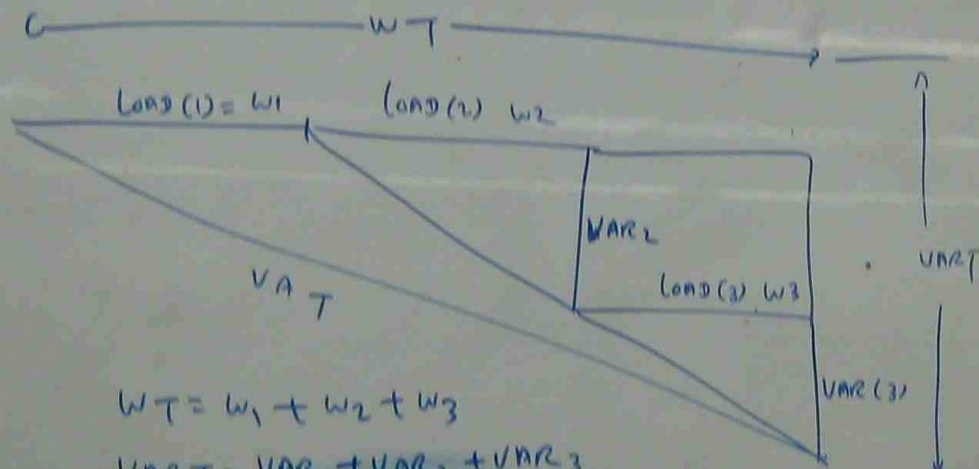INDUSTRIAL LOADS ARE INDUCTIVE LOADS. THAT CAUSES THE LAGGING POWER FACTOR




$$W_T = W_1 + W_2 + W_3$$

$$VAR_T = VAR_1 + VAR_2 + VAR_3$$

$$V_{A_T} = \sqrt{W_T^2 + VAR_T^2}$$

$$P.F._T = \frac{W_T}{V_{A_T}}$$

CONNECT THE GIVEN CIRCUIT

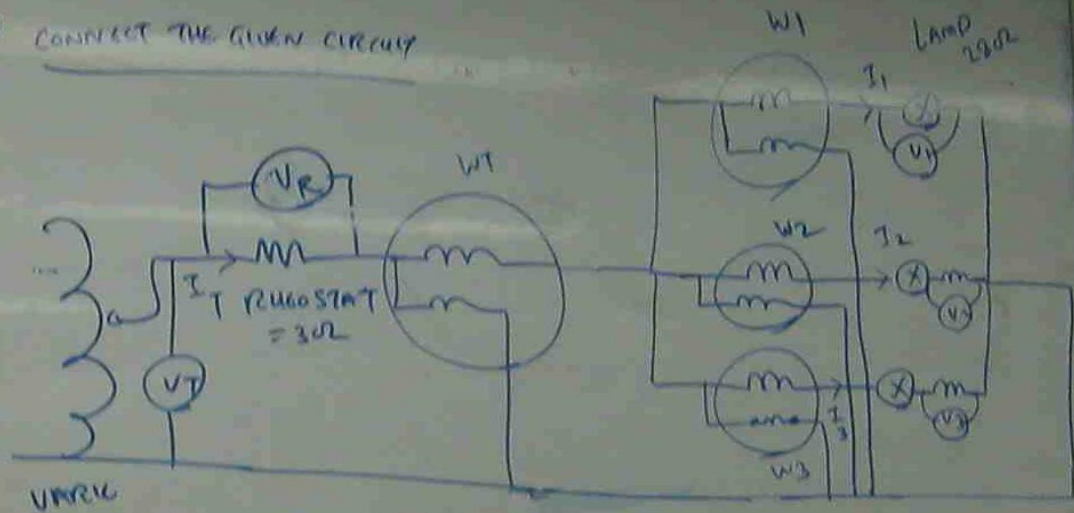

CONNECT THE GIVEN CIRCUIT

IN JECT VOLTAGE

TAKE THE READINGS OF

$V_T, V_R, W_T, W_1, W_2, W_3, V_1, V_2, V_3$

FILL IN TABLE

$V_T$	$V_R$	$I_T = \frac{V_0}{Z_T}$	$W_T$	$V_{AT} = V_T I_T$	$V_{AR} = I_T^2 R$	$W_1$	$V_1$	$I_1 = \frac{V_1}{Z_{01}}$	$V_{A1} = V_1 I_1$	$V_{AR1} = \sqrt{V_{A1}^2 - W_1^2}$	$\theta_1 = \tan^{-1} \frac{V_{AR1}}{W_1}$	$PF_1 = \cos \theta_1$
							$W_2$	$I_2 = \frac{V_2}{Z_{02}}$	$V_{A2} = V_2 I_2$	$V_{AR2} = \sqrt{V_{A2}^2 - W_2^2}$	$\theta_2 = \tan^{-1} \frac{V_{AR2}}{W_2}$	$PF_2 = \cos \theta_2$
							$W_3$	$I_3 = \frac{V_3}{Z_{03}}$	$V_{A3} = V_3 I_3$	$V_{AR3} = \sqrt{V_{A3}^2 - W_3^2}$	$\theta_3 = \tan^{-1} \frac{V_{AR3}}{W_3}$	$PF_3 = \cos \theta_3$

Then plot the power triangle


① ALL INDUCTANCES ARE SET TO ZERO AND TAKE THE READINGS AND FIL IN TABLE AGAIN


② COMPARE ORIGINAL  $W_T$  WITH  $W_T$  WHEN INDUCTANCES ARE ZERO.


\_\_\_\_\_  $V_{AR}$  WITH  $V_{AR}$  \_\_\_\_\_

\_\_\_\_\_  $V_{AT}$  WITH  $V_{AT}$  \_\_\_\_\_

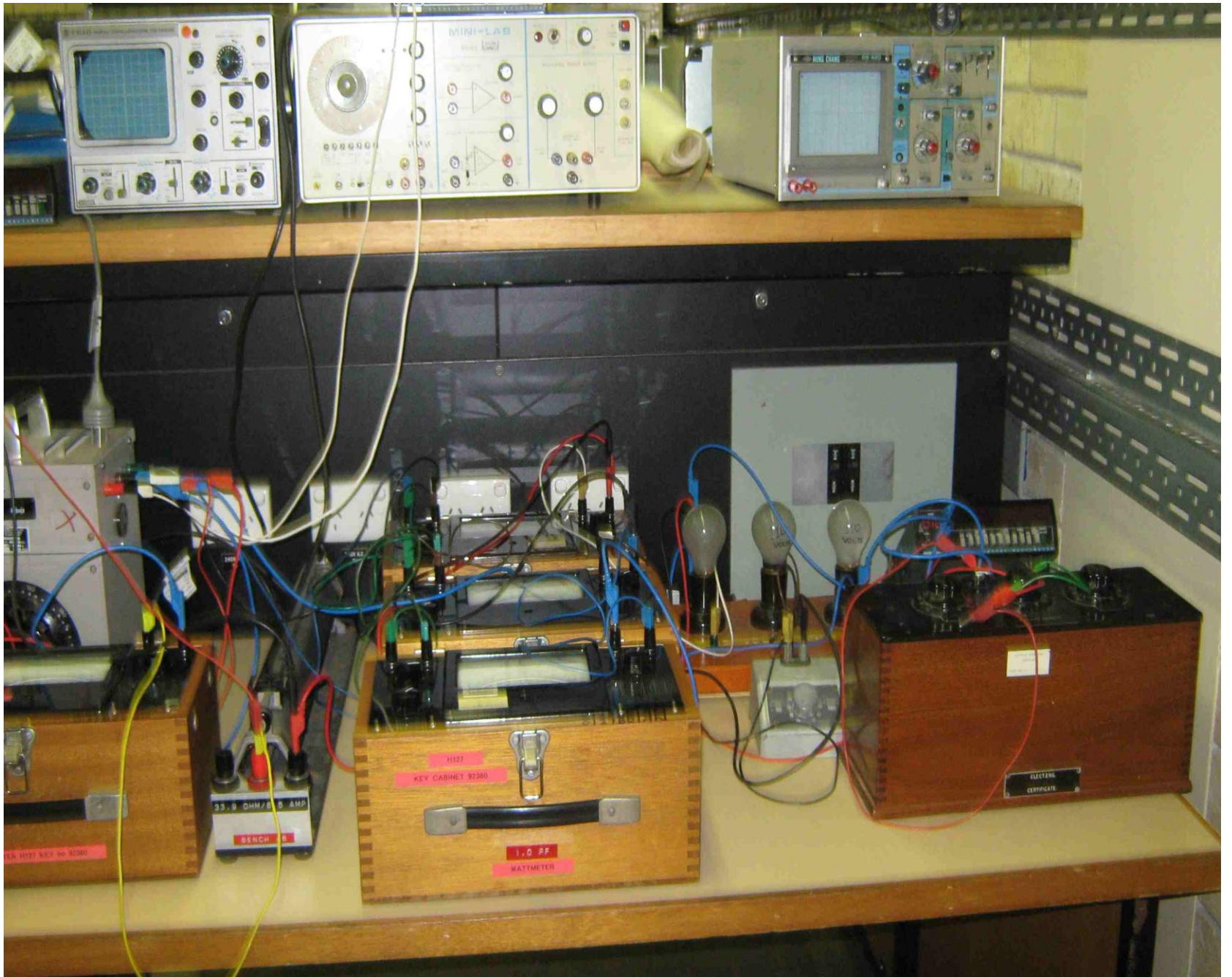\_\_\_\_\_ POWER FACTOR WITH POWER FACTOR \_\_\_\_\_



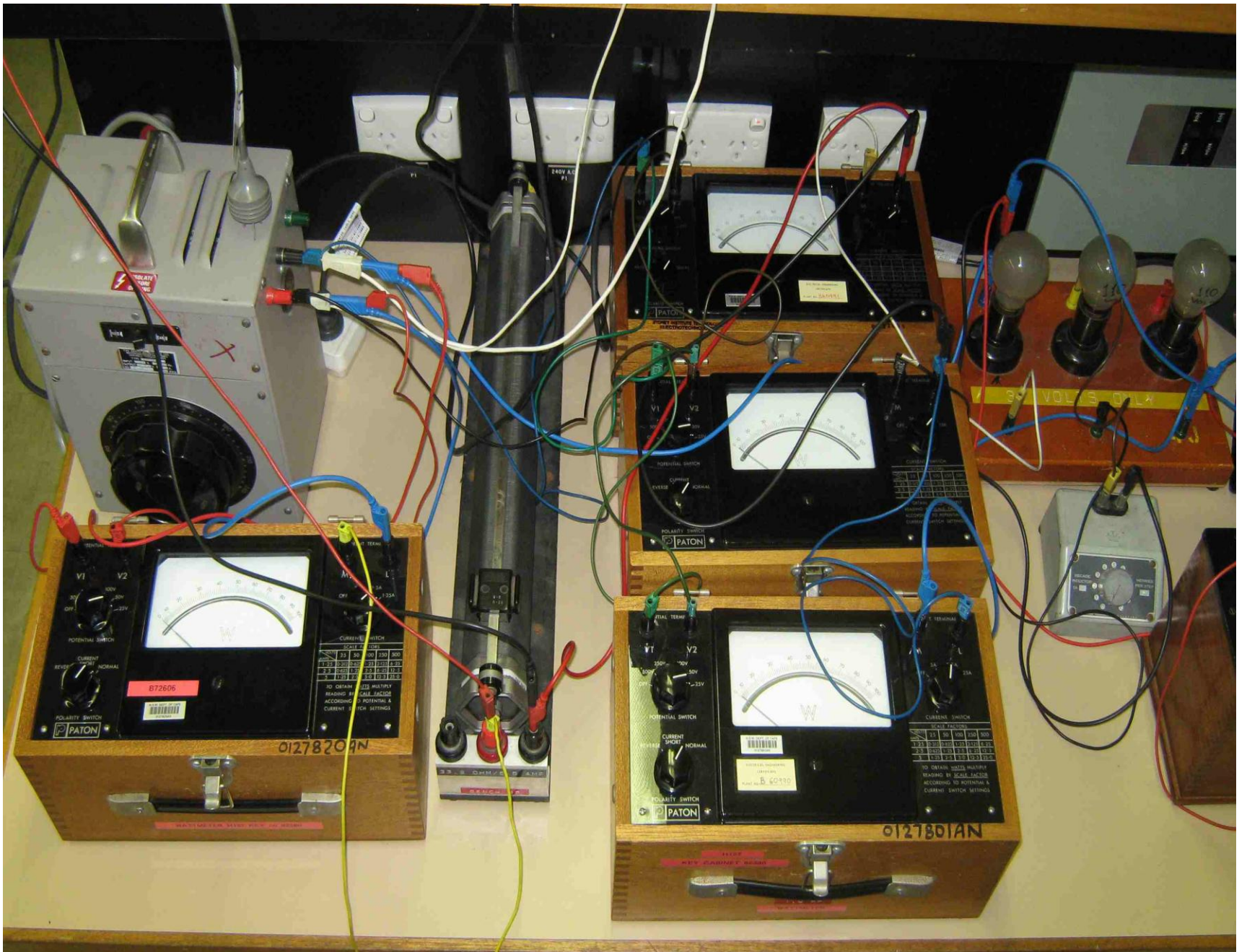

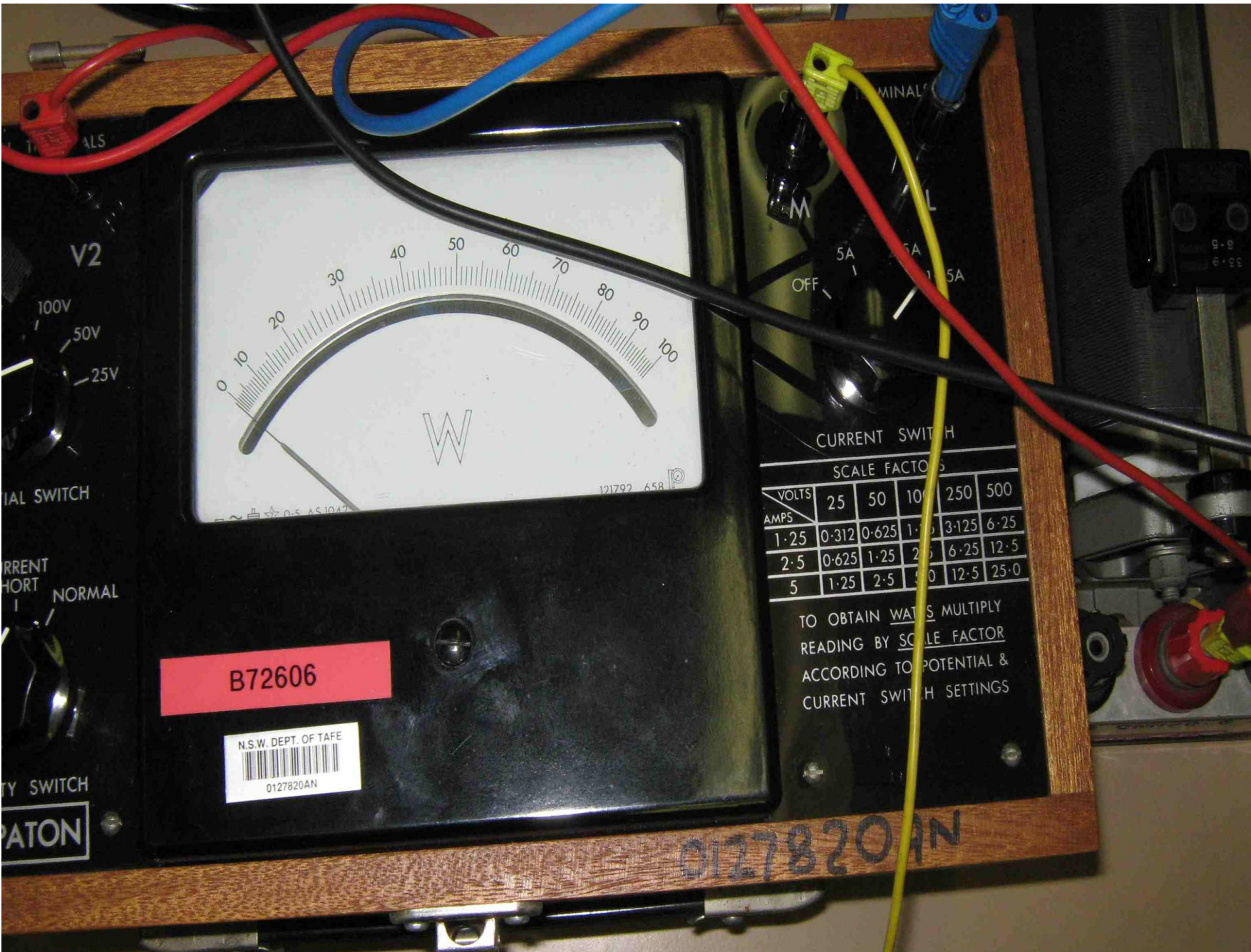

B72606

N.S.W. DEPT. OF TAFE  
0127820AN

CURRENT SWITCH

SCALE FACTORS	
VOLTS	25 50 100 250 500
AMPS	
1.25	0.312 0.625 1.25 3.125 6.25
2.5	0.625 1.25 2.5 6.25 12.5
5	1.25 2.5 5 12.5 25.0

TO OBTAIN WATTS MULTIPLY READING BY SCALE FACTOR ACCORDING TO POTENTIAL & CURRENT SWITCH SETTINGS

0127820AN



POTENTIAL TERMINALS

V1

V2

500V 250V 100V 50V 25V  
OFF

POTENTIAL SWITCH

REVERSE CURRENT SHORT NORMAL

POLARITY SWITCH

**P** PATON



N.S.W. DEPT OF TAPE  
0127801AN

ELECTRICAL ENGINEERING  
CERTIFICATE  
B 60990  
PLANT NO. B 60990

CURRENT SWITCH


M L  
OFF 5A 2.5A 1.25A

CURRENT SWITCH


VOLTS AMPS	SCALE FACTORS				
	25	50	100	250	500
1.25	0.312	0.625	1.25	3.125	6.25
2.5	0.625	1.25	2.5	6.25	12.5
5	1.25	2.5	5.0	12.5	25.0


TO OBTAIN WATTS MULTIPLY  
READING BY SCALE FACTOR  
ACCORDING TO POTENTIAL &  
CURRENT SWITCH SETTINGS


0127801AN

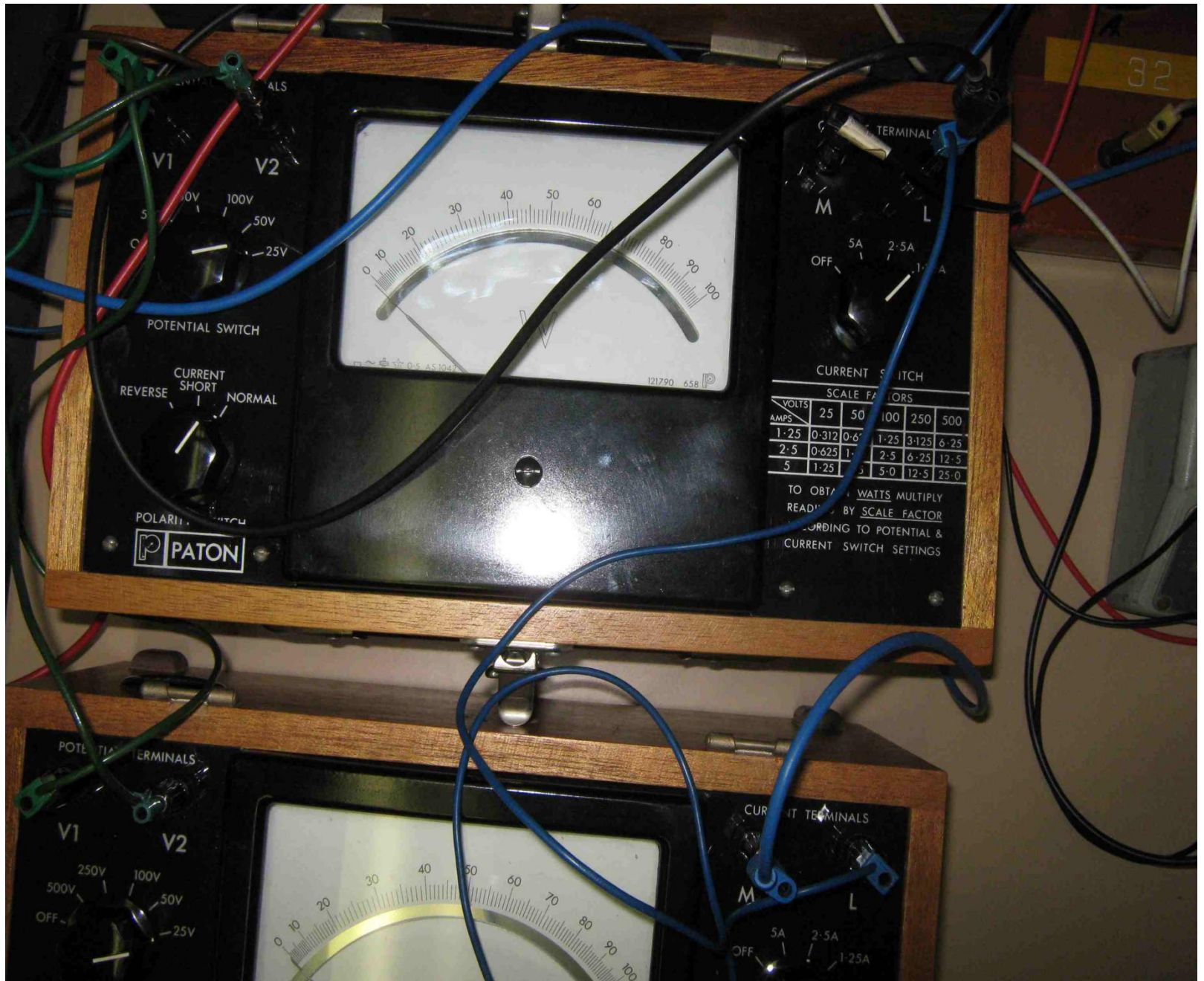



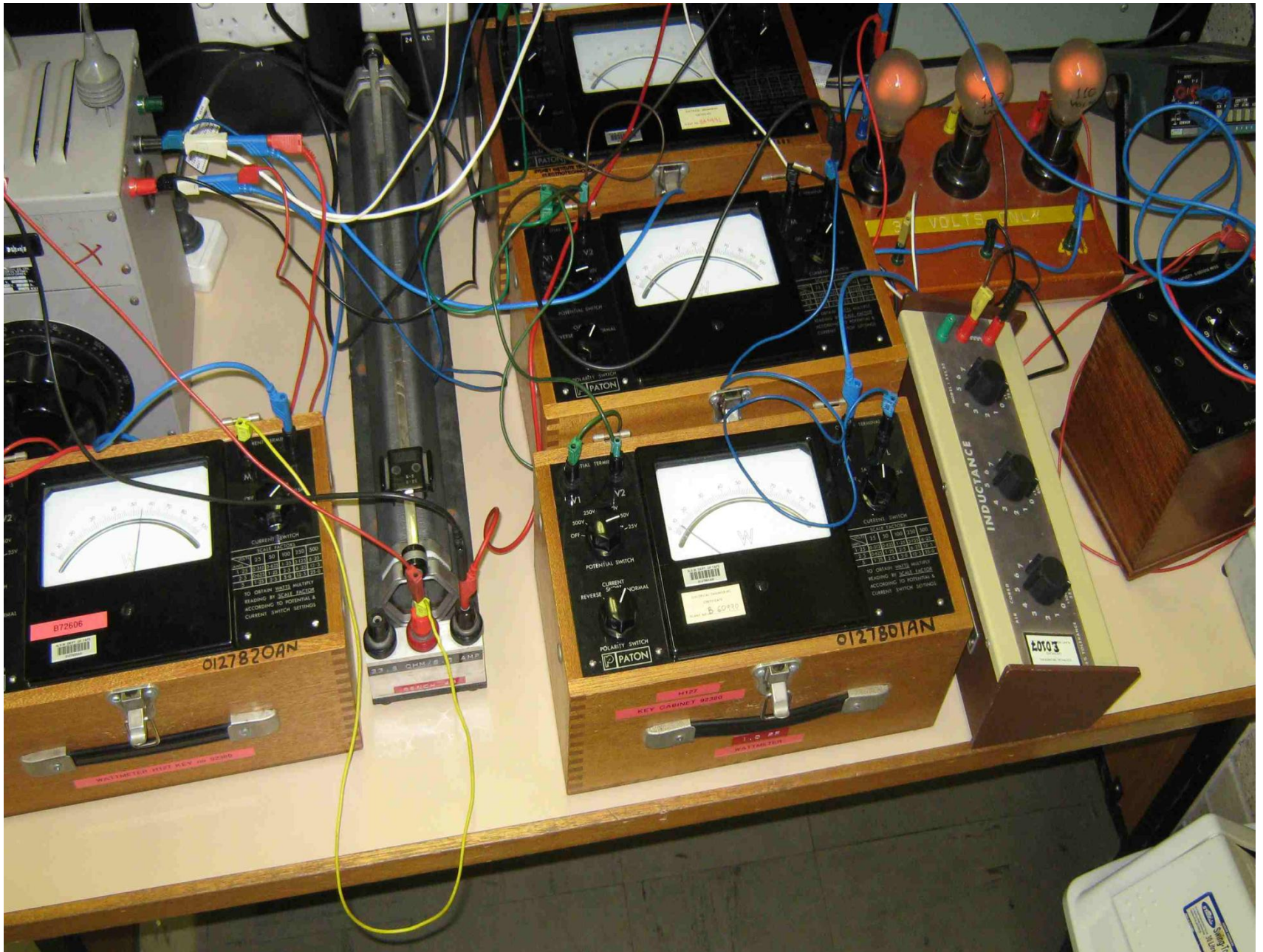

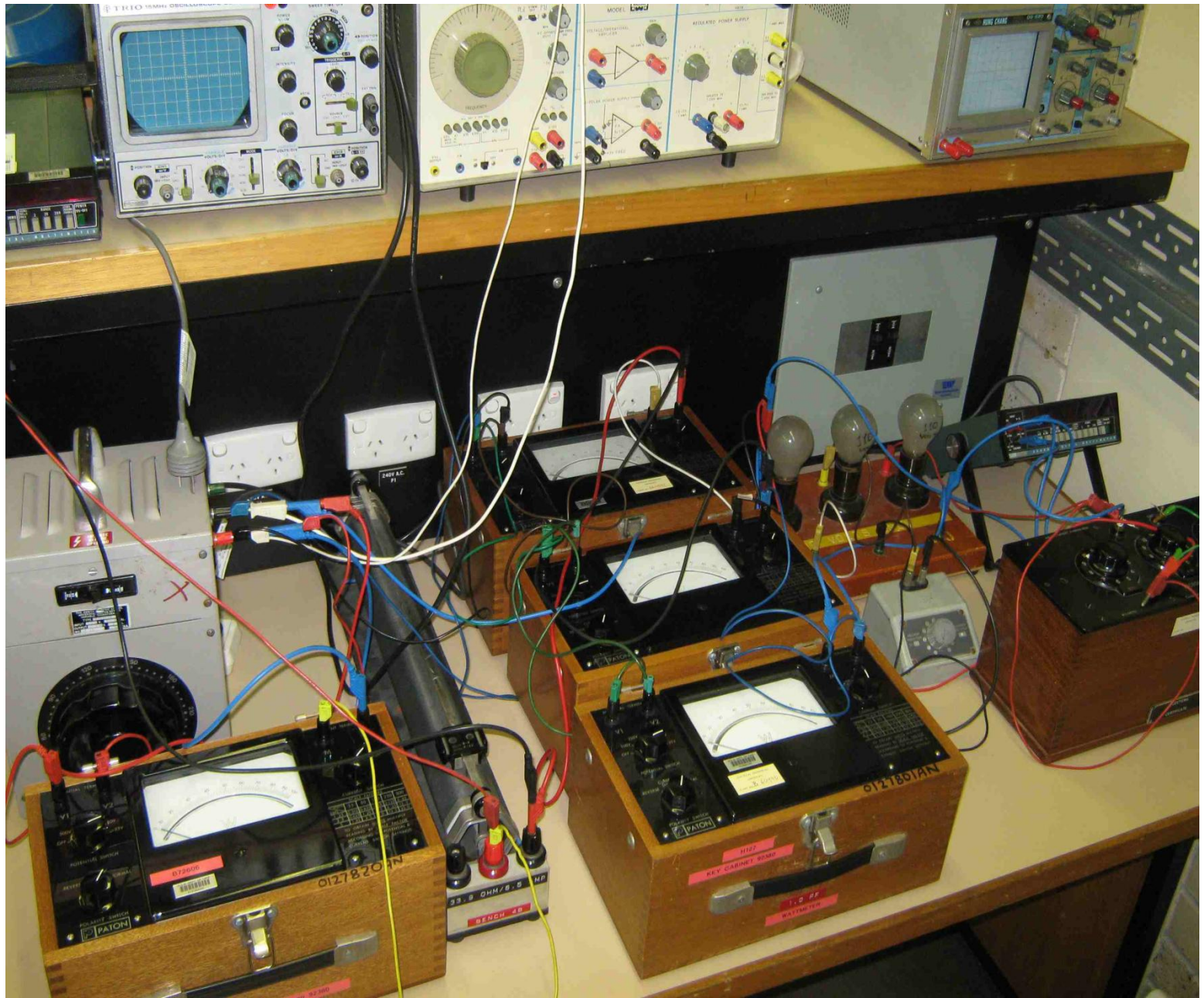

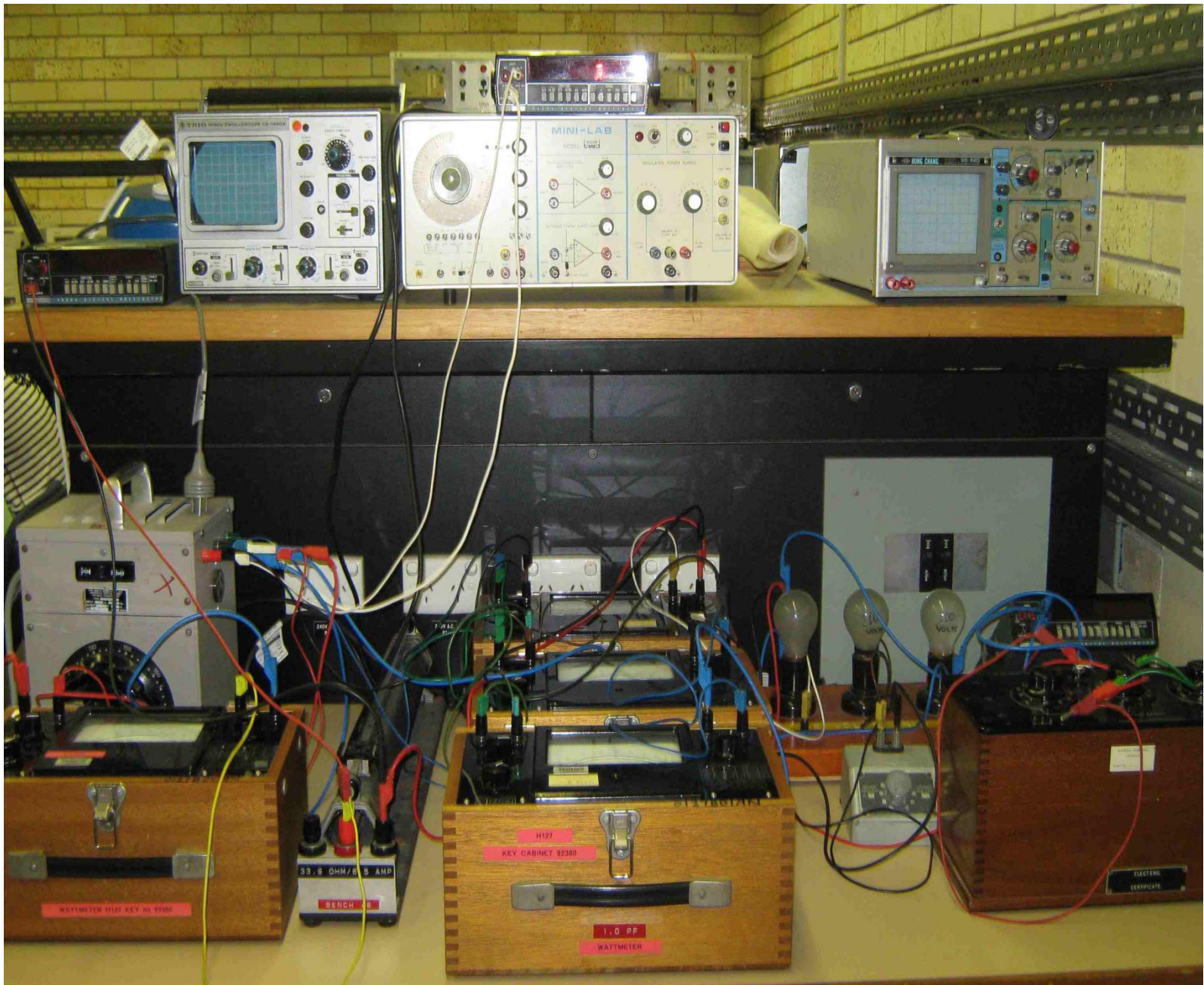

WATTMETER H127 KEY IN 92380


55.5 OHM/6.5 AMP

BENCH 93

H127  
KEY CABINET 92380

1.0 PF  
WATTMETER

ELECTRICAL  
CERTIFICATE

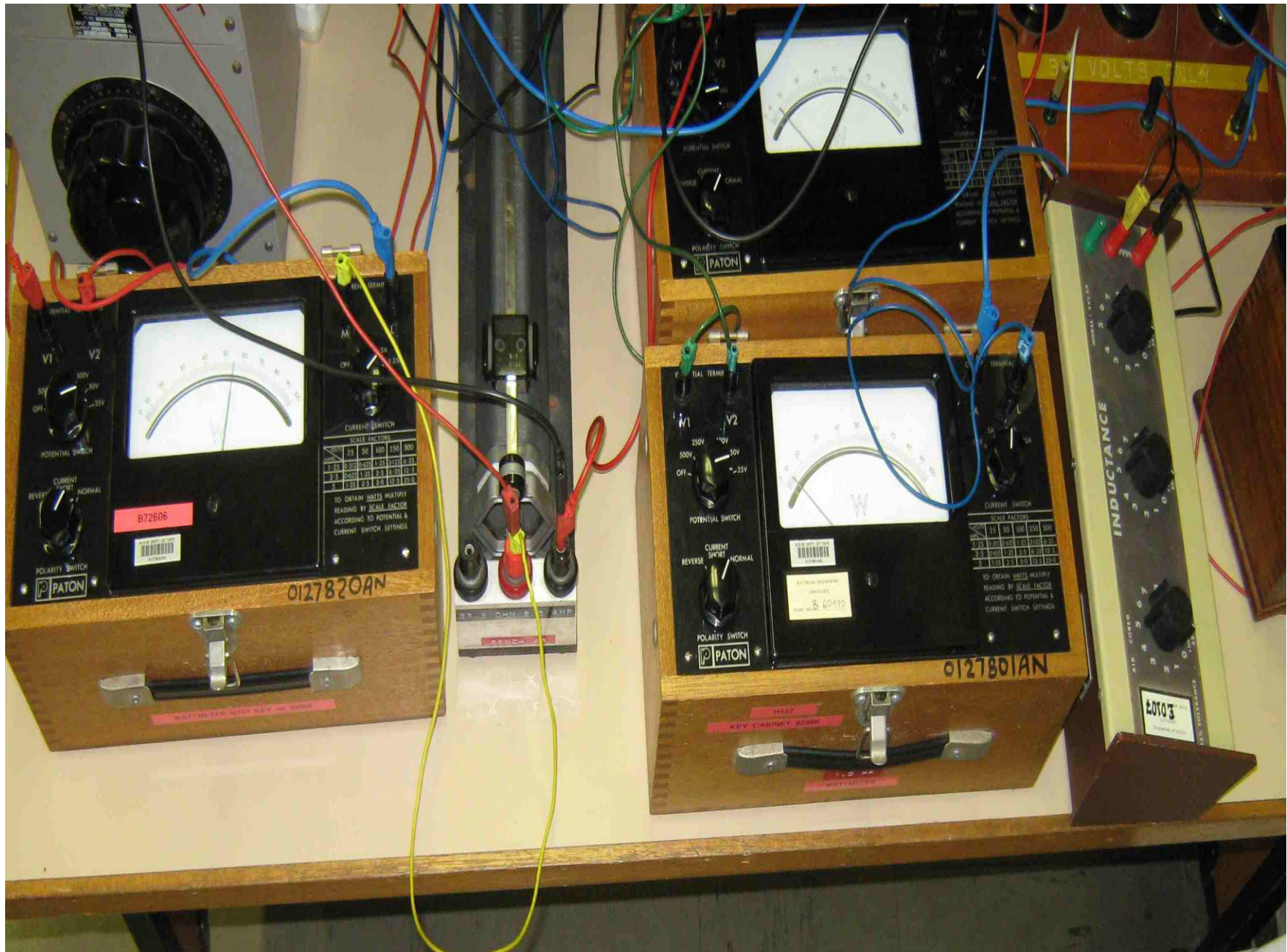

SCALE FACTORS

SCALE	25	50	100	250	500
1000	0.25	0.50	1.00	2.50	5.00
100	0.025	0.050	0.100	0.250	0.500
10	0.0025	0.0050	0.0100	0.0250	0.0500
1	0.00025	0.00050	0.00100	0.00250	0.00500

TO OBTAIN WATTS MULTIPLY READING BY SCALE FACTOR ACCORDING TO POTENTIAL & CURRENT SWITCH SETTINGS

SCALE FACTORS

SCALE	25	50	100	250	500
1000	0.25	0.50	1.00	2.50	5.00
100	0.025	0.050	0.100	0.250	0.500
10	0.0025	0.0050	0.0100	0.0250	0.0500
1	0.00025	0.00050	0.00100	0.00250	0.00500

TO OBTAIN WATTS MULTIPLY READING BY SCALE FACTOR ACCORDING TO POTENTIAL & CURRENT SWITCH SETTINGS

INDUCTANCE

SCALE	0.1	0.2	0.5	1.0	2.0	5.0	10	20	50	100
1000	0.001	0.002	0.005	0.010	0.020	0.050	0.100	0.200	0.500	1.000
100	0.0001	0.0002	0.0005	0.0010	0.0020	0.0050	0.0100	0.0200	0.0500	0.1000
10	0.00001	0.00002	0.00005	0.00010	0.00020	0.00050	0.00100	0.00200	0.00500	0.01000
1	0.000001	0.000002	0.000005	0.000010	0.000020	0.000050	0.000100	0.000200	0.000500	0.001000

TO OBTAIN INDUCTANCE MULTIPLY READING BY SCALE FACTOR ACCORDING TO POTENTIAL & CURRENT SWITCH SETTINGS



DIAN

CURRENT SWITCH

SCALE FACTORS	
25	50
100	250
500	
0.312	0.625
1.25	2.5
6.25	12.5
25	50
125	250
500	

101007

POTENTIAL & CURRENT SWITCH SETTINGS

SCALE FACTORS	
25	50
100	250
500	
0.312	0.625
1.25	2.5
6.25	12.5
25	50
125	250
500	

# INDUCTANCE

MODEL : SVL 33

AIR CORED

0 1 2 3 4 5 6 7 8 9 10

x100mH  
35mA

0 1 2 3 4 5 6 7 8 9 10

x10mH  
60mA




0 1 2 3 4 5 6 7 8 9 10

x1mH  
75mA

ELECTRICAL ENGINEERING  
CERTIFICATE  
30107

±5% TOLERANCE



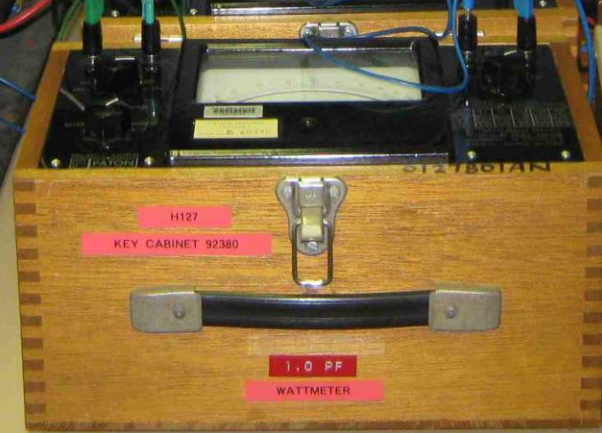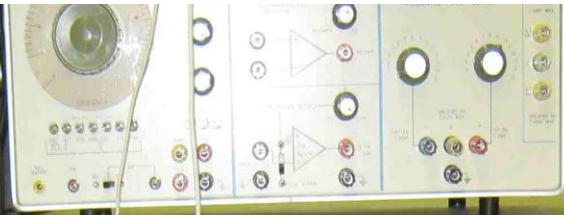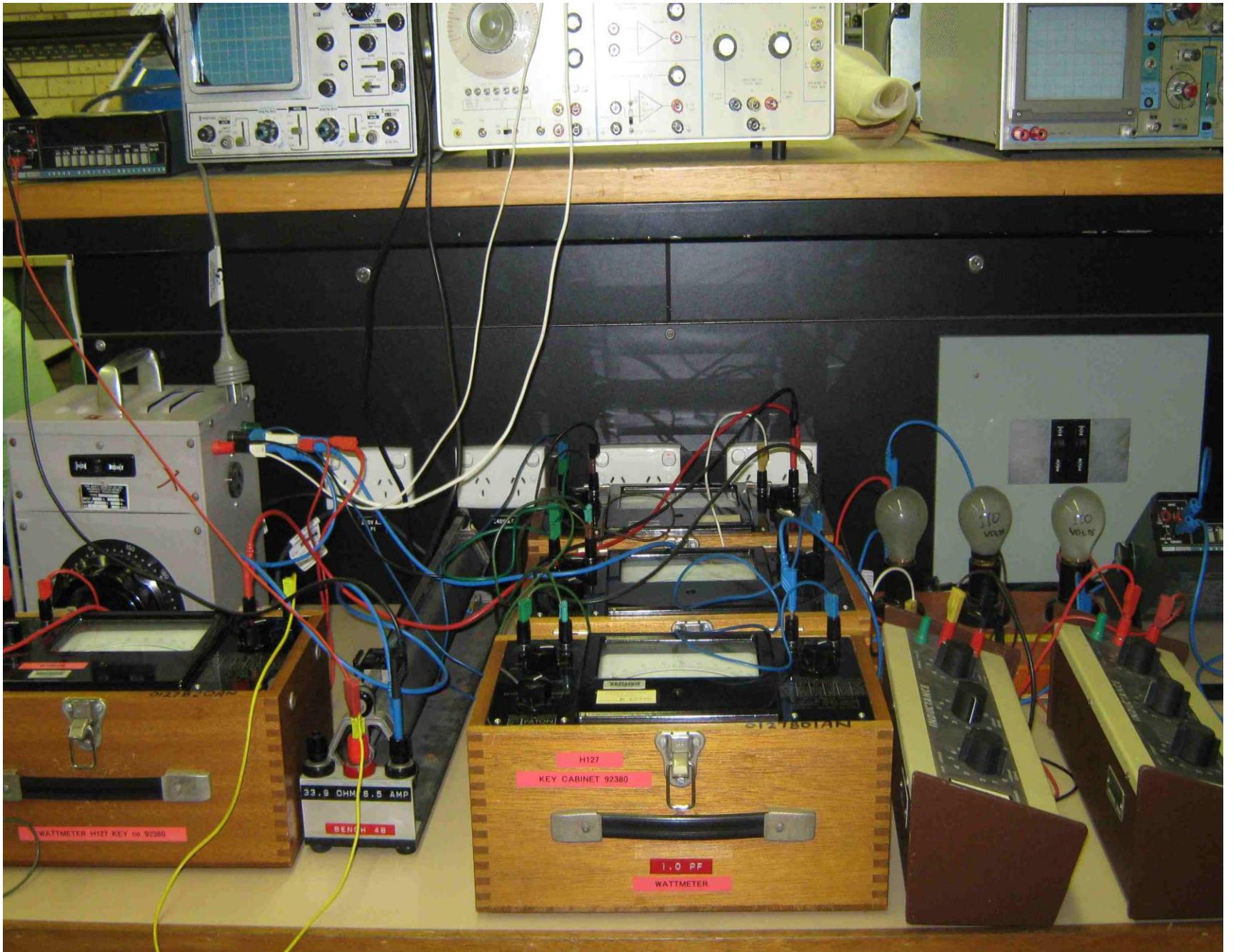
















































 






# ELECTRICAL DISTRIBUTION PRACTICAL (1)
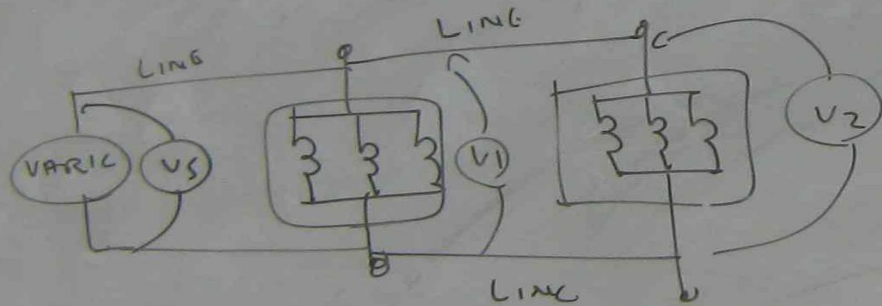
## LOAD CENTRE


COMPARING SERIES CONNECTED LOAD GROUPS AND PARALLEL CONNECTED LOAD GROUPS IN TERM OF VOLTAGE DROP AND VOLTAGE REGULATION

$$\text{VOLTAGE REGULATION} = \frac{\text{VOLTAGE AT GENERATOR} - \text{VOLTAGE AT LOAD}}{\text{VOLTAGE AT GENERATOR}} \times 100$$



CONNECT THE ABOVE CIRCUIT

VARIC VOLTAGE $V_S$	$V_1$	$\% \text{Reg} = \frac{V_S - V_1}{V_S} \times 100$	$V_2$	$\% \text{Reg} = \frac{V_S - V_2}{V_S} \times 100$

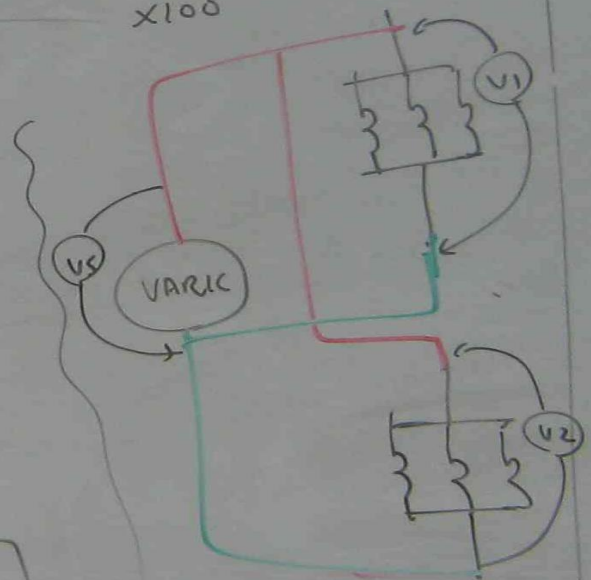

$V_S$	$V_1 = V_2 =$	$\% \text{Reg} = \frac{V_S - V_1}{V_S} \times 100$


FIND THE DIFFERENCE & MAKE COMMENT

any

wire

wire

TOTAL

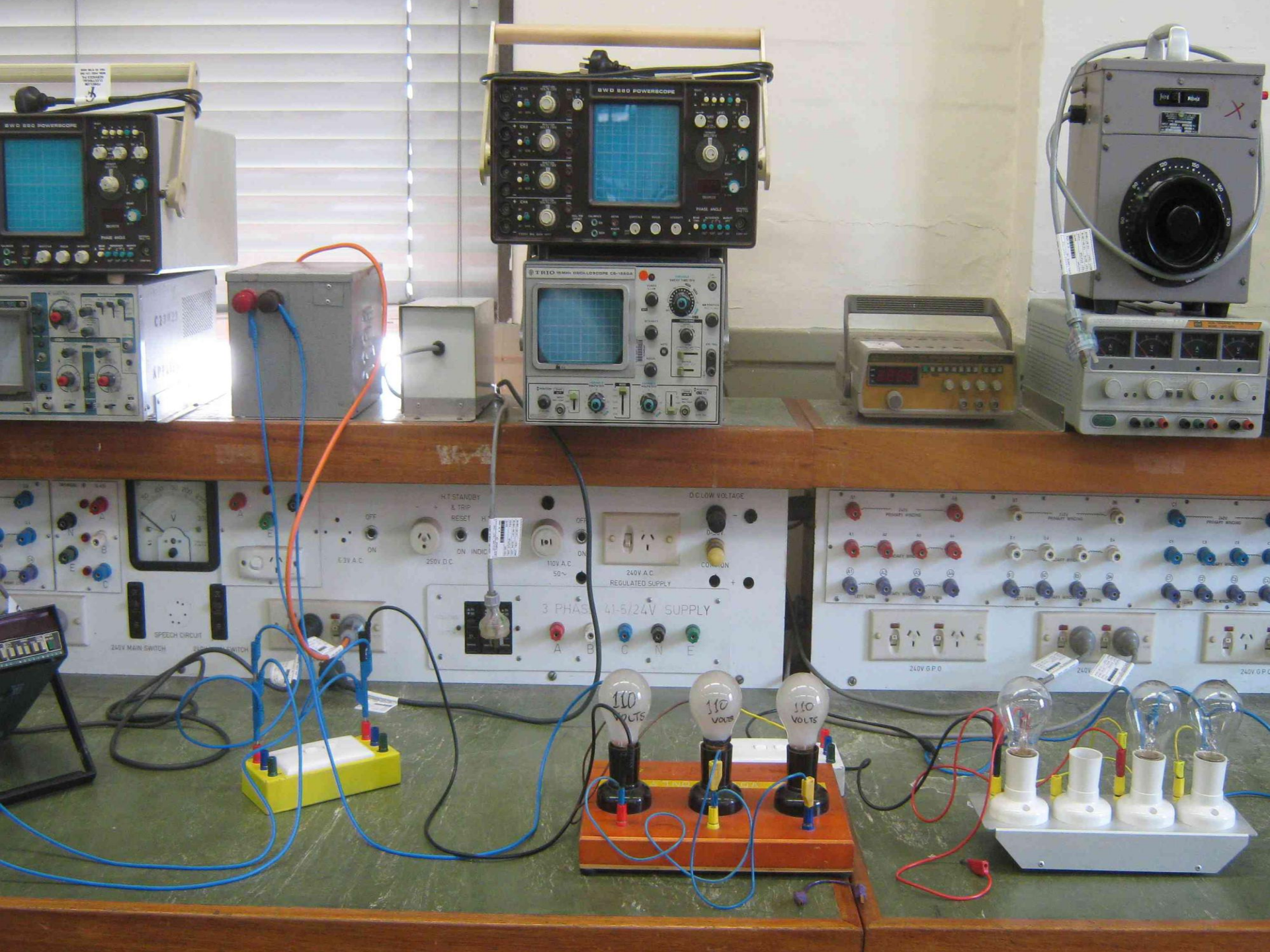

BWD 880 POWERSCOPE

BWD 880 POWERSCOPE

TEO OSCILLOSCOPE CO-1454


C3722


HT STANDST & TRIP RESET  
E.3V A.C. 250V D.C. 110V A.C. 50~ 240V A.C. REGULATED SUPPLY  
3 PHASE 41-5/24V SUPPLY  
D.C. LOW VOLTAGE  
240V G.P.O. 240V G.P.O.

110 VOLTS  
110 VOLTS  
110 VOLTS

110 VOLTS  
110 VOLTS  
110 VOLTS



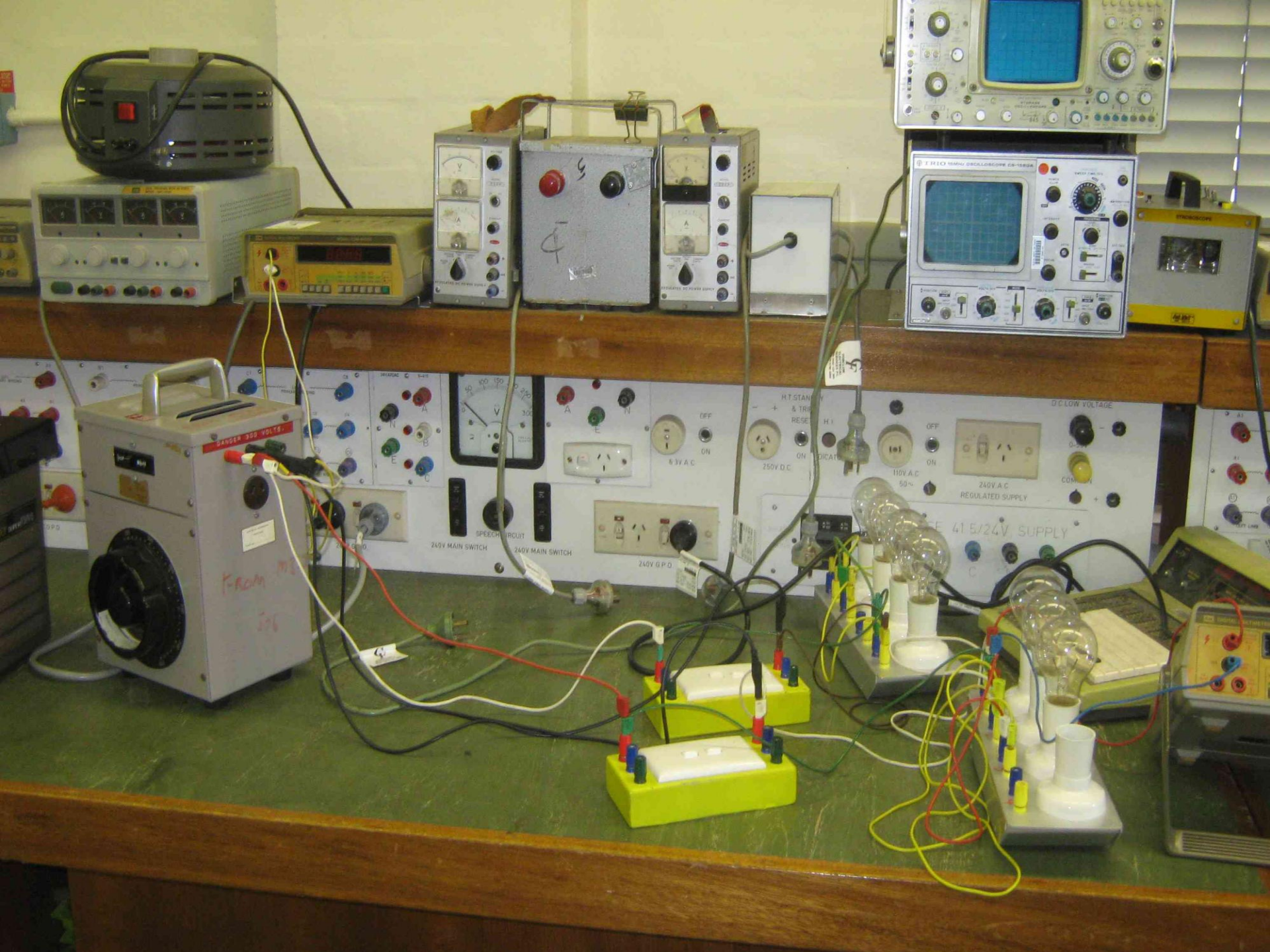

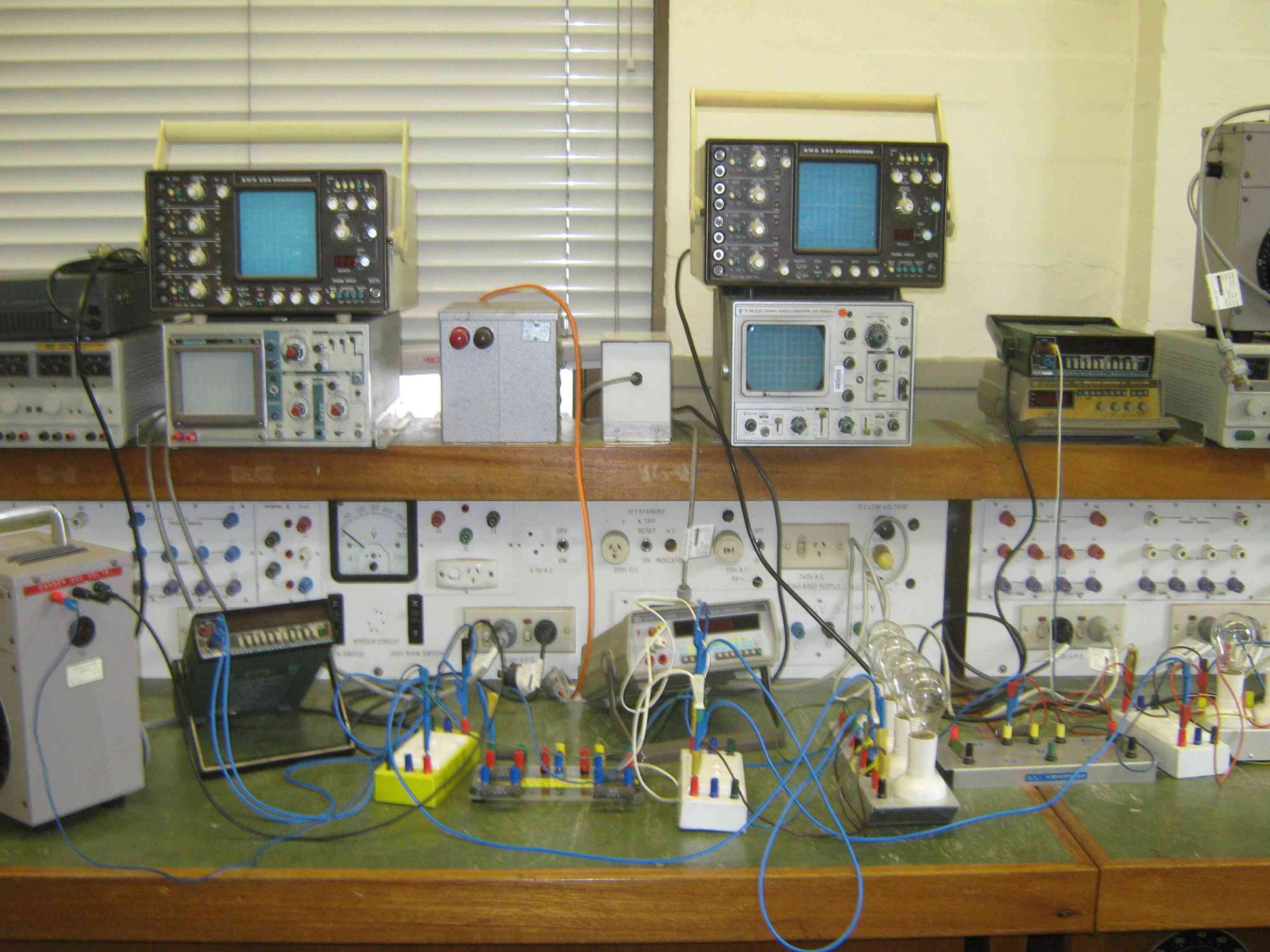


# PRACTICAL (2) ELECTRICAL DISTRIBUTION (FOR TEST 2)

## MEASUREMENT OF OVER HEAD LINE INSULATOR CAPACITANCE

### INSTRUCTION

CONNECT THE GIVEN CIRCUIT

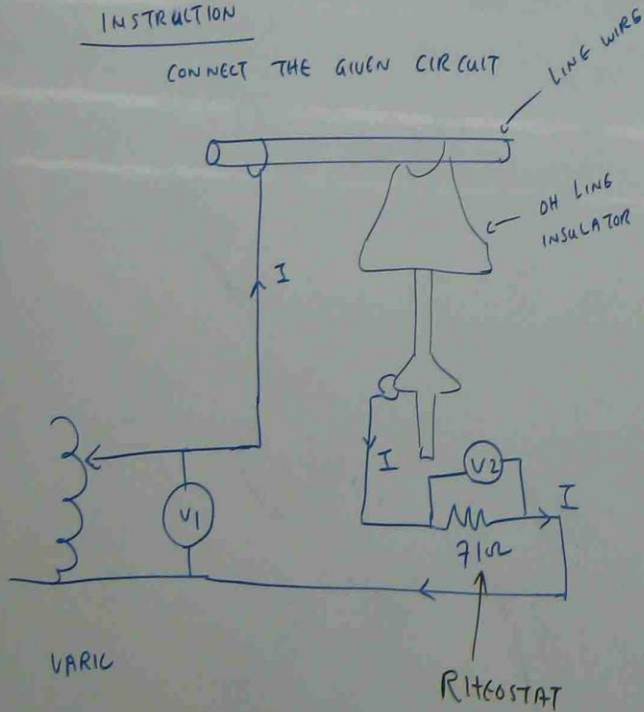

INJECT  $V_1 = 80V$

MEASURE  $V_2 =$

$$I = \frac{V_2}{\text{RHEOSTAT RESISTANCE (71}\Omega\text{)}}$$

$$X_c = \frac{V_1 - V_2}{I}$$

$$C_{80V} = \frac{1}{2\pi f X_c}$$

SUBSTITUTE  $f = 50\text{Hz}$

REPEAT FOR  $V_1 = 90V$  &  $100V$


$V_1$	$V_2$	$V_1 - V_2$	$I = \frac{V_2}{71\Omega}$	$X_c = \frac{V_1 - V_2}{I}$	$C = \frac{1}{2\pi f X_c}$
80V					$C_{80V} =$
90V					$C_{90V} =$
100V					$C_{100V} =$

$$C = \frac{C_{80} + C_{90} + C_{100}}{3} \text{ F}$$

THEN SWITCH OFF THE SUPPLY AND OBSERVE WHAT HAPPENS TO  $V_1$ ?
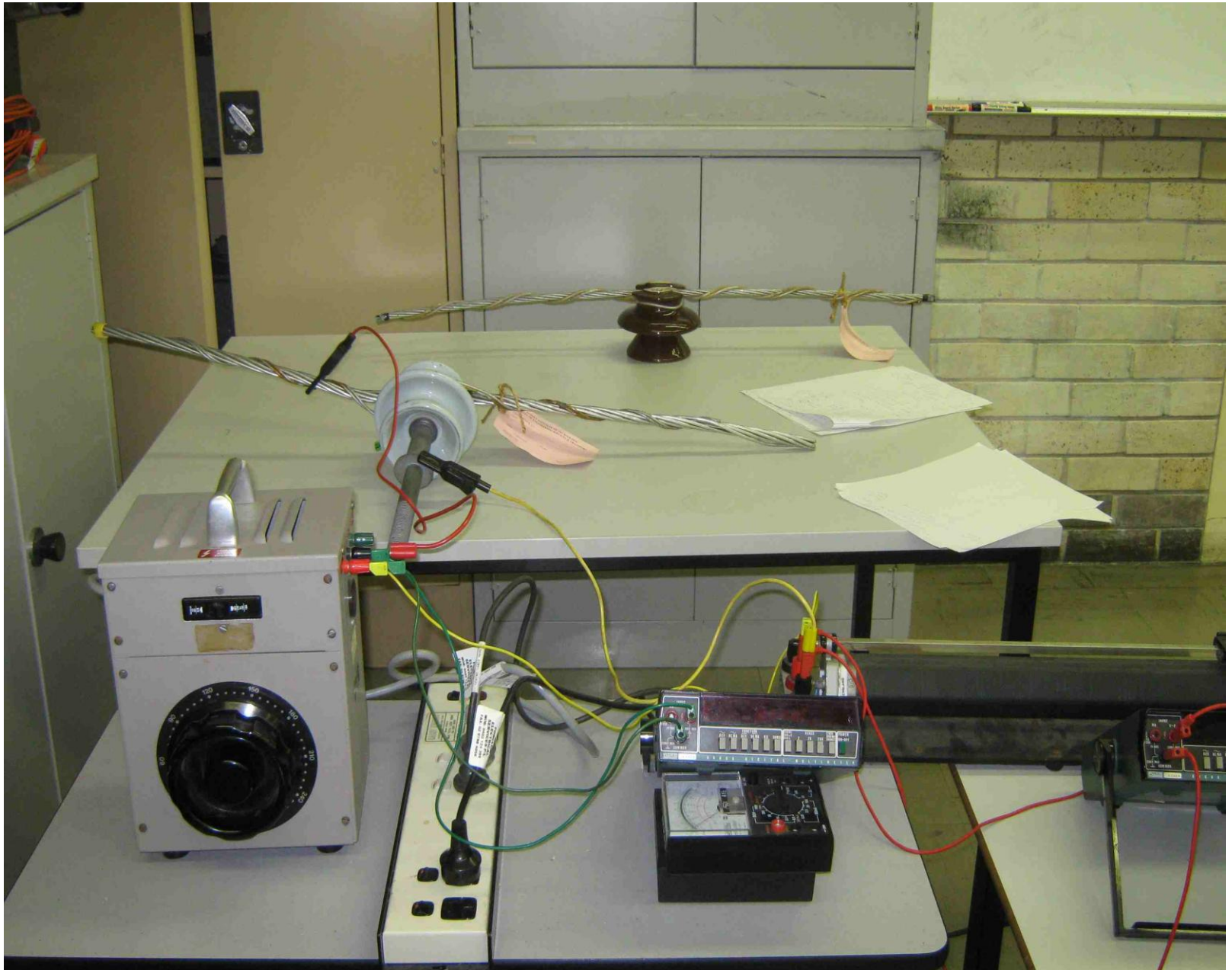
### QUESTION


THE LINE INSULATOR IS RECENTLY TAKEN OUT FROM THE LINE. WHAT WILL YOU DO BEFORE TOUCHING IT?





# PRACTICAL ① OPERATION PRINCIPLE OF OVER CURRENT RELAY

CONNECT THE GIVEN RELAY CIRCUIT

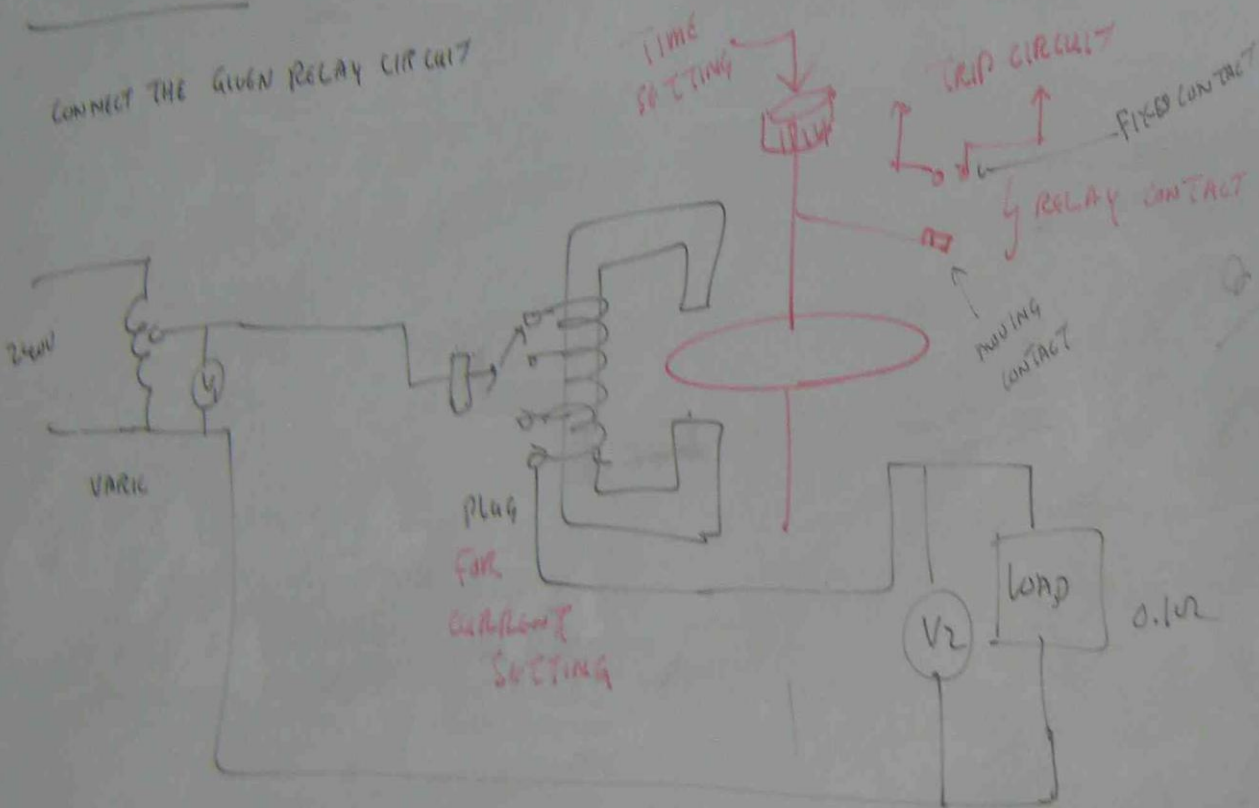

WHEN YOU ADJUST THE TIME SETTING TO GET CLOSER BETWEEN MOVING AND FIXED CONTACT, WHAT WILL HAPPEN TO RELAY OPERATION TIME?

WHAT ARE THE PLUG SETTINGS?

FILL THE TABLE

INJECTION VOLTAGE $V_1$	RELAY BURDEN LOAD VOLTAGE $V_2$	RELAY CURRENT = $\frac{V_2}{\text{LOAD RESISTANCE } 0.1\Omega}$
----------------------------	---------------------------------------	-----------------------------------------------------------------





# ELECTRICAL DISTRIBUTION PRACTICAL (4)

UG CABLE

## UNDERGROUND CABLE CAPACITANCE TEST


(1) STUDY THE GIVEN CALCULATION

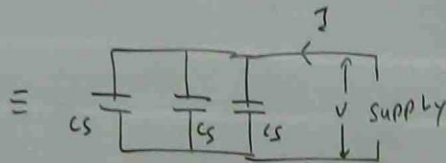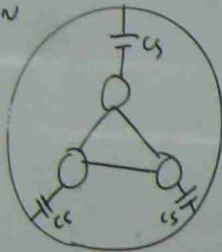

$$X_{C1} = \frac{U}{I}$$

$$3C_s = \frac{1}{2\pi f X_{C1}}$$
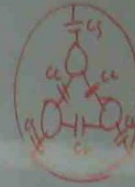
$$C_s = \frac{1}{3 \times 2\pi f X_{C1}}$$



$C_c$  = CAPACITANCE BETWEEN CONDUCTORS

$C_s$  = CAPACITANCE BETWEEN CONDUCTOR & SHEATH

APPLY  $V_1 = 80V$ , SET RHEOSTAT =  $20\Omega$

MEASURE  $V_2$

$$V = V_1 - V_2$$


$$I = \frac{V_2}{\text{Rheostat (R)}}$$

$$X_{C1} = \frac{V_1 - V_2}{\frac{V_2}{\text{Rheostat (R)}}}$$

$$C_s = \frac{1}{3 \times 2\pi f X_{C1}}$$


$$= \text{MF}$$

(2) CONNECT THE GIVEN CIRCUIT

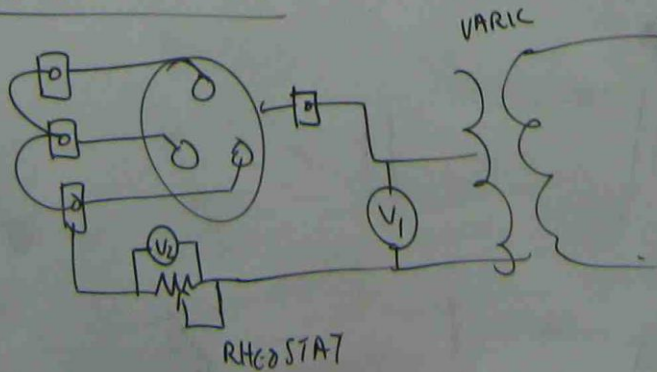



(3) STUDY THE GIVEN CALCULATION

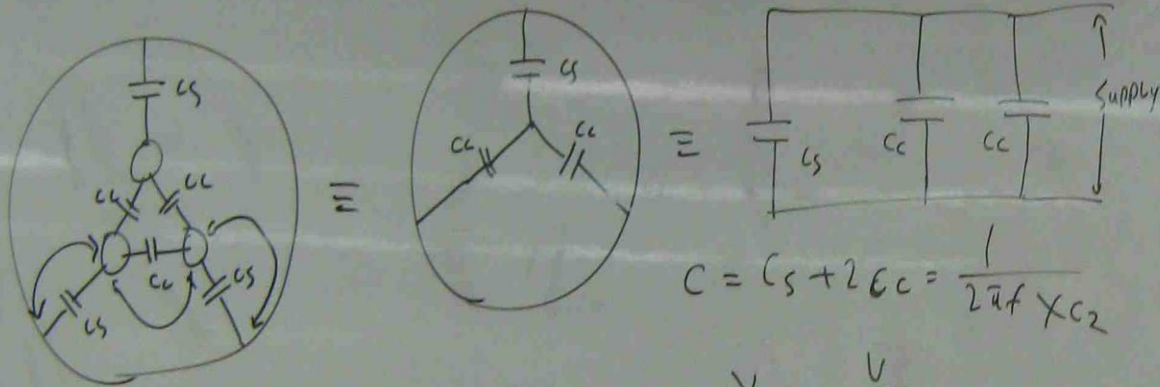

$$C = C_s + 2C_c = \frac{1}{2\pi f X_{C2}}$$

$$X_{C2} = \frac{V}{I}$$

SET  $V_1 = 80V$


$$X_{C2} = \frac{V_1 - V_2}{I}$$

$$X_{C2} = \frac{V_1 - V_2}{V_2 \text{ Rheostat (R)}}$$


$$C_s + 2C_c = \frac{1}{2\pi f X_{C2}}$$

THEN CALCULATE  $C_c$


CONNECT THE GIVEN CIRCUIT

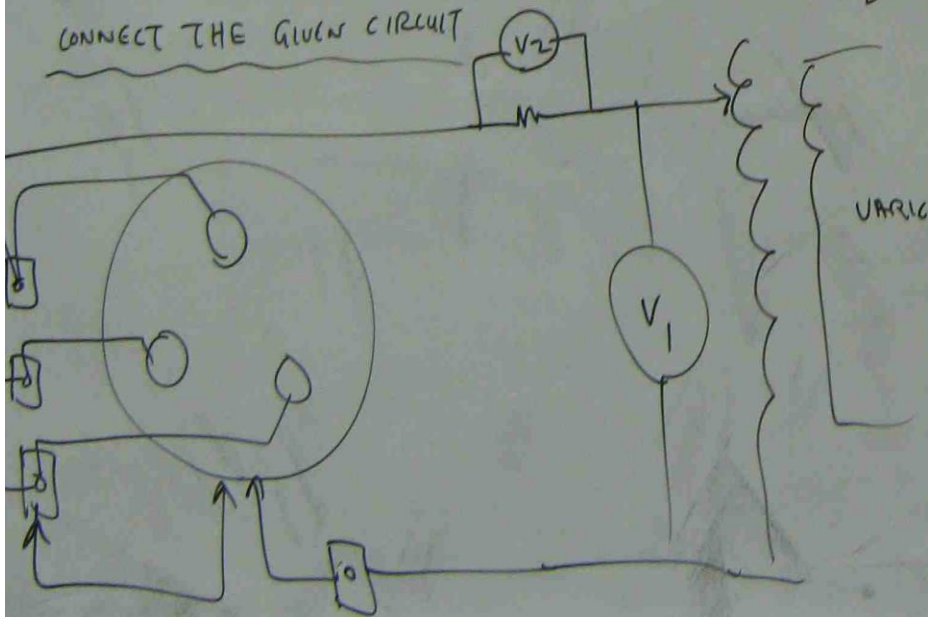


(2) CONNEC

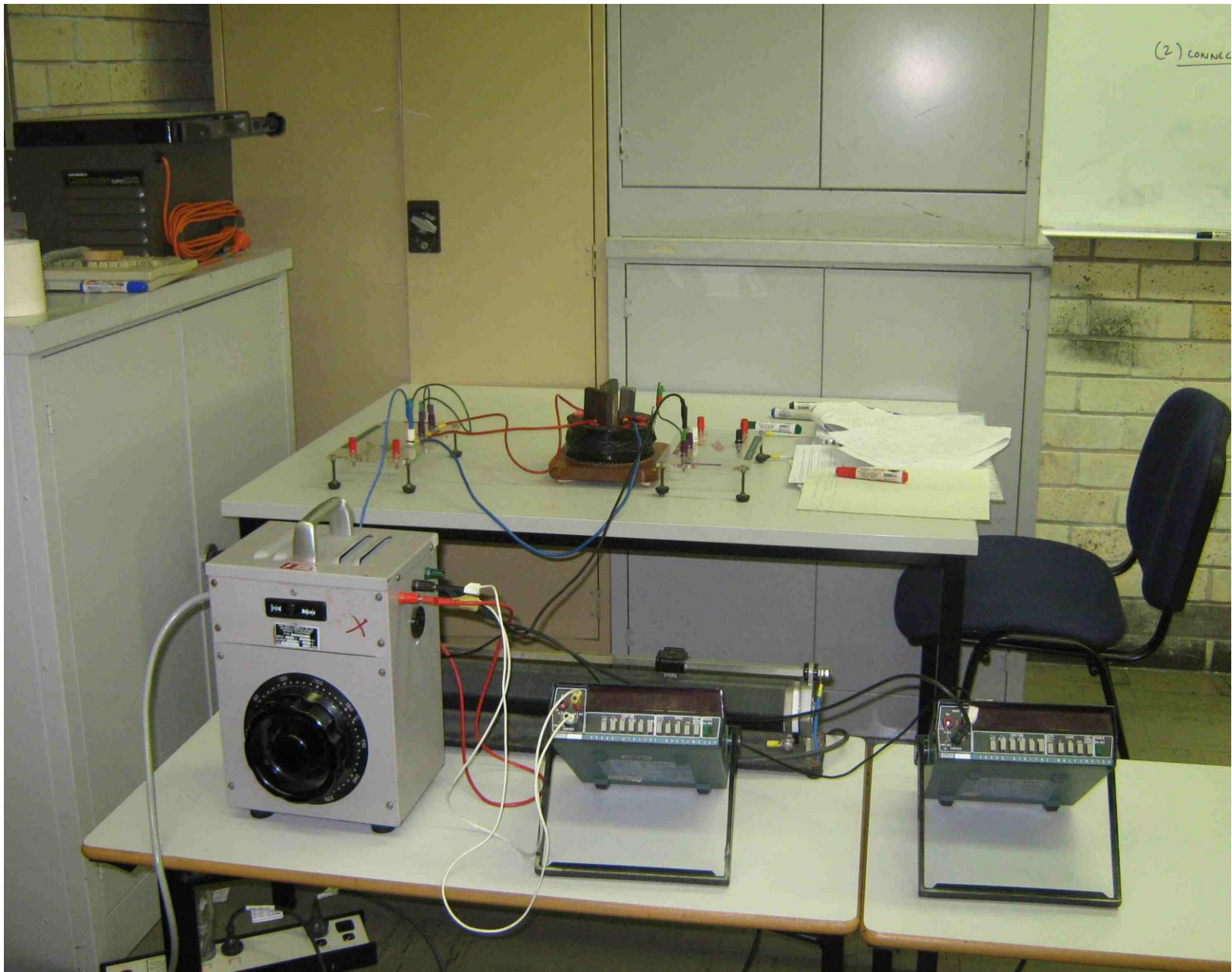



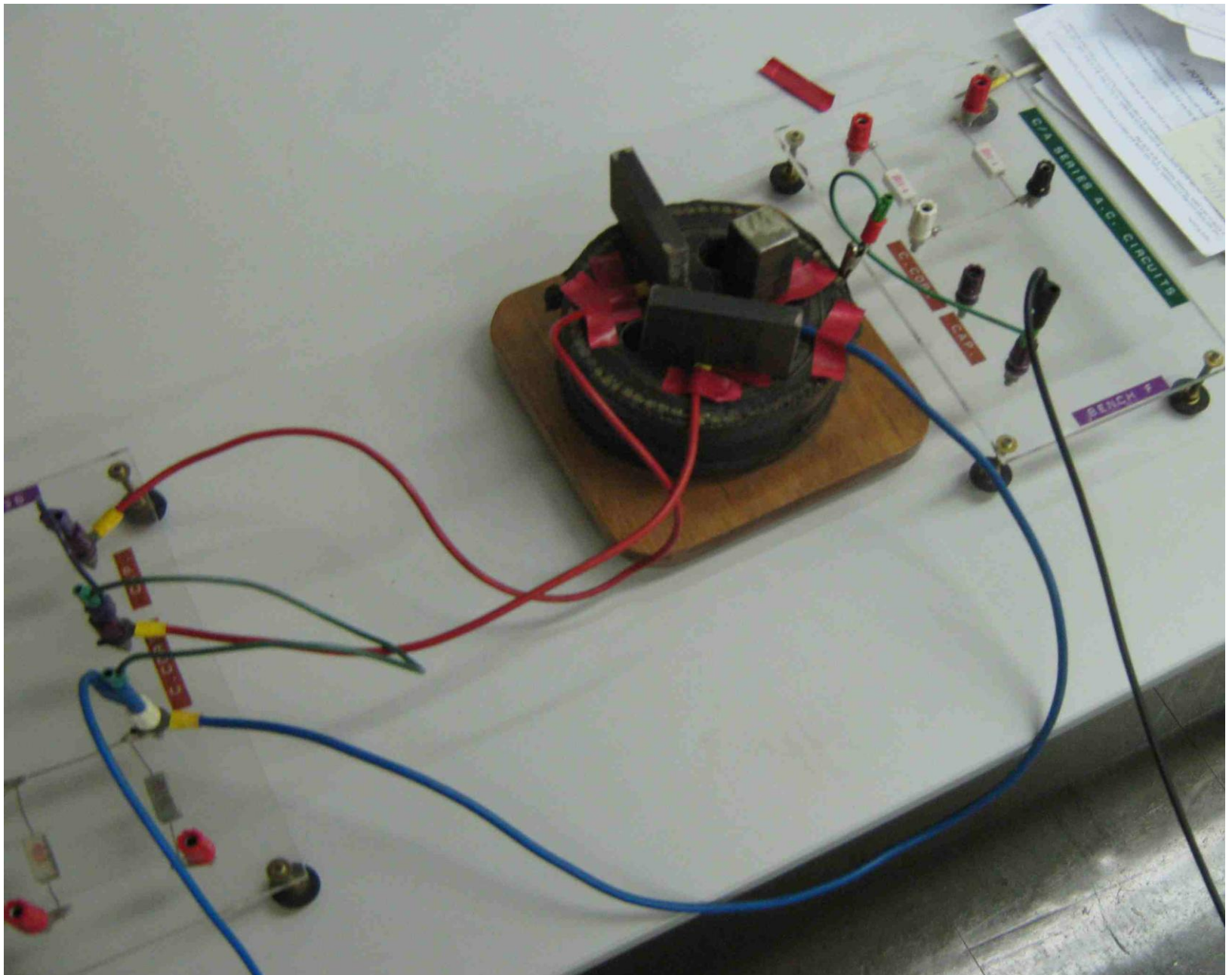

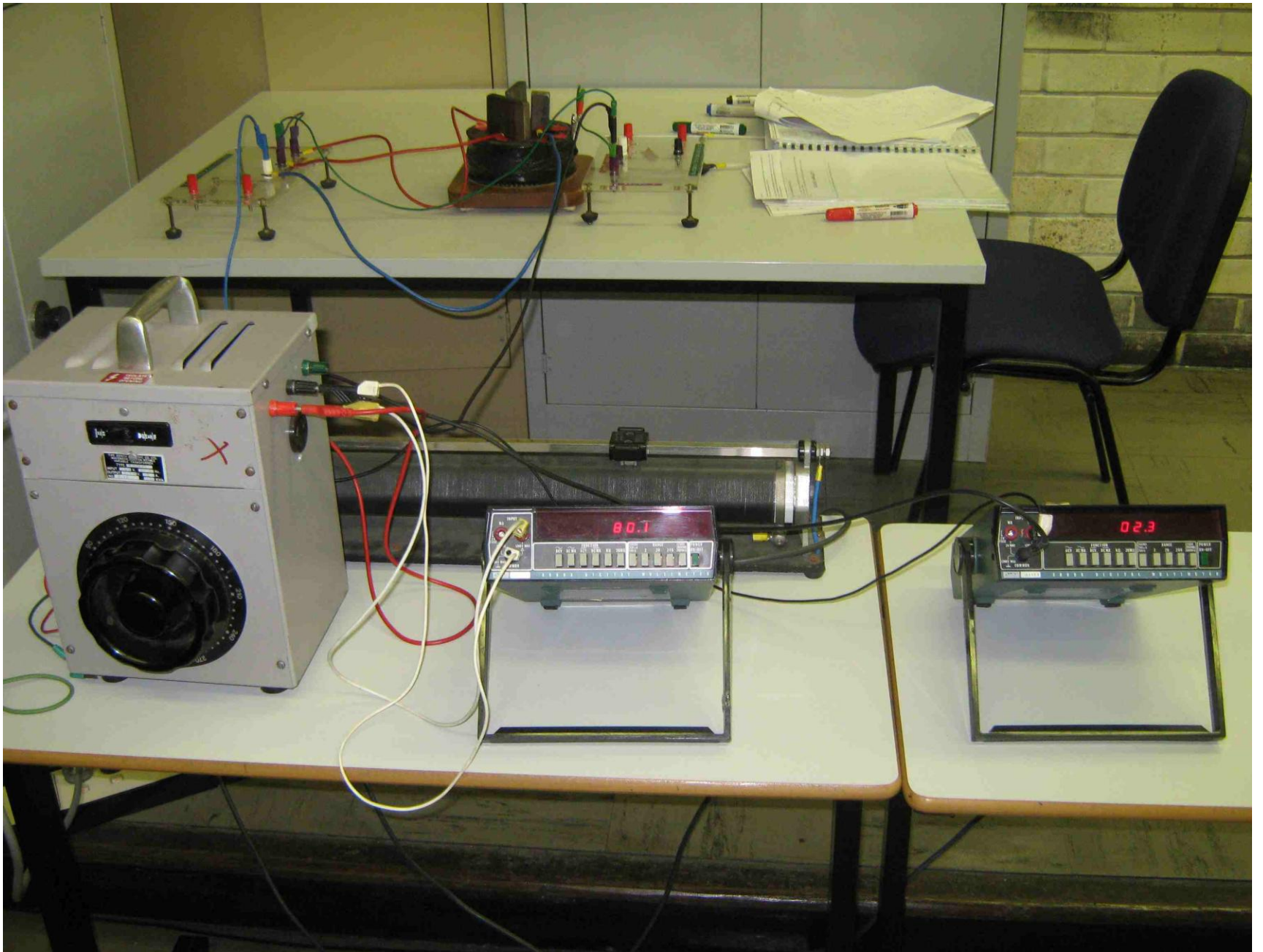




PRACTICAL (2) (FOR TEST (3))

VOLTAGE PROFILE CHART OF DISTRIBUTION SYSTEM


CONNECT THE GIVEN CIRCUIT

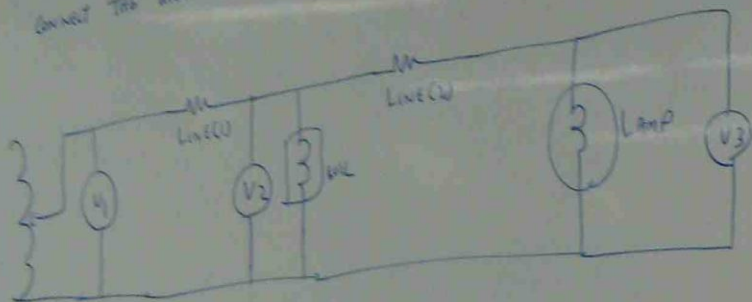

$V_1 = 7V$


MEASURE  $V_2$  &  $V_3$

THEN PLOT THE VOLTAGE PROFILE CHART

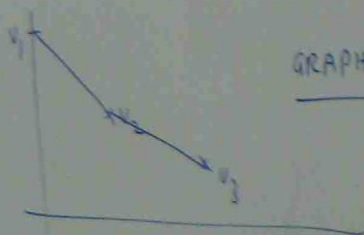

GRAPH (1)


THEN INSERT ANOTHER COIL AS FOLLOWS

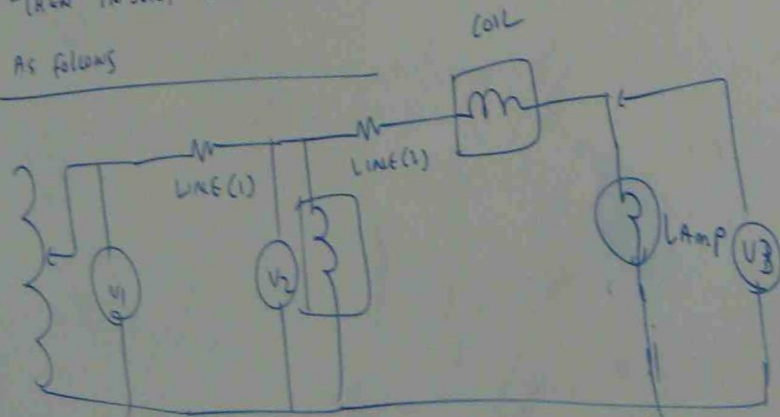

$V_1 = 7V$

MEASURE AGAIN  $V_2, V_3$

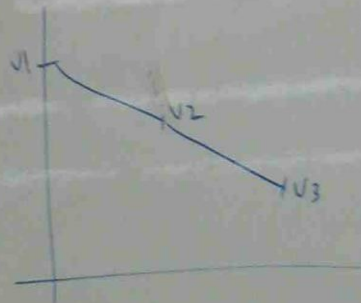THEN PLOT THE VOLTAGE PROFILE CHART AGAIN




COMPARE THE VOLTAGE SLOP BETWEEN  $V_2$  &  $V_3$  OF GRAPH (1) & (2)

COMMENT THE DIFFERENCE


PROVIDE THE REASON.

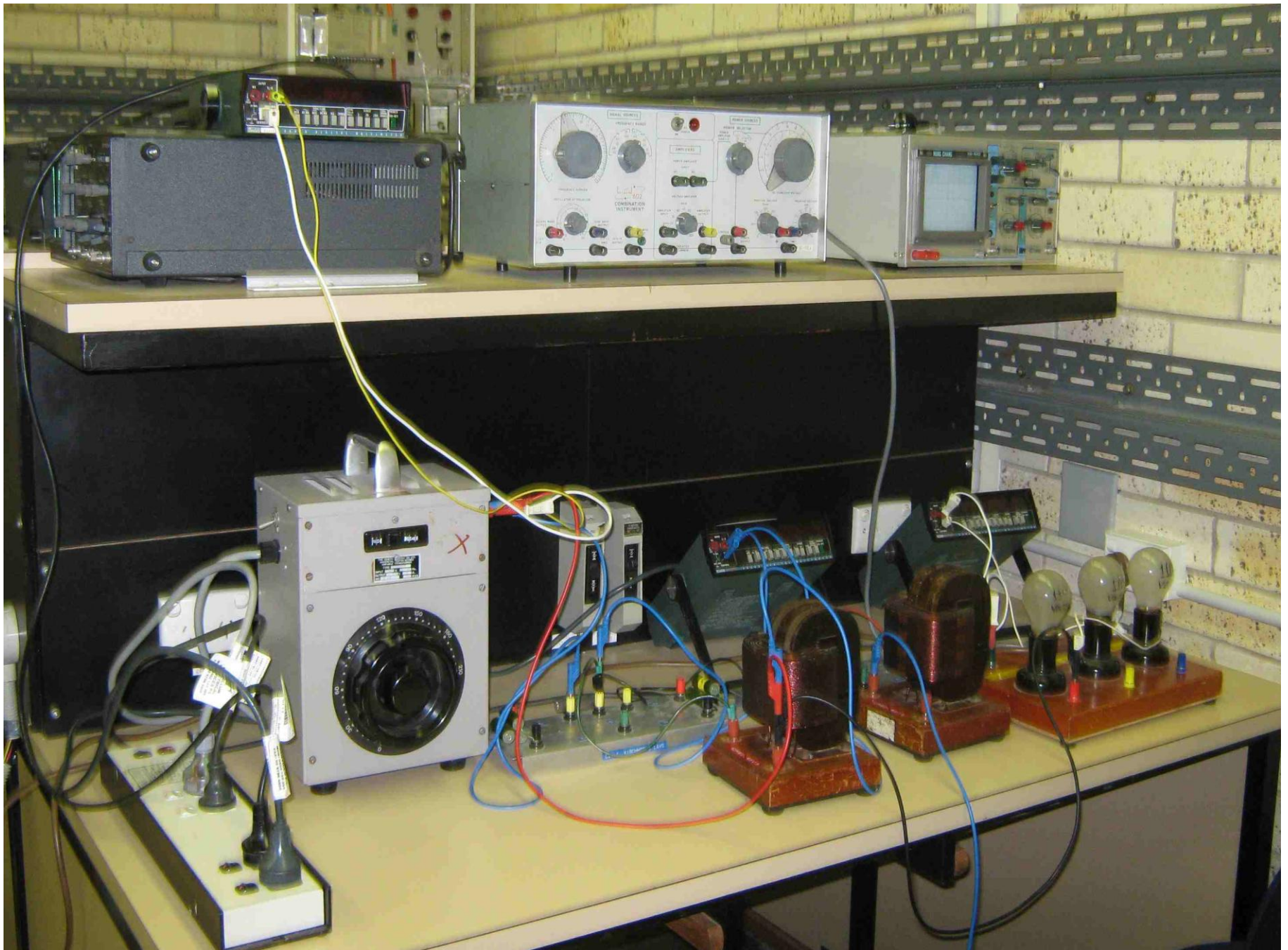QUESTION

FROM VOLTAGE PROFILE CHART, WHAT CAN YOU KNOW?






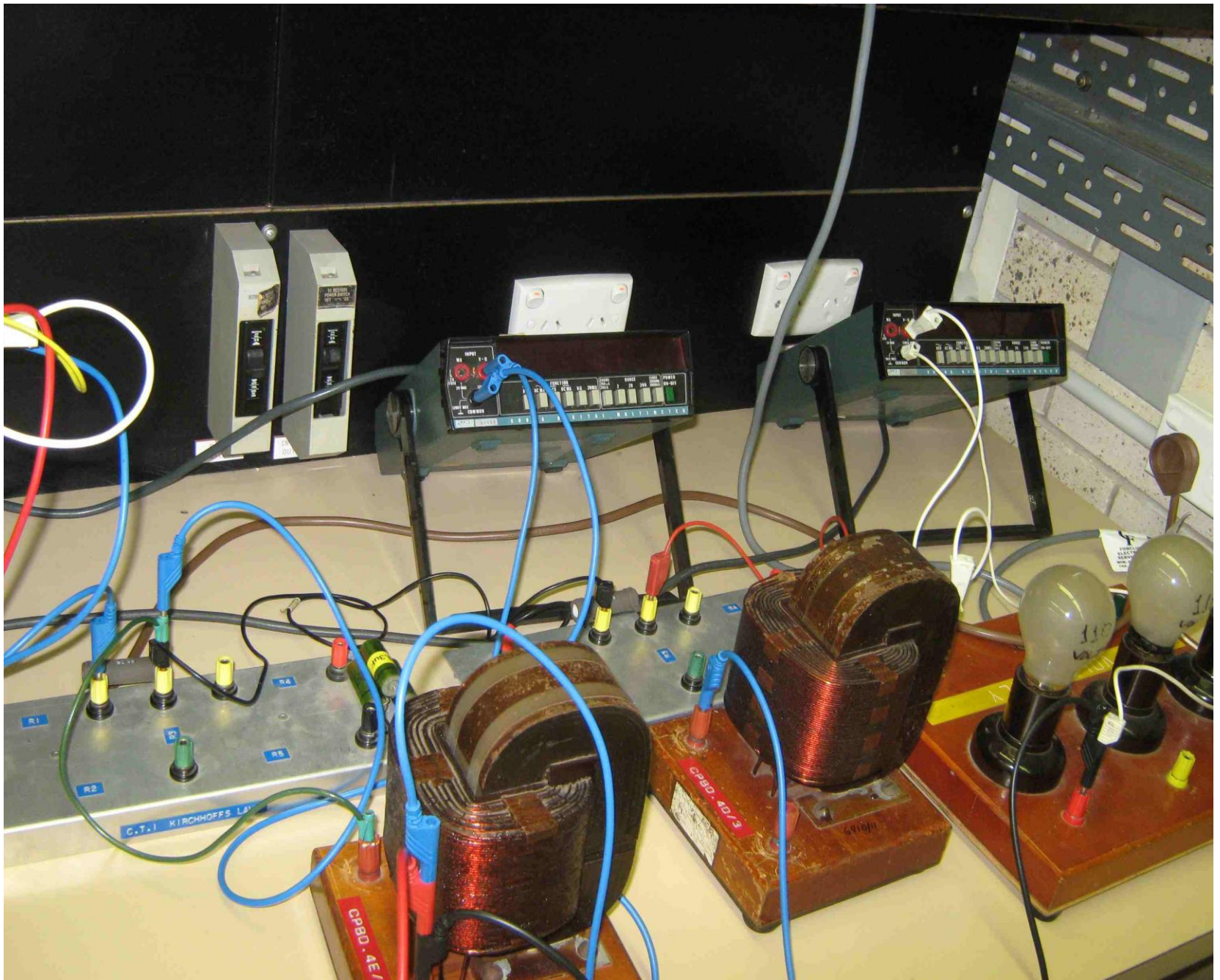




# PRACTICAL (T & $\Pi$ ) EQUIVALENT CIRCUITS

## T EQUIVALENT CIRCUIT

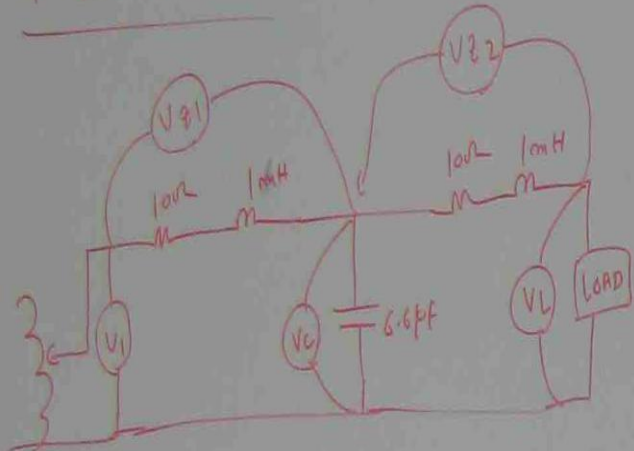


$V_1$	$V_{E1}$	$V_{E2}$	$V_L$	$V_V$
1.5V				


## $\Pi$ EQUIVALENT CIRCUIT

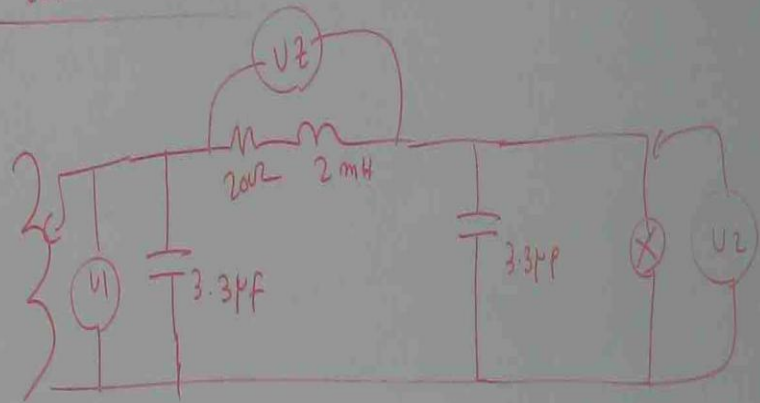


$V_1$	$V_E$	$V_L$
1.5V		


COMPARE  $V_L$  OF  $\Pi$  & T CIRCUITS

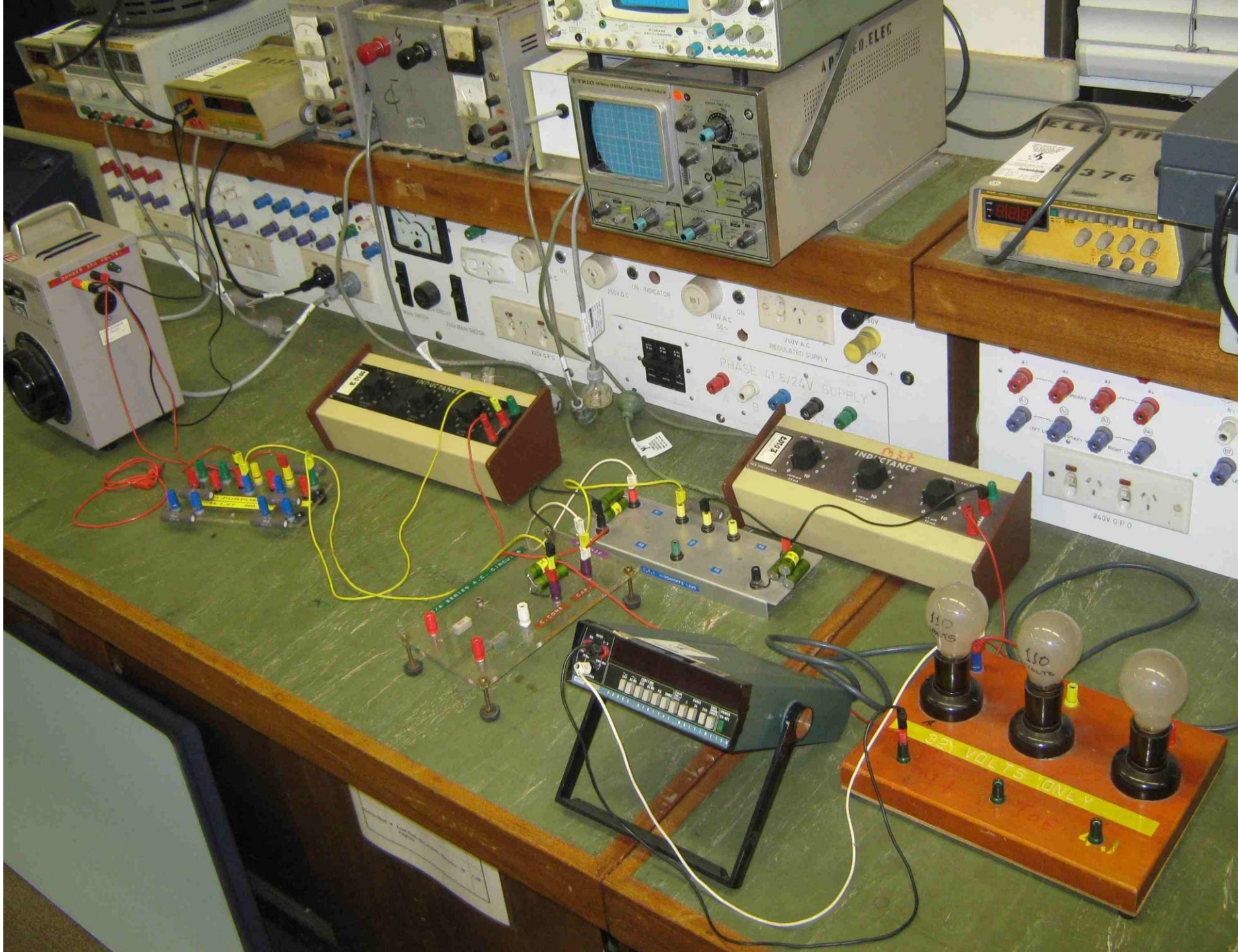

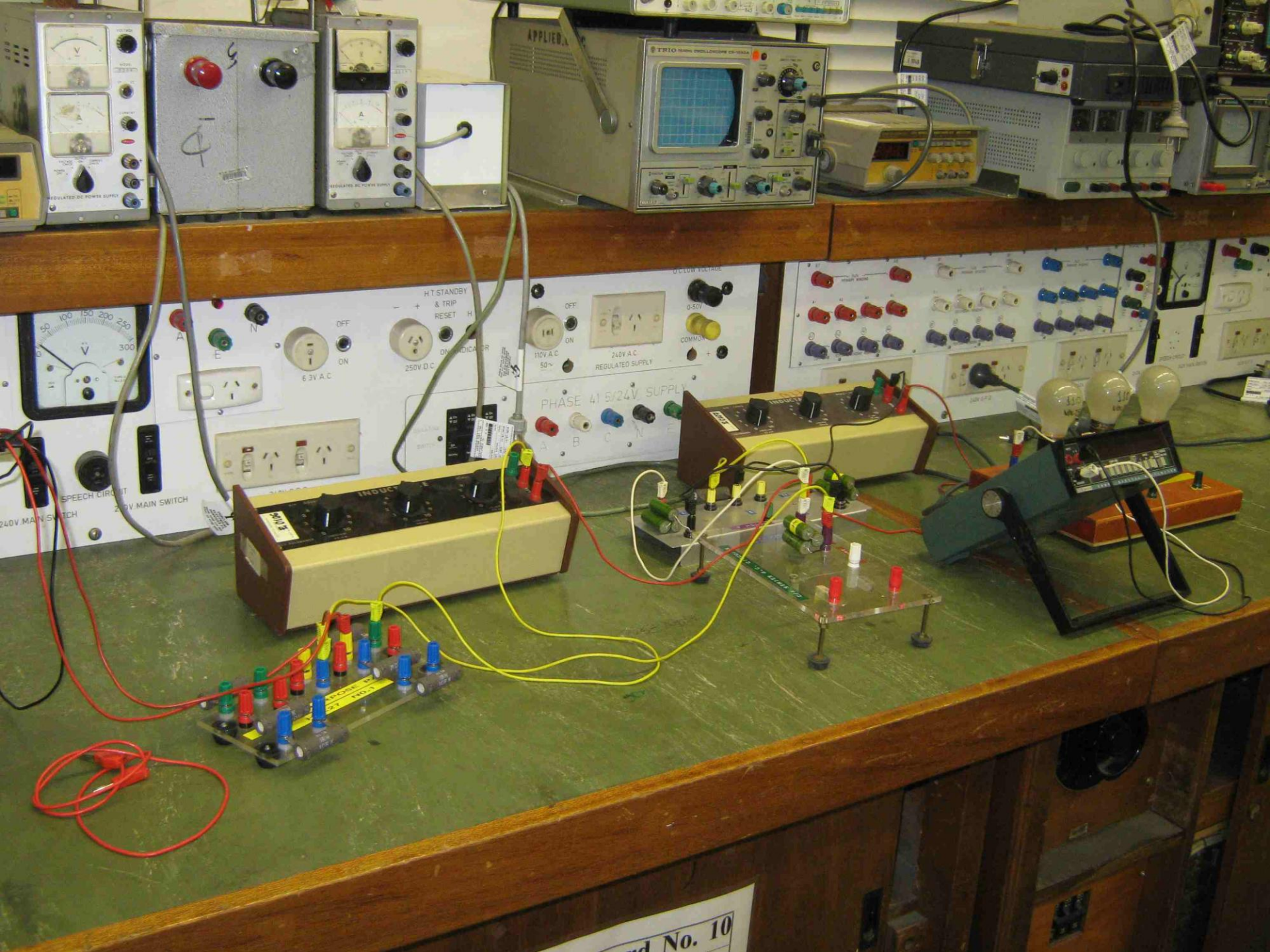

No. 10

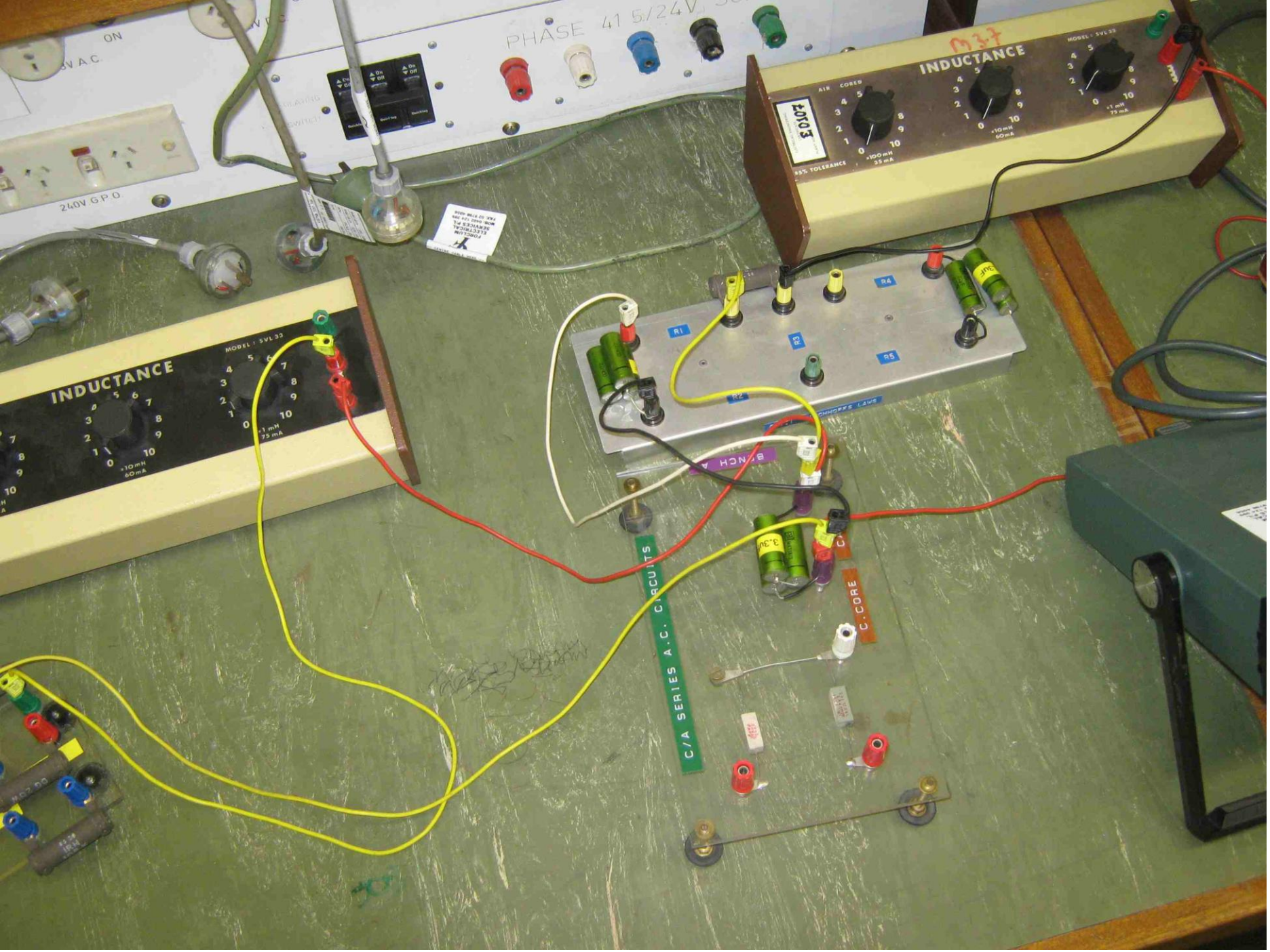


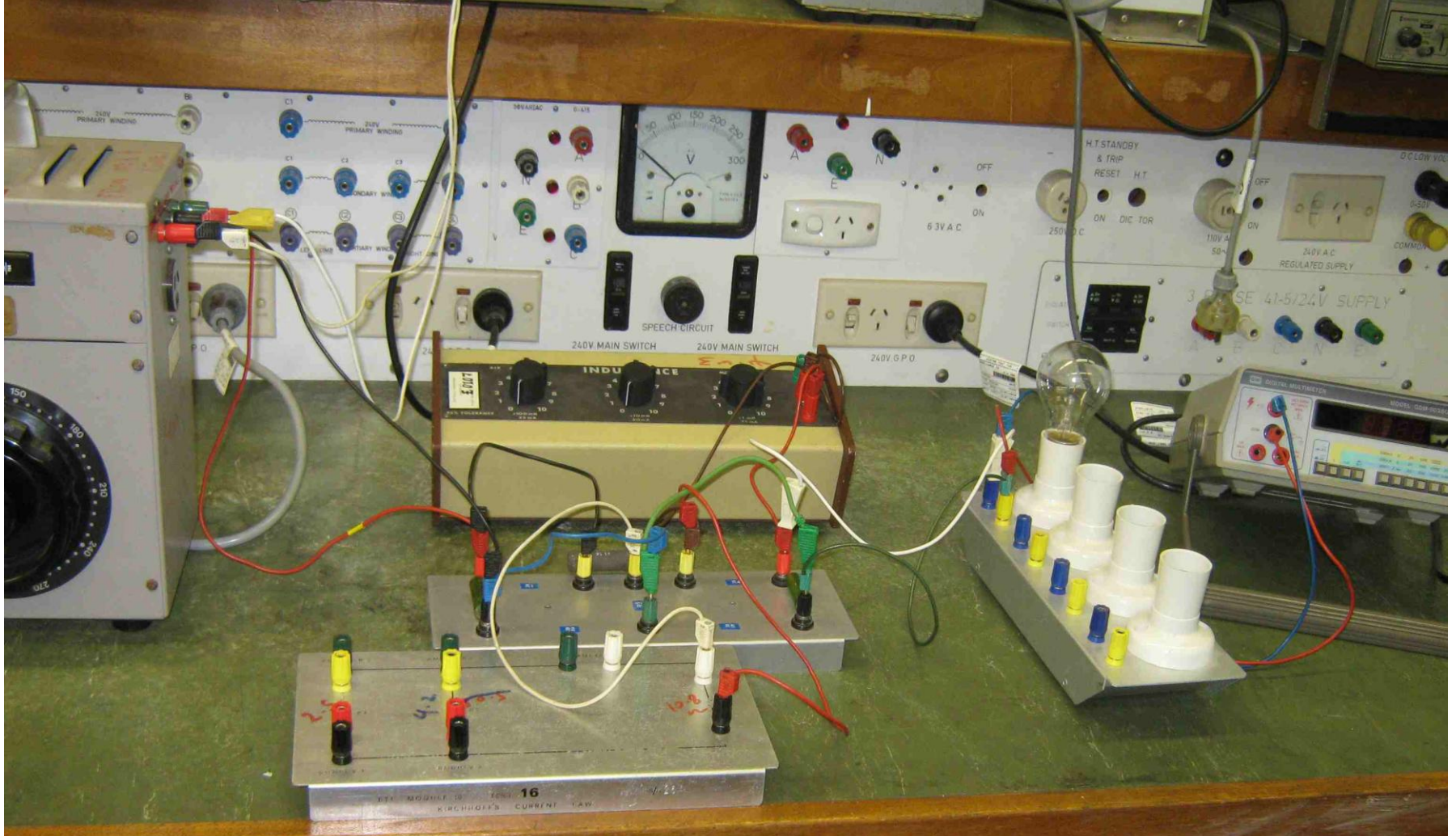


## Cupboard No. 8

Top Shelf	<ul style="list-style-type: none"> <li>Circuit Breaker Panels - 6 x 10 Amperes</li> <li>Quicklog CB</li> </ul>	8 off
Bottom Shelf	<ul style="list-style-type: none"> <li>Load Bank (fan cooled) - Resistive - 30 Amperes</li> </ul>	1 off

Em.d

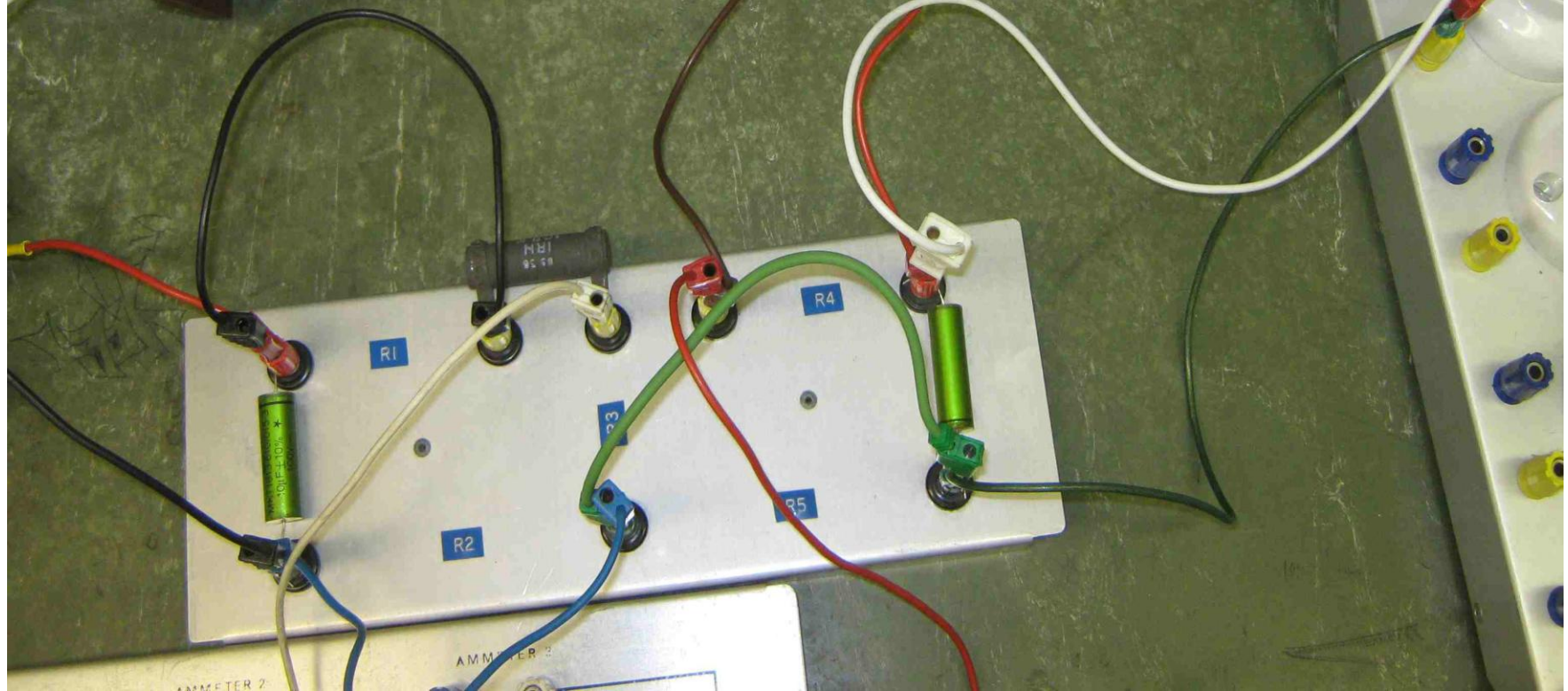



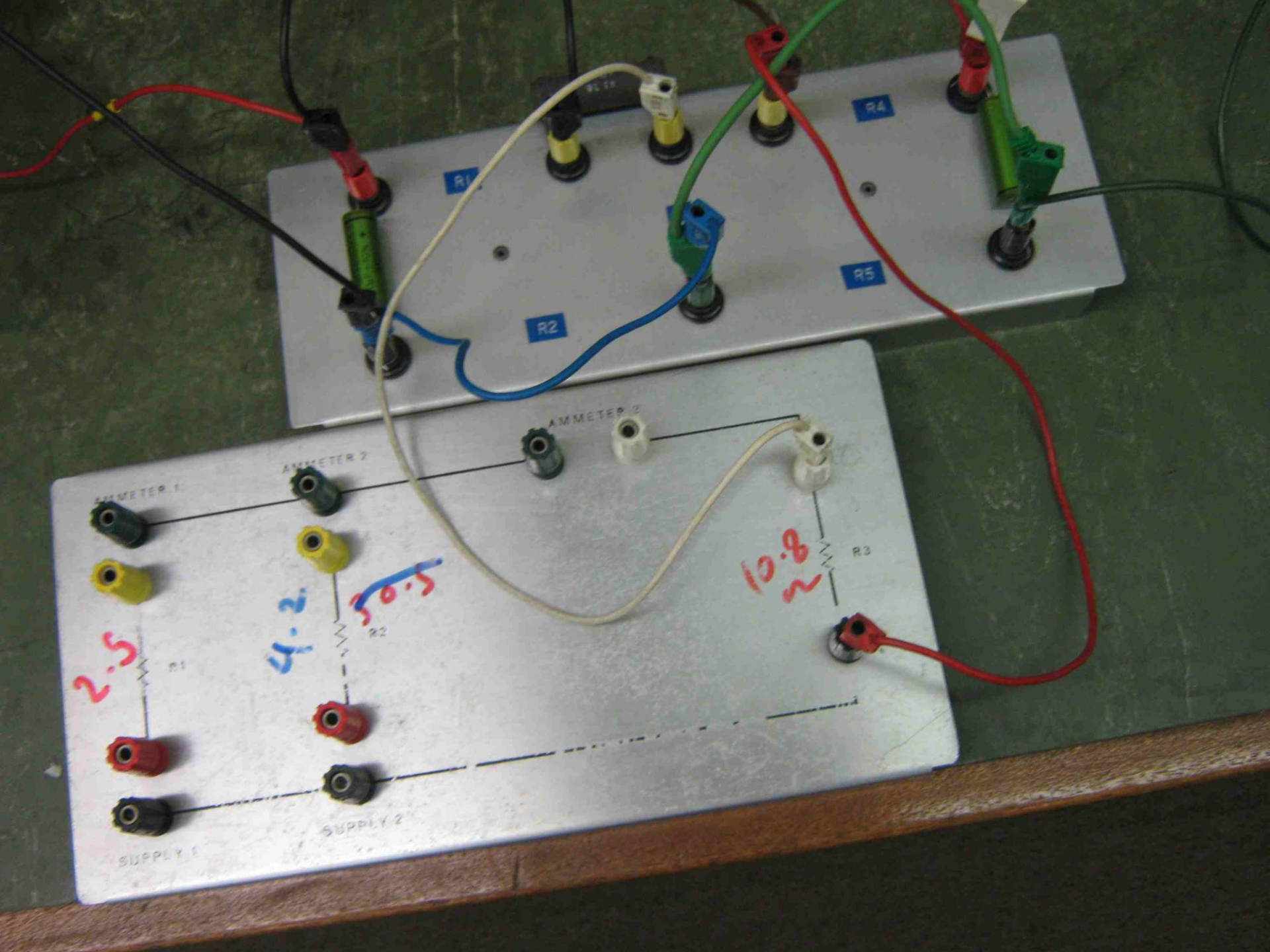

Top breadboard with resistors R1, R2, R3, R4, and R5. R1 is a green resistor, R2 is a blue resistor, R3 is a black resistor, R4 is a yellow resistor, and R5 is a black resistor. A yellow wire connects R2 on the top board to R2 on the bottom board.

Bottom breadboard with two ammeters (AMMETER 1 and AMMETER 2), two supplies (SUPPLY 1 and SUPPLY 2), and three resistors (R1, R2, R3). R1 is a yellow resistor with a handwritten value of 2.5. R2 is a yellow resistor with a handwritten value of 4.2. R3 is a resistor with a handwritten value of 10.8. A handwritten value of 30.5 is written in blue and red ink. A red wire is connected to R3.


R2


R5

BENCH A


C/A SURVIVES A.C. CIRCUITS

C-CORE CAP.

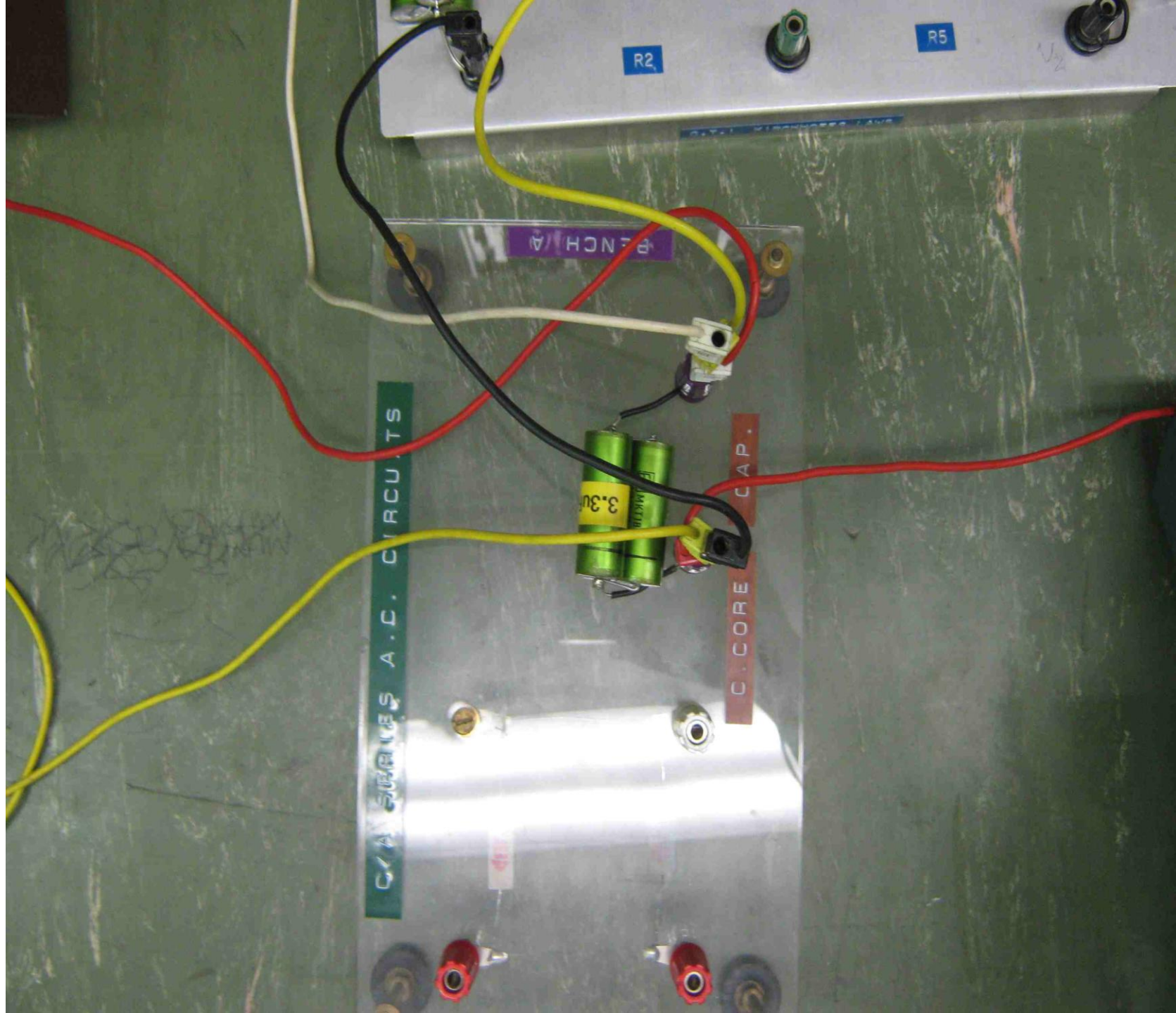

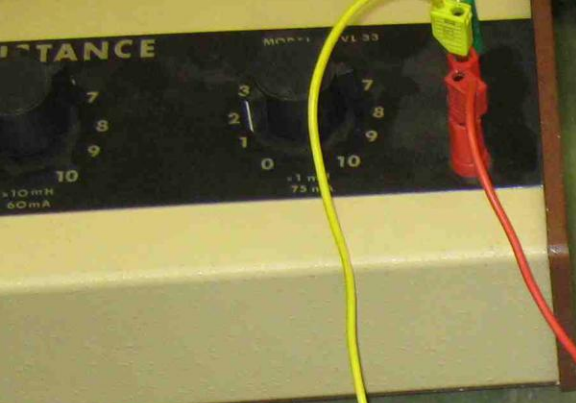

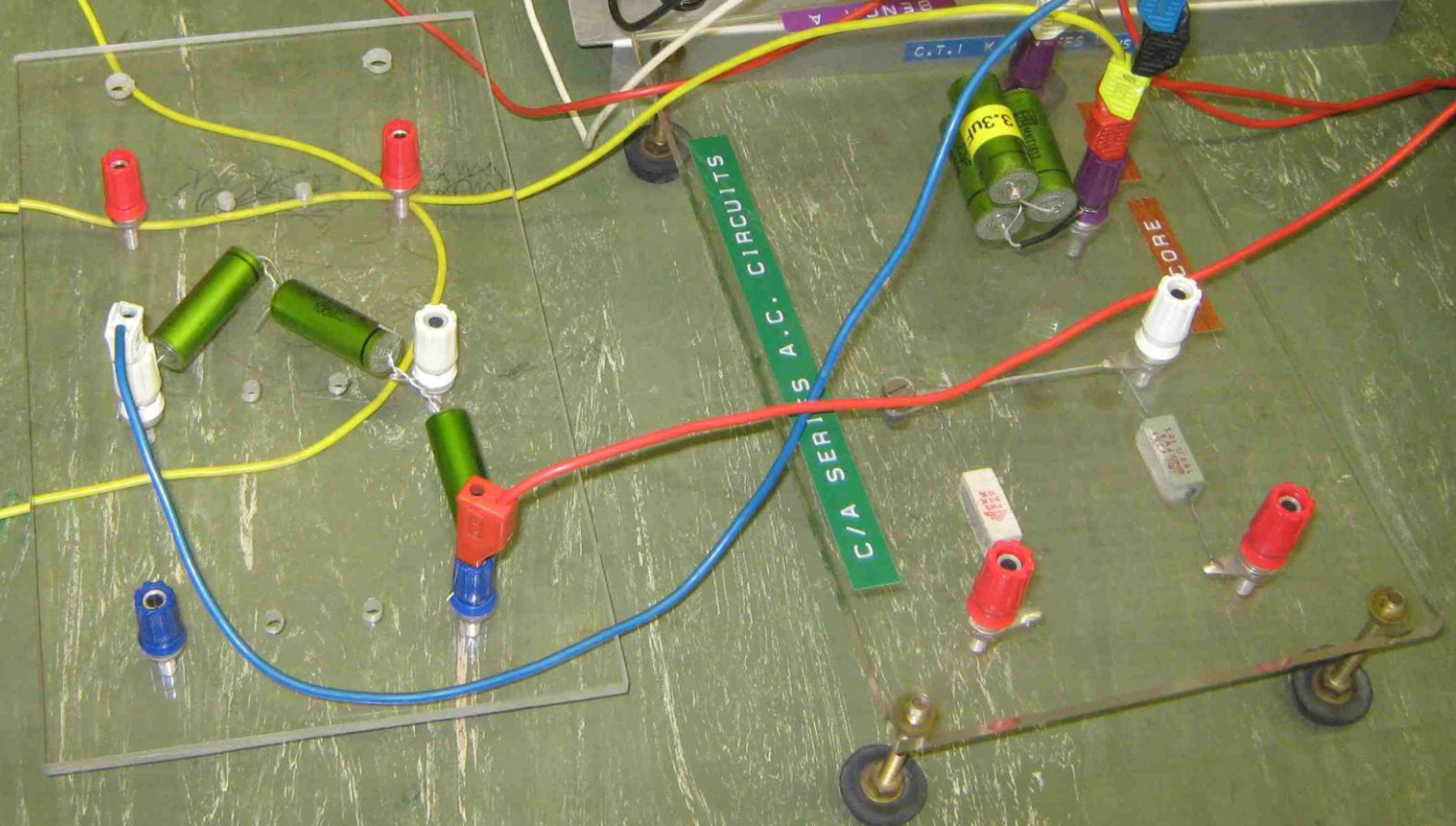HOW TO USE THE  
METER  
FOR MEASURING  
RESISTANCE  
AND CAPACITANCE



CORE

100K

100K