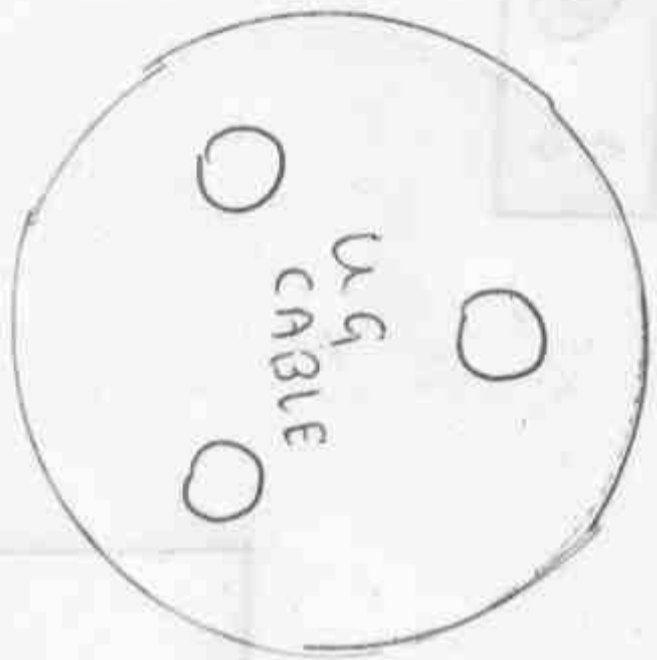



VARIC





PROT 21251



UG  
CABLE

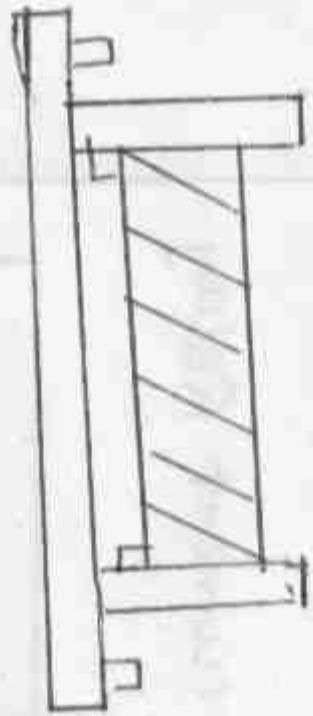

RESISTOR

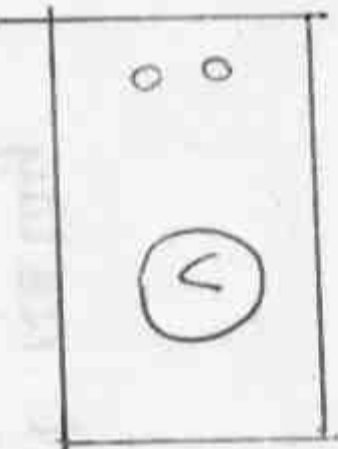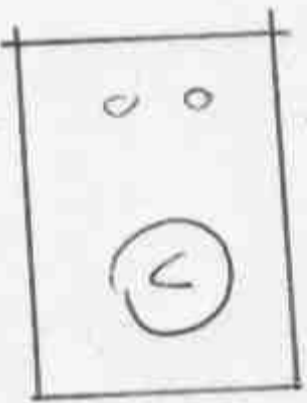

④ / ⑧ U.G. CABLE CAPACITANCE TEST.



2500 V



④ / ②

# ELECTRICAL DISTRIBUTION PRACTICAL (4)

UG CABLE

## UNDERGROUND CABLE CAPACITANCE TEST


(1) STUDY THE GIVEN CALCULATION

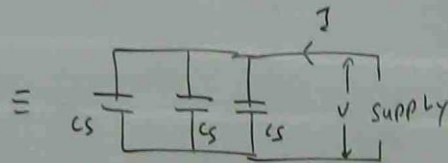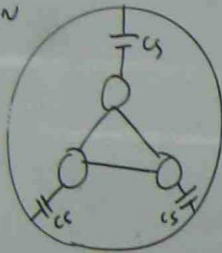

$$X_{C1} = \frac{U}{I}$$

$$3C_s = \frac{1}{2\pi f X_{C1}}$$
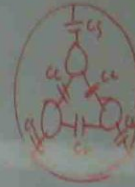
$$C_s = \frac{1}{3 \times 2\pi f X_{C1}}$$



$C_c$  = CAPACITANCE BETWEEN CONDUCTORS

$C_s$  = CAPACITANCE BETWEEN CONDUCTOR & SHEATH

APPLY  $V_1 = 80V$ , SET RHEOSTAT =  $20\Omega$

MEASURE  $V_2$

$$V = V_1 - V_2$$


$$I = \frac{V_2}{\text{Rheostat (R)}}$$

$$X_{C1} = \frac{V_1 - V_2}{\frac{V_2}{\text{Rheostat (R)}}}$$


$$C_s = \frac{1}{3 \times 2\pi f X_{C1}}$$

$$= \text{MF}$$

(2) CONNECT THE GIVEN CIRCUIT

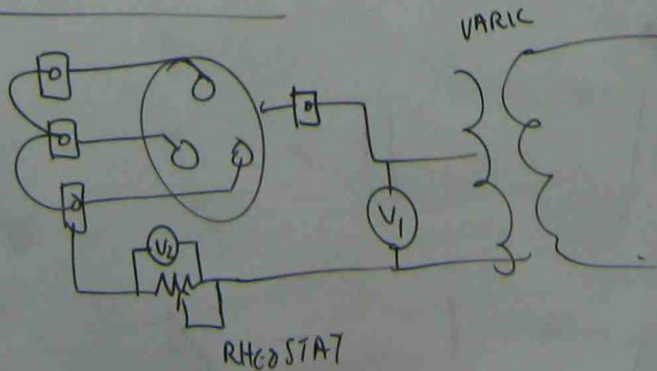

(3) STUDY THE GIVEN CALCULATION

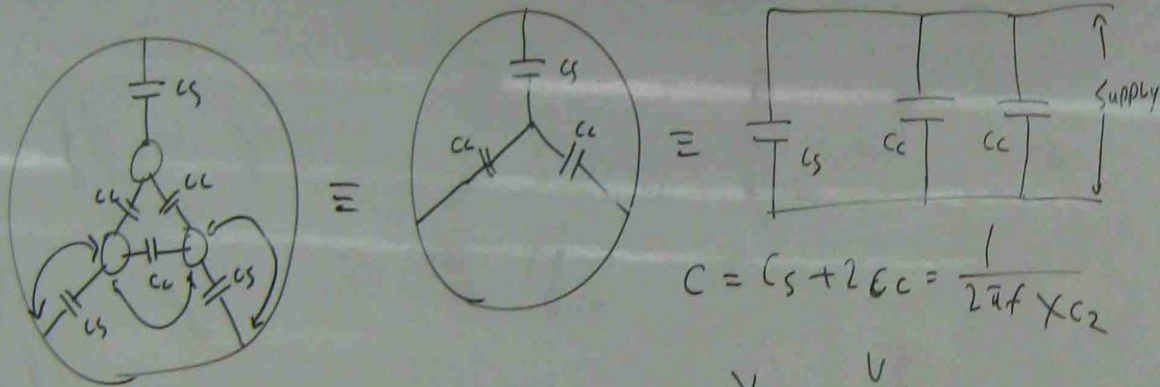

$$C = C_s + 2C_c = \frac{1}{2\pi f X_{C2}}$$

$$X_{C2} = \frac{V}{I}$$

SET  $V_1 = 80V$


$$X_{C2} = \frac{V_1 - V_2}{I}$$

$$X_{C2} = \frac{V_1 - V_2}{V_2 \text{ Rheostat (R)}}$$

$$C_s + 2C_c = \frac{1}{2\pi f X_{C2}}$$

THEN CALCULATE  $C_c$

CONNECT THE GIVEN CIRCUIT

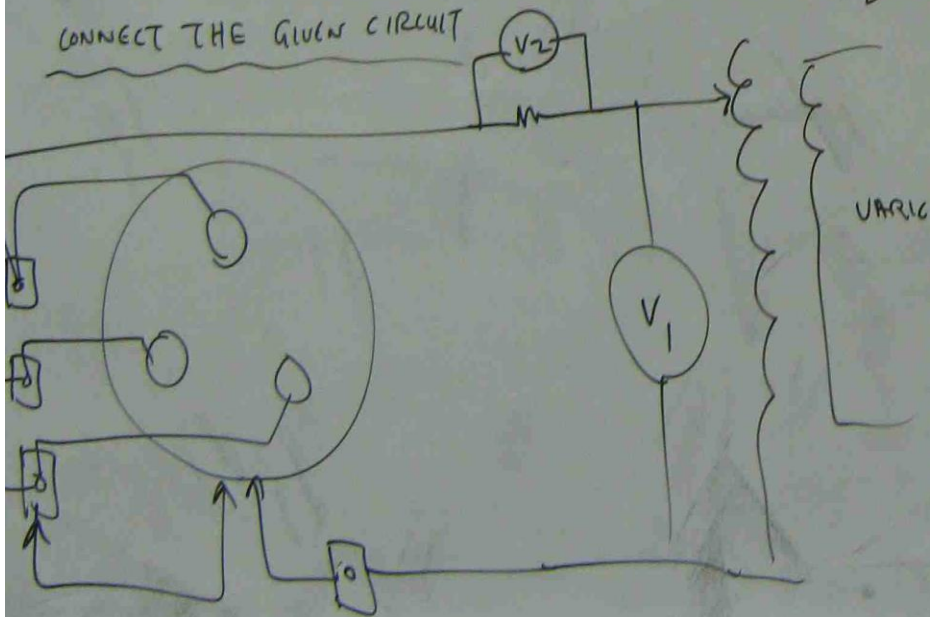

(2) CONNEC

