

TECHNOLOGICAL UNIVERSITY (THANLYIN)



နည်းပညာတက္ကသိုလ် (သန်လျင်)



Exercise Book

Name : IQY TECHNICAL COLLEGE
Roll No : ELECTRICAL TRADES COLLEGE
Subject : FINANCE 1

Vision

To become internationally recognized, high-ranking university that educates highly qualified engineers and architects in building the nation towards the development of Myanmar.

Mission

To contribute to the development of our nation and society through the pursuit of engineering education with high international standing and training the human resource developments for local needs

Motto

"Our Technology to develop our Nation"

2016 Target

- ASEAN University Network & AUN-QA Program Level 4 အသိအမှတ်ပြု AUN Certified University
- Engineering Education Accredited University (MEngC) & Engineering Education Accredited University အသိအမှတ်ပြု
- ISO 9001:2008 (Quality Management System) Certified University အသိအမှတ်ပြု
- ISO Standard အသိအမှတ်ပြု (Continual Improvement) အသိအမှတ်ပြု



I Q Y

Date: 6th August, 2018

After renovation,

Advance Diploma - Ks 500,000
 Professional - Ks 600,000




Advance Diploma - Ks 500,000 - 10%
 to H/c for renovation

Professional Diploma - Ks 600,000
 * Ks 100,000 out of Ks 600,000
 to our H/c for renovation


- CL0044 ✓
- EL0020
- EL0008 ✓
- EL0029 ✓
- EL0010 ✓
- EL0019
- EL0021 ✓



Date: _____

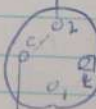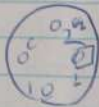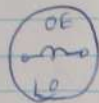

REP

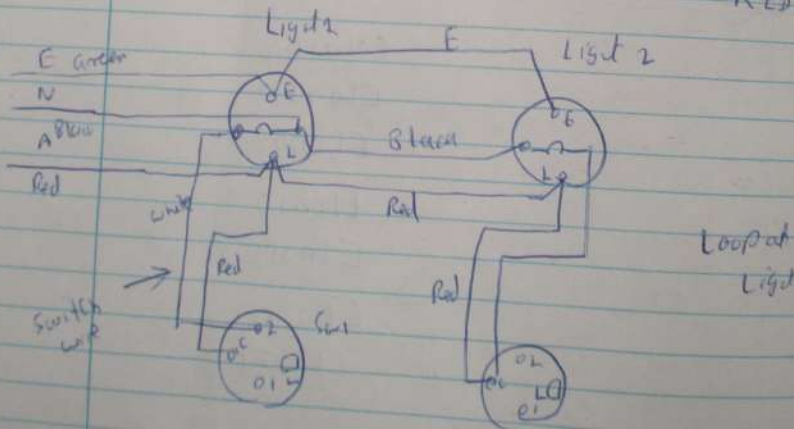


IPEM
Institution of
Engineers

Managing Director
President


Secretary
& Executive

Treasurer
Treasurers

Board of Directors

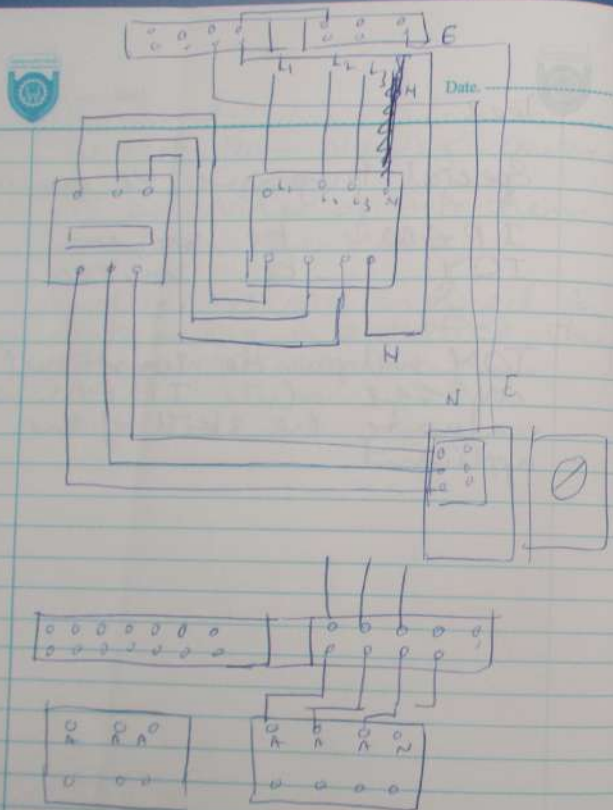

C00044+46
Date _____

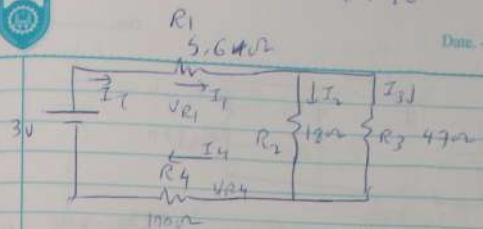

$$R_{23} = \frac{18 \times 47}{18 + 47} = \frac{846}{65} = 12.9 \approx 13$$

$$R_T = R_1 + R_{23} + R_4 = 5.6 + 13 + 100 = 118.6 \approx 118.9$$

$$I_T = \frac{V}{R_T} = \frac{3}{118.9} = 0.025 \text{ Amp}$$

$$I_T = 0.025 \text{ Amp}, I_1 = 0.025 \text{ Amp}, I_4 = 0.025 \text{ Amp}$$

$$V_{R1} = I_1 R_1 = 0.025 \times 5.6 = 0.14 \text{ V}$$

$$V_{R4} = I_4 R_4 = 0.025 \times 100 = 2.5 \text{ V}$$


$$V_{R2/R3} = V_T - (V_{R1} + V_{R4}) = 3 - (0.14 + 2.5) = 3 - 2.64 = 0.36 \text{ V}$$

$$I_2 = \frac{V_{R2}}{R_2} = \frac{0.36}{18} = 0.02 \text{ Amp}$$

$$I_3 = \frac{V_{R3}}{R_3} = \frac{0.36}{47} = 0.0077 \text{ Amp}$$



Date: _____

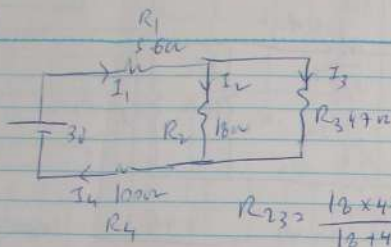

$$R_{23} = \frac{16 \times 47}{16 + 47} = \frac{846}{63} = 13.01 \Omega$$

$$R_T = R_1 + R_{23} + R_4 = 5.6 + 13.01 + 100 = 118.6 \Omega$$

$$I_T = I_1 = I_4 = \frac{3}{118.6} = 0.0252 \text{ A}$$

$$I_T = 0.0252 \text{ A} \quad \frac{41}{55}$$

$$V_{R1} = I_T R_1 = 0.0252 \times 5.6 = 0.1416 \text{ A}\cdot\text{V}$$

$$V_{R4} = I_T R_4 = 0.0252 \times 100 = 2.52 \text{ V}$$

$$V_{R23} = V_T - (V_{R1} + V_{R4})$$





$$= 3 - (0.1416 + 2.52) = 3 - (2.66) = 0.3384 \text{ V}$$

$$I_{R2} = \frac{V_{R23}}{R_2} = \frac{0.3384}{16} = 0.0188 \text{ A}$$

$$I_{R3} = \frac{V_{R23}}{R_3} = \frac{0.3384}{47} = 0.0072 \text{ A}$$



Date: _____

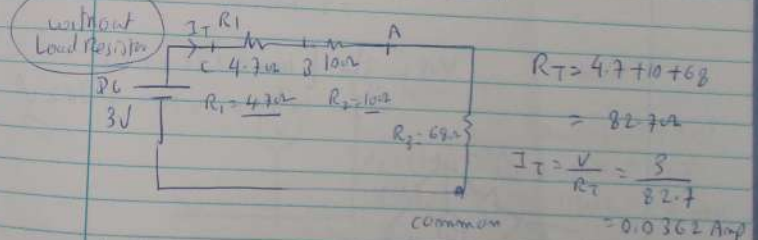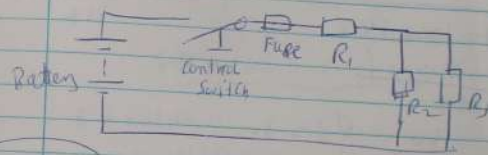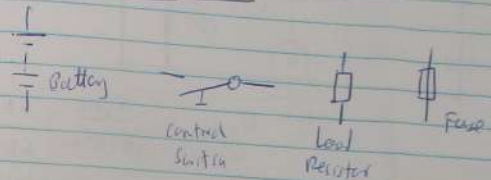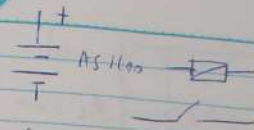

$$R_T = 4.7 + 10 + 68 = 82.7 \Omega$$


$$I_T = \frac{V}{R_T} = \frac{3}{82.7} = 0.0362 \text{ A}$$

Voltage at C = 3V

$$\text{voltage at B} = 3V - I_T [I_T \times R_1] = 3 - 0.0362 \times 4.7 = 2.8298 \text{ V}$$

$$\text{voltage at A} = 3 - I_T [R_1 + R_2] = 3 - 0.0362 [10 + 4.7] = 3 - 0.0362 \times 14.7 = 2.467 \text{ V}$$

Date: _____

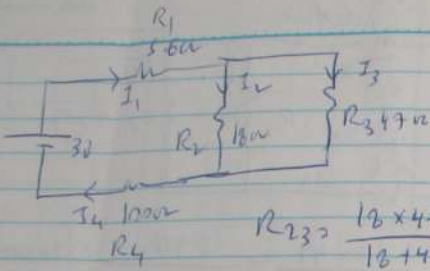

$$R_{23} = \frac{18 \times 47}{18 + 47} = \frac{846}{65} = 13.01 \Omega$$

$$R_T = R_1 + R_{23} + R_4 = 5.6 + 13.01 + 100 = 118.6 \Omega$$

$$I_T = I_1 = I_4 = \frac{3}{118.6} = 0.0252 \text{ Amp}$$

$$V_{R1} = I_1 R_1 = 0.0252 \times 5.6 = 0.1416 \text{ AmV}$$

$$V_{R4} = I_4 R_4 = 0.0252 \times 100 = 2.52 \text{ V}$$




$$V_{R23} = V_T - (V_{R1} + V_{R4}) = 3 - (0.1416 + 2.52) = 3 - (2.66) = 0.3384 \text{ V}$$

$$I_2 = \frac{V_{R23}}{R_2} = \frac{0.3384}{18} = 0.0188 \text{ A}$$

$$I_3 = \frac{V_{R23}}{R_3} = \frac{0.3384}{47} = 0.0072 \text{ A}$$



Date: _____

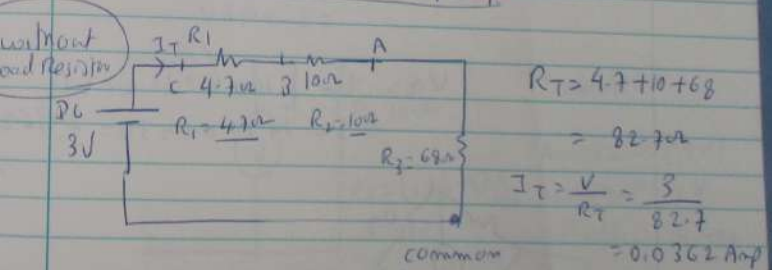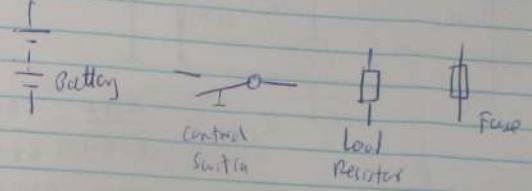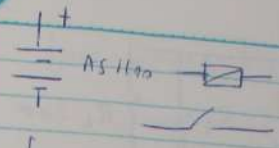

$$R_T = 4.7 + 10 + 68 = 82.7 \Omega$$

$$I_T = \frac{V}{R_T} = \frac{3}{82.7} = 0.0362 \text{ Amp}$$

Voltage at c = 3V


$$\text{voltage at B} = 3V - I_T [I_T \times R_1] = 3 - 0.0362 \times 4.7 = 2.8298 \text{ V}$$

$$\text{voltage at A} = 3 - I_T [R_1 + R_2] = 3 - 0.0362 [4.7 + 10] = 3 - 0.362 \times 14.7 = 2.467 \text{ V}$$



With load resistor

Date: _____

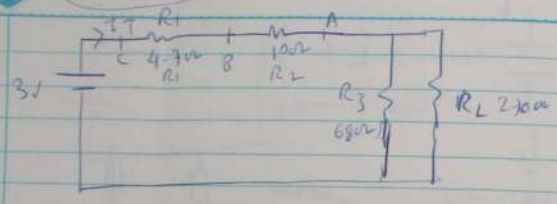


$$R_3 \parallel R_L = \frac{R_3 R_L}{R_3 + R_L} = \frac{68 \times 2000}{68 + 2000} = \frac{68 \times 2000}{339} = 54.3 \Omega$$

$$I_T = \frac{3}{4.7 \times 10^3 + 54.3} = \frac{3}{69} = 0.0434 \text{ mA}$$

$$V_C = 3V, \quad V_B = 3 - 0.0434 \times 4.7 = 2.796V$$
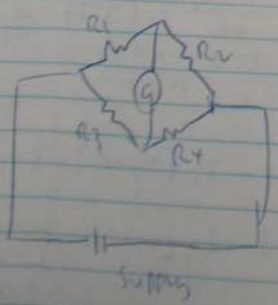
$$V_A = 3 - [10 + 4.7] \times 0.0434 = 3 - 14.7 \times 0.0434 = 2.362V$$




$$\frac{10.5 \times 1050}{11050} =$$





Date: _____


Low resistance

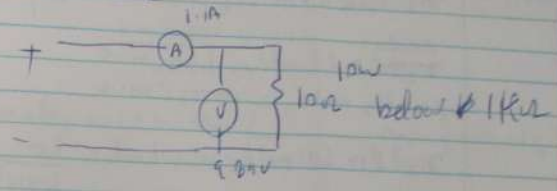

High Resistance

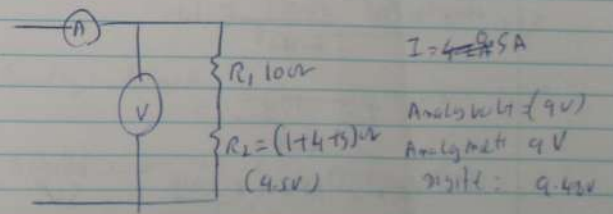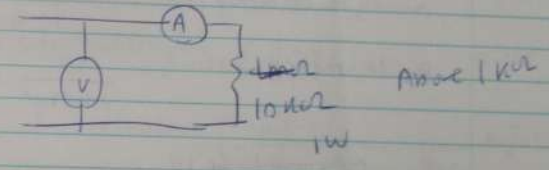

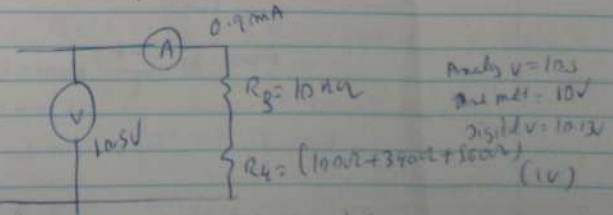$I = 4 \text{ mA}$
 Analy with 9V
 Analy with 9V
 digit: 9.42V



Analy V = 10V
 Anal met = 10V
 digit V = 10.1V
 (1V)

$$\frac{1050}{10500 + 1050} \times 10.5 = 0.99V = 1V$$



Sensitivity value of

Date: _____

Digital C.M.S.S. = 30kΩ / 20V f.s.d

Analog multimeter 1.005mA 50V f.s.d
Analog meter = 0.05C.M.S.

$$\text{Digital multimeter sensitivity} = \frac{20}{30 \times 10^3} \text{ V/}\Omega$$

$$\text{Analog multimeter sensitivity} = \frac{50}{100000} \text{ V/}\Omega$$

$$\text{Analog meter sensitivity} = \frac{30}{0.05 \times 1000} \text{ V/}\Omega$$

R_x measured 4.5V

$$\text{Sensitivity} = \frac{20}{30 \times 10^3} \times 10$$

$$I = \frac{10V}{20k\Omega} =$$

$$V_{R_x} = 10 \times \frac{4.5}{20k\Omega} = 5V$$

$$\text{Error} = \frac{5-4.5}{5} \times 100 = 0.5 \times 100 = 10\%$$



Date: _____

$$\frac{10.5}{10.5 + 10} \times 100 = 51.19\% \quad \frac{10.5}{11050} \times 100 = 0.949\%$$

① Analog volt meter = $\left(\frac{9}{10+10} \text{ mA} \right) \times 10 = 4.5V$

Analog multimeter = $\left(\frac{9}{10+10} \text{ mA} \right) \times 10 = 4.5V$

Digital multimeter = $\left(\frac{9.43A}{k\Omega} \right) \times 10 = 4.91V$

② Analog Voltmeter = $\left(\frac{10.5}{10000 + 1050} \text{ A} \right) \times 10000$
 $= \frac{10.5 \times 10000}{11050} = 1V$

Analog multimeter = $\frac{10}{11050} \times 10000 = 0.95V$

Digital = $\frac{10.13}{11050} \times 10000 = 0.962V$

③ $C = \frac{A_{eff} \cdot \epsilon_0 \cdot \epsilon_r}{d}$ For $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$
 $\epsilon_r = 1$

$C = 2.01 \times 10^{-6} \text{ F}$ $A_{eff} = 30 \times 10^{-3} \times 20 \times 10^{-3}$

$d = 0.0001 \text{ m}$ $\epsilon_r = 7$

$A_{eff} = \frac{C \cdot d}{\epsilon_0 \cdot \epsilon_r} = \frac{0.01 \times 10^{-6} \times 0.0001}{8.85 \times 10^{-12} \times 7}$

$A_{eff} = A(N-1)$

N = total number of parallel plate

$$A_{eff} = \frac{0.01 \times 10^{-6} \times 0.08 \times 10^{-3} \times 10^{12}}{8.85 \times 7}$$

$$= \frac{0.01 \times 0.08 \times 10^3}{8.85 \times 7} = 0.0129$$

$$A_{eff} = A(N-1)$$

$$0.0129 = 80 \times 10^{-3} \times 20 \times 10^{-3} (N-1)$$

$$0.0129 = 600 \times 10^{-6} (N-1)$$

$$N = \frac{0.0129}{600 \times 10^{-6}} + 1 = 22 + 1 = 23$$

①

$$C_1 \ Q = VC = 1.5 \times 6.8 = 10.2 \mu C$$

$$C_2 \ Q = VC = 1.3 \times 1 = 1.3 \mu C$$

$$C_3 \ Q = VC = 0.3 \times 47 = 14.1 \mu C$$

$$C_1 \ Q = VC = 3.08 \times 6.8 = 20.94 \mu C$$

$$C_2 \ Q = VC = 3.09 \times 1 = 3.09 \mu C$$

$$C_3 \ Q = VC = 3.09 \times 1 = 3.09 \mu C$$

$$L = RC = 23 = R \times 47 \times 10^{-6}$$


$$R = \frac{2.3 \times 10^6}{47}$$

$$L = RC \rightarrow 202 = R \times 47 \times 10^{-6}$$

$$R = \frac{202 \times 10^6}{47}$$

Table 2 A current down curve
 at 237 sec, 63% of supply voltage current 2.97A
 $R = \frac{V}{I} = \frac{1.9}{2.97 \times 10^{-6}} = \frac{1.9}{2.97 \times 10^{-6}} = 0.639 \text{ m}\Omega$

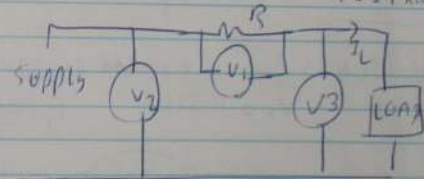At voltage built up curve
 at 337 sec 63% of supply voltage obtained
 (and value is) 1.034mA
 $\therefore R = \frac{V}{I} = \frac{1.9}{1.034 \times 10^{-6}} = 1.83 \text{ m}\Omega$



$$P_L = V_3 I_L \cos \phi$$

$$V_1 = I_L R$$

$$V_2 = \sqrt{V_1^2 + V_3^2 + 2V_1 V_3 \cos \phi}$$

$$V_2 = \sqrt{V_1^2 + V_3^2 + 2(I_L R) V_3 \cos \phi}$$

$$V_2^2 = V_1^2 + V_3^2 + 2R P_L$$

$$\therefore P_L = \frac{V_2^2 - V_1^2 - V_3^2}{2R}$$

E L 00 20


34 Power
 3 PL (Real)
 APPARENT
 $I_L^2 R$
 $P_t = \frac{P_{app}}{P_{real}} = \frac{I_L^2 R}{P_{real}}$



Date: _____

meter reads X

CONNECTION

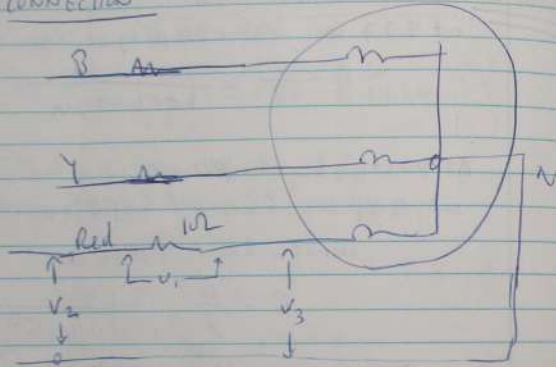

P1

$$v_2 = 24.55V \quad v_3 = 24.37V$$

$$v_1 = 0.335V$$

$$P_1 = \frac{24.55^2 - 0.335^2}{2 \times 1} = 4.34W$$

P2

$$P_2 = \frac{24.3^2 - 0.304^2}{2 \times 1} = 2.26W$$

$$v_2 = 24.3V \quad v_3 = 24.18V$$

$$v_1 = 0.304V$$

P3

$$P_3 = \frac{24.4^2 - 0.324^2}{2 \times 1} = 1.97W$$

$$v_2 = 24.4V \quad v_3 = 24.32V$$

$$v_1 = 0.324V$$



Date: _____

Total Power = $P_1 + P_2 + P_3 = 4.34 + 2.26 + 1.97 = 6.645W$

Avg = $I_1 = \frac{0.335V}{10\Omega} = 0.335A$

$I_3 = \frac{0.328}{10\Omega} = 0.328A$

$I_2 = \frac{0.304}{10\Omega} = 0.304A$

$I_{L,avg} = \frac{0.335 + 0.328 + 0.304}{3} = 0.322A$

$\sqrt{3} E_L I_L \cos\phi = 3\phi \text{ Power}$

$1.7321 \times 42.5 \cos\phi = 6.645$

$\cos\phi = PF = \frac{6.645}{1.7321 \times 42.5 \times 0.322} = 0.28$

$\int_0^{\pi} 42.3 \sin\theta \times 0.335$

$+ \int_0^{\pi} 42.3 \sin\theta \times 0.304$

$+ \int_0^{\pi} 42.3 \sin\theta \times 0.328$


$N_F = 23.96VA$

$PT = 4.34 + 2.26 + 1.97$


$= 6.645$

$PF = \frac{6.645}{23.96}$

$= 0.28$

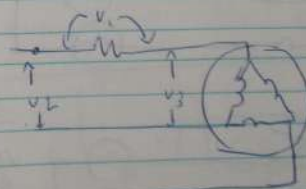

meter PF correct

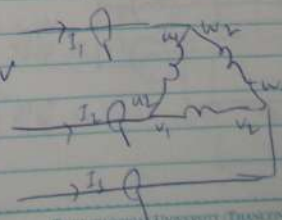

42V Y-B

42V R-Y

42V B-R

$I_2 = 1.60A$ | $I_3 = 0.8$

$I_4 = 1.60A$ | $I_1 = 0.8$




TECHNOLOGICAL UNIVERSITY (TUM)

Apparent power = $\sqrt{3} E_L I_L = 1.732 \times 42.3 \times 0.8 \times$
 $= 58.6$

TRAF = 16.37

Date: 16/37
 PF = 16.37

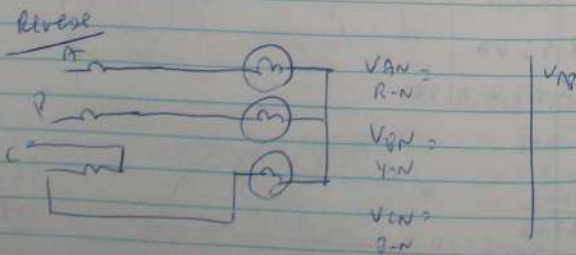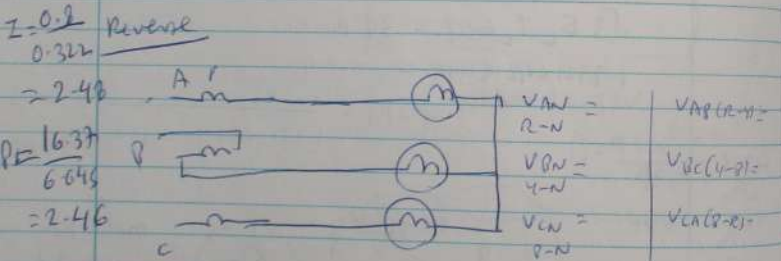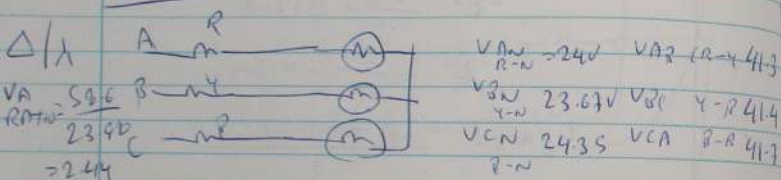
$\left(\frac{42.3}{\sqrt{3}} + \frac{42.3}{\sqrt{3}} + \frac{42}{\sqrt{3}} \right) 0.8 \text{ Power} = \sqrt{3} E_L I_L \cos \phi$
 $= 1.732 \times 42.3 \times 0.8 \times 0.28$
 $= 16.4 \text{ W}$




NORMAL

4/2/24

Date

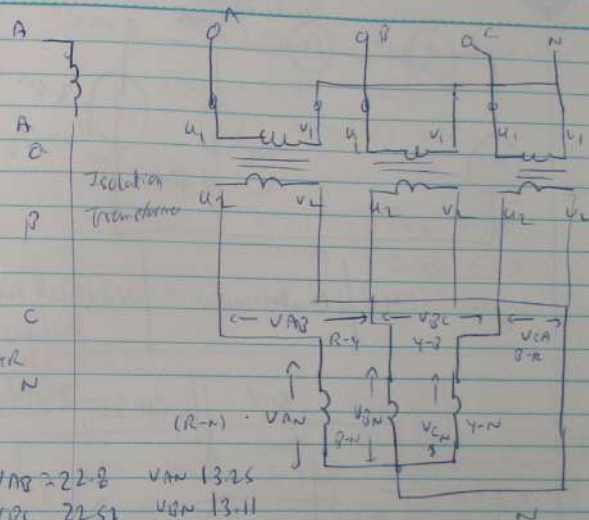

REVERSE

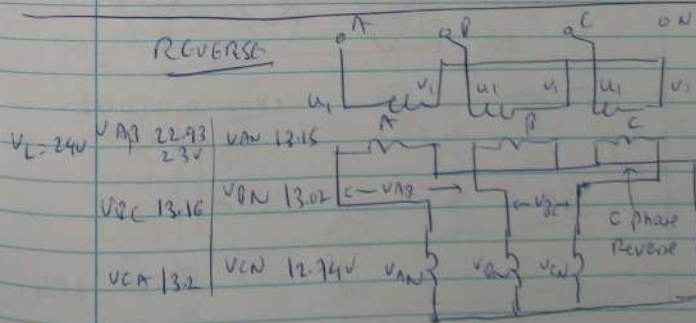

CONCLUSION: If supply polarity reverse


it can affect the output voltage



Date: _____


9.134V
5.8uA

$R_1 = 21 \Omega$

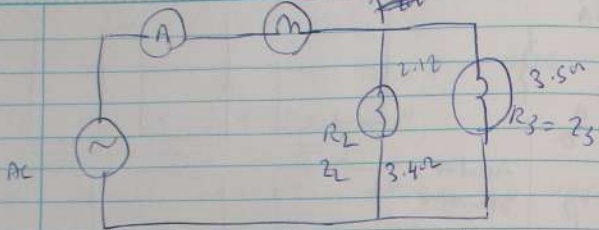

3.4V / main menu | vertical scale
50V/div

30V // CH1 = digital U = 30.4V

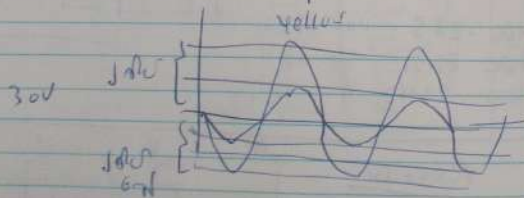

24V

$$\frac{12}{50} \sqrt{300} \approx 0.4$$



Date: _____



3.1

Table 1

AC	$I_T = 1.15A$	$I_{R_3} = 0.59A$
	$I_{R_1} = 1.15A$	$I_{R_2} = 0.62A$
	$V = 24V = 12V$	

Table 2 DC


	$V_T = 12V$
	$I_T = 1A$ $I_{R_1} = 0.50A$
	$I_{R_2} = 1A$ $I_{R_3} = 0.6A$
	$V_{R_1} = 9V$ $V_{R_2} = 3V$ $V_{R_3} = 3V$

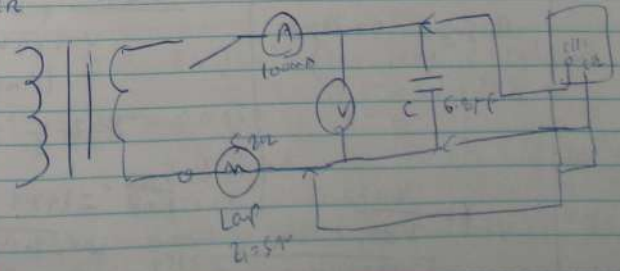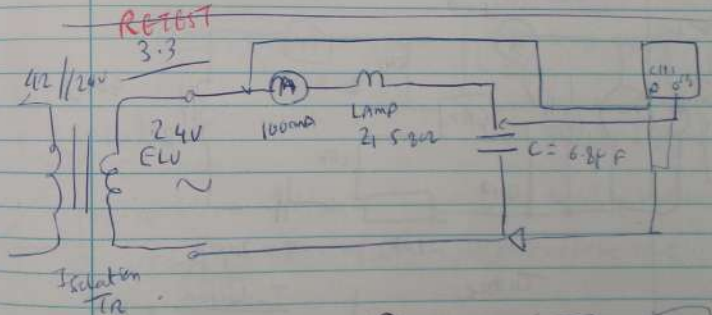



$$f \rightarrow 100\text{Hz} \quad X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 100 \times 1000}$$

Date: 21.08.2016
 Group: 23402

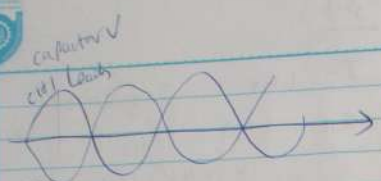

CH1 = 10V/div
 CH2 = 10V/div
 V = 12V
 $X = Z \frac{V}{I} = \frac{12}{34 \times 10^{-3}} = 352.9 \quad I = 34\text{mA}$

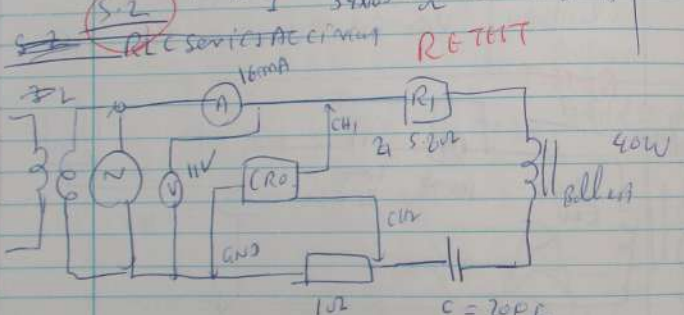


Table	Inductor
$R = 5.2 \Omega$	$q = 2R$
$C = 20\text{pF}$	$V = 5.49\text{V}$
$V_C =$	$I = 16\text{mA}$
$X_C = \frac{1}{2\pi f C}$	$X = Z \frac{V}{I} \quad X = \sqrt{Z^2 - R^2}$
$= \frac{1}{2 \times 3.14 \times 100 \times 20 \times 10^{-12}} = 159$	$Z = \frac{5.49}{16 \times 10^{-3}} = 343 \Omega$
	$X = \sqrt{343^2 - 9.2} = 342.22 \Omega$
	$L = \frac{342.22}{2\pi \times 100} = 1.09\text{mH}$



$$V_{\text{eff}} = \frac{V_{\text{eff}} Z}{1000} = \text{Table 41}$$

$$= \frac{2.55 \times 75 \times 60}{1000} = 11.475\text{V}$$

Table (2)

$X_L = V = 5.49\text{V} \quad Z = \frac{V}{I} \quad X = \sqrt{Z^2 - R^2}$
 $R = 9.2 \quad I = 16\text{mA}$
 $X_C = V = 10.85\text{V} \quad X = \frac{V}{I} \quad X_C = \frac{1}{2\pi f C}$
 $f = 50.2\text{Hz} \quad I = 16\text{mA} \quad C = \frac{1}{2\pi f X_C}$
 $\phi_L =$
 circuit $Z = \frac{12\text{V}}{16\text{mA}} \quad \phi =$

Table	measured
Supply $V = 14\text{V}$	$V_R = 0.32\text{V}$
$I = 16\text{mA}$	5.8mA
	$V_C = 10.92\text{V}$ (Capacitor)
	$V_L = 5.51\text{V}$ (Inductor)

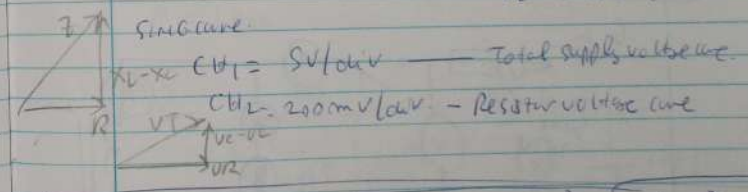


Table 34

$$V = 12\text{V} \quad Z = \sqrt{5.2^2 + (343 - 159)^2} = \sqrt{5.2^2 + 184^2} = 184 \Omega$$

$$I = \frac{12}{184} = 0.0652 = 65.2\text{mA}$$


$$\phi = \tan^{-1} \frac{184}{5.2} = 88.19^\circ$$

Table 34	
$V_R = 0.0652 \times 9.2 = 0.594\text{V}$	
$V_C = 0.0652 \times 159 = 10.3\text{V}$	
$V_L = 0.0652 \times 343 = 22.36\text{V}$	
$X_{90} = 9.06$	
$16\text{mm} \times 1.47\text{mm} \rightarrow 1.47\text{mm}$	



Date: _____

3-2

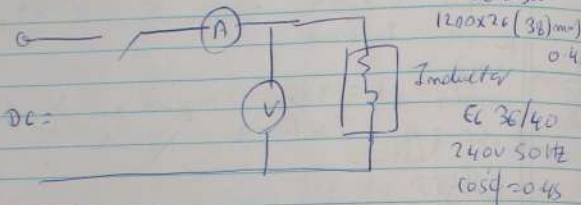


DC: 12-3V Supply
 $A_1 = 3.30-3.3A$
 $V = 12V$
 AC: $V = 24V$ Supply = 24.6V
 $I = 62mA$


Inductor
 $E_L = 36/40$
 $240V 50Hz$
 $\cos\phi = 0.45$

Power 3W
 $R = \frac{123}{0.33} = 372\Omega$
 $X = \sqrt{390^2 - 372^2} = 394\Omega$

6-2

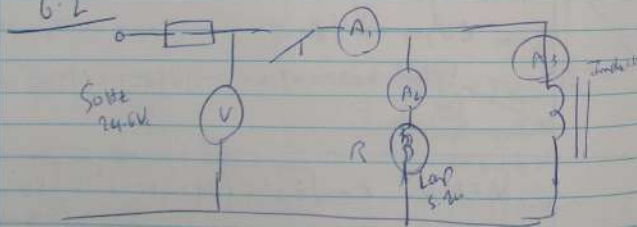

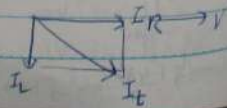24V
 $A_1 = 1.5A$
 $A_2 = 1.42$ Resistor
 $A_3 = 50mA$ Ind



$$Z_c = \frac{1}{\frac{1}{5.0} + \frac{1}{4.2} + \frac{1}{7.59 \cdot 23}} \times 24 = \frac{24}{50 \times 10^{-3}} = 480\Omega$$


$$X_c = \frac{24}{30 \times 10^{-6}} = 800\Omega$$

$$X = \sqrt{480^2 + 800^2} = 920\Omega$$

$$I = \frac{24}{920} = 26.1mA$$

~~RETEST~~

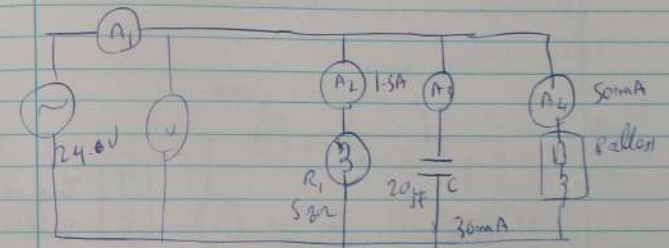$R = 5.8\Omega$ $C = 20\mu F$
 Ballast $q = R \cdot V = 5.4V$ $I = 10mA$
 $Z = \frac{V}{I} \rightarrow X = \sqrt{22} \cdot R$



$A_1 = 1.98A$

7-3


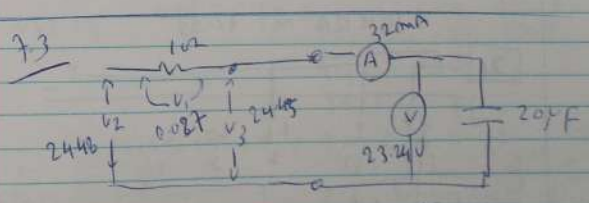
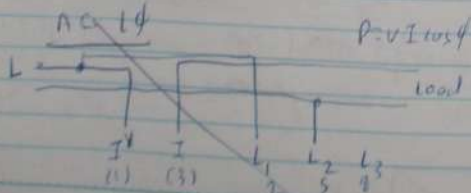
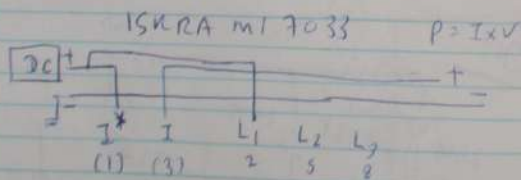
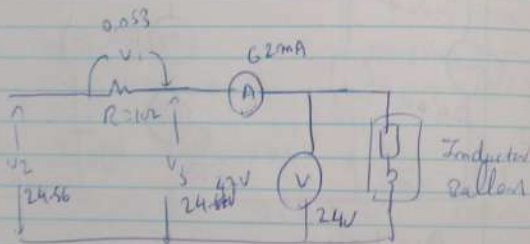


Fig (2)

$$\frac{1}{R} + \frac{1}{R} + \frac{1}{jX_c} = \frac{1}{Z}$$



$$= 5.8\Omega$$

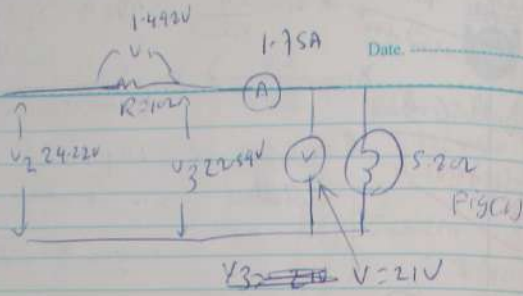

Technological University (TUM)



3φ AC $P = \sqrt{3} V I \cos \phi$

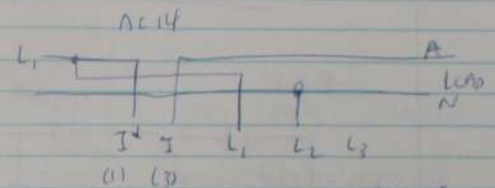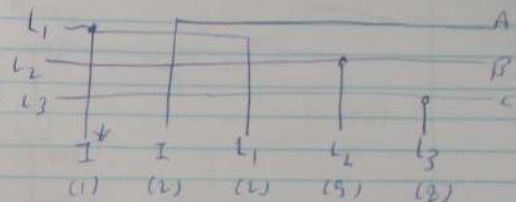


$V = 50$
 $n = 1$
 $\cos \phi$

$M \pm 7033$

$\cos \phi = 0.04$

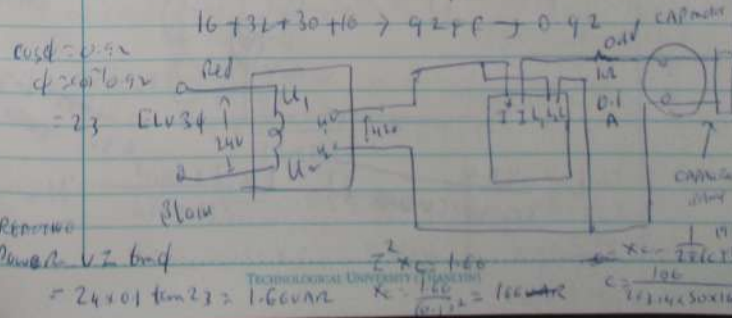$16 \mu F \rightarrow 0.55$
 $31 \mu F \rightarrow 0.5$
 $30 \mu F \rightarrow 0.5$



$$P_T = (60 \times 10^{-3})^2 \times 5.8 + \frac{(24.16^2 - 24^2 - 1.5^2)}{2 \times 5.8}$$

$$= 0.02 + 0.47 = 0.49 \text{ W}$$

2-3-2

$$V_A = 24.16 \times 60 \times 10^{-3} = 1.44 \text{ VA}$$

Fig 2)


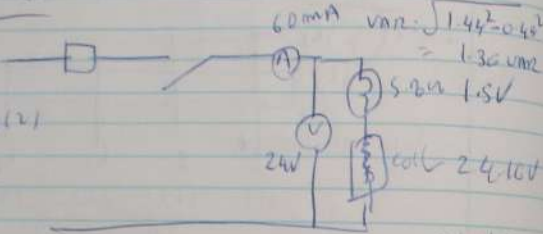



Fig 3)

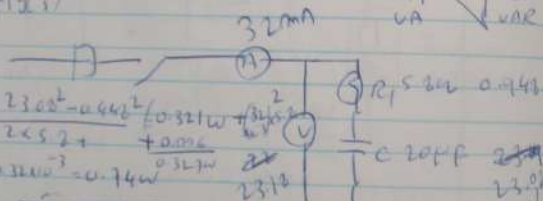

$$P = \frac{23.12^2 - 23.02^2 - 0.44^2}{2 \times 5.2} + \frac{0.321 \text{ W} + 0.006}{0.52 \text{ W}}$$




$$P = 23.12 \times 32 \times 10^{-3} = 0.74 \text{ W}$$

Fig 4)

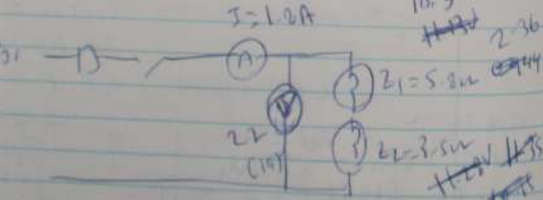

$$L = \frac{22.5}{2 \times 3.14 \times 50} = 0.0003$$
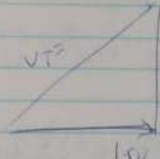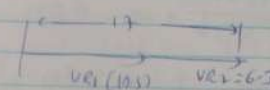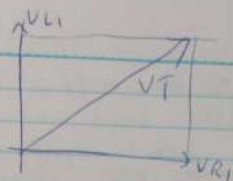
$$L = \frac{22.5 \times 10^{-3}}{2 \times 3.14 \times 50} = 716.1$$



$$V_T = \sqrt{24.16^2 + 1.5^2} = 24.17 \text{ V}$$

Risu

- over voltage supply 2 m use only 4V supply
- CR0 ground and CRT ground conduct m 8 use isolation to
- over voltage damage CRT component m 2 check voltage and power rating of CRT electron gun approx
- Electrolytic capacitor can be damaged by AC or long periods m 2 check capacitor

$$R_T = 5.8 + \frac{3.4 \times 3.5}{3.4 + 3.5} = 5.8 + 1.72 = 7.52$$

$$I_T = \frac{12}{7.52} = 1.59 \text{ A}$$

$$V_{R1} = 1.59 \times 5.2 = 9.25 \text{ V}$$

$$I_{R2} = \frac{V_{R2}}{R2} = \frac{12 - 9.25}{2.26} = 1.24$$

$$I_{R2} = \frac{2.14}{2.26} = 0.94$$

$$I_{R2} = \frac{2.14}{2.26} = 0.94$$



Date: _____

$$I_T = \frac{1.59 \times 1.23}{1.55} \times 100 = 27.7A$$

$$I_{R2} = \frac{0.6 - 0.22}{0.6} \times 100 = 2.5\%$$

$$I_{R3} = \frac{0.75 - 0.73}{0.75} \times 100 = 6.4\%$$

$$V_{R1} = \frac{9.255 - 9.234}{9.255} \times 100 = 0.77\%$$


$$V_{R2} = \frac{2.74 - 2.71}{2.74} \times 100 = 0.7\%$$

$$P_1 = 1.8 \times 123^2 = 277 \text{ W}$$

$$P_2 = 0.62 \times 3.4 = 1.308 \text{ W}$$

$$P_3 = 0.58^2 \times 3.5 = 1.174 \text{ W}$$

$\frac{1.7}{50}$

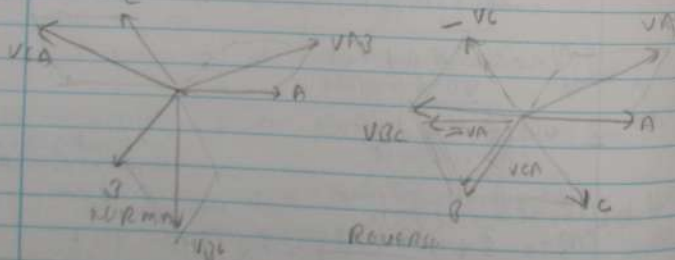

Date: _____

Ca Electric motor Education

CME (Aust) Pty Ltd

Serial no 1909-3528

model 71-3-L004

41.5VAC 44Watt 1.6A 136C RPM
34 Soltz

Insulation class F Connection External X/Δ


Italy made Type Am 712 BM

IEC 60034 3rd no 1994 4202

Insul Δ T(F) 1P5C S1 TCC 1A of 40C

Hz	Kw	V	A	min	cosφ
50	0.37	Δ 115	4.4	1370	0.67
		X 200	2.5		

Colour	Significant figure	multiply	Tolerance %
BLACK	0	x1	
BROWN	1	x10	1(F)
RED	2	x100	2(G)
ORANGE	3	x1K	
YELLOW	4	x10K	
GREEN	5	x100K	0.5(S)
BLUE	6	x1M	0.25(F)
VIOLET	7	x10M	0.1(G)
GREY	8	x100M	0.05(M)
WHITE	9	x1G(10 ⁹)	0.05(N)
Gold		x0.1	5
Silver		x0.01	

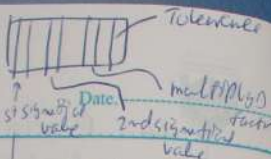

Resistor	Color 1	Color 2	Color 3	Color 4	Calculated Resistance	Measured Resistance	within tolerance
R1	Brown 1	Black 0	Blue 10	Gold 5%	$10 \times 10^1 = 100 \Omega$	99.5	NO
R2	Brown 1	Black 0	Brown 1	Gold 5%	$10 \times 10^0 = 10 \Omega$	9.95	YES
R3	Red 2	Red 2	Orange 100	Gold 5%	$22 \times 10^2 = 2200 \Omega$	2160	YES
R4	Brown 1	Black 0	Orange 100	Gold 5%	$10 \times 10^2 = 1000 \Omega$	995	YES
R5	Yellow 4	Blue 6	Red 100	Gold 5%	$46 \times 10^2 = 4600 \Omega$	4600	YES
R6	Brown 1	Black 0	Yellow 1000	Gold 5%	$10 \times 10^3 = 10000 \Omega$	9950	YES
R7	Red 2	Red 2	Gold 0.1	Gold 5%	$22 \times 0.1 = 2.2 \Omega$	2.16	YES
R8	Red 2	Red 2	Brown 10	Gold 5%	$22 \times 10 = 220 \Omega$	216	YES
R9	Orange 3	Orange 3	Brown 10	Gold 5%	$33 \times 10 = 330 \Omega$	324	YES
R10	Green 5	Blue 6	Brown 10	Gold 5%	$56 \times 10 = 560 \Omega$	557	YES
R11	Blue 6	Green 5	Brown 10	Gold 5%	$68 \times 10 = 680 \Omega$	674	YES
R12	Brown 1	Black 0	Black 1	Gold 5%	$10 \times 1 = 10 \Omega$	10.2	YES



Resistor	Resistance	Calculated Tolerance	Resistance Range	Measured Resistance	within tolerance
R6	100 ohm	±5%	95 ohm - 105 ohm	99.5 ohm	YES
R7	2.2 ohm	±5%	2.09 ohm - 2.31 ohm	2.16 ohm	YES
R8	220 ohm	±5%	209 ohm - 231 ohm	216 ohm	YES
R9	330 ohm	±5%	313.5 ohm - 346.5 ohm	324 ohm	YES
R10	560 ohm	±5%	532 ohm - 588 ohm	557 ohm	YES
R11	680 ohm	±5%	646 ohm - 714 ohm	674 ohm	YES
R12	10 ohm	±5%	9.5 ohm - 10.5 ohm	10.2 ohm	YES

7.3 NTC
<https://www.thinksrs.com/downloads/programs/thermcalc/>

NTC model calculator/ntccalculator.htm

Table 7.3	Room Temp	Temp setting	Temp setting 2
NTC	25°C	3°C	50°C
NTC	100 ohm	632 ohm	2170 ohm
NTC	109.93 ohm	113.6 ohm	119.34 ohm

TECHNOLOGICAL UNIVERSITY, TIANJIN
<http://www.knowledgelab.com/ntc-thermistor-calculator/>

PTC

<https://us.fluxcal.com/pt100-calculator>

Date: _____

LDR Resistance measurement

<https://dcaclab.com/experiments/53771-ldr-simulat>

logit 2mA
 100
 15V 15A
 15V 15A

$$S.G = \frac{6.8 \times C}{6.8 + C} \rightarrow 38.08 + 5.6C = 6.8C$$




$$(6.8 - 5.6)C = 38.08$$

$$C = \frac{38.08}{1.2} = 31.74F$$

To achieve 5.6pf ?


$$\frac{6.8 \times 47}{6.8 + 47} = \frac{3196}{115} = 27.79F$$
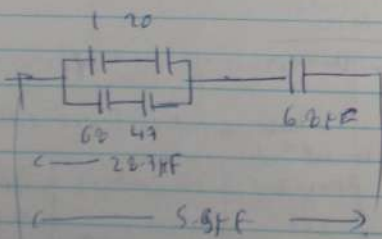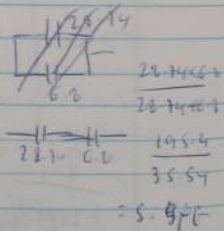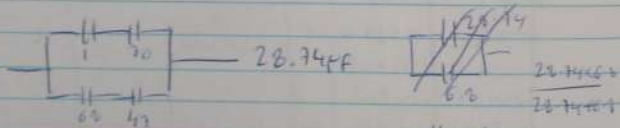
$$\frac{1 \times 20}{1 + 20} \rightarrow 0.95F$$




2.3.2 Fig(3)

Date: _____

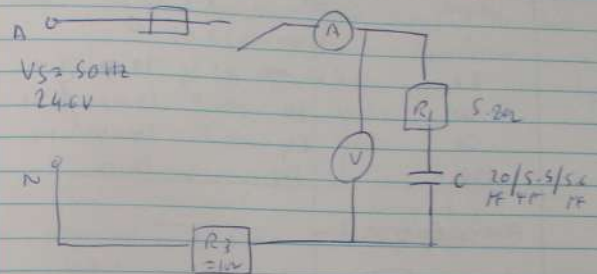

C	Current	VT	VR	VC	φ
20PF	320mA	23.12V	0.95	23.02	87°
5.5PF	460mA	24.6V	0.105	24.49	20.7°
5.6 PF					

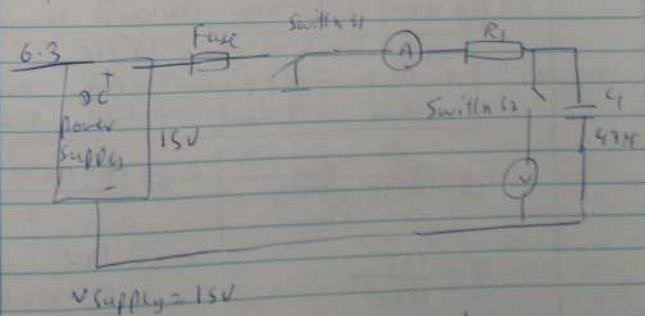

V supply = 15V
 Voltmeter disconnected, Charge capacitor → discharge
 voltmeter connected, Charge capacitor → discharge



Date: _____

Time second	Current mA	voltage volt
0	26.0	0
20	66	13.97
40	76	13.97
60	64	14.04
120	54	14.12

Average (charging) time

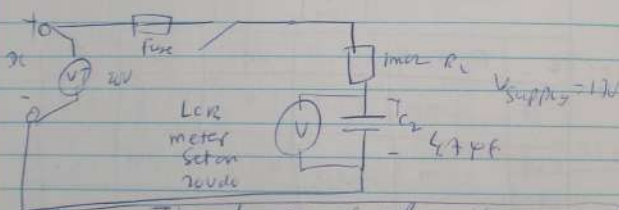


Table 6.2	Time to reach supply voltage			
	Trial 1	Trial 2	Trial 3	Average
	12-14 sec	12-14 sec	12-14 sec	12-14

Table 6.3	63% of supply voltage = 12.6V			
	Trial 1	Trial 2	Trial 3	Average
	4-6 sec	4-6 sec	4-6 sec	4-6 sec

$$R_{avg} = \frac{V_{avg}}{I_{avg}} \quad V_{avg} = \frac{13.97 + 13.97 + 14.04 + 14.12}{4} = 14V$$

$$R = \frac{14V}{65 \times 10^{-6}} = 215384 = 215.38 \text{ k}\Omega$$

$$I_{avg} = \frac{66 + 76 + 64 + 54}{4} = 65 \text{ mA}$$

TECHNOLOGICAL UNIVERSITY (TANALYN)



Date: _____

NTC		PTC	
→ Original Resistance	10.35 kΩ	← Original Resistance	0.449 kΩ
Heat 1	10.26	Heat 1	
Heat 2	7.67	Heat 2	
Heat 3	3.99	Heat 3	

original	original
original	0.449 kΩ
Heat 1	422
Heat 2	405
Heat 3	

At 3000 Insulation Resistance Test 8-3-6.2
The integrity of insulation is stressed by applying a dc current at 100V for low voltage circuits

$$R = \frac{V}{I}$$

$$R_T = R_1 + \alpha R_2 R_1 (1 + \alpha \Delta L)$$

$$\frac{1}{R_T} = \frac{1}{R_{12}} + \frac{1}{R_{34}} + \frac{1}{R_5}$$

$$R_T = \frac{R_{12} \times R_{34} \times R_5}{R_{12}R_{34} + R_{34}R_5 + R_{12}R_5}$$

532V
536V

TECHNOLOGICAL UNIVERSITY (TANALYN)